

48783

# Radio — HOW TO TEST YOUR RADAR DETECTOR

# Electronics

FEBRUARY 1990

TECHNOLOGY - VIDEO - STEREO - COMPUTERS - SERVICE

## BUILD THIS FREQUENCY PROBE

Our 100-MHz frequency counter is the size of a logic probe!

## TEST YOUR VIDEO HEADS

This VCR service tool will save you time and money

## DISPLAY OF THE FUTURE!

New miniature display will revolutionize computers, videogames, and even TV

## CIRCUIT COOKBOOK


Dozens of pre-amps, playback amps, mixers, filters, and more

## BUILD AN AUDIO EXPANDER

Put movie-theater sound in your living room
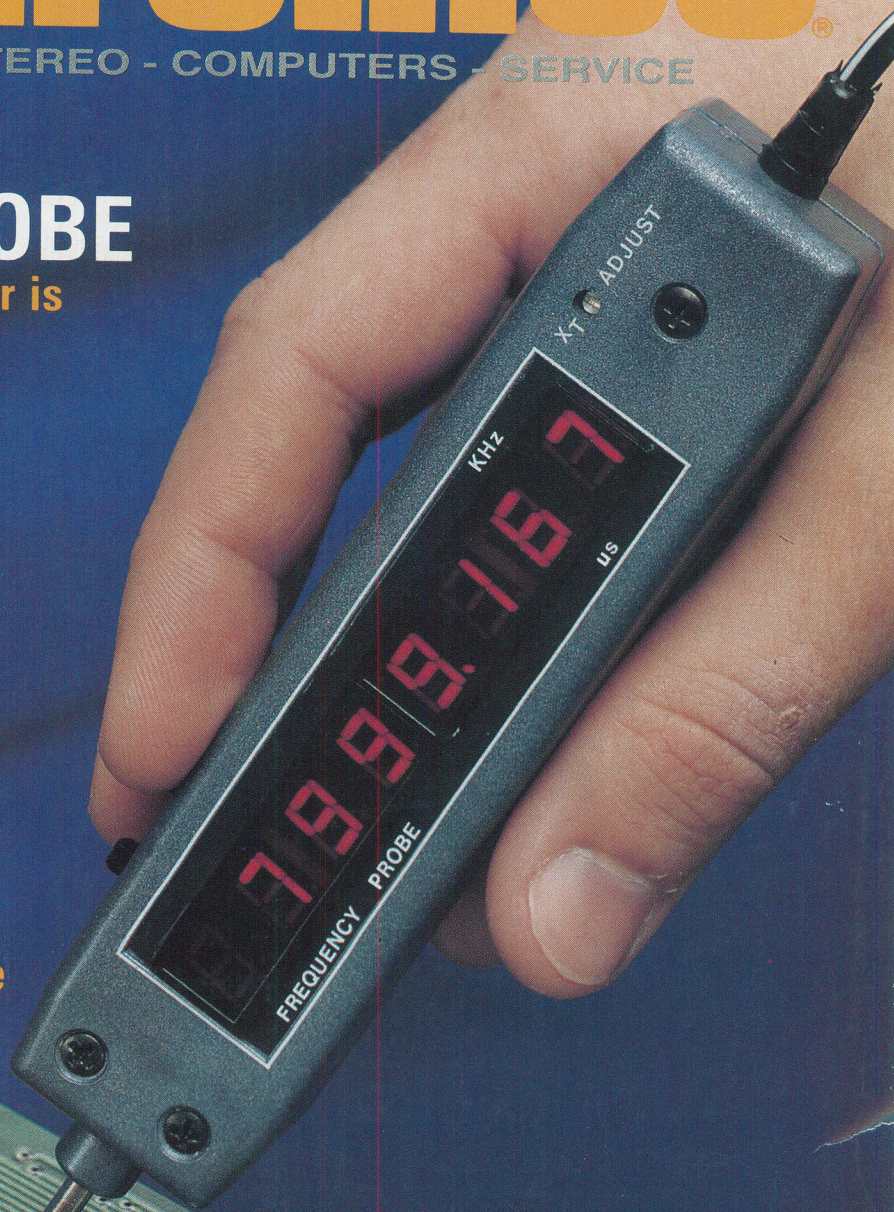
## COMPUTER DIGEST

Build the Port-A-Matic and keep track of your computer's port accesses



Plus: ★ Hardware Hacker  
★ Audio Update  
★ Video News  
★ And Lots More!



\$2.50 U.S.  
\$2.95 CAN

A  
GERNSBACK  
PUBLICATION



FLUKE



PHILIPS



# Great Choice.

**More professionals in more industries make Fluke their first choice in multimeters.**

Fluke DMMs. Reliable. Accurate. Powerful. Tough. Versatile. Easy to use and simple to operate. Backed by the longest, most comprehensive warranty in the business. Made in the U.S.A. In short, Fluke makes meters you can bet your reputation on.

**More choice.** No matter what the job, there's a Fluke to handle it.

There's the new 80 Series—the most powerful, most complete test and measurement system available in a handheld package.

The popular 70 Series—simply put, the most requested DMM in the world, with nearly 2 million units in service since 1984. And the Fluke 21 and 23—70 Series simplicity in high-visibility yellow.

The Fluke 25 and 27—the most rugged meters ever built, totally sealed against water, dust and other contaminants.

And the precise 8060 Series—with the versatility of a test lab, the accuracy of a bench instrument, and the convenience of a handheld.

**Smart choice.** Compare Fluke DMMs with any other handheld. No one else gives you as much meter for your money. And no other meter costs less to own.

**Your choice.** For the name of your nearest Fluke distributor, call toll-free **1-800-44-FLUKE, ext. 33.** And make a great choice.

John Fluke Mfg. Co., Inc. P.O. Box C9090 M/S 250C Everett, WA 98206. U.S.: (206) 356-5400. Canada: (416) 890-7600. Other Countries: (206) 356-5500. © 1989 John Fluke Mfg. Co., Inc. All rights reserved. Ad No. 0491-F70

FROM THE WORLD LEADER  
IN DIGITAL MULTIMETERS

FLUKE


CIRCLE 121 ON FREE INFORMATION CARD







## ON THE COVER

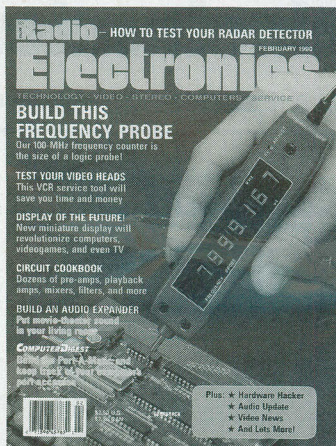

If you do any kind of electronics troubleshooting on a regular basis, then a frequency counter is a must-have. The problem is that most frequency counters are too cumbersome to take along on a field job. However, our 100-MHz frequency probe will easily fit in your shirt pocket, and take accurate measurements. Turn to page 31 for details.

## COMING NEXT MONTH

### THE MARCH ISSUE GOES ON SALE FEBRUARY 1.

#### BUILD A UNIVERSAL LABORATORY POWER SUPPLY

Two fully floating supplies offer outputs of 0–50 volts DC at 5–5 amps, plus fixed +5-volt logic supply adjustable from 0 to 3 amps.

#### THE ION METER

Discover the concentration of negative and positive ions in your environment—it could be affecting the way you feel.

#### BUILD AN AUDIO LIMITER

Eliminates distortion due to overdriving an audio amplifier.

#### ALL ABOUT BATTERIES

Ni-Cd's, alkaline, carbon-zinc, lithium—which one is right for your application?

#### AUDIO AMP COOKBOOK

Dozens of practical IC audio power-amplifier circuits that are easy to build

#### COMPUTER DIGEST

A 68705-based, keyless entry system is programmed for top security!

As a service to readers, RADIO-ELECTRONICS publishes available plans or information relating to newsworthy products, techniques and scientific and technological developments. Because of possible variances in the quality and condition of materials and workmanship used by readers, RADIO-ELECTRONICS disclaims any responsibility for the safe and proper functioning of reader-built projects based upon or from plans or information published in this magazine.

Since some of the equipment and circuitry described in RADIO-ELECTRONICS may relate to or be covered by U.S. patents, RADIO-ELECTRONICS disclaims any liability for the infringement of such patents by the making, using, or selling of any such equipment or circuitry, and suggests that anyone interested in such projects consult a patent attorney.

RADIO-ELECTRONICS, (ISSN 0033-7862) February 1990. Published monthly by Gernsback Publications, Inc., 500-B Bi-County Boulevard, Farmingdale, NY 11735 Second-Class Postage paid at Farmingdale, NY and additional mailing offices. Second-Class mail registration No. 9242 authorized at Toronto, Canada. One-year subscription rate U.S.A. and possessions \$17.97, Canada \$23.97, all other countries \$26.97. All subscription orders payable in U.S.A. funds only, via international postal money order or check drawn on a U.S.A. bank. Single copies \$2.50. © 1990 by Gernsback Publications, Inc. All rights reserved. Printed in U.S.A.

**POSTMASTER:** Please send address changes to RADIO-ELECTRONICS, Subscription Dept., Box 55115, Boulder, CO 80321-5115.

A stamped self-addressed envelope must accompany all submitted manuscripts and/or artwork or photographs if their return is desired should they be rejected. We disclaim any responsibility for the loss or damage of manuscripts and/or artwork or photographs while in our possession or otherwise.

## Radio-Electronics®

Hugo Gernsback (1884-1967) founder

M. Harvey Gernsback,  
editor-in-chief, emeritus

Larry Steckler, EHF, CET,  
editor-in-chief and publisher

#### EDITORIAL DEPARTMENT

Brian C. Fenton, editor

Marc Spiwak, associate editor

Daniel Goodman, technical editor

Teri Scaduto, assistant editor

Jeffrey K. Holtzman  
computer editor

Robert Grossblatt, circuits editor

Larry Klein, audio editor

David Lachenbruch  
contributing editor

Don Lancaster  
contributing editor

Richard D. Fitch  
contributing editor

Kathy Campbell, editorial assistant

#### ART DEPARTMENT

Andre Duzant, art director

Injae Lee, illustrator

Russell C. Truelson, illustrator

#### PRODUCTION DEPARTMENT

Ruby M. Yee, production director

Robert A. W. Lowndes,  
editorial production

Karen S. Tucker  
advertising production

Marcella Amoroso  
production assistant

#### CIRCULATION DEPARTMENT

Jacqueline P. Cheeseboro  
circulation director

Wendy Alanko  
circulation analyst

Theresa Lombardo  
circulation assistant

Michele Torrillo, reprint bookstore

Typography by Mates Graphics  
Cover photo by Diversified Photo  
Services

Radio-Electronics is indexed in  
Applied Science & Technology Index  
and Readers Guide to Periodical Literature.

Microfilm & Microfiche editions are  
available. Contact circulation department  
for details.

Advertising Sales Offices listed  
on page 96.




The  
Audit  
Bureau  
of Circulation




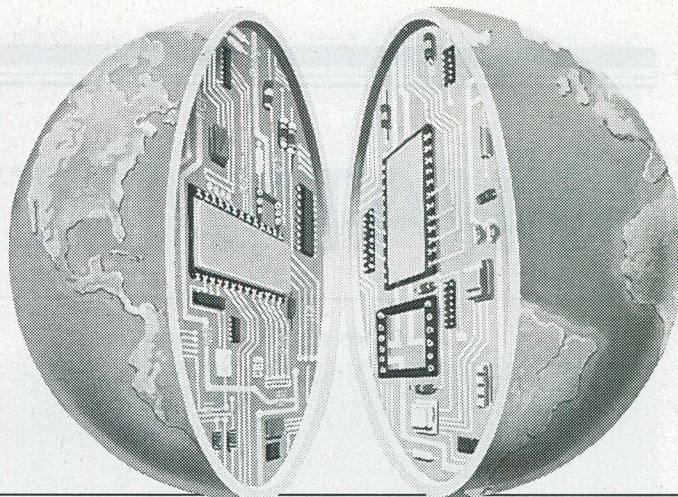
# WITH CIE, THE WORLD OF ELECTRONICS CAN BE YOUR WORLD, TOO.



**L**ook at the world as it was 20 years ago and as it is today. Now, try to name another field that's grown faster in those 20 years than electronics. Everywhere you look, you'll find electronics in action. In industry, aerospace, business, medicine, science, government, communications—you name it. And as high technology grows, electronics will grow. Which means few other fields, if any, offer more career opportunities, more job security, more room for advancement—if you have the right skills.


## **SPECIALISTS NEED SPECIALIZED TRAINING.**

It stands to reason that you learn anything best from a specialist, and CIE is the largest independent home study school specializing exclusively in electronics, with a record that speaks for itself. According to a recent survey, 92% of CIE graduates are employed in electronics or a closely related field. When you're investing your time and money, you deserve results like that.
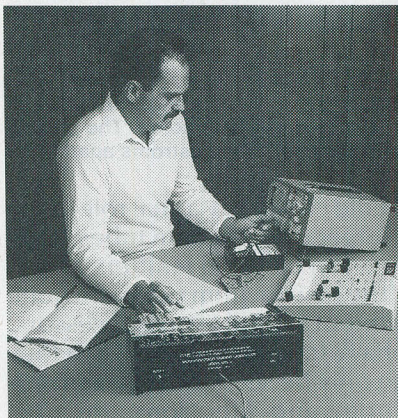
## **INDEPENDENT STUDY BACKED BY PERSONAL ATTENTION.**

We believe in independent study because it puts you in a classroom of one. So you can study where and when you want. At your pace, not somebody else's. And with over 50 years of experience, we've developed proven programs to give you the support

such study demands. Programs that give you the theory you need backed with practical experience using some of the most sophisticated electronics tools available anywhere, including our Microprocessor Training Laboratory with 4K of random access memory. Of course, if you ever have a question or problem, our instructors are only a phone call away.



## **START WHERE YOU WANT, GO AS FAR AS YOU WANT.**

CIE's broad range of entry, intermediate, and advanced level courses in a variety of career areas gives you many options. Start with the Career Course that best suits your talents and interests and go as far as you want—all the way, if you wish, to your Associate in Applied Science Degree in Electronics Engineering Technology. But wherever you start, the time to start is **now**. Simply use the coupon below to send for your **FREE** CIE catalog and complete package of career information. Or phone us, toll-free, at **1-800-321-2155** (in Ohio, 1-800-523-9109). Don't wait, ask for your free catalog now. After all, there's a whole world of electronics out there waiting for you.

# CIE

**Cleveland Institute of Electronics, Inc.**

1776 East 17th Street, Cleveland, Ohio 44114

Member NHSC

Accredited Member National Home Study Council

ARE-159

**CIE** **Cleveland Institute of Electronics, Inc.**  
1776 East 17th Street, Cleveland, Ohio 44114

**YES...** I want to learn from the specialists in electronics—CIE. Please send me my **FREE** CIE school catalog, including details about CIE's Associate Degree program, plus my **FREE** package of home study information.

Name (print): \_\_\_\_\_

Address: \_\_\_\_\_

City: \_\_\_\_\_ State: \_\_\_\_\_ Zip: \_\_\_\_\_

Age: \_\_\_\_\_ Area Code/Phone No.: \_\_\_\_\_ / \_\_\_\_\_

Check box for G.I. Bill bulletin on educational benefits:


☐ Veteran ☐ Active Duty

**MAIL  
TODAY!**



# WHAT'S NEWS

## Tubes making a comeback?

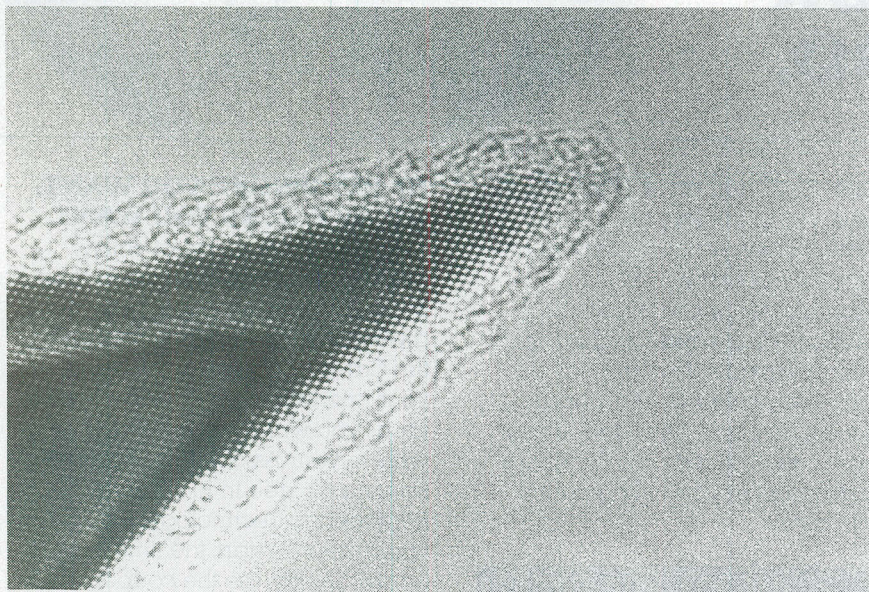

**THIS TRANSMISSION ELECTRON MICROGRAPH** of a silicon needle shows a radius of curvature of less than 10 angstroms—the distance of only a few atoms. The closely spaced lines are the 111 planes of the silicon atoms, spaced 3.13-angstroms apart.

Scientists at Bellcore (Middletown Township, NJ)—collaborating with scientists from the New Jersey Institute of Technology, the University of California at Davis, and Lawrence Livermore National Laboratory in California—have created a silicon needle whose tip is 50,000 times smaller than the diameter of a human hair. Only the width of a few atoms at its tip, the

needle could play a vital role in the resurgence of vacuum tubes, serving as an electron emitter.

The new vacuum tubes are quite different from their predecessors. Today's tubes are so small that they can only be seen through a microscope, and electrons are produced in them by applying voltage to a very sharp tip, rather than using a hot filament. While the

new vacuum-tube technology is still in its infancy, it could nevertheless offer several advantages over transistors. Electrons can be made to travel much faster in a vacuum tube than in a solid-state transistor, permitting faster speeds for data transmission. Vacuum tubes are also much less susceptible to temperature changes and various types of radiation, so they might be more suitable for use in hostile environments such as those that are found in outer space and nuclear reactors.

The problem facing researchers has been to create an emitter tip sharp enough to produce many electrons at low voltage. Until now, the sharpest tips were between 20 to 40 nanometers wide. By applying an oxidation-treatment process to tiny silicon cones, the research team has developed tips that are less than 1-nanometer wide. (A human hair is 50,000-nm wide; the diameter of an atom is about three tenths of a nanometer.) The microscopic silicon tips can produce substantially more electrons while using less voltage. Besides vacuum-tube applications, the needles could be used for examining atoms with scanning tunneling microscopes and as biological probes for medical research.

## Diamond-film technology

A new diamond-film-coating process created by Professor Rointan Bunshah, Dr. Chandra Deshpande, and colleagues at UCLA's School of Engineering and Applied Science offers key advantages over the deposition methods that are currently in use.

The new technique removes obstacles that have limited the applications of diamond-film technology—particularly the inability to deposit high-quality, smooth,

transparent, and non-faceted diamond films. Called *Plasma-Assisted Physical Vapor Deposition (PAPVD)*, the process involves using an electron beam to evaporate graphite to form carbon vapors. The vapors are introduced into a gas-plasma that contains hydrogen. When the material to be coated is held in the gas plasma, the resulting reaction deposits a diamond film on the material's surface that has all of the required attributes. The process is also

done at lower temperatures — 350°C, as compared to 850–1000°C.

The PAPVD process opens up a broad range of novel industrial applications, including protection of high-cost infrared and UV optical components, heat sinks for high-power and microwave devices, diaphragms for high-fidelity loudspeakers, and very-high-speed microelectronic devices that can operate at temperatures much higher than current silicon and gallium-arsenide devices. R-E




# Radio Shack Parts Place<sup>SM</sup>

## BIG SELECTION AND LOW PRICES—COME IN TODAY!
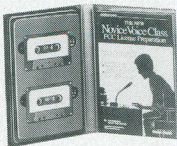
### Join the Fun of Ham Radio

Novice and General Class  
Study Packages Prepared by  
Gordon West, WB6NOA


**19<sup>95</sup>** Each Durable Storage  
Binder Included



**Novice.** Two self-paced code cassettes, study guide with exam questions, answers and full explanations, FCC Form 610. #62-2402

**General.** The speedy way to upgrade! Includes test questions, answers and explanations, two speed-building code tapes. #62-2404

### RS-232 Connectors and Accessories

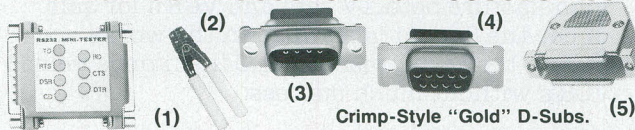


- (1) **Inline RS-232 Tester.** Seven LEDs pinpoint problems fast. D-sub 25. #276-1401 ..... **14.95**  
(2) **D-Sub Pin Crimper.** This pro-quality tool accepts #20, #24 and #28 pins. #276-1595 ..... **9.95**

#### Crimp-Style "Gold" D-Subs. (5)

Fig.	Description	Cat. No.	Each
3	Male-9	276-1427	.99
4	Female-9	276-1428	1.19
..	Male-25	276-1429	2.49
..	Female-25	276-1430	2.99


(5) **9-Position Hood.** #276-1513, 1.49  
**25-Position Hood.** #276-1536 .. 1.99

### Battery Special-Order Service

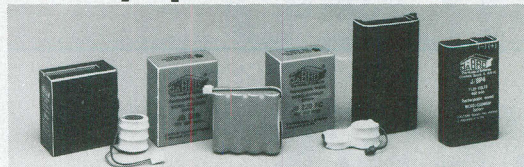


In addition to our large in-store stock, Radio Shack can now supply almost any battery. Our expanding selection even includes special batteries for walkie-talkies and pagers. Batteries are sent from our warehouse to the Radio Shack near you. Never a postage charge!

### Super Speaker Accessories

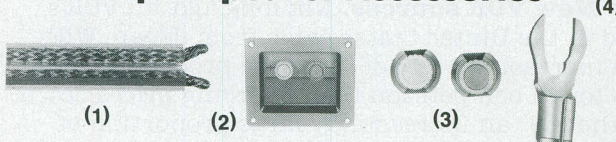


- (1) **MEGACABLE™.** 12-ga. braided pure copper. #278-1268 ..... **Per Foot 99¢**  
(2) **Speaker Terminal Plate.** For large speaker wires. Features special-design 3/4" diameter knobs. Mounts in 3/8 x 2 1/8" hole. #274-626 ..... **4.99**  
(3) One red, one black knob as above, less plate. #274-619 ..... **Set of 2/5.95**  
(4) **Large Gold-Plated Terminals.** 4 red, 4 black. #64-401 ..... **Set of 8/4.99**

### Project Lighting

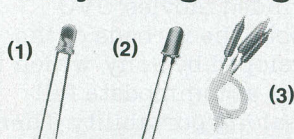


- (1) **Jumbo 5000 mcd LED.** Big, bright. #276-086 ..... **4.99**  
(2) **Blinking LED Indicators.** Red. #276-036 ..... **1.29**  
**Green.** #276-030 ..... **1.29**  
(3) **12-Volt Flashing Lamps.** #272-1097 ..... **Set of 3/1.29**

### Switch Bargains

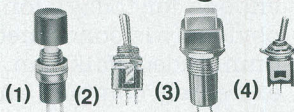


- (1) **SPST Momentary Button.** #275-1556 ..... **1.99**  
(2) **SPDT Toggle.** 5A at 125VAC. 7/16" stem. #275-603 ..... **1.59**  
(3) **SPST Push On/Push Off.** 3A at 250VAC. #275-617 .. **1.39**  
(4) **PC-Mountable Light-Duty SPST.** #275-645 ..... **1.99**

### Inductor Values

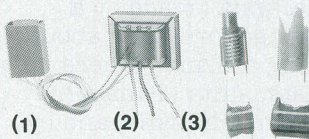

- (1) **1:1 Audio Transformer.** Z: 600-900Ω. #273-1374 ..... **3.59**  
(2) **Audio Output Transformer.** #273-1380 ..... **1.69**  
(3) **Inductor Assortment.** 30 pieces! #273-1601 ..... **1.98**

### Posts and Plugs

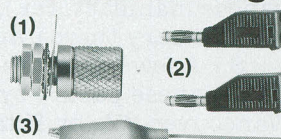


- (1) **Metal Grounding Post.** With knurled grip. #274-667 ... **99¢**  
(2) **Stackable Banana Plugs.** #274-734 ..... **Set of 2/1.59**  
(3) **14" Test Cables With Clips.** #278-1156 ..... **Set of 10/3.99**

### Hobby Motor



For robotics, models, projects. 8300 RPM maximum. Operates 1 1/2 to 3VDC. About 1 1/2" long, 1 1/16" dia. #273-223 ..... **99¢**


### TNC Adapters

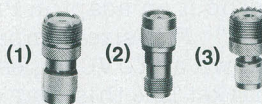

Here's just a sample of our big selection of RF adapters.


Fig.	Accepts	Plugs Into	Cat. No.	Each
1	PL-259	Female TNC	278-118	3.49
2	TNC Male	TNC Female	278-143	3.99
3	PL-259	Mini UHF	278-174	3.99

### Lighted Switches

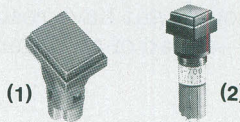


- (1) **SPST.** Rated 5A at 250VAC. Includes 12-volt lamp. UL listed. #275-678 ..... **6.99**  
(2) **SPDT Push-On/Push-Off.** Rated 3A at 125VAC. Includes 12-volt lamp. #275-676 ..... **6.49**

### "Gold" Adapters

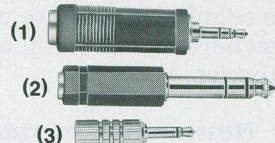


- (1) Accepts 1/4" stereo plug. Plugs into 1/8" stereo jack. #274-875 ..... **2.99**  
(2) Accepts 1/8" stereo plug. Plugs into 1/4" stereo jack. #274-876 ..... **2.99**  
(3) Accepts 1/8" stereo plug. Plugs into 1/8" mono jack. #274-877 ..... **2.99**

### Soldering Accessories

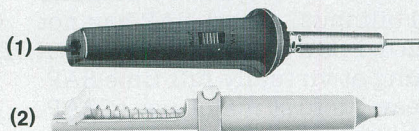

- (1) **Dual-Wattage Iron.** Go from 15 to 30 watts with the flick of a switch. Has a replaceable tip and it's 8 1/4" long. UL listed AC. #64-2055 ..... **8.95**  
**Chisel Tip.** #64-2056 ..... **1.19**  
**Replacement Tip.** #64-2065 ..... **99¢**  
(2) **Vacuum Desoldering Tool.** #64-2120 ..... **6.95**

### Extra-Feature LCD DVM

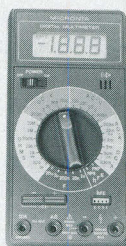

**79<sup>95</sup>**  
**Capacitance and HFE Ranges**

Top-quality digital volt-ohmmeter with an easy-to-read 0.5" LC display. Measures AC/DC volts and current, resistance, capacitance, transistor gain. With probes. #22-194

### B-Board and Jumpers



- (1) **Deluxe Breadboard.** Molded 2 1/4 x 6 1/2" board is mounted on a 7 x 4" steel base with rubber feet. Features 640 plug-in points and three binding posts. #276-169 ..... **19.95**  
(2) **Breadboard Jumper Wire Kit.** Includes 140 insulated, pre-stripped wires in a handy, snap-shut box. #276-173 ..... **Set 4.95**

Over 1000 items in stock! Binding Posts, Books, Breadboards, Buzzers, Capacitors, Chokes, Clips, Coax, Connectors, Fuses, Hardware, ICs, Jacks, Knobs, Lamps, Multitesters, PC Boards, Plugs, Rectifiers, Resistors, Switches, Tools, Transformers, Transistors, Wire, Zeners, More!

Prices apply at participating Radio Shack stores and dealers

**Radio Shack<sup>®</sup>**  
**The Technology Store<sup>SM</sup>**  
A DIVISION OF TANDY CORPORATION



# VIDEO NEWS



**DAVID LACHENBRUCH,**  
CONTRIBUTING EDITOR

• **New VCR sources.** Not long ago, all VCR's sold in the United States came from Japan. With the increasing costs of Japanese production and the tough competition that is forcing prices down in the U.S., an increasingly large proportion of VCR's are now coming from other Far-Eastern countries. In the first seven months of 1989, more than 30% of all VCR's imported into this country came from sources other than Japan. Major source countries were Thailand (mostly Emerson recorders produced there by Orion, a Japanese manufacturer), Malaysia (made by a JVC subsidiary there), and Singapore. How about the U.S.? A few VCR's are being assembled here from Japanese parts—by Matsushita (Panasonic) in Vancouver, WA; by Hitachi in California; and by Toshiba in Tennessee.

In the same period, the major sources for imported color-TV sets were—in order of quantities—Mexico, Taiwan, Korea, Malaysia, Singapore, and mainland China. Japan came in seventh, followed by Hong Kong and Canada. Where did the U.S. rank as a source of color TV sets sold here? Despite what you might have read elsewhere, it was number one—ahead of all other countries.

• **New names in video.** Two well-known audio names are entering the video field—neither of them for the first time. Aiwa, which was a pioneer in Beta VCR's but has been out of the field for several years, is now moving back with VHS recorders. Aiwa, owned by Sony, will concentrate on high-end, four-head models. The company is also surveying the TV market, but has decided to stay out for the time being because of the tough price competition in that field.

Sansui, however, plans to jump into the television-receiver as well as the VCR field with both feet. The venerable producer of high-end audio products had fallen on hard times, but recently received a fresh transfusion of capital from the British firm, Polly Peck International, which is acquiring 51% of Sansui stock in an extremely rare instance of a western firm acquiring control of a major Japanese company. Polly Peck, which produces consumer-electronics equipment in the Far East and Turkey, plans to

manufacture both TV sets and VCR's for sale under the Sansui label. Also in the works are Sansui-brand fax machines. Sansui once fielded VCR's without much success.




• **Movies on VHS-C?** One of the top priorities of JVC, inventor of VHS recording, is lengthening the recording time of the miniature VHS-C (for "compact") cassette to two hours. To date, the recording time in the SLP mode on the longest playing VHS-C cassette is 90 minutes—not quite enough for today's long-winded movies. JVC obviously is concerned about the inroads of the 8mm Video Walkman, developed by Sony, which is extremely compact and can accommodate full-length movies with carry-along portability. There are two Video Walkman models, both with LCD color screens. The VHS-C format is doing well in Japan and Europe, particularly for camcorders, but in the U.S. it is lagging behind 8mm. In addition to a longer-playing cassette, another high priority for JVC is the development of a VCR that can play both VHS and VHS-C cassettes without an adaptor. Prototypes of those so-called "F/C" (Full-size/Compact) recorders have been shown and JVC hopes to have them on the market late this year or early in 1991.

• **SAP is rising.** In 1984, when the FCC approved Multichannel TV Sound (MTS), the breakthrough involved more than stereophonic audio. In addition to stereo sound, each TV station was authorized to transmit a Secondary Audio Program (SAP). Although a few stations have transmitted bilingual sound, SAP has not been widely utilized. PBS's flagship station, WNET, New York, is aiming at virtually full-time SAP some time this year. Its first major use of SAP was for descriptive commentary for the blind accompanying the musical, "Show Boat." WNET also is planning to add a Spanish translation of the "MacNeil-Lehrer News Hour," and might even present the BBC World Service from shortwave transmissions—as well as music, book readings, and even countdowns for videotaping—all on its extra audio channel. Out of about 550 TV stations with MTS capability, approximately 100 are equipped to transmit a SAP channel.

**R-E**


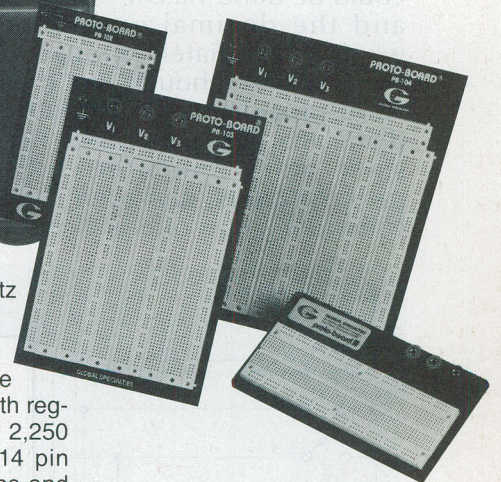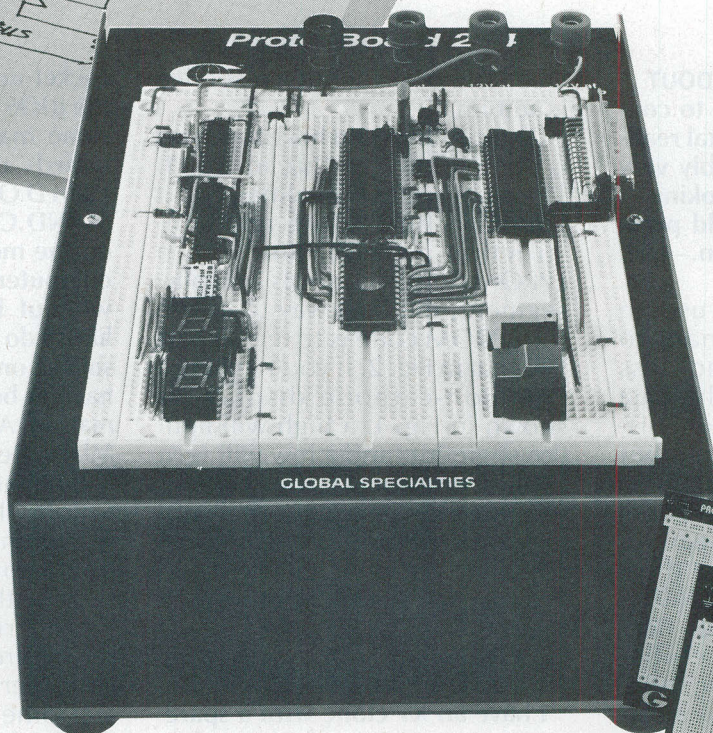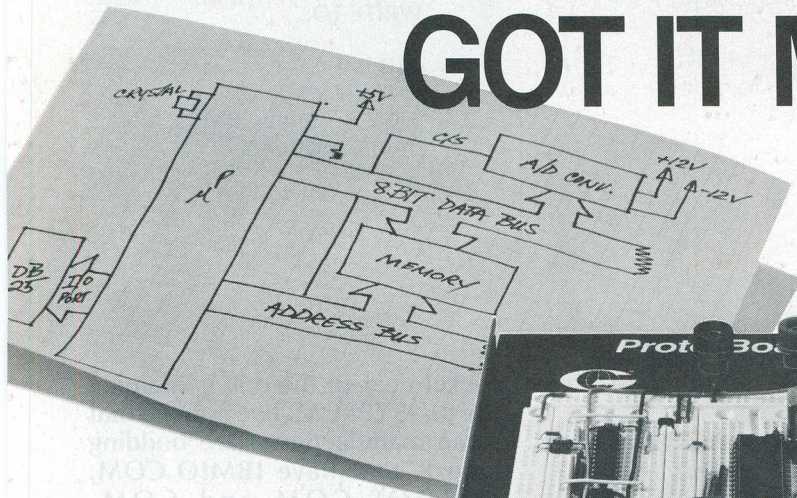
# ONCE YOU'VE GOT IT DESIGNED, YOU'VE GOT IT MADE.



Now you can take those hot, new logic or block design diagrams, and quickly, easily bring them up to reality...in minutes...without solder!

Build circuits as fast as you can think. Test. Modify. Expand. Without burned-out parts or burnt fingers. Save time, money...and prove that you know that you're talking about... before you use your CAD.

Specify PROTO BOARD Brand, Today's recognized Standard for Quality in breadboarding. Here are five expandable breadboards, offering countless arrays of solderless sockets and bus strips that emulate pc board layouts. Pop in components. Pop them out again. Microprocessors. Memory. Large DIPs. Tiny discretes. Makes no difference. The patented aluminum backplane lets you work at

frequencies from DC to half-a-GigaHertz or 500MHz.

**Need power?** A powered PROTO BOARD Brand offers up to triple voltage power supplies, +5V, +12V, -12V, with regulated/current limited DC power. Over 2,250 tie points with 24 IC capacity and 14 pin DIPs. Super for TTL, CMOS, Op-Amps and microprocessor circuits. And lots more.

Best of all, your hassle-free American-made PROTO BOARD Brand comes with an unlimited lifetime guarantee on all the breadboard sockets. Prices are so modest, you'll wonder why you waited this long to specify PROTO BOARD Brand. Order today.



## GLOBAL SPECIALTIES

*Easy does it!*™



Call toll-free for details  
**1-800-572-1028**

Global Specialties. An Interplex Electronics Company.  
70 Fulton Terrace, New Haven, CT 06512.  
Telephone: (203) 624-3103. © Interplex Electronics 1989.  
All Global Specialties breadboarding products made in USA.

CIRCLE 184 ON FREE INFORMATION CARD

A0010



# Ask R-E

## WRITE TO:

ASK R-E  
Radio-Electronics  
500-B Bi-County Blvd.  
Farmingdale, NY 11735

### BINARY TO DIGITAL READOUT

I'm looking for a circuit to convert 8-bit binary into a digital readout. The solution is probably very simple and I'm just overlooking it. I'd be grateful if you could point me in the right direction.—H. Vaughn, Mt. Airy, NC.

The easiest way is to use an EPROM to translate binary to decimal. Think of the address pins as inputs and use the data outputs to drive a 7-segment display. Entering the binary number could be done via DIP switches, and the decimal equivalent would immediately appear on the display. Although that'd involve programming an EPROM, doing that is much easier now since most computer clubs, parts suppliers, and even some computer shops offer it as a ser-

vice. The cost for such a service is minimal.

The circuit you'd have to set up is something like that in Fig. 1. The parts count is minimal, and it could be built using any construction method. Since each EPROM output controls a display segment, the best way to create the EPROM code is to use a chart like that in Fig. 2. If you're using a common-cathode display, as shown in Fig. 1, a high will light the segment, and a low will turn it off. Common-anode displays work just the opposite. That subject was covered in considerable detail in recent issues of "Drawing Board," so you should look them up.

### DOS ON A MOTHERBOARD I have an XT clone with a spare

socket next to the one containing the BIOS EPROM. I've noticed that some manufacturers are building boards that have IBMIO.COM, IBMDOS.COM and COM-MAND.COM burnt into EPROM's on the motherboard. That lets the computer boot DOS immediately without loading from a disk. I'd like to do the same using the empty socket on my motherboard, but I haven't been able to get any information. Any ideas?—T. Dunn, No. Miami Beach, FL.

Several, but first some observations. I've never seen the ads you mentioned and, although I don't doubt you've seen them, I'd take them with a grain of salt. You're right in assuming that those three ROM files would give you a permanent DOS, but there are some things you're probably overlooking.

IBM DOS (and IBMIO.COM and IBMDOS.COM which are part of PC-DOS) is owned exclusively by IBM. People sell it, but I've never heard of it being licensed for use in a PROM. IBM is very quick to jump on copyright infringement. MS-DOS is the version that's licensed to various manufacturers. The history of DOS and the reasons behind the two versions are interesting, but both are proprietary. Be careful that what you're buying is legal before you whip out your credit card.

If it's legal, and you want to do the same thing yourself, you need some information on your motherboard's EPROM sockets. Although there's a wide variety of XT clone boards around (a gross

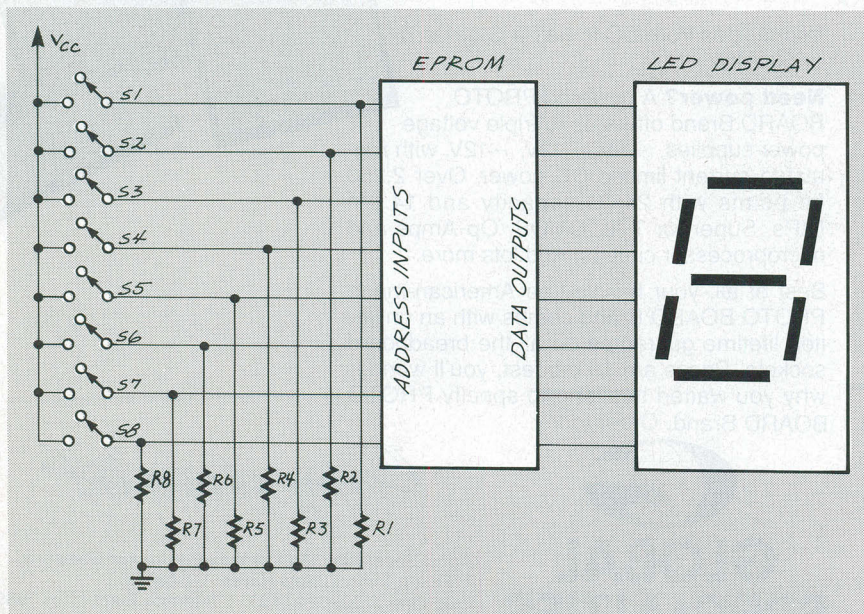


FIG. 1



# Discover Your Career Potential In The Fast Growing Field Of High-Tech Electronics!

CIE Gives You The Training You Need to *Succeed...*  
At Your Own Pace...& In Your Own Home!

If you're anxious to get ahead ...and build a *real* career...you owe it to yourself to find out about the Cleveland Institute of Electronics!

CIE can help you discover *your* career potential in the fast growing field of high-tech electronics. A career that will challenge and excite you every day...reward you with a powerful feeling of personal accomplishment...and deliver a level of financial security you may have only dreamed of before!

As the leading school in home-study electronics, CIE has helped over 150,000 students in the U.S.A. and over 70 foreign countries get started in this exciting field. To find out how CIE could be helping *you*...read on...then send for a CIE catalog TODAY!

## A Growing Need For Trained Professionals!

The career opportunities shown here are only a few of the challenging, high-paying careers you could enjoy as an electronics technician.

You could be the "brains" behind the scenes of an exciting TV broadcast...trouble-shoot life-saving medical equipment...design exotic new aeronautics systems...CIE's job-oriented programs offer you the quickest possible path to the career of your dreams! And CIE also features military and union re-training, to build on what you already know.

## Dozens Of Fascinating Careers To Choose From!

Even if you aren't sure which career is best for you, CIE can get you started with core lessons applicable to *all* areas of electronics. As you advance, CIE makes job opportunities available to you through the bimonthly school paper, *The Electron*.




Data Communications




Automotive Electronics



Avionics

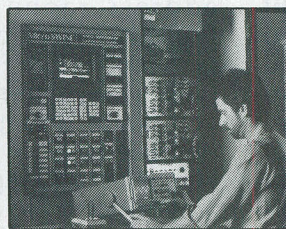

Computer-Assisted Manufacturing

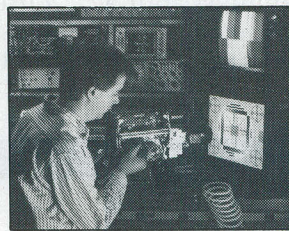

Consumer Electronics



Military Electronics

## Personal Training From A Renowned Faculty.

Unlike the impersonal approach of large classroom study, CIE offers you one-on-one instructional help 6 days a week, toll-free. Each CIE lesson is authored by an independent specialist, backed by CIE instructors who work directly with you to answer your questions and provide technical assistance when you need it.

## Practical Training... At Your Own Pace.

Through CIE, you can train for your new career while you keep your present job. Each course allows a generous completion time, and there are no limitations on how fast you can study. Should you already have some electronics experience, CIE offers several courses which start at the intermediate level.

## "State-Of-The-Art" Facilities & Equipment.

In 1969, CIE pioneered the first electronics laboratory course, and in 1984, the first Microprocessor Laboratory. Today, no other home study school can match CIE's state-of-the-art equipment. And all your laboratory equipment is included in your tuition cost. There is no extra charge—it's yours to use while you study at home and on the job after you complete your course!

## Earn Your Degree To Become A Professional In Electronics!

Every CIE course you take earns you credit towards the completion of your Associate in Applied Science Degree, so you can work towards your degree in stages. And CIE is the only school that awards you for fast study, which can save you thousands of dollars in obtaining the same electronics education found in four-year Bachelor's Degree programs!

**Send For Your Catalog Today!**



## CIE World Headquarters

Cleveland Institute of Electronics, Inc.  
1776 East 17th St., Cleveland, Ohio 44114

ARE-160

☐ **YES!** Please send me your independent study catalog (For your convenience, CIE will have a representative contact you—*there is no obligation.*)

Print Name \_\_\_\_\_



Address \_\_\_\_\_ Apt # \_\_\_\_\_

City/State/Zip \_\_\_\_\_

Age \_\_\_\_\_ Area Code/Phone No. \_\_\_\_\_

Check box for G.I. Bill bulletin on educational benefits: ☐ Veteran ☐ Active Duty

**Mail This Coupon Today!**

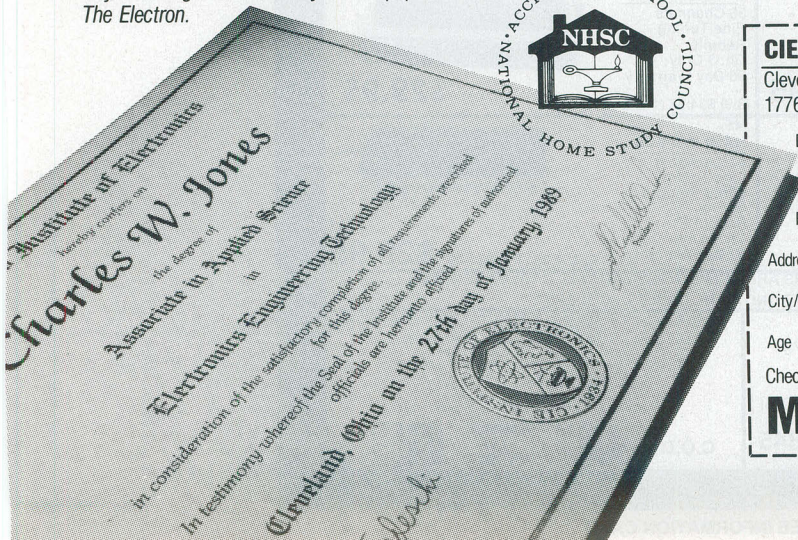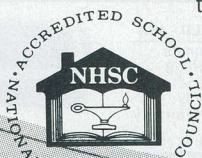



EPROM TRUTH TABLE										
INPUTS		OUTPUTS								
BINARY DATA	HEX DATA	D7 DP	D6 'G'	D5 'F'	D4 'E'	D3 'D'	D2 'C'	D1 'B'	D0 'A'	HEX DATA LED'S LIT
0000	0	0	0	1	1	1	1	1	1	3F 0
0001	1	0	0	0	0	0	1	1	0	06 1
0010	2	0	1	0	1	1	0	1	1	5B 2
0011	3	0	1	0	0	1	1	1	1	03 3

FIG. 2

understatement), most have empty socket space to let them copy IBM's PC and XT motherboards.

The IBM boards had a stripped-down BASIC in ROM on the motherboard. When you bought DOS (you did buy it, I hope), you got a file called BASICA.EXE. That BASIC wasn't the complete language; it was an overlay that enhanced the ROM version, that could only be run if you already had the more primitive half on the motherboard. Since clone makers want to produce clones, putting empty sockets on the motherboard was as close as they could legally get.

Real IBM's have five 64K ROM's on the motherboard, one for BIOS, and four for BASIC0. Given that, you can assume that the empty socket on your motherboard is mapped to the same address range occupied by BASIC0 on the real IBM boards, or F6000h-FDFFFh. Since you only have one empty socket on your board, I'd guess that it was designed for a 27256 EPROM. That'd let one chip hold the same amount of code as the four 64K PROM's on the IBM board. That is just an educated guess, but a pretty good one. The BIOS, of course, is mapped from FE000h-FFFFFh.

Unless your motherboard is radically different than those I've seen, its EPROM space is limited to 32K bytes (the addresses for BASIC0), and the 8K bytes used by BIOS, or a total of 40K to play around with. Since DOS usually takes up at least 60K for DOS 2X, and 80K for DOS 3X, it'd take mirrors and a lot of heavy equipment to squeeze both DOS and the BIOS into the available address space. But wait, there's more bad news.

DOS was designed for a particular place in memory, inside the 640K memory space. The EPROM space on your motherboard is way outside that, so you'd probably be faced with having to rewrite the DOS code (jumps, destinations, and any absolute address references). You could do that, but assuming you overcame those obstacles, you'd have a pretty strange version of DOS, and upgrading to a new version would be a Herculean task. The basic conclusion is, that you'll probably be better off if you boot DOS like the rest of us. **R-E**

## MOVIE TIME

### CABLE CONVERTERS

**NEW!**


78 Channel Wireless Remote • Remote Fine Tuning • Parental Control  
10 dB Amplifier Favorite Channel Memory • Fine Tune Centering  
24 MONTH WARRANTY

<p>(#1) V7800-3 V7800-2</p> <p>15 Lot <b>\$62.95</b></p> <p>10 Lot <b>\$64.95</b></p> <p>(3-9) \$69.95 (1-2) \$89.95</p>		<p>(#2) with Volume &amp; Mute Control Last Channel Recall Audio...Output * Decoder Loop</p> <p>10 Lot <b>\$79.95</b></p> <p>(3-9) \$89.95 (1-2) \$109.95</p>
<h3>JERROLD</h3>		
<p>(#3) <b>JERROLD - 450</b> 68 Channels Automatic Fine Tune Rebuilt Ch. 3 Only 90 Day Warranty</p> <p>(3-9) \$63.95 (1-2) \$73.95</p>		<p>(#4) <b>JERROLD - JSX</b> 36 Channels Fine Tuning Rebuilt Ch. 3 Only 90 Day Warranty</p> <p>(3-9) \$34.95 (1-2) \$39.95</p>
<h3>MOVIE TIME REPLACEMENT HAND UNITS</h3>		
<p> <b>\$14.95</b> 24 Lot</p> <p>Single Lot \$24.95</p>	<p>#6 JERROLD-550 #7 JERROLD-450 #9 JERROLD-400 #10 TEXSCAN AND MORE</p> <p>(13-23) \$16.95 (2-12) \$19.95</p>	<p>(#5) <b>HAMLIN - 4000</b> 42 Channels Fine Tuning Wired Remote or Set top Rebuilt Ch. 2 Only 90 Day Warranty</p> <p>(3-9) \$34.95 (1-2) \$39.95</p>
<p>ALL OF THE ABOVE CABLE CONVERTERS ARE COMPATIBLE WITH ALL CABLE DECODERS * NONE OF THE ABOVE UNITS ARE CABLE DECODERS</p>		
<h3>MOVIE TIME</h3> <p>20203 N.E. 15th Court • Miami, FL 33179 FAX: (305) 653-8102</p> <p>For More Information Call For Orders Only Call</p> <p><b>1-305-652-1981 1-800-843-9845</b></p>		
<p>Minimum Shipping Charge \$6.50 + \$1.00 for ea. additional converter or 25 for ea. Hand Unit. BLUE Label 2nd day air: \$12.50 Min. + \$3.50 for additional converter, or .80 for ea. Hand Unit. RED Label 1st day air: \$18.50 Min. + \$3.50 for additional converter, or \$1.00 for ea. Hand Unit. Puerto Rico, Hawaii &amp; Alaska add \$5.00. No COD Orders will be shipped by Air. Shipping Charges are not Refundable.</p> <p>C.O.D.   </p>		



# HITACHI SCOPES AT DISCOUNT PRICES

## Digital Storage Scopes

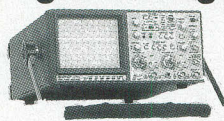


VC-6025 20MS/S  
50MHz Bandwidth  
2K Word Memory  
Capacity  
**\$2349.00**

Advanced storage functions create new dimensions in scopes such as one shot observation, flicker free display, bright display for even high speed event, trace observation for low speed event, hard copy by plotter and data output to computer.

VC-6045 100MHz 40MS/S 4K word Memory cap (call)

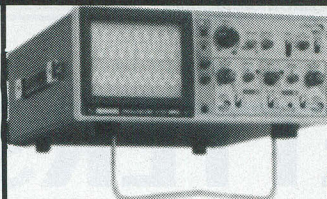All Hitachi scopes include probes, schematics, and Hitachi's 3 year worldwide warranty on parts and labor. Many accessories available for all scopes.




V-212

**\$435**

List \$595  
Save \$160

DC to 20MHz  
Dual Channel

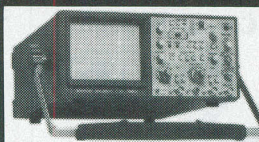

V-1060

List \$1595

**\$1,359**

- DC to 100MHz
- Dual Channel
- Delayed Sweep
- CRT Readout
- Sweep Time
- Autoranging
- Trigger Lock
- 2mV Sensitivity

V-422	40MHz	D.T., 1mV sens, DC Offset Vert Mode Trigger, Alt Mag	
V-423	40MHz	D.T., 1mV sens, Delayed Sweep, DC Offset, Alt Mag	
V-425	40MHz	D.T., 1mV sens, DC Offset, CRT Readout, Cursor Meas	
V-660	60MHz	D.T., 2mV sens, Delayed Sweep, CRT Readout	
V-1065	100MHz	D.T., 2mV sens, Delayed Sweep, CRT Readout, Cursor Meas	
V-1100A	100MHz	Q.T., 1mV sens, Delayed Sweep, CRT Readout, DVM, Counter	
V-1150	150MHz	Q.T., 1mV sens, Delayed Sweep, Cursor Meas, DVM, Counter	

LIST	PRICE	SAVE
\$940	\$740	\$200
\$1,025	\$825	\$200
\$1,070	\$849	\$221
\$1,295	\$1,145	\$150
\$1,895	\$1,670	\$225
\$2,450	\$2,095	\$355
\$3,100	\$2,675	\$425

## ELENCO PRODUCTS AT DISCOUNT PRICES

### 20MHz Dual Trace Oscilloscope



**\$375**  
**MO-1251**

- 6" CRT
- Built in component tester
- TV Sync


### FREE DMM

with purchase of  
ANY SCOPE

#### SCOPE PROBES

P-1 65MHz, 1x, 10x	\$19.95
P-2 100MHz, 1x, 10x	\$23.95

### 35MHz Dual Trace Oscilloscope

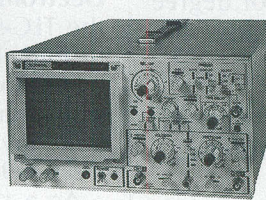


**\$495**  
**MO-1252**

- High Luminance 6" CRT
- 1mV Sensitivity
- 6KV Acceleration Voltage
- 10ns Rise Time
- X-Y Operation • Z Axis
- Delayed Triggering Sweep

Top quality scopes at a very reasonable price. Contains all desired features. Two 1x, 10x probes, diagrams and manual. Two year guarantee.

### PRICE BREAKTHRU on Auto Ranging DMMs

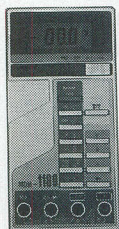


3 to choose from:  
MDM-1180 **\$24.95**  
MDM-1181 **\$27.95**  
MDM-1182 **\$29.95**

- 3 1/2 LCD Display
- 27 Functions
- Auto/Manual Ranges
- Audible Continuity
- Data Hold (MDM-1182)
- .1% Accuracy (MDM-1181)


True RMS 4 1/2  
Digit Multimeter  
**\$135**  
**M-7000**

.05% DC Accuracy  
.1% Resistance  
with Freq. Counter  
and deluxe case

### Bench DMMs

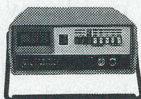

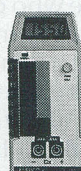
**M-3500** 3 1/2 digit **\$125**  
**M-4500** 4 1/2 digit **\$175**  
3 1/2% accy 4 1/2% accy



Multimeter with  
Capacitance and  
Transistor Tester  
**\$55** **CM-1500**

Reads Volts, Ohms,  
Current, Capacitors,  
Transistors and  
Diodes with case

### Digital Capacitance Meter

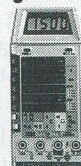

**CM-1550**  
**\$58.95**

9 Ranges  
.1pf-20,000ufd  
.5% basic accy  
Zero control  
with case

### Digital LCR Meter



**LC-1801**  
**\$125**

Measures  
Coils 1uH-200H  
Caps .1pf-200uf  
Res .01-20M



AC Current Meter  
**ST-1010**  
**\$69.95**

1000 Amps  
Data/Peak Hold  
8 Functions  
Deluxe Case

### Solderless Breadboards



9430 1,100 pins **\$15**  
9434 2,170 pins **\$25**  
9436 2,860 pins **\$35**  
All have color  
coded posts

9436 SHOWN


### AC Clamp-On



Current Adapter  
**ST-265**  
**\$25.00**

0-1000A AC  
Works with  
most DMM

### Wide Band Signal Generators

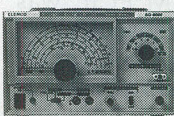

**SG-9000** **\$129**  
RF Freq 100K-450MHz  
AM Modulation of 1KHz  
Variable RF output

**SG-9500 with Digital Display  
and 150MHz built-in Freq Ctr \$249**

### TRIPLE POWER SUPPLY XP-620



Assembled **\$65**  
Kit **\$45**

Contains all the desired features for  
doing experiments. Features short  
circuit protection all supplies

2 to 15V at 1A,  
-2 to -15V at 1A  
(or 4 to 30V at 1A)  
and 5V at 3A


### Function Generator Blox



**#9600**  
**\$28.95**

Provides sine, tri, squ wave  
from 1Hz to 1MHz  
AM or FM capability

### Decade Blox

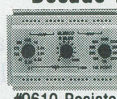

**#9610 or  
#9620**  
**\$18.95**

**#9610 Resistor Blox**  
47 ohm to 1M & 100K pot  
**#9620 Capacitor Blox**  
47pf to 10MFD

### Digital Triple Power Supply

**XP-765**



**\$249**


Fully Regulated, Short circuit protected with  
2 Limit Cont., 3 Separate supplies

**XP-660 with Analog Meters \$175**

0-20V at 1A  
0-20V at 1A  
5V at 5A

### Quad Power Supply

**XP-580**

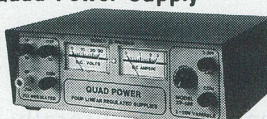

**\$59.95**


Fully regulated and  
short circuit protected

**XP-575 without meters \$39.95**

2-20V at 2A  
12V at 1A  
5V at 3A  
-5V at 5A
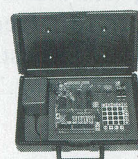
### LEARN TO BUILD AND PROGRAM COMPUTERS WITH THIS KIT!

INCLUDES: All Parts, Assembly and Lesson Manual



**MODEL  
MM-8000**

**\$129.00**

Starting from scratch you build a complete system. Our Micro-Master trainer teaches you to write into RAMs, ROMs and run a 8085 microprocessor, which uses similar machine language as IBM PC. You will write the initial instructions to tell the 8085 processor to get started and store these instructions in permanent memory in a 2816 EPROM. Teaches you all about input and output ports, computer timers. Build your own keyboard and learn how to scan keyboard and display. No previous computer knowledge required. Simple easy to understand instruction teaches you to write in machine language.

### Four-Function Frequency Counters



**F-100 120MH**  
**\$179**

**F-1000 1.2GH**  
**\$259**

Frequency, Period, Totalize,  
Self Check with High Stabilized Crystal Oven  
Oscillator, 8 digit LED display

### GF-8016 Function Generator with Freq. Counter

**\$249**



Sine, Square, Triangle  
Pulse, Ramp, 2 to 2MHz  
Freq Counter .1 - 10MHz

**GF-8015 without Freq. Meter \$179**

**WE WILL NOT BE UNDERSOLD!**

UPS Shipping: 48 States 5%

(\$10 Max) IL Res., 7% Tax



**C & S SALES INC.**

1245 Rosewood, Deerfield, IL 60015

(800) 292-7711 (708) 541-0710

**15 Day Money Back Guarantee**


**2 Year Warranty** Prices subject to change

**WRITE FOR FREE CATALOG**



Put Professional Knowledge and a  
**COLLEGE DEGREE**  
in your Technical Career through

## HOME STUDY

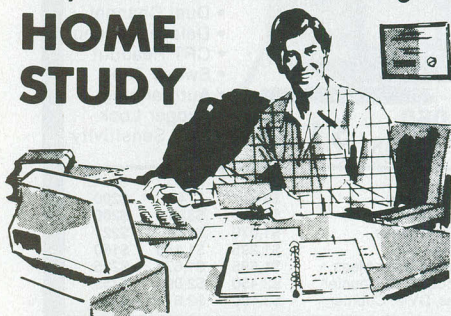

Add prestige and earning power to your technical career by earning your Associate or Bachelor degree through directed home study.

Grantham College of Engineering awards accredited degrees in  
**electronics and computers.**

An important part of being prepared to *move up* is holding the right college degree, and the absolutely necessary part is knowing your field. Grantham can help you both ways—to learn more and to earn your degree in the process.

Grantham offers two degree programs—one with major emphasis in **electronics**, the other with major emphasis in **computers**. Associate and bachelor degrees are awarded in each program, and both programs are available completely by correspondence.

No commuting to class. Study at your own pace, while continuing on your present job. Learn from easy-to-understand lessons, with help from your Grantham instructors when you need it.

Write for our free catalog (see address below), or phone us at toll-free 1-800-955-2527 (for catalog requests only) and ask for our "degree catalog."

Accredited by  
the Accrediting Commission of the  
National Home Study Council

**GRANTHAM**  
College of Engineering  
10570 Humbolt Street  
Los Alamitos, CA 90720

# LETTERS

## DIGI-COMPASS PARTS

I've heard from a number of "Digi-Compass" builders (**Radio-Electronics**, November 1989) that the TLC-548 ADC IC is impossible to find. It has been discontinued by Radio Shack, although it's possible that some stores may have still have a few available (part #276-1796, \$6.95).

As a special service to **Radio-Electronics** readers, I will supply the part for \$6.95. Those who don't want to download the software file can also purchase that from me, for \$6.00. (That might be cheaper than downloading the 100K file at 1200 baud from the RE BBS.) It will be supplied on a 360K PC data floppy diskette.

To order, please send a check or money order only (California residents add 6.5% sales tax) plus \$1.75 shipping and handling to Digital Products Company, c/o Thomas E. Black, 134 Windstar Circle, Folsom, CA 95630. This offer is subject to change and is valid for a short time only.

Thanks for publishing my article. I'm thrilled that it has stirred up some interest.

THOMAS E. BLACK  
Folsom, CA

## PCjr PROBLEMS

As a long-time reader of **Radio-Electronics**, I'd like to say thanks. Over the years I have literally taught myself how to design, build, program, and implement my own single-board computers from the articles and information you have presented. I have used what I learned to advance my career from a simple warehouseman to an operational research technician—and I'll be going back to school shortly to obtain the piece of paper that says I know what I know I know. It was your magazine

4/25/90 11:45 PM  
JERRY M. M. M.  
4/25/90 11:45 PM  
4/25/90 11:45 PM



## LETTERS

RADIO-ELECTRONICS  
500-B 81-COUNTY BOULEVARD  
FARMINGDALE, NY 11735

and the interesting projects and theories that your staff brings to attention that stirred my interest and helped improve my life. I owe you a great deal.

Now, after all this time, I need to ask for some personal assistance from your readers and staff:

I recently fell into a tremendous piece of luck, and purchased an IBM PCjr (Peanut) for \$30.00 at a garage sale. I've decided to use this machine for a dedicated process control in real time. Does anyone know where I can obtain any documentation for hard wiring my own interface boards for its very limited expansion slots, or where I can get a pin-out designation for same? I contacted IBM and, after finally finding someone who even remembered the IBM PCjr, was disappointed to find that IBM no longer has anything to do with any attachments or peripherals. It seems that IBM has virtually disowned the product.

Thanks again for all your help.  
SHAWN D. BOBBITT  
403 Green Street, #1  
Martinez, CA 94553

## UP TO DATE

I was amused with Michael Catudal's letter (**Radio-Electronics**, December 1989), chastising the magazine for not keeping up with "new technology."

In late 1995, the Galileo Probe will start its descent to a moon of Neptune. What will control its last 45 seconds before it is crushed by atmospheric pressure? Why, the venerable RCA 1802 microprocessor, of course. Remember



the old "Cosmac Elf"?

As I recall, **Radio-Electronics** had a construction project on that in the 1970's!! I wonder if the project manager thought the designer was nuts when he saw the 1802 in the design. I think not.

Keep up the good work.

JOHN CONNELLY

Naperville, IL

### BELATED THANKS

I just want to show my appreciation for the article and BASIC program, "Coping With Coils," that appeared in the November 1988 issue of **Radio-Electronics**. When I first got that issue, I didn't really look at the story, since I wasn't in need of any coils. Recently, however, I had to calculate coil sizes for several inductances, and I happened to remember seeing the program. I used it on my PC, and it worked much better than I expected—particularly in that it lets you select various wire and form sizes to determine the best arrangement.

Another thing I discovered from using the program was that there is a mathematical correlation between AWS wire gauges and equivalent inch diameter. I always thought that gauge sizes were just arbitrary. It's one of the most useful programs I've ever worked with.

J.F. BURTON

Downers Grove, IL

### PC BOARD RECIPE

I would like to share the results of my experiments with re-flow solder plating of homemade printed-circuit boards with other **Radio-Electronics** readers. After the board is etched, but before drilling, the resist can be removed with a little paint stripper, and the copper can be cleaned with a mixture of vinegar and salt.

Solder can be smeared onto the PC board with a hot iron with a wide tip. Use a minimum of solder. At this point, the board looks ugly; the solder now needs to be re-flowed to provide a uniform solder surface.

A hot bath of peanut oil (available at the supermarket) can facilitate the reflow process. I have found that heating the peanut oil slowly with the PC board sup-


ported above the surface of the pan with standoffs works well. If the board rests on the bottom surface of the pan it will de-laminate the fiberglass. I placed a piece of solder into the oil to determine when the temperature is high enough to reflow the solder; using a thermometer should work even better. The board can then be removed with tongs and wiped with a rag to remove the excess solder. It can then be dipped again to provide a shiny surface. It can be

cleaned with some kind of grease-cutting cleaner (like Era, liquid Tide, or Freon TF) to remove the oily film.

That method will surely benefit those experimenting with surface-mount technology. I've tried electroless tin plating, but after building circuits on reflow-soldered boards I'll never go back to unplated copper or tin-plated copper again.

RON DOZIER

Wilmington, DE

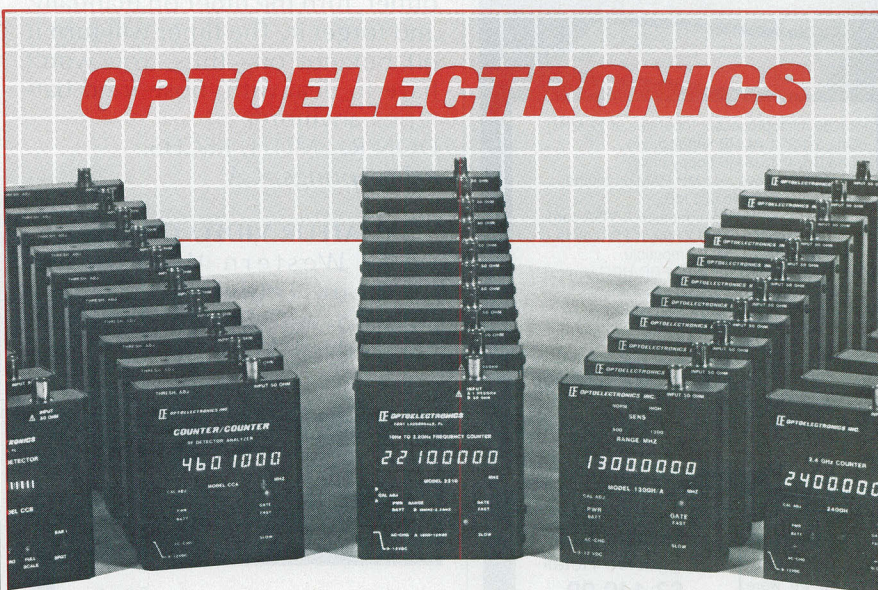

## You Have Counted on Us for 15 Years

You have counted on OPTOELECTRONICS Hand Held Frequency Counters to be the best quality, to be affordable and reliable. We have been there for you with Frequency Counters that are compact and ultra sensitive.

And more and more of you are counting on us, technicians, engineers, law enforcement officers, private investigators, two-way radio operators, scanner hobbyists, and amateur radio operators, just to name a few.

### Hand Held Series Frequency Counters and Instruments

MODEL	2210	1300H/A	2400H	CCA	CCB
RANGE: FROM TO	10 Hz 2.2 GHz	1 MHz 1.3 GHz	10 MHz 2.4 GHz	10 MHz 550 MHz	10 MHz 1.8 GHz
APPLICATIONS	General Purpose Audio-Microwave	RF	Microwave	Security	Security
PRICE	\$219	\$169	\$189	\$299	\$99
SENSITIVITY					
1 KHz	< 5 mv	NA	NA	NA	NA
100 MHz	< 3 mv	< 1 mv	< 3 mv	< .5 mv	< 5 mv
450 MHz	< 3 mv	< 5 mv	< 3 mv	< 1 mv	< 5 mv
850 MHz	< 3 mv	< 20 mv	< 5 mv	NA	< 5 mv
1.3 GHz	< 7 mv	< 100 mv	< 7 mv	NA	< 10 mv
2.2 GHz	< 30 mv	NA	< 30 mv	NA	< 30 mv

ACCURACY ALL HAVE +/- 1 PPM TCXO TIME BASE.

All counters have 8 digit red .28" LED displays. Aluminum cabinet is 3.9" H x 3.5" x 1". Internal Ni-Cad batteries provide 2-5 hour portable operation with continuous operation from AC line charger/power supply supplied. Model CCB uses a 9 volt alkaline battery. One year parts and labor guarantee. A full line of probes, antennas, and accessories is available. Orders to U.S. and Canada add 5% to total (\$2 min, \$10 max). Florida residents, add 6% sales tax. COD fee \$3. Foreign orders add 15%. MasterCard and VISA accepted.

Orders to U.S. and Canada add 5% to total (\$2 min, \$10 max). Florida residents, add 6% sales tax. COD fee \$3. Foreign orders add 15%. MasterCard and VISA accepted.

### OPTOELECTRONICS INC.

5821 N.E. 14th Avenue • Fort Lauderdale, Florida 33334  
1-800-327-5912 FL (305) 771-2050 FAX (305) 771-2052



**PACKARD BELL**  
America grew up listening to us. It still does.

## PACKMATE 286 COMPUTER WITH VGA COLOR MONITOR



30 MB  
Hard Drive!  
3-1/2" &  
5-1/4"  
Drives!

- 80286 microprocessor (operates at 12 MHz).
- One 3-1/2" 1.44 MB floppy drive.
- One 5-1/4" 1.22 MB floppy drive
- 30 MB hard drive. • 1 MB RAM on mother-board: expandable to 3 MB.
- Includes VGA 14" color monitor & VGA card.
- High res. monitor: 480 x 600, & 256 colors.
- IBM compatible. • AT compatible.
- 8 expansion slots. • Dual FDD/HDD controller.
- 2 half height drive cavities exposed.
- 1 half height drive cavity enclosed.
- 2 serial ports. • 1 parallel port.
- System configuration in CMOS with battery back-up.
- Included software: MS DOS 3.3 & GW BASIC.
- 145W Universal power supply.
- Socket for 80287 co-processor on motherboard.
- Zero wait state. • One Year Warranty!

**FACTORY NEW! FACTORY PERFECT!**

Due to a special arrangement, we were able to obtain a large inventory of these computers with color monitors. As a result, we can now offer them to you at **HUGE SAVINGS!**

Manufacturer's  
Suggested Retail

**\$3,449.00**

**DAMARK PRICE:**

**\$1499**

Item No. B-1729-132142  
Insured Ship/Hand.: \$39.00

**FOR FASTEST  
SERVICE CALL  
TOLL FREE  
1-800-729-9000**



**DAMARK INTERNATIONAL, INC.**

6707 Shingle Creek Parkway, Minneapolis, MN 55430  
Customer Service • 612-566-4940

Please rush me: **Packard Bell Computer(s)**  
@ \$1499 each, plus \$39.00 s/h each. Item  
No. B-1729-132142. **MN res. add 6% sales tax.**

Name \_\_\_\_\_  
Address \_\_\_\_\_  
City, State, Zip \_\_\_\_\_  
☐ Check ☐ VISA ☐ MasterCard ☐ Discover  
Card No. \_\_\_\_\_  
Exp. Date \_\_\_\_/\_\_\_\_ Ph. # (\_\_\_\_) \_\_\_\_\_  
Signature \_\_\_\_\_

**DELIVERY TO 48 U.S. STATES ONLY**

## NO MORE FRIED BATTERIES

For those of you who have numerous handheld transceivers—and, therefore, numerous batteries—here's an idea for a battery-charger shutoff that I have used for some time. Obtain the "garden-variety" light-timer from any drug-store, market, or junkbox. Remove the cam that turns the timer ON, leaving only the OFF cam intact. Plug the battery charger into the timer and set the timer to the appropriate time (8 hours or whatever). Then plug the timer in an AC outlet, turn the timer on manually, and forget it. The timer will turn it off but not on—thus, you won't have to deal with those fried batteries anymore.

DON R. SMITH, K6CHS  
Palm Springs, CA

## AMATEUR VIDEO CONTEST

The Western Washington Amateur Television Society (WWATS) and Amateur Television Quarterly (ATVQ) are sponsoring a


contest for licensed amateur-radio operators. To enter, you must submit by March 1, 1990 a video tape about ham radio that you make on your home video equipment (VHS, Beta, or 8mm). It can be about any aspect of ham radio, and can be a documentary, educational, technical, or entertainment film. It must be less than 15 minutes in length and be made using only consumer-grade equipment. All licensed amateur-radio operators (except members and families of members of WWATS and ATVQ and publishers and staff of ham-radio magazines) are eligible to win some fantastic prizes including an ICOM IC 1275 1.2-GHz transceiver and an AEA FS430 ATV transceiver.

Entry forms and complete rules and regulations for the contest can be obtained by writing to the address below.

WWATS/ATVQ VIDEO CONTEST  
353 South 116th Street  
Seattle, WA 98168

R-E
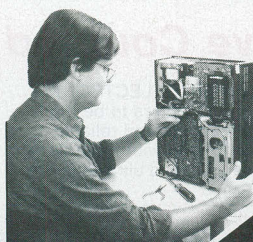
## LEARN VCR CLEANING/MAINTENANCE/REPAIR EARN UP TO \$1000 A WEEK, WORKING PART TIME FROM YOUR OWN HOME!



Secrets  
Revealed!

**NO Special  
Tools or  
Equipment  
Needed.**

**EARN UP TO \$60  
AN HOUR AND  
MORE!**

## THE MONEY MAKING OPPORTUNITY OF THE 1990'S

**IF** you are able to work with common small hand tools, and are familiar with basic electronics (i.e. able to use voltmeter, understand DC electronics)...

**IF** you possess average mechanical ability, and have a VCR on which to practice and learn... then we can teach **YOU** VCR maintenance and repair!

**FACT:** up to 90% of ALL VCR malfunctions are due to simple MECHANICAL or ELECTRO-MECHANICAL breakdowns!

**FACT:** over 77 million VCRs in use today nationwide! Average VCR needs service or repair every 12 to 18 months!

Viejo's **400 PAGE TRAINING MANUAL** (over 500 photos and illustrations) and **AWARD-WINNING VIDEO TRAINING TAPE** reveals the **SECRETS** of VCR maintenance and repair—"real world" information that is **NOT** available elsewhere!


Also includes all the info you'll need regarding the **BUSINESS-SIDE** of running a successful service operation!

## FREE INFORMATION

**CALL TOLL-FREE 1-800-537-0589**

Or write to: Viejo Publications Inc.  
3540 Wilshire BL. STE. 310  
Los Angeles, CA 90010 Dept. RE

## CABLE TV DESCRAMBLERS!

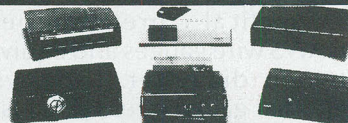

## BARGAIN HEADQUARTERS!

• JERROLD • TOCOM • HAMLIN  
• SCIENTIFIC ATLANTA • ZENITH

Oak M35B ONLY \$60


6 month warranty! We ship C.O.D.  
Lowest retail/wholesale prices!

**FREE CATALOG:**

Global Cable Network  
1032 Irving St. Suite 109  
S.F., CA 94122

**ORDER TODAY! 800-327-8544**
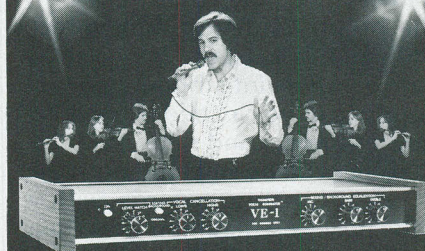
## SINGERS! REMOVE VOCALS FROM RECORDS AND CDs!



## SING WITH THE WORLD'S BEST BANDS!

An Unlimited supply of Backgrounds from standard stereo records! Record with your voice or perform live with the backgrounds. Used in Professional Performance yet connects easily to a home component stereo. This unique product is manufactured and sold Exclusively by LT Sound - Not sold through dealers. Call or write for a Free Brochure and Demo Record.

**LT Sound**, Dept. RL-3, 7980 LT Parkway  
Lithonia, GA 30058 (404) 482-4724  
Manufactured and Sold Exclusively by LT Sound  
**24 HOUR PHONE DEMO LINE: (404) 482-2485**



# EQUIPMENT REPORTS

## Sony CRF-V21 Visual World-Band Receiver

*The first of a new breed of communications receivers.*



CIRCLE 25 ON FREE INFORMATION CARD

IF WE ASKED THE READERS OF THIS MAGAZINE what features they would want in a communications receiver, we'd probably get a long and greatly varied list. At the top of the list would be frequency coverage from below the standard broadcast band up through 30 MHz, followed by the ability to receive AM and SSB signals. Undoubtedly, extensive memory and scanning features would be a popular request as well.

We doubt, however, if many people would request the ability to decode RTTY (Radio TeLeTYpe) and radio facsimile. Although those features are desired, they're not expected on a communications receiver. Well, Sony Corporation (Sony Drive, Park Ridge, NJ 07656) apparently ignored standard expectations when building their CRF-V21. They've packed so many features in the receiver that it's likely to become the new standard against which all other communications receivers are judged.

XXXX 221748Z  
P1CN5 CWIS 221500  
ICE CONDITIONS AND FORECAST FOR THE WESTERN ARCTIC  
ISSUED AT 1500 UTC SATURDAY 22 JULY 1989 BY  
ENVIRONMENT CANADA ICE CENTRE OTTAWA

ICE EDGE ESTIMATED FROM THE COAST NEAR HERSHELL ISLAND  
D TO 6920N  
13500W TO 6940N 13735W TO 7040N 13600W TO CAPE BATHURST  
T. MOSTLY  
OPEN TO VERY OPEN DRIFT INSIDE THE ICE EDGE SOUTH OF 7  
ON.  
THE SOUTHERN EDGE OF MIXED ICE LIES ABOUT 50 MILES OFF  
THE  
TUK PENINSULA AND ABOUT 80 MILES OFF THE ALASKA COAST  
AS FAR WEST  
AS BARTER ISLAND  
HONTHORWINE INCREASES TO ABOUT 100 MILES  
NORTH OF BARROW.

FIG. 1

### Basic specifications

The CRF-V21 receives long-, medium-, and shortwave broadcasts from 9 kHz through 30 MHz; FM broadcasts from 76 through 108 MHz; satellite frequencies of 137.62 and 141.12 MHz; and, assuming an optional dish is used,

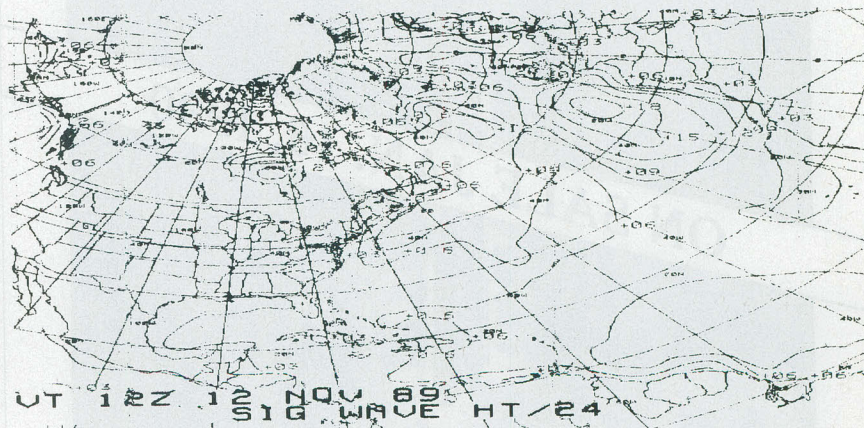


FIG. 2

1.691 and 1.6945 GHz. Audio-detection modes include AM wide, AM narrow, wideband FM, narrowband FM, USB, and LSB. The CRF-V21 can also decode and print RTTY, radio fax, and satellite fax broadcasts.

While most people are familiar with what is available on the standard broadcast and shortwave broadcast bands, RTTY and radio fax is a mystery to most—most of us know only the sounds that such transmissions make. The ability to

decode fax and RTTY adds another dimension to monitoring and DX-ing. Figures 1–3 give a good feel for the types of activity that exists on the airwaves.

Figure 1 is a partial printout of a broadcast from Environment Canada that lists ice conditions for the western Arctic. Figure 2 is a transmission from the Naval Eastern Oceanography Center in Norfolk, Virginia that shows wave heights in the Atlantic. Figure 3 is a satellite image from GOES, the Geostationary Orbiting Environmental Satellite. While that is the sort of image that the satellite capability makes possible, we received the image as it was rebroadcast from Norfolk. We did not have the opportunity to give the satellite ca-

pability a workout. All the images here were received using Sony's active telescopic antenna, which is supplied as standard equipment with the receiver. Satellite reception requires the optional AN-P1200 satellite dish.

### Microprocessor power

The CRF-V21 offers a host of features that its microprocessor control makes possible. For example, up to 50 "pages" of memory can be stored. Each page can hold



# NEXT MONTH IN Popular Electronics

## Exciting Features, Projects, Reports, & Columns

### ● EXPERIMENTS IN ELECTROPHOTOGRAPHY

Explore the world of Kirlian photography, Lichtenberg figures, and more

### ● MODEL TRAIN AND SLOT-CAR CONTROLLER

Build a model controller that outperforms many more-expensive commercial units

### ● RECEIVER CIRCUITS YOU CAN BUILD

Cook up a radio that meets your needs with these useful circuits

### ● A VISION SYSTEM FOR ROBOTIC TOYS

Give your robotic creations the gift of sight

## Popular Electronics

MARCH 1990



ON SALE JAN. 16, 1990

### And there is more!

**PRODUCT REPORTS**—Zenith VM7150 Camcorder, MicroTac Software French Assistant, and more

**DX LISTENING**—What's new at the Voice of America

**COMPUTER BITS**—The king of the Pascal programming hill

**CIRCUIT CIRCUS**—Shortwave converters, active antennas, and RF filters and more

**HAM RADIO**—Awards for award-winning hams

**SCANNER SCENE**—DX possibilities for scanner enthusiasts

PICK UP Popular Electronics AT YOUR FAVORITE NEWSSTAND, CONVENIENCE STORE, OR SUPERMARKET.



FIG. 3

up to seven stations, for a total of 350 stations. An identification tag can also be stored along with each page. We found that feature especially useful for finding the best frequency for a given time. For example, in one page, we programmed seven different frequencies on which the BBC broadcast. By calling up our "BBC" page, we found that we were able to easily switch between the seven entries to find the best possible reception conditions.

On another page, we stored some stations we happened across on the 25-meter band. Rather than listen and log the transmission times, we decided to let the receiver do the work for us. Using simple menu-chosen commands, we instructed the receiver to monitor the frequencies on that memory page for a 12-hour period. A printout of the activity is shown in Fig. 4. It shows rather clearly that there is a five-hour period where little activity takes place. While any active shortwave listener knows when the 25-meter band is active, that particular feature is invaluable when you're trying to determine the broadcast times and signal strength of, for example, a news bureau's wire service transmissions.



Of course, most SWL's would never be content in letting the receiver find stations to listen to. But even as you hunt around the bands finding new stations, the CRF-V21 has ways to make the task of logging easier. A single push of a button will feed all of the display information to the built-in high-resolution printer. A sample printout, which also serves to illustrate the amount of information that the receiver's huge LCD read-

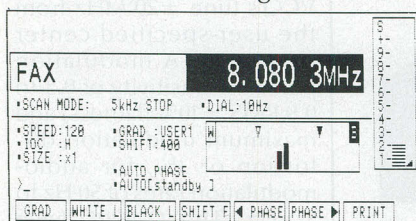


FIG. 4

out supplies, is shown in Fig. 5.

The receiver offers three scanning modes. First, it's possible to scan through the entire frequency range of the receiver. The receiver has enough "smarts" to change

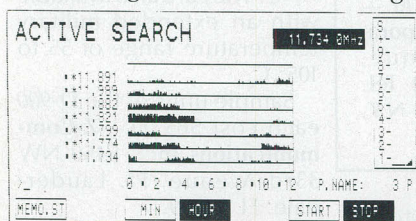


FIG. 5

the scanning steps and reception mode based on the frequency. For example, in the range between 88 and 108 MHz, the receiver would automatically set the reception mode to wideband FM, and the step frequency to 50 kHz. (It is possible to override any of the presets.) The second scanning mode allows the user to select the upper and lower limits between which scanning will take place. The third scanning mode scans only those stations stored in memory.

As if those scanning modes aren't adequate, Sony adds yet another way to search for broadcasting stations: a spectrum analyzer. Any part of the receiver's frequency coverage can be examined in spans of 200 kHz, 1 MHz, or 5 MHz. Fig. 6 shows a display of the activity of a 200-kHz segment in the 25-meter band. It is also possible to use a pointer to tune into only those stations that are strong enough to guarantee good recep-

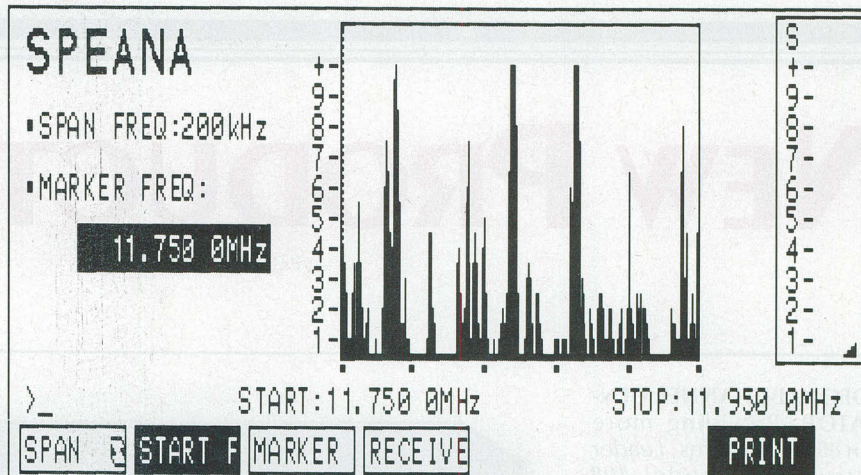


FIG. 6

tion. To those of us who take noise, interference, and fading as a necessary consequence of shortwave listening, the ability to bypass inter-station static and to stop at only clear, strong broadcasts is almost eerie.

We had a lot of fun examining Sony's CRF-V21. This review only touched the surface of the receiver's capabilities. For example, we've mentioned only a handful of

the receiver's 7 knobs, 10 jacks, and 59 pushbuttons (many of which serve several different functions). If not for the \$6000 price tag, we'd buy one tomorrow.

Despite the price, we expect that there is a market for this innovative receiver. The most enthusiastic shortwave enthusiasts will want one, as will, perhaps, government and embassy personnel, and navigators.

R-E

M O R E T H A N

LOGIC



## 286 SupersPort Laptop by Heathkit®

Your logical source for quality computer and electronic product needs, the **FREE Heathkit Catalog** is your key to a fun and exciting hobby. The Heathkit Catalog contains powerful kit laptop and desktop computers, test instruments, weather equipment, and home theater components, plus self-study electronics courses. Order your **FREE Heathkit Catalog** today! It's the logical thing to do!

**1-800-44-HEATH**  
(1-800-444-3284)

Send to: Heath Company, Dept. 020-854  
Benton Harbor, Michigan 49022

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_

State \_\_\_\_\_

Zip \_\_\_\_\_

A subsidiary of Zenith Electronics Corporation

CIRCLE 86 ON FREE INFORMATION CARD



# NEW PRODUCTS

**VIDEO/ALL-CHANNEL GENERATOR.** Providing more than 80 test patterns, *Leader Instruments'* model 408 gen-lockable NTSC Video Test Signal Generator outputs in composite, S-VHS, RGB, Y, R-Y, and B-Y formats with RF channel coverage of all broadcast and cable channels. A sampling of those test patterns includes multiburst, video sweep, SMPTE color bars, modulated and unmodulated staircase, convergence, and crosshatch.

A menu-driven, multi-purpose data-control panel with LCD is used to set up channel frequencies and video signal-level specifica-



CIRCLE 10 ON FREE INFORMATION CARD

tions. On-screen programming makes the 408 easy to use. Control of key video-signal levels—such as burst, sync, luminance, chrominance, and setup—is provided, along with RF-frequency selection. As many as 100 sets of video-level specifications can be stored

in memory, ready for instant recall.

The model 408 multi-format video/all-channel generator costs \$3,395.00.—**Leader Instruments Corporation**, 380 Oser Avenue, Hauppauge, NY 11788; Tel. 1-800-645-5104 (in NY, 516-231-6900).

—120 dBc/Hz at 25 kHz. The VCO's tune  $\pm 20$  MHz from the user-specified center frequency. A modulation port has sensitivity of 0.3 to 0.9 RMS  $\pm 10\%$  flatness, and maximum modulation distortion of 3%, for audio-modulation rates of 50 Hz to 5 kHz. The D-900's have buffered outputs of  $+3 \pm 2$  dBm and operate off 8- or 12-volts DC at 25 and 40 mA, respectively. The completely enclosed VCO's have a standard operating-temperature range of 0 to 70° C. They are also available with an extended military temperature range of 55 to 105° C.

Sample units of the D-900 each cost \$85.00.—**Z-Communications Inc.**, 5450 NW 33rd Avenue, Ft. Lauderdale, FL 33309.

**DIGITAL PANEL METER.** A battery-powered, 3½-digit panel meter, the DP-176S from *Acculex*, offers true single-ended (built-in negative rail generator) input and very wide primary-power operation—from +3.5 to +7.5 volts DC at only 145 mA. That extremely low power drain allows up to 8000 hours—one year—of continuous operation from any battery source in that range. The meter can also be used for mobile, portable, and other applications using a 12-volt DC automotive-type battery with voltage divider. It is easy to mount, requiring only a small screwdriver; an optional bezel kit is available.

The DP-176S uses a highly accurate, dual-slope-integrating ADC in conjunction with a single-ended input, an integral DC-to-DC converter, and common-mode rejection ratio of 85 dB. It can be configured for analog inputs from  $\pm 200$  mV




CIRCLE 11 ON FREE INFORMATION CARD

through  $\pm 200$  volts DC. The enhanced-contrast LCD has user-selectable decimal-point placement, external-reference capability for ratiometric measurements, and an all-digits test pin for checking full functionality. Other features include automatic polarity change-over, over- and under-range indication, 100-megohms input impedance, and an input-offset adjustment.

The DP-176S digital panel meter costs \$64.00; the optional bezel kit (B-1B) costs \$3.00.—**Acculex**, A Metra-Byte Company, 440 Myles

Standish Blvd., Taunton, MA 02780.

**RADIO VCO'S** Z-Communications' D-900 Series of 700- to 1000-MHz Voltage-Controlled Oscillators (VCO's), based upon coaxial resonator technology, are designed for use in cellular phones and for commercial and military radio applications, where low noise and high stability are required. The series has exceptional phase-noise characteristics of  $-95$  dBc/Hz at 1 kHz,  $-105$  dBc/Hz at 5 kHz, and

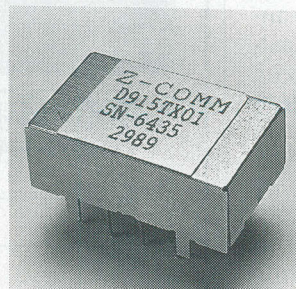

CIRCLE 12 ON FREE INFORMATION CARD

**AC CURRENT METER.** Designed for use by hobbyists as well as electricians, servicemen, and technicians,



CIRCLE 13 ON FREE INFORMATION CARD

*Elenco's* ST-1010 AC current meter is reliable and completely portable. It measures AC current up to 1000 amperes, and has nine functions: AC and DC volts, resistance, AC current, diode test, data hold, peak hold, audible continuity, and in-



sulation test (with an optional 500-volt insulation-tester unit. The hand-held instrument features a 3½-digit LCD readout, a wrist strap, and a carrying case. It runs for 150–200 hours on a standard 9-volt battery.

The ST-1010 AC current meter costs \$99.00.—**Elenco Electronics, Inc.**, 150 West Carpenter Avenue, Wheeling, IL 60090.

**DATA-ACQUISITION SYSTEM.** Hewlett-Packard's HP 75000 System 10 is a data-acquisition package that requires no programming to collect data and obtain results. All the necessary measurement hardware and menu-driven software to attach to a personal computer are included in the system. For a total solution, a PC/printer option is available that provides the user with an HP Vectra PC and an HP QuietJet printer.

System 10's hardware includes a 5½-digit multi-meter and a thermocouple-relay multiplexer for accurate temperature measurements on as many as 16 thermocouples. Two other multiplexers are also included, providing more than 100 channels of high-accuracy measurements. Two counters are available: a 4-channel counter measures counts, frequency, period, pulse width, interval, and up/down counts on signals up to 4 MHz and a 3-channel counter measures those same functions (except up/down) to 1 GHz. A 4-channel digital/analog device allows users to output either voltage or current on each channel. A built-in quad 8-bit digital I/O card allows the system to control devices and sense whether they are on or off. An HP 75000 B-size cardcage contains five empty slots that can be used with a variety of other plug-in measurement cards. Additional cards can be factory installed if they are ordered at the same time as the system.

LABTECH NOTEBOOK data-acquisition software is used. The flexible, menu-driven package allows users



CIRCLE 14 ON FREE INFORMATION CARD

to set up multiple-scan lists that can be scheduled to begin at user-determined times and executed at user-determined rates. The display can be customized, and data can be stored in various formats. An on-line learning aid is included. Color graphics screens show the user how to attach transducers to the System 10 and how to create setups on LABTECH NOTEBOOK. The software contains both Fast Fourier Transform and curve-fit analysis routines, and a seamless link to Lotus 1-2-3 is provided if you wish to do custom analysis and data sorting.

The HP 75000 System 10 costs \$5,750.00, and the PC/printer option costs an additional \$4,650.00.—**Hewlett-Packard Company**, Inquiries, 19310 Pruneridge Avenue, Cupertino, CA 95014; Tel. 1-800-752-0900.

**COMPUTER/CONNECTOR HARDWARE.** Collections of computer and connector hardware—consisting of turnable jack screws, "D" subminiature jack screws, and captive screws—are offered by **Keystone Electronics**. The Turnable Jack Screw selections, primarily used to secure computer connections, are available in a variety of configurations and are supplied with or without screwdriver slots. The turnable jack screws have knurled heads and are available in lengths from 1.75 to 4.5 inches with 4–40 threaded lengths, and in 0.125- to 0.250-inch diameters. They are made of steel with a choice of black zinc-plate, yellow chromate, or nickel-plate finishes.

The "D" Subminiature Jack Screws include 0.250-, 0.312-, and 0.625-inch lengths, and are made of

# CONNECTION PROTECTION

SWITCHES & RELAYS  
EDGE CONNECTORS  
PLUGS & SOCKETS  
POTENTIOMETERS  
CONNECTING CABLES  
TERMINAL STRIPS  
GOLD PLATED CONNECTORS  
BATTERY CONTACTS



## CRAMOLIN®

Even the finest equipment in the world cannot guarantee noise-free operation. One "dirty" connection anywhere in the electrical path can cause unwanted noise or signal loss.

### "MORE THAN A CONTACT CLEANER"

**CRAMOLIN®** is a fast-acting, anti-oxidizing lubricant that cleans and preserves all metal surfaces, including gold.

When applied to metal contacts and connectors, **CRAMOLIN®** removes resistive oxides as it forms a protective molecular layer that adheres to the metal surfaces and maintains maximum electrical conductivity.

#### CRAMOLIN® - USED BY THOSE WHO DEMAND THE BEST:

Bell & Howell	Hewlett Packard	MCI(Sony)	Nakamichi
Boeing	John Fluke Mfg.	Motorola	RCA
Capitol Records	McIntosh Labs	NASA	Switchcraft
			SINCE 1956

**CAIG LABORATORIES INC.**

1175-O Industrial Ave., (P.O. Box J) - Escondido, CA 92025-0051 U.S.A. • (619) 743-7143

CIRCLE 50 ON FREE INFORMATION CARD

# CABLE TV

## TB-3 (Tri-Bi) or SA-3

### Quantity Prices

10	20
<b>\$48.</b> Each	<b>\$43.</b> Each
50	100
<b>\$39.</b> Each	<b>\$35.</b> Each

Hours open 10:00 am to 4:00 pm Eastern time  
Minimum order 5 units 55.00 ea.  
Dealers wanted. We ship COD.

### King Wholesale

**1-800-729-0036**

Fax number 6173400053

"No one beats the King's prices!"

# DESCRAMBLERS



# CABLE - TV

## band-stop filters

- FOR ELIMINATION OF SEVERE INTERFERENCE
- FOR "CENSORING" OF ADULT BROADCASTS

NEW ADDRESS  
↓



- ATTENUATION - 45 dB TYPICAL
- BANDWIDTH - 4 MHz AT 5 dB POINTS
- INSERTION LOSS - 2 dB

MODEL	TUNING RANGE	FOR CHANNELS	PASSBAND	PRICE	SHIPPING/HANDLING
23H	50-66 MHz	2,3 (or 6 meter ham)	50-300 MHz	\$30	FREE
46FM	66-108 MHz	4,5,6 (or any FM)	50-300 MHz	\$30	FREE
1417	120-144 MHz	14(A) 15(B) 16(C) 17(D)	50-400 MHz	\$30	FREE
1822	144-174 MHz	18(E) 19(F) 20(G) 21(H) 22(I)	50-400 MHz	\$30	FREE
713	174-216 MHz	7,8,9,10,11,12,13	50-400 MHz	\$30	FREE

**3 for \$72 - 10 for \$180 - mix & match**

Call Toll Free For C.O.D. or Send Check To Order

**No Shipping Charges**


- Shipped Within 3 Days
- 30 Day Money Back Guarantee

**FACTORY DIRECT FROM**

**Star Circuits**

P.O. Box 94917  
Las Vegas, NV 89193-4917

**1-800-433-6319**

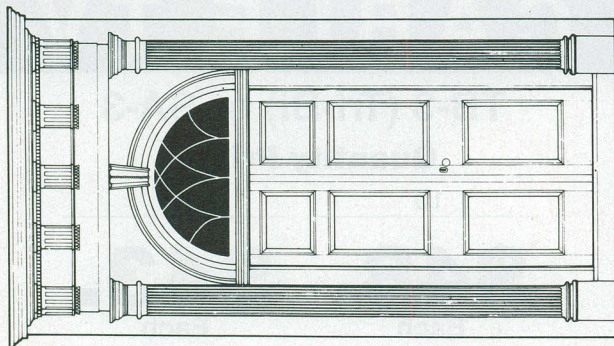

## PRESERVATION PLAN ON IT

Planning on restoring a house, saving a landmark, reviving your neighborhood?

Gain a wealth of experience and help preserve our historic and architectural heritage. Join the National Trust for Historic Preservation.


Make preservation a blueprint for the future.

Write:

National Trust for Historic Preservation  
Department PA  
1785 Massachusetts Ave., N.W.  
Washington, D.C. 20036

zinc-plated, gold-irridite steel that meets military standards. The devices are packaged both in bulk and in kits, and are complete with flat washers, lock washers, and nuts.

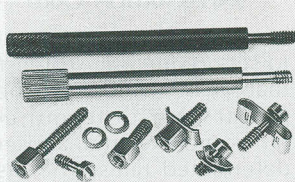The *Captive Screw* set comes with "U" clips, sad-




**CIRCLE 15 ON FREE INFORMATION CARD**

dle washers, and bow-tie retaining clips, in a variety of lengths and sizes. The captive screw group is also made of zinc-plated steel with gold irridite.

The Computer/Connector hardware collections range in price from \$6.00 per hundred to \$11.00 per hundred, depending upon the quantity ordered.—**Key-stone Electronics Corp.**, 31-07 20th Road, Astoria, NY 11105-2017.

**SCOPE PROBE.** Specially designed for durability and interference-free performance, *TPI's SP150* 150-MHz scope probe features risetime faster than 1.5 nanoseconds. Its design eliminates external interference and cable microphonics. The probe is sealed against moisture to withstand 95% humidity at 40°C. Specially designed strain relief and connector crimp more than triple the cable life of previous designs. The *SP150's* switch has self-cleaning contacts for longer life, and its ground lead is replaceable.

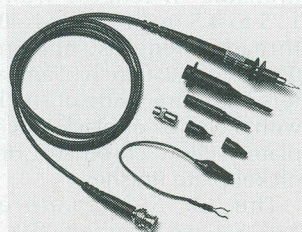The model *SP150* scope probe costs \$40.00.—**Test**



**CIRCLE 16 ON FREE INFORMATION CARD**

**Probes Inc.**, 9178 Brown Deer Road, San Diego, CA 92121; Tel. 1-800-643-8382.

### DIGITAL MULTIMETERS.

The *Soar 3200 Series DMM's* (models 3210, 3220, and 3230) combine the features of a state-of-the-art digital multimeter with an analog bar-graph display. The 3½-digit 3200-count display provides high resolution, and the 32-segment bar-graph display is well-suited for reading that change—peaking, nulling, and observing trends. All of the meter's functions are selected with an 8-position rotary switch and test; the meter automatically selects the range with the greatest accuracy and resolution. The function and measurement range are displayed on the LCD.

Models 3220 and 3230 have a RANGE button that pre-



**CIRCLE 17 ON FREE INFORMATION CARD**

vents the instrument from changing ranges, which saves time for repetitive go-no-go checks. Those two models each have an audible continuity feature that sounds a "beep" when the circuit under test is closed. When the DATA-H button on the model 3230 is pressed, the meter captures the measurement, beeps, and locks it on the display. All models come with test leads, manual, batteries, fuse, and a 3-year warranty.

The models 3210, 3220, and 3230 digital multimeters are each very affordably priced under \$100.00.—**HMC**, P.O. Box 526, Canton, MA 02021.



# NEW LIT


**ELECTRONIC-/COMPUTER-PARTS.** Geared to the needs of manufacturers, engineers, and researchers, as well as hobbyists, students, and computer buffs, the *American Design Components*



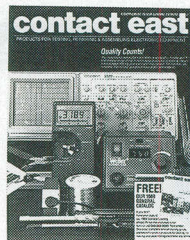**CIRCLE 21 ON FREE INFORMATION CARD**

*nents* catalog features components such as IC's, crystals, connectors, switches, batteries, LED's, semiconductors, and power supplies. It also features computer-related products including disc drives, monitors, add-on boards, and complete computers. The 36-page, fully illustrated catalog is free.—**American Design Components**, 815 Fairview Avenue, Fairview, NJ 07022; 800-776-3700.

**TOOLS AND TEST EQUIPMENT.** The *1989 Supplement to Contact East's General Catalog* includes a wide range of top brand-name products for testing, repairing, and assembling all types of electronic equipment. The 47-page, full-color booklet describes all products in full detail with specifications, photos, and prices. The products come with an "iron-clad" guarantee, and are shipped under Contact East's "same-day




**CIRCLE 22 ON FREE INFORMATION CARD**

shipment" policy to ensure fast delivery.

The *1989 Supplement* is free.—**Contact East**, 335 Willow Street South, North Andover, MA 01845; 508-682-2000.

**VIDEO-TAPE TIPS.** Providing answers to many of the questions that video enthusiasts are likely to have when they begin using camcorders, *The Maxell Video Tape Handbook* is filled with information on selecting tapes, producing videos that people will enjoy watching, and caring for video hardware. It explains

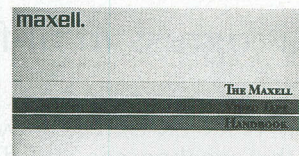
the different types of video tapes available and how to choose the right one. The booklet offers helpful hints on achieving interesting, high-quality videos using advanced "plot" planning, effective lighting, and how to use different lenses. Simple maintenance procedures to prolong the life of video tapes and equipment are also included, along with a handy glossary of camcorder terminology.



**CIRCLE 23 ON FREE INFORMATION CARD**

*The Maxell Video Tape Handbook* is free upon request; send a self-addressed, stamped, legal-size envelope with \$.75 postage.—**Maxell Video Guide Offer**, P.O. Box 4623, Monticello, MN 55365-4623.

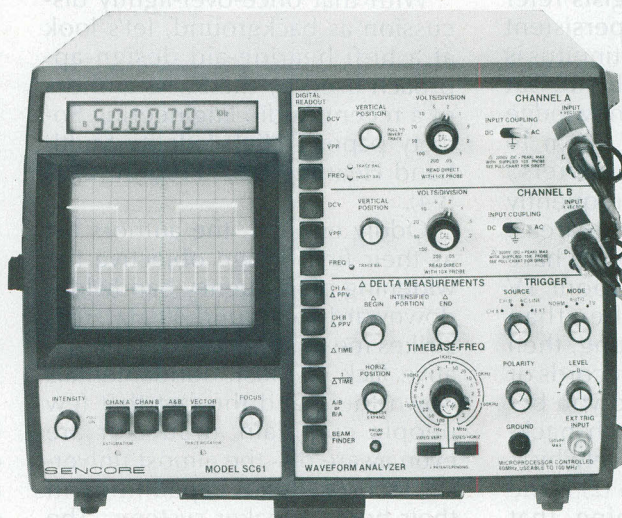**With Just One Probe Connection, You Can Confidently Analyze Any Waveform To 100 MHz, 10 Times Faster, 10 Times More Accurately, Absolutely Error Free, Guaranteed — Or Your Money Back!**



**SC61 Waveform Analyzer™**  
**Patented**  
**\$3295**

There are other digital readout oscilloscopes, but none of them completely eliminate graticule counting and calculations like the SC61 Waveform Analyzer. The innovative, time-saving AUTO-TRACKING™ digital readout automatically gives you every waveform parameter you need for fast troubleshooting.

The SC61 Waveform Analyzer is a triple patented high performance scope that provides you with a digital LCD read-out of all key waveform parameters (DC volts, peak-to-peak volts, and frequency) at the push of a button, and all with one probe connection.

Other time-saving features include exclusive ECL sync circuits that allow you to lock quickly onto waveforms up to 100 MHz. Plus, with 3000 volts of input protection, you never have to worry about an expensive front end repair job.

Call **1-800-SENCORE** to find out more about what the SC61 can do for your service business. In Canada call **1-800-851-8866**.

**SENCORE**

3200 Sencore Drive, Sioux Falls, SD 57107

100% American Made

**CIRCLE 189 ON FREE INFORMATION CARD**



# AUDIO UPDATE

## Progress in hi-fi hearing-aid design.

IT IS AN UNFORTUNATE FACT OF LIFE that weaknesses and disabilities begin to appear and multiply as we get older. Or as someone once said, "Time marches on—and leaves its heelprints on our bodies." Particularly troubling to those of us involved, professionally or otherwise, in audio pursuits is the gradual impairment of our hearing. In general, it takes three main forms: (1) an overall loss of sensitivity, which means that most sounds have to be louder to be heard at a satisfactory level, (2) a loss of relative high-frequency sensitivity, and (3) a loss of dynamic range, which audiologists refer to as "recruitment." (A persistent ringing in the ears called tinnitus is also a major hearing problem, but the present state of our knowledge and technology doesn't seem to offer much hope to its sufferers.)

As we get older, we frequently have problems in all three areas. For example, if you need to have the sound of your bedroom TV turned up slightly higher than your wife's preferred setting, then problem (1) is at work. If records or tapes that once bothered you because they had too much background hiss sound relatively hiss-free these days, problem (2) is the probable cause. (Assuming, that is, that you haven't upgraded to quieter audio equipment.) An early warning of problem (3) is an increased sensitivity to—and annoyance with—loud noises produced by motorcycles, lawnmowers, subway screeching, politicians, and so forth. Its proverbial manifestation is the old lady who demands that you speak up be-

cause she can't hear you—and then complains that you are shouting at her when you do.

Obviously, the main emphasis in hearing-aid design has always been to restore or enhance speech intelligibility. That is certainly a laudable goal, but anyone with a hearing loss who was interested in listening to music through an aid was inevitably left frustrated by distortions in the input and output transducers and inadequacies in signal bandwidth, noise, overload, and so forth.

### Hi-fi hearing aid

With that once-over-lightly discussion as background, let's look at a hi-fi hearing-aid design approach used by the Swiss authors of a recent Audio Engineering Society paper ("High Fidelity Multi-band Hearing Aid," Preprint 2793 B-4).

Oddly enough, the authors list as their first design objective the widening of frequency bandwidth downward to around 40 Hz. That strikes me as strange given the relative lack of music fundamentals down there and the fact that few people complain about—or are even aware of—the almost universal lack of 40-Hz capabilities in their home speaker systems. The author's choice of low-end cutoff frequency may have been influenced by the fact that their test subject for the aid design was a professional violoncello player.

The next step involved evaluating the "equal-loudness contours" of the potential hearing-aid user. In other words, at each level, how much gain had to be applied to

equivalent strength frequencies for each to be heard as equivalently loud? When you think about it, it becomes obvious that the key to enhancing the audio quality of a hearing aid is to tailor its response to the specific needs of the user. Merely adding amplification as was done in the earliest aids simply results in ear overload at some frequencies and inadequate boost at others.

Today's conventional aids are all frequency-contoured to conform to the user's specific needs, but the hi-fi aid designers went a step further: They split the right- and left-ear channels each into three bands (40–400 Hz, 400 Hz–4 kHz, 4–8 kHz), each band having its own adjustable compression ratios and levels. The compression ratios can be adjusted from 1:1 (no compression) to 4:1 for each of the six bands. In addition, each channel has its own external Baxandall bass and treble tone controls and level controls to allow user adjustment of the aid's response within the basic parameters set by the internal calibrations.

Standard miniature input and output transducers were, of course, not up to the requirements of the hi-fi aid. The authors chose a somewhat bulky electrodynamic omnidirectional microphone (which feeds both channels) over the smaller, but noisier, electret type. Conventional sealed electrodynamic headphones intended for high-quality Walkman use served nicely as output transducers. Since, according to its picture, the prototype hi-fi aid and its phones



LARRY KLEIN,  
AUDIO EDITOR



could easily be mistaken for a Walkman, I expect that anyone wearing it to a live event will receive some strange glances from other concertgoers.

### The digital future

As might be supposed, digital redesign is high on the agenda for hearing-aid design. In general, digitalization offers little for low-gain, straight-forward aids meant to correct minor hearing deficits. But when the demands are for multiple wide bandwidth, compressible channels, and simplified, but precise, tailoring to the specific needs of the user, then digital comes into its own. Although there was no attempt to incorporate digital circuitry in the hi-fi aid, the designers stated strongly that digital technology should ultimately be introduced into the equalization and compression stages. Altering the parameters of their existing prototype analog aid is a laborious and delicate task that digitalization will vastly simplify.

At least one U.S. company (Maico Hearing Instruments 612/832-4400) makes a "digital hybrid" aid whose parameters are programmable over a wide range. The manufacturer claims the availability of a million and a half settings, any of which can be stored by a built-in digital memory programmed by an external computer. That enables fairly rapid and

precise conformation to the hearing needs of the user—and simplified readjustment as those needs change over time. Another U.S. company (Nicolet Instruments 800/843-1055) is the first company to have available a fully digital unit, but details were not available at press time.

It seems safe to say that in the next year or two we should see the introduction of a variety of fully digital aids. That implies that there's an A/D converter after the input microphone and fully digital signal processing from that point on. For those who can afford such devices—and I expect them to be very expensive—the sound that they deliver will be a cut above what is presently available. But no one ever said that good hi-fi equipment comes cheap!

### System imbalance


**Q.** After a long struggle to find the reason for my having to operate the balance control on my preamplifier at the 3-o'clock position, I traced the difficulty to my speakers rather than my amplifier or preamp. It turned out that a readjustment of the midrange control on one of my speakers cured the problem. What would account for that?

**A.** The frequencies that contribute to the ear's perception of "loudness" are mostly in the mid-range. (You can confirm that for yourself by noting the small effect on the overall loudness of music produced by boosting or cutting the highs and lows with the outermost sliders of a ten-band graphic equalizer.) Hence, any control intended to boost or cut the mid-frequencies in a speaker, system will also necessarily influence its relative "efficiency."

R-E

STATEMENT OF OWNERSHIP, MANAGEMENT AND CIRCULATION			
1. TITLE OF PUBLICATION			
RADIO-ELECTRONICS		2. DATE OF FILING	
3. FREQUENCY OF ISSUE		4. ANNUAL SUBSCRIPTION PRICE	
MONTHLY		12 \$17.97	
5. COMPLETE MAILING ADDRESS OF KNOWN OFFICE OF PUBLICATION (Street, City, County, State and Zip Code) (Not printer)			
500-B BI-COUNTY BLVD., FARMINGDALE, NY 11735			
6. COMPLETE MAILING ADDRESS OF THE HEADQUARTERS OF LEGAL WORKS OFFICE OF THE PUBLISHER (Not printer)			
500-B BI-COUNTY BLVD., FARMINGDALE, NY 11735			
7. FULL NAME AND COMPLETE MAILING ADDRESS OF PUBLISHER, EDITOR AND MANAGING EDITOR (The owner must not be blank)			
PUBLISHER (Name and Complete Mailing Address)			
LARRY STECKLER 500-B BI-COUNTY BLVD., FARMINGDALE, NY 11735			
EDITOR (Name and Complete Mailing Address)			
BRIAN FENTON 500-B BI-COUNTY BLVD., FARMINGDALE, NY 11735			
MANAGING EDITOR (Name and Complete Mailing Address)			
8. OWNER (If owned by a corporation, its name and address must be stated and also immediately thereunder the names and addresses of stockholders owning or holding 1 percent or more of total amount of stock. If not owned by a corporation, the names and addresses of the individual owners must be given. If owned by a partnership or other unincorporated firm, its name and address as well as that of each individual must be given. If the publication is published by a proprietorship, its name and address must be stated.) (Name must be completed)			
FULL NAME COMPLETE MAILING ADDRESS			
GERBACH PUBLICATIONS, INC. 500-B BI-COUNTY BLVD., FARMINGDALE, NY			
LAWRENCE STECKLER 500-B BI-COUNTY BLVD., FARMINGDALE, NY			
9. KNOWN BONDHOLDERS, MORTGAGEES, AND OTHER SECURITY HOLDERS OWNING OR HOLDING 1 PERCENT OR MORE OF TOTAL AMOUNT OF BONDS, MORTGAGES OR OTHER SECURITIES (If none are held, so state)			
NONE			
10. FOR COMPLETION BY NONPROFIT ORGANIZATIONS AUTHORIZED BY MAIL AT SPECIAL RATES (Section 312.2 (b)(3) (b)(4) (b)(5) (b)(999) (b)(1000)			


# Give.



## American Heart Association

WE'RE FIGHTING FOR YOUR LIFE


# ATTENTION! ELECTRONICS TECHNICIANS



## EARN YOUR B.S.E.E. DEGREE THROUGH HOME STUDY

Our New and Highly Effective Advanced-Placement Program for experienced Electronic Technicians grants credit for previous Schooling and Professional Experience, and can greatly reduce the time required to complete Program and reach graduation. No residence schooling required for qualified Electronic Technicians. Through this Special Program you can pull all of the loose ends of your electronics background together and earn your B.S.E.E. Degree. Upgrade your status and pay to the Engineering Level. Advance Rapidly! Many finish in 12 months or less. Students and graduates in all 50 States and throughout the World. Established Over 40 Years! Write for free Descriptive Literature.

### COOK'S INSTITUTE OF ELECTRONICS ENGINEERING

 4251 CYPRESS DRIVE JACKSON, MISSISSIPPI 39212

CIRCLE 58 ON FREE INFORMATION CARD



## ORDER FROM JAN FOR CRYSTAL CLEAR COMMUNICATION

- YOUR RELIABLE SOURCE SINCE 1965
- QUICK DELIVERY
- PRICED RIGHT
- EMERGENCY ORDER SERVICE AVAILABLE

FOR FREE CATALOG, CALL OR WRITE:

### JAN CRYSTALS

P.O. BOX 06017  
FORT MYERS, FL 33906  
(813) 936-2397

## TOLL-FREE: 1-800-JAN-XTAL (526-9825)

FAX ORDERS: 1-813-936-3750

CIRCLE 104 ON FREE INFORMATION CARD



# Learn to troubleshoot and service today's computer systems as you build a fully XT-compatible micro, complete with 640K RAM and powerful 20 meg hard drive

## Train the NRI Way— and Earn Good Money Servicing Any Brand of Computer

Jobs for computer service technicians will almost double in the next 10 years according to Department of Labor statistics, making computer service one of the top 10 growth fields in the nation.

Now you can cash in on this exciting opportunity—either as a full-time industry technician or in a computer service business of your own—once you've mastered electronics and computers the NRI way.

NRI's practical combination of "reason-why" theory and hands-on building skills starts you with the fundamentals of electronics, then guides you through more sophisticated circuitry all the way up to the latest advances in computer technology.

---

### Train With a Powerful XT-Compatible – Now With 20 Meg Hard Drive and 640K RAM!

---

To give you hands-on training with the absolute in state-of-the-art computer technology, NRI includes the powerful new Packard Bell VX88 computer as the centerpiece of your training. As you assemble this fully IBM XT-compatible micro from the keyboard up, you actually see for yourself how every section of your computer works.



You build this powerful Packard Bell VX88 computer, all the while gaining a true mastery of computer electronics. Best of all, it's yours to keep for all your professional and personal computing needs.




You assemble and test your computer's "intelligent" keyboard, install the power supply and 5¼" disk drive, then interface the high-resolution monitor. But that's not all.

Your hands-on training continues as you install a powerful 20 megabyte hard disk drive—today's most-wanted computer peripheral—now included in your course to dramatically increase the data storage capacity of your computer while giving you lightning-quick data access. Plus you work with exclusive word processing, database, and spreadsheet software, yours to use for your own professional and personal applications.

As you build your computer, performing key demonstrations and experiments at each stage of assembly, you get the confidence-building, real-



Your NRI computer training includes all this: • NRI's unique Discovery Lab® for circuit design and diagnosis • NRI's hand-held digital multimeter featuring "talk-you-through" instructions on audio cassette • A digital logic probe that lets you visually examine computer circuits • The new Packard Bell VX88 computer with "intelligent" keyboard, 360K double-sided, double-density disk drive, 640K RAM, 16K ROM • 20 megabyte hard disk drive • Bundled software including MS-DOS, GW-BASIC, word processing, spreadsheet, and database programs • Packard Bell reference manuals with programming guidelines and schematics.

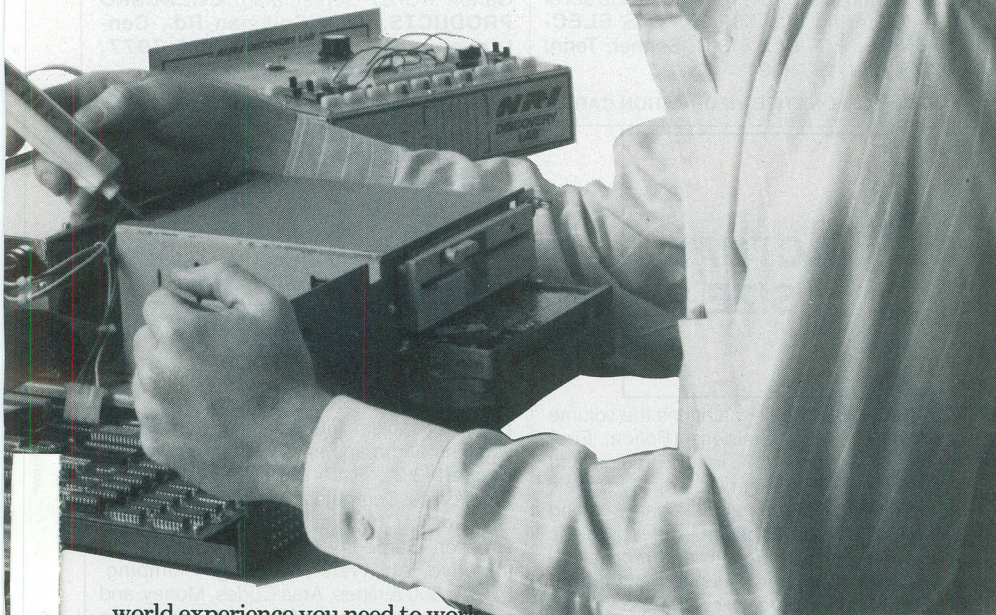

world experience you need to work with, troubleshoot, and service today's most widely used computer systems.

### New! Explore the Latest Advances in Voice Synthesis

Now NRI also includes innovative hands-on training in voice synthesis, one of today's most exciting and widely applied new developments in computer technology.

You now train with and keep a full-featured 8-bit D/A converter that attaches in-line with your computer's parallel printer port. Working with the exclusive text-to-speech software also included with your course, you explore the fascinating technology behind both digitized and synthesized computer speech.

NRI's new hands-on training in voice synthesis is just one more way you get the confidence-building experience you need to feel at home with the latest advances in computer technology.

# NEW!

## Includes 20 meg Hard Drive

prepared to take advantage of today's opportunities in computer service. You learn at your own convenience in your own home.

No classroom pressures, no night school, no need to quit your present job until you're ready to make your move. And all throughout your training, you've got the full support of your personal NRI instructor and the NRI technical staff, always ready to answer your questions and help you whenever you need it.


### FREE 100-Page Catalog Tells More

Send today for NRI's big, 100-page catalog that describes every aspect of NRI's innovative computer training, as well as hands-on training in other growing high-tech career fields. If the coupon is missing, write to: NRI School of Electronics, McGraw-Hill Continuing Education Center, 4401 Connecticut Avenue, NW, Washington, DC 20008.

**NRI** School of Electronics

McGraw-Hill Continuing Education Center  
4401 Connecticut Avenue, NW  
Washington, DC 20008

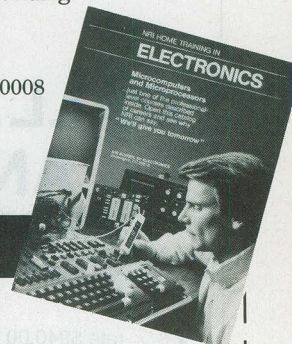IBM is a registered trademark of International Business Machines Corporation



### No Experience Needed, NRI Builds It In

This is the kind of practical, hands-on experience that makes you uniquely

### SEND TODAY FOR FREE CATALOG!

**NRI**

McGraw-Hill Continuing Education Center  
4401 Connecticut Avenue, NW, Washington, DC 20008

☒ CHECK ONE FREE CATALOG ONLY

- ☐ Computer Electronics
- ☐ TV/Video/Audio Servicing
- ☐ Robotics
- ☐ Electronic Music Technology
- ☐ Security Electronics
- ☐ Digital Electronics Servicing

- ☐ Telecommunications
- ☐ Industrial Electronics
- ☐ Electronic Circuit Design
- ☐ Basic Electronics
- ☐ Bookkeeping & Accounting
- ☐ Building Construction
- ☐ Automotive Servicing

- ☐ Air Conditioning, Heating, & Refrigeration
- ☐ Small Engine Repair
- ☐ Electrician
- ☐ Locksmithing
- ☐ Travel Careers
- ☐ Paralegal
- ☐ Computer Programming

Name (Please print)

Age

Street

City/State/Zip

We'll give you tomorrow.

Accredited Member National Home Study Council

10-010




# Radio-Electronics mini-ADS



**SIMPLY SNAP THE WAT-50 MINIATURE FM TRANSMITTER** on top of a 9v battery and hear every sound in an entire house up to 1 mile away! Adjustable from 70-130 MHZ. Use with any FM radio. Complete kit **\$29.95 + \$1.50 S + H**. Free shipping on 2 or more! COD add \$4. Call or send VISA, MC, MO. **DECO INDUSTRIES, Box 607, Bedford Hills, NY 10507. (914) 232-3878.**

CIRCLE 127 ON FREE INFORMATION CARD

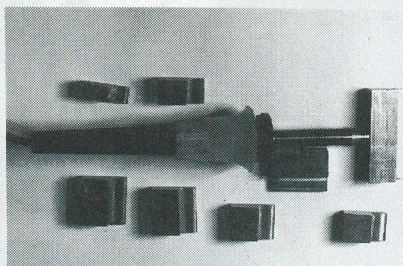


**REMOVE IC'S FASTER** with this simple invention than any other method, including \$6,000.00 vacuum desoldering stations. Salvages hundreds of good IC's per hour from junk boards, and also speeds up repairs. Won't damage IC's or circuit board. Removes 6 thru 40 pin IC's. This is a money making labor saving tool. Order now. Complete set of 8 desoldering bits **\$89.95. VRS ELECTRONICS, P.O. Box 813-R, Selmer, Tenn. 38375. (601) 287-1594.**

CIRCLE 183 ON FREE INFORMATION CARD



**GET YOUR RECHARGE CATALOG FREE...EARN BIG \$\$ IN YOUR SPARE TIME**—All supplies and Do-It-Yourself kits with complete instructions available. Supplies cost from **\$9.95** in qty and you can sell recharged toner cartridges for **\$40.00** to **\$55.00** each. Printers include HP LaserJet and Series II, Apple LaserWriter, QMS, etc. Canon PC-25 Copier also. **CHENESKO PRODUCTS, 62 N Coleman Rd., Centereach, NY 11720, 516-736-7977, 800-221-3516, Fax: 516-732-4650**


CIRCLE 190 ON FREE INFORMATION CARD

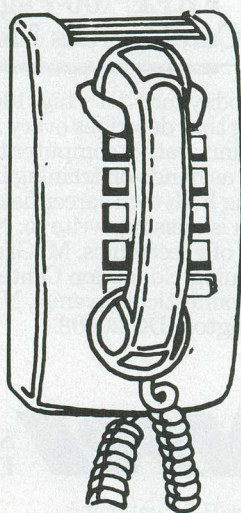

**ACTUAL SIZE**

The **REGEN-I** module maintains the volume level of amateur, business (Police, Fire, Power, Fleet, etc.), CB, marine radios and scanners. The **REGEN-I** will amplify signals and attenuate a strong audio signal keeping volume at a nearly constant level regardless of incoming signal strength and reduce un-squelched FM hiss. Simple installation. **\$49.95** phone orders OR **\$39.95** Pre-paid, mail orders only. **EMULATION ASSOCIATES, 520 GLENBROOK RD, STE 203-B, STAMFORD, CT 06906 SALES: 203-356-1632 FAX: 203-323-9044**

CIRCLE 192 ON FREE INFORMATION CARD

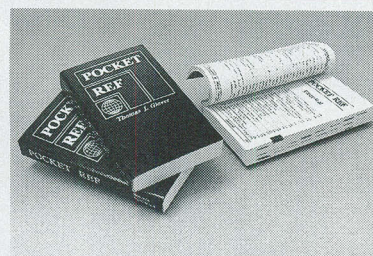

**AMAZING POCKET REFERENCE**.: 480 pages of tables, formulas, constants, conversions and maps and **it fits in your shirt pocket!** (3.2" x 5.4" x 0.6") Chapters include Electronics, Computers, Math, Tools, Glues & Solvents, Chemistry & Physics, Construction, Carpentry, Geology, Hardware, Automotive, Air, Water, Welding, Plumbing, Pipe, 1-800 Airlines, Area Codes, Money, and much, much more. **\$9.95 + \$2.00 shipping** (Colorado inc. 56¢ tax). Check/Visa/MC. **Sequoia Publishing, Inc., Dept. 951, P.O. Box 620820, Littleton, CO 80162.**

CIRCLE 179 ON FREE INFORMATION CARD

**CALL NOW AND RESERVE YOUR SPACE**


- 6 x rate \$940.00 per each insertion.
- Fast reader service cycle.
- Short lead time for the placement of ads.
- We typeset and layout the ad at no additional charge.

Call **516-293-3000** to reserve space. Ask for Arline Fishman. Limited number of pages available. Mail materials to: mini-ADS, RADIO-ELECTRONICS, 500-B Bi-County Blvd., Farmingdale, NY 11735.



**CABLE TV CONVERTERS AND DE-SCRAMBLERS SB-3 \$79.00 TRI-BI \$95.00 MLD-\$85.00 M35B \$89.00 JRX-DIC \$129.00** Special combos available. We ship COD. Quantity discounts. Call for pricing on other products. Dealers wanted. **FREE CATALOG.** We stand behind our products where others fail. One year warranty. **ACE PRODUCTS, P.O. Box 582, Saco, ME 04072 (207) 967-0726.**

CIRCLE 75 ON FREE INFORMATION CARD

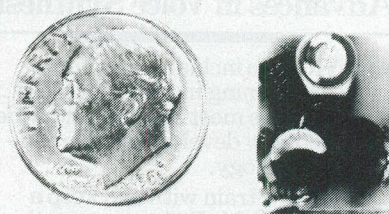

**THE MODEL WTT-20 IS ONLY THE SIZE OF A DIME**, yet transmits both sides of a telephone conversation to any FM radio with crystal clarity. Telephone line powered - never needs a battery! Up to 1/4 mile range. Adjustable from 70-130 MHZ. Complete kit **\$29.95 + \$1.50 S + H**. Free Shipping on 2 or more! COD add \$4. Call or send VISA, MC, MO. **DECO INDUSTRIES, Box 607, Bedford Hills, NY 10507. (914) 232-3878.**

CIRCLE 127 ON FREE INFORMATION CARD




# BUILD THIS

TEST EQUIPMENT HAS SURE COME A long way since the days of the bulky analog meter. The newest generation of portable test gear boasts features that would make technicians of a decade ago green with envy. Single instruments can measure everything; voltage, resistance, capacitance, logic levels, and even frequency. In fact, an entire test bench of equipment can now be packed away in a shirt pocket, and carried easily to the source of the trouble.

As good as those new meters are, they still have a few limitations that can be rather disconcerting at times. Frequency measurement is a good example; the highest range on most portable DMM-sized instruments is usually less than 1 MHz, and the 3-1/2–4-1/2 digit LED displays on most meters don't offer much resolution. It seems as if most manufacturers add frequency measurement as an afterthought. As newer designs hit the market, those shortcomings will improve. But why wait? You can build the frequency probe described here. It offers benchtop performance at a fraction of what you'd expect to pay.

The frequency probe is a unique combination of a logic probe and an 8-digit, 100-MHz frequency counter. It uses only three IC's,

## 100 MHz FREQUENCY PROBE

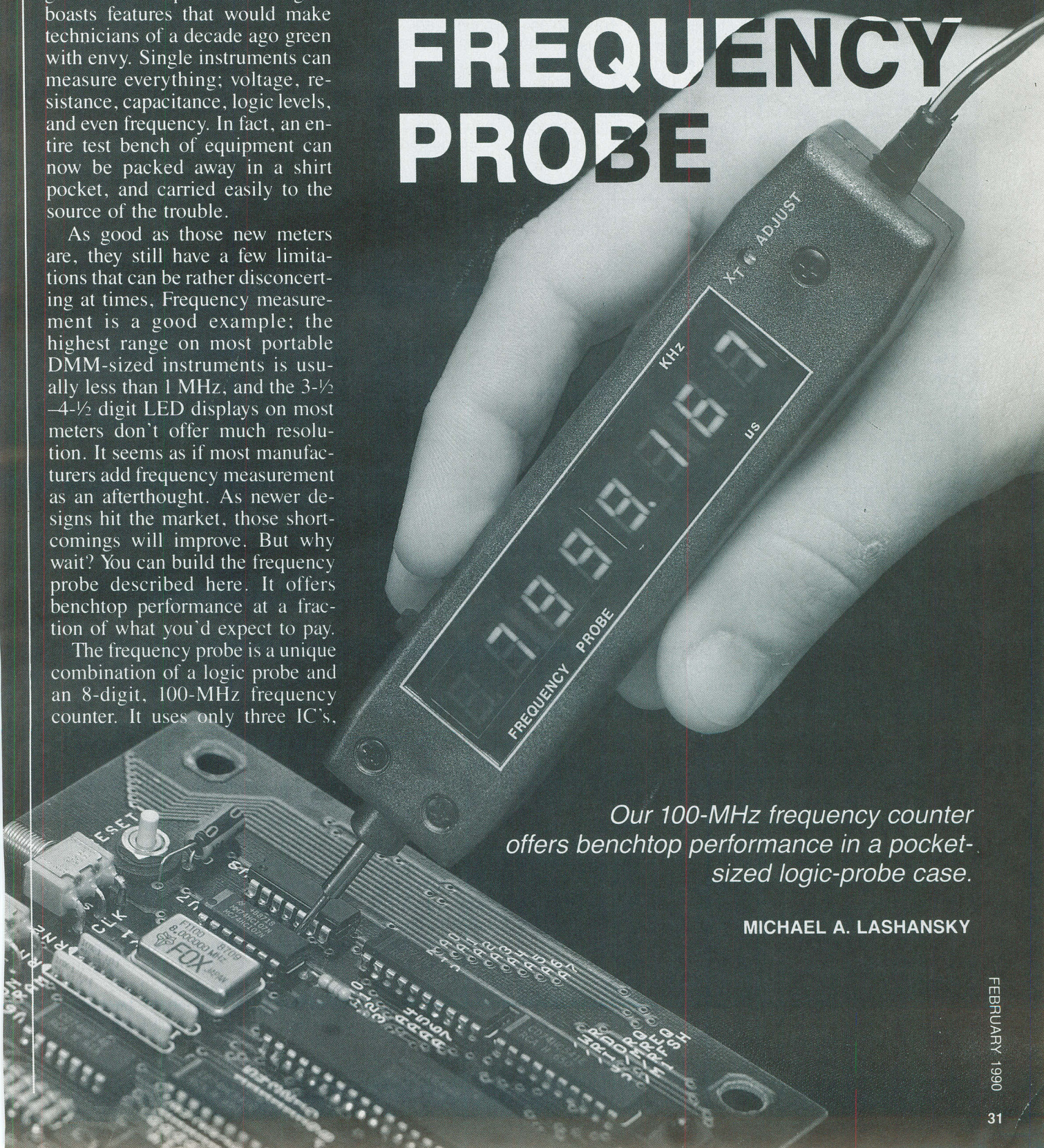

*Our 100-MHz frequency counter offers benchtop performance in a pocket-sized logic-probe case.*

MICHAEL A. LASHANSKY



TABLE 1—FREQUENCY PROBE SPECIFICATIONS

Parameter	Waveform Type	Condition	Performance (*)	
			Frequency	Period
Measurement Range	Any	Unmodified PC Board, XTAL1 is 1 MHz	00000.000—99999.999 X 1 kHz, 10-s gate	00000.500—99999.999 X 1 $\mu$ s, 10-s gate
		Modified PC Board (see text), XTAL1 is 1 MHz	000000.00—099999.99 X 1 kHz, 1-s gate	000000.50—099999.99 X 10 $\mu$ s, 1-s gate
		Unmodified PC Board, XTAL1 is 10 MHz	00000.000—0999.999 X 10 kHz, 1-s gate	00000.500—99999.999 X 10 $\mu$ s, 1-s gate
		Modified PC Board (see text), XTAL1 is 10 MHz	000000.00—009999.99 X 10 kHz, 0.1-s gate	000000.50—099999.99 X 1 $\mu$ s, 0.1-s gate
Input Sensitivity	Sinusoid	N/A	35 mV p-p	
	Square	N/A	50 mV p-p	
Maximum Period	Any	N/A	2 MHz	
Logic High	Any	N/A	3 VDC	
Logic Low	Any	N/A	1.8 VDC	
Supply Voltage	Any	N/A	4.5–15 VDC	
Maximum Current	Any	N/A	190 mA DC	
Input Impedance	Any	n/A	51 ohms	

(\*) NOTE: All leading zeros are suppressed during normal operation of the frequency probe for both frequency and period measurement, and are reproduced here merely for illustration.

and fits in a standard logic-probe case, modified for the purposes of the 8-digit LED display. Table 1 lists the probe's specifications. It features switchable AC/DC coupling and both frequency- and period-measurement capability. The builder of the probe can modify the useful frequency range by selecting a different crystal, and can also modify the gate time (or sampling time) by making a simple PC-board modification. The effects of the modifications are summarized in Table 1, and we'll discuss how they're made shortly.

The probe can be powered either by the circuit-under-test, or by connecting its leads to +9-volts DC.

Building the probe isn't difficult, but it requires care and patience, because the components are very tightly packed.

### Circuit operation

Figure 1 shows the block diagram of the frequency probe. The input can be AC- or DC-coupled to the divide-by-10 prescaler, whose output is fed to the main counter section and the LED display block. That counts the prescaler pulses, and includes the necessary logic for the 8-digit LED display. The logic block indicates with LED1 and LED2 which coupling mode is in use, and indicates logic levels.

The frequency-probe schematic is

shown in Fig. 2. S1 either DC-couples the input through R1, or AC-couples it through C1. The center pole of S1 goes to the clock-pulse input (CP) of IC1, a National Semiconductor 11C90 prescaler. The 11C90 is an ECL divide-by-10 prescaler, uses +5 volts, has TTL-output, and operates over a DC–650 MHz bandwidth with only an RF-bypass capacitor on  $V_{CC}$ . Input sensitivity for AC-coupling is 350 mV p-p from DC–100 MHz, and 250 mV p-p above 100 MHz. The frequency response of the 11C90 is shown in Fig. 3, but that's the guaranteed minimum, and actual performance can exceed it substantially. S2 is located between the frequency counter and the LED display, and selects between the frequency- and period-measurement modes.

Triggering is simplified in IC1 by connecting the reference terminal (pin 15) to clock pulse (pin 16). By doing so, the probe input is automatically centered about the input threshold. A 50% duty cycle gives the fastest operation, and since the flip-flops are master-slaves with offset input thresholds, there are no minimum frequency restrictions. That ensures that the circuit will operate with inputs with very slow rise and fall times. The 11C90 can divide-by-10 or -11 depending on the levels on pins 1 and 2 ( $M_1$  and  $M_2$ ). A logic low on those pins places the divider into divide-by-11 mode, while tying them high produces divide-by-10 mode. IC1 is enabled by tying pin 1 (CHIP ENABLE) and pin 14 (ASYNC MASTER SET) low.

There are two  $V_{EE}$  terminals (pins 12 and 13). The TTL output operates from the same  $V_{CC}$  and  $V_{EE}$  levels as the counter, but a separate pin is used for the TTL  $V_{EE}$ . That minimizes noise coupling when the TTL-output switches, and reduces power consumption by leaving pin 12 open when the ECL outputs are used. Because the IC operates linearly with the transistors always on, the current drawn can go up to 80 mA, with 35 mA typical. Thus, the IC's run pretty warm, but heat-sinking isn't needed.

The TTL-output of IC1 is pulled up to CMOS levels by R6 and connected to the clock input of IC2, an ICM7216B frequency counter. The 7216B has gating, timebase, latching, decoding, and 8-digit LED display-driver circuitry. In addition, the 7216B measures period, frequency ratios ( $f_A/f_B$ ), time intervals, or total



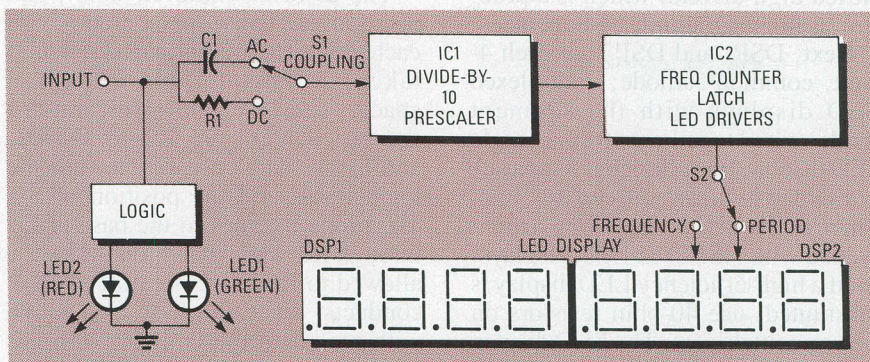


FIG. 1—FREQUENCY PROBE BLOCK DIAGRAM; the input is either AC- or DC-coupled to the divide-by-10 prescaler (IC1) then sent on to the counting (IC2) and LED display (DSP1 and DSP2) blocks.

counts. Due to limited space, only the frequency and period functions were used.

The 7216B has a 10-MHz crystal timebase, and accepts inputs up to 10-MHz, which are divided internally by  $10^5$ . Inputs are gated with that clock for a period determined by the RANGE INPUT (pin 14) setting, and passed to the main counter. The RANGE INPUT automatically adjusts the LED display

decimal place, and allows longer gate periods for lower frequency inputs. When prescalers like IC1 are used, XTAL1 should be scaled accordingly. Thus, the input was divided-by-10 using IC1 and a 1-MHz crystal. That multiplies the internal gate time by 10 (from the original range times), allowing 100-MHz measurements with 1-Hz resolution.

Also, the 7216B has 10-ms, 100-

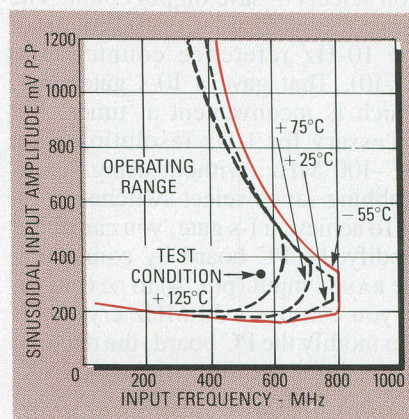


FIG. 3—SENSITIVITY OF IC1 AS A FUNCTION of sinusoidal input amplitude in mV p-p vs. frequency, for  $-55^{\circ}\text{C}$ ,  $25^{\circ}\text{C}$ ,  $75^{\circ}\text{C}$ , and  $125^{\circ}\text{C}$ .

ms, 1-s, and 10-s gate times. Selection of the gate time and decimal-point location is achieved by connecting the range input (pin 14) through R10 to digit-driver terminals D1-D4 (pins 4-7). The digit-drivers are time-multiplexed with the range, control, external decimal point, and func-

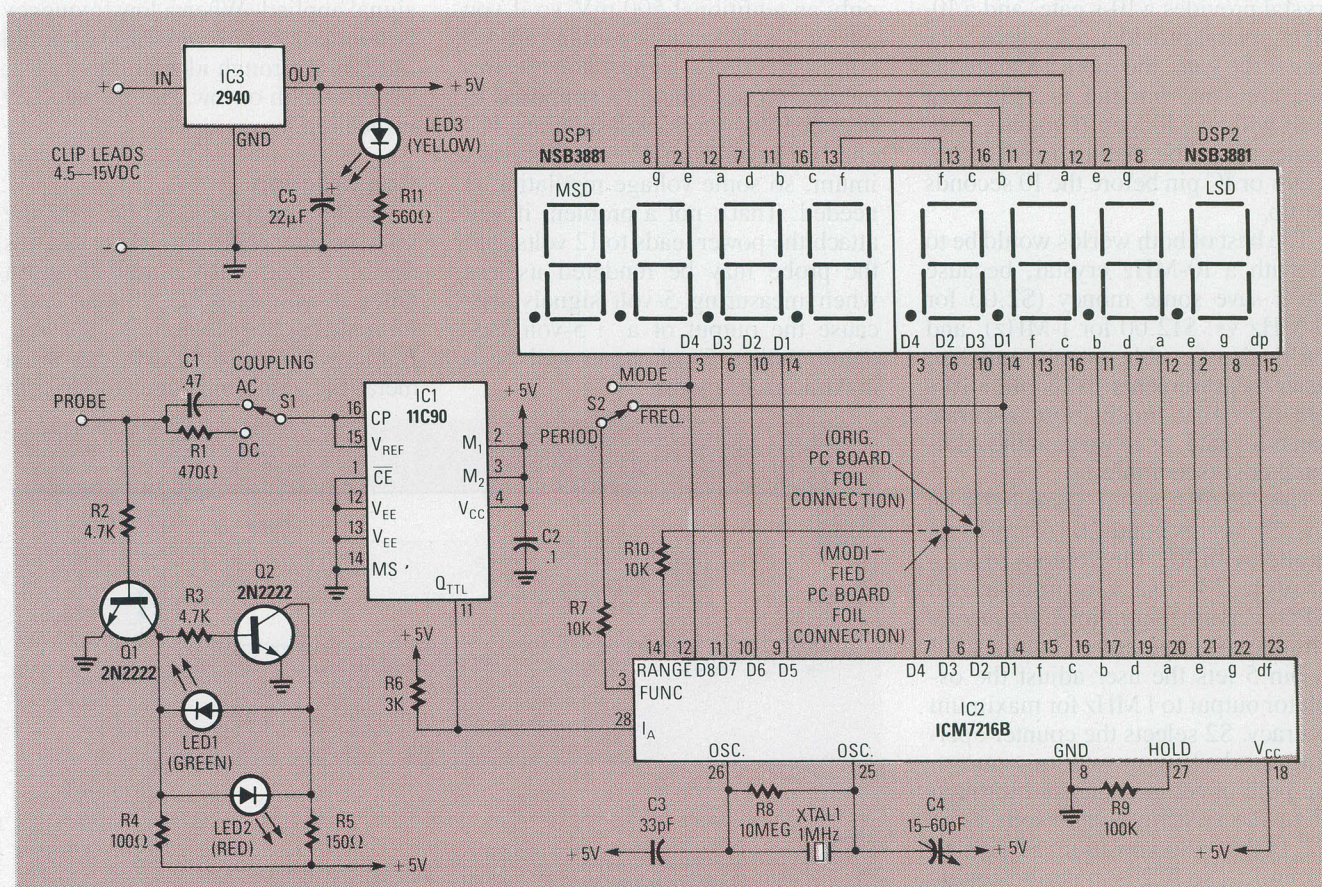


FIG. 2—SCHEMATIC DIAGRAM FOR THE FREQUENCY PROBE. Note the dotted line connecting R10 with pins 5 or 6 of IC2; that variable connection controls the decimal point and total count appearing on DSP1 and DSP2. The relative intensities and durations of ON/OFF time for LED1 (green) and LED2 (red) give a rough indication of logic level and duty cycle.



tion selects to save on pin count. The range was fixed at 1 s, or 100 counts of the 10-Hz reference counter (100 Hz/10). That gave a 10-s gate time, which is inconvenient at times, but necessary for 1-Hz resolution from DC–100 MHz, without using space-grabbing range-select switches.

To achieve a 1-s gate, you can either modify the PC board by connecting the RANGE input (pin 14) to D2 (pin 6), or you can use a 10-MHz crystal. If you modify the PC board, the decimal place shifts one digit right (XXXX-XX.XX instead of XXXXX.XXX), and the least-significant digit means 10 Hz, not 1 Hz. The interpretation of the display remains as multiples of 1 kHz, but the absolute range of the probe increases from 10 MHz to 100 MHz. To do that, cut the foil on the component side from pin 5 of IC2, and solder a jumper from the foil side to pin 6.

If you change the crystal frequency, the decimal place stays unchanged (XXXXXX.XXX before and after); the LED display value reads in multiples of 10 kHz instead of 1 kHz. A 1-MHz crystal provides a 10-s gate, and a 10-MHz crystal provides a 1-s gate. The longer the gate, the more accurate the measurement, but the measurement itself will take longer. If you use a 10-s gate, the probe might slip off a connector or IC pin before the 10 seconds are up.

The best of both worlds would be to go with a 10-MHz crystal, because you'll save some money (\$2.00 for 10-MHz vs. \$12.00 for 1-MHz), and you'll also be able to take quicker, easier measurements. After all, a 10-s gate isn't that much more accurate than a 1-s gate, as to warrant the additional cost (see Table 1).

The 7216B crystal goes between pins 25 (OSC IN) and 26 (OSC OUT) in parallel with R8. Pin 26 goes to  $V_{CC}$  through C3; use a nonpolarized (NPO) version to minimize frequency drift due to temperature. Trimmer C4 on pin 5 lets the user adjust the oscillator output to 1 MHz for maximum accuracy. S2 selects the counter operating mode (FREQUENCY OR PERIOD). The pole of S2 is connected through R7 to the FUNCTION INPUT (pin 3) of IC2. In the PERIOD position, S2 goes to D8 (pin 12), so IC2 is in period counting mode. In FREQUENCY position, S2 is connected to D1 (pin 4). Also, R7 and R8 prevent false triggering due to AC-coupled signals from the multi-

plexed digit drivers, which is a problem at higher multiplex frequencies.

Next, DSP1 and DSP2 are each 4-digit, common-cathode, multiplexed LED displays with the segment anodes wired together to form a single LED display. Each digit has a separate cathode which is sourced by IC2. Current-limiting resistors aren't needed with NSB3881 LED displays, but if a high-efficiency LED display is substituted, use 40-ohm resistors on the segment drivers. The LED display multiplex rate is directly related to the crystal frequency. For a 10-MHz crystal, the multiplex rate of the LED display is 500 Hz; the 1-MHz crystal yielded a 50-Hz rate. As was shown in Fig. 2, pin 28 (HOLD) is grounded through R9, which pulls pin 28 low, and allows the internal counter contents to be displayed after each measurement cycle.

Power is supplied by IC3, a National Semiconductor 2940 low-voltage dropout +5-volt regulator. Ordinary voltage regulators need an input voltage at least 2 volts above the desired output. The 2940, however, needs only an additional 500 mV, so if you put in 5 volts you're guaranteed 4.5 volts out. That's a must for the frequency probe, since it's supposed to operate from 4.5–15 volt supplies. IC1 and IC2 need from 4.5–6 volts maximum, so some voltage regulation is needed. That's not a problem if you attach the power leads to 12 volts, but the probe may be rendered useless when measuring 5-volt signals, because the output of a +5-volt regulator with a 5-volt input will be a maximum of 3 volts.

The 2940 is, however, noisy, and needs a filter capacitor, sometimes on each side. The output capacitor (C3) takes up considerable PC-board space. The level-indicating circuit composed of Q1, Q2, R2–R5, LED1, and LED2, is a easy way to indicate logic levels and the position of S1. The probe tip goes to the base of Q1 through R2, and when brought low or allowed to float, Q1 is cutoff and Q2 conducts, since the base is positive with regard to the emitter. With Q2 conducting, LED1 should light. Touching the probe to a logic high makes Q1 and Q2 complement states (Q1 conducting and Q2 cutoff), and LED2 should light.

That feature indicates the position of S1 since, in DC-coupled mode, the reference voltage of IC1 is coupled through R1 and R2 to the base of Q1. That's about 3 volts (a logic high), so LED2 should light. In AC-coupled mode, no DC voltage from IC1 is passed to the base of Q1, and it's allowed to float (a logic low), so LED1 lights. That's a useful way of visually checking the coupling mode with no signal applied. When a low frequency is applied, LED1 and LED2 should light, and a rough idea of duty cycle, whether high or low, can be made by inspection.

### Construction

You should use the PC board in the kit (see the parts list), because it's double-sided with plated-through holes. If you wish to etch your own, foil patterns are given in PC Service. Before soldering the PC board, use a metal file along the edges to get it to

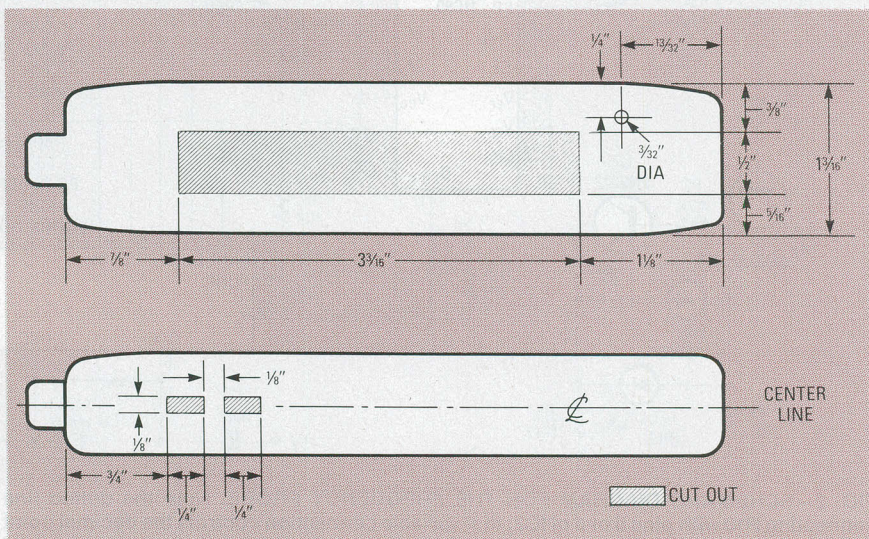


FIG. 4—THE FREQUENCY PROBE CASE. Cutout dimensions for DSP1, DSP2, and C4 are shown in (a). Cutout dimensions for S1 and S2 are shown in (b).



## PARTS LIST

All resistors are 1/8-watt, 5%, unless otherwise indicated.

R1—470 ohms, 1/4-watt  
R2, R3—4700 ohms  
R4—100 ohms, 1/4-watt  
R5—150 ohms, 1/4-watt  
R6—3000 ohms  
R7, R10—10,000 ohms  
R8—10 Megohms, 1/4-watt  
R9—100,000 ohms  
R11—560 ohms, 1/4-watt

### Capacitors

C1—0.47  $\mu$ F, ceramic  
C2—0.1  $\mu$ F, ceramic  
C3—33 pF, nonpolarized (NPO) ceramic  
C4—15–60 pF trimmer (Active Components # 17016)  
C5—22  $\mu$ F, tantalum

### Semiconductors

IC1—11C90 National Semiconductor 650-MHz, divide-by-10 prescaler  
IC2—ICM7216B Intersil 8-digit, frequency counter/timer  
IC3—2940 National Semiconductor +5-volt regulator

Q1, Q2—2N2222 NPN transistor  
DSP1, DSP2—NSB3881 National Semiconductor 4-digit, 7-segment LED display

LED1—green light-emitting diode (miniature)

LED2—red light-emitting diode (miniature)

LED3—yellow light-emitting diode (miniature)

### Other components

XTAL1—1- or 10-MHz crystal (case size HC49)

S1, S2—SPDT switch (Active Components # 22196)

**Miscellaneous:** Logic-probe case with probe tip and clip leads (Global Industries # CPT-1), solder, wire, etc.

**NOTE:** A complete kit of parts, logic-probe case, and carrying case is available for \$139.95 U.S. or \$159.95 Canadian from Tristat Electronics, 66A Brockington Crescent, Nepean, Ontario, Canada K2G 5L1, (613) 225-9883. The kit without the PC board is \$117.95 U.S. or \$137.95 Canadian (Visa orders welcome). The PC board alone is \$22.00 U.S. or \$25.00 Canadian. All orders require \$6.00 for shipping and handling. The sources for certain components are Active Components, 1023 Merival Road, Ottawa, Ontario, Canada K1Z 6A6, (613) 728-7900, and Electrosonic, 1100 Gordon Baker Road, Willowdale, Ontario, Canada M2H 3B3, (416) 494-1555.

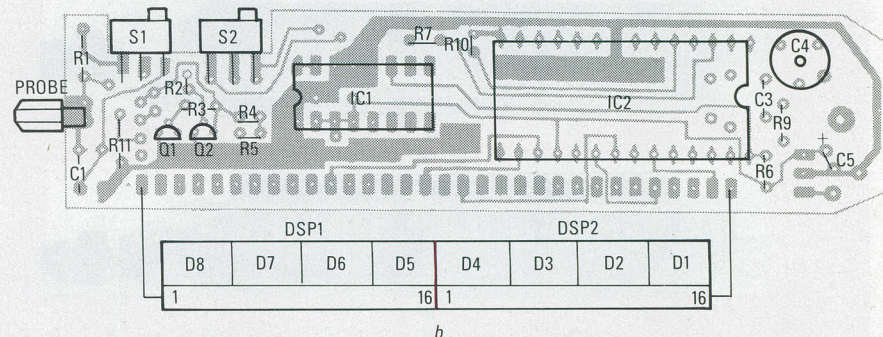
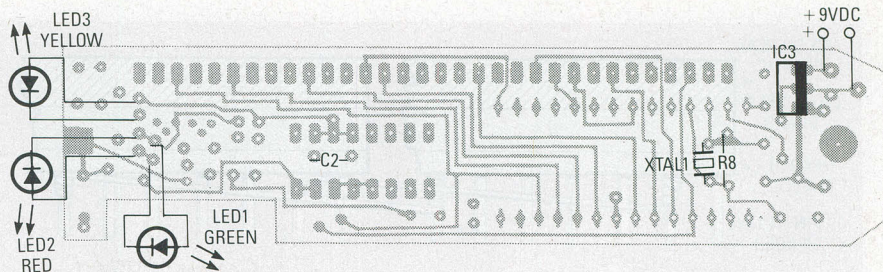


FIG. 5—THE PARTS-PLACEMENT DIAGRAM for the frequency probe, showing the foil (a) and component (b) sides. In (a), both IC3 and XTAL1 are bent flat.

fit in the case. If you're using the case in the parts list, clip the four plastic standoffs extending from the top with a pair of wire cutters as close to the base as possible. Next, cut the openings for the LED display and switches in the case as shown in Figs. 4-a and b. The case is polyethylene, so it can be cut initially with an X-acto knife, and finished with a jeweler's file or emery board.

Solder S1 and S2 first; clip the leads so their length is identical to that of the pads. Next, place each on top of its pads, and secure with solder, tweezers, or tape. Solder the three terminals to the pads, and repeat for the other switch. The bodies of S1 and S2 should fit snugly into the recess in the PC board, and the fronts of both switches should line up with the edge of the PC board. Then, solder all parts except IC3 and LED1–LED3, which go on the foil side. When soldering a component on a two-sided PC board without plated-through holes, you must solder the leads on both sides of the board. You must also solder short pieces of wire through any holes that do not have component leads going through them. Mount C2 on the foil side, leaving a slight space. Solder the leads as they go through the component side, clip as close as possible,

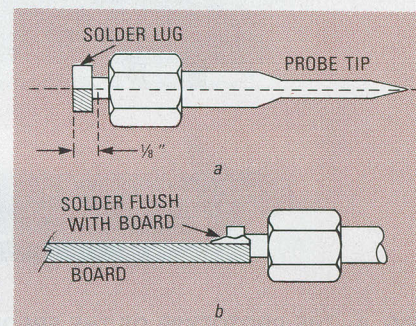


FIG. 6—TO MOUNT THE LOGIC PROBE TIP onto the frequency probe PC board, file 1/8-inch of the bottom of the hex-nut-shaped solder lug flat down to the centerline of the logic probe tip. Then, solder it flush to the correct pad on the component side of the PC board.

and inspect for poor solder joints. Care here will go a long way to having the probe work on power-up.

Next, install XTAL1; it lies flat along the PC board surface, so bend the leads at a 90° angle as close to the crystal housing as possible. Use heat-shrink tubing or electrical tape to insulate the housing against the foils. Next, solder R8, IC1, and IC2, inserting from the component side, and solder all the pins on the foil side. Solder the rest of the component-side components, paying attention to the parts-placement diagram of Fig. 5-a and b. Also, R2–R7 and R10 are mounted



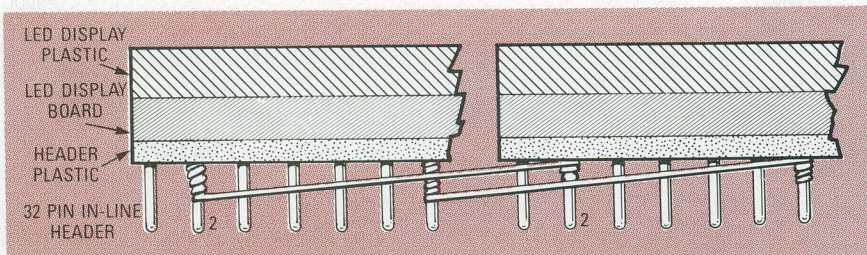


FIG. 7—YOU MUST CONNECT pins 2, 7, 8, 11, 12, 13, and 16 of DSP1 to the corresponding pins of DSP2 using wirewrap.

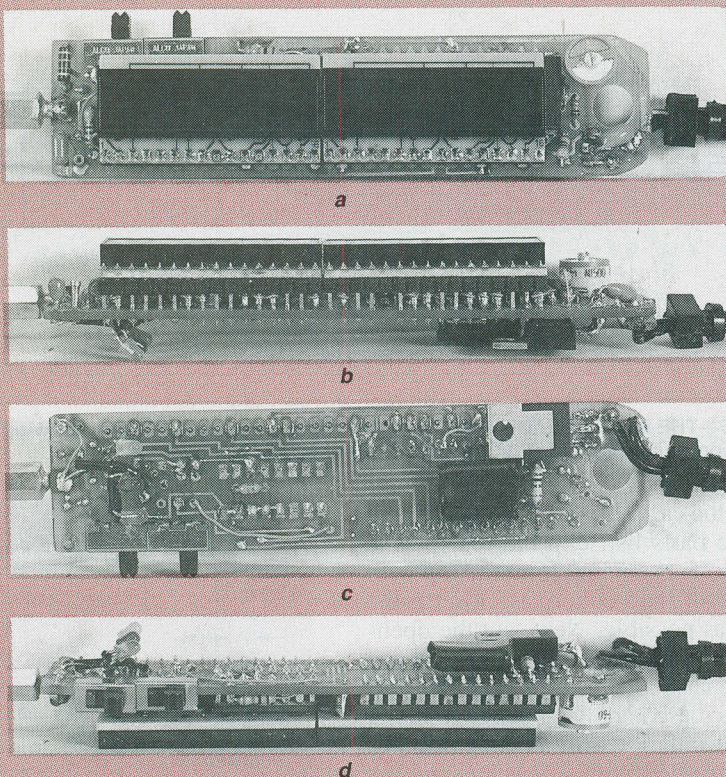


FIG. 8—THE PROTOTYPE OF THE FREQUENCY PROBE; note the callouts. Views are shown from the component side (a), edge-on showing the header strip for DSP1 and DSP2 (b), from the foil side (c), and edge-on showing C4, IC2, IC1, S1 and S2, from left to right (d).

vertically, and R1, R9, and R11 horizontally on the PC board.

The foil layout for C4 should accept different size trimmers, but they shouldn't exceed 0.5-inch in height or diameter. Strip 1 inch of insulation from the leads of the alligator clips. Solder the white stripped lead to the positive pad on the foil side, and the black lead to the negative pad. The probe tip should be 0.125 inch down to its center line as shown in Fig. 6-a, and soldered flush to the component side as shown in Fig. 6-b. Once the probe is soldered, let it sit for awhile because it'll get pretty hot.

The 8-digit LED display is composed of two National Semiconductor NSB3881 4-digit displays DSP1 and DSP2, and their segment anodes have

to be wired together to form one complete display. Insert a 32-pin, single in-line male header through the underside of the LED display boards (LED side up), so that the LED display sits on the header insulation strip. Solder the LED display to the header from the top; don't apply excessive heat, or the LED display pads may lift. Using wirewrap or fine insulated wire, connect the pins of DSP1 indicated in Fig. 7 to the corresponding pins of DSP2.

If you use wirewrap, use 4–5 turns because you'll need to leave about 1/4-inch of header pin bare to insert into the PC board. Wirewrap is recommended, and once the pin has been wrapped, a little solder will ensure that the connection is sound. Once

DSP1 and DSP2 are wired correctly, insert the header into the PC board until the back of the LED display board touches the top of IC1 and IC2, and solder the header in place.

Fig. 8 shows the prototype from several perspectives, with component callouts. Fig. 8-a was taken from above and shows DSP1, DSP2, and the component side of the PC board, Fig. 8-b from the side of the header for DSP1 and DSP2, Fig. 8-c shows the PC board from the foil side, and Fig. 8-d shows the fronts of S1 and S2. The completed PC board fits very tightly in the PC board case, so there are several specific actions to take to ensure proper operation. Just note that there are several minor differences between the prototype and the plans we're giving you, so don't worry if you see something in the photos that does not agree with the plans.

### Checkout and calibration

To check out the probe, connect the alligator clips to a 9-volt battery; the LED display should read 0.000 if it works. If not, use a meter to check voltages. Look for +5 volts on pin 3 of IC3; if it's not +5 volts, the display might be upside down. If it keeps changing, or segments flicker on and off, there's probably a cold joint. If you lightly flex the PC board, you'll usually find the trouble. If the LED display reads 0.000, you can calibrate the probe.


Connect a 500-Hz signal to the probe tip, and adjust C4 until the LED display reads correctly. Aim for maximum accuracy at the low end, because errors there will be substantial, compared to signals at 50 MHz or more. Next, try different frequency signals, and adjust C4 until satisfied. You don't need a function generator to check high-end operation; the average household has sources of suitable high-frequency test signals. Two examples used on the prototype were a Fisher-Price remote infant monitor (50 MHz), and an R/C model-car transmitter (72 MHz). To do that, just connect the clips to 9-volts DC, hold the probe nearby, and read the LED display.

The frequency probe can be used for RF, but is primarily for high-frequency logic circuits. When measuring a signal, use the second or later gating for best accuracy. Once you've gained experience with the probe, you'll be surprised by its simplicity. **R-E**



# BUILD THIS

## RADAR DETECTOR TESTER

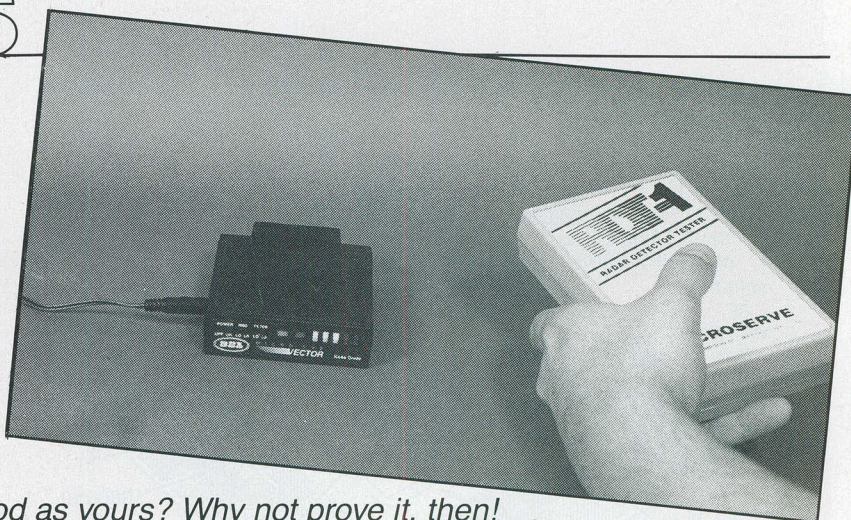

*Is your friend's radar detector as good as yours? Why not prove it, then!*


JOHN B. AYER

HAVE YOU EVER WONDERED HOW SENSITIVE your radar detector is? Or have you ever had someone tell you that their detector was better than yours? Until now, the average radar-detector owner had no way to prove or disprove any claims made by the manufacturers concerning the performance of the various detectors on the market.

The radar-detector tester pictured in this article is an easy-to-build, low-power X- or K-band radar transmitter. With the device's low-level emissions, you do not need a license to use it. The average detection range is 12 feet, which is more than enough to determine the sensitivity of your radar detector. You can then do a side-by-side test with your friend who's been telling you his detector is better!

### Operation

The heart of the circuit (see Fig. 1) is a one-transistor oscillator that operates at a fundamental frequency of 1169.44 MHz. The 9th harmonic of

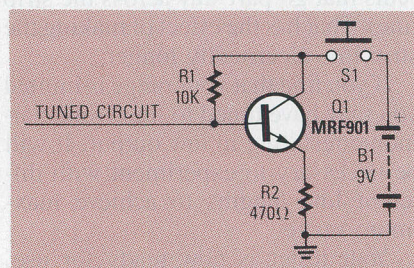

**FIG. 1—THE HEART OF THE X-BAND UNIT** is a one-transistor oscillator that operates at a fundamental frequency of 1169.44 MHz; the 9th harmonic of that frequency is 10.525 GHz, which happens to be the center of the X-band police radar assignment.

that frequency is 10.525 GHz, which happens to be the center of the X-band police radar assignment. The K-band unit operates at a fundamental of 1857.7 MHz with the 13th harmonic falling at 24.150 GHz. As you probably have guessed, 24.150 GHz is right in the center of the K-band police radar assignment.

The oscillator uses a microwave transistor in order to maximize the X- or K-band output. The fundamental frequency is determined by the tuned circuit that is attached to the base of the transistor. The tuned circuit consists of a 50-ohm strip line that is etched onto a PC board, and then cut to the proper length during the tuning procedure.

The printed circuit board is made out of double-sided copper-clad teflon with fiberglass reinforcement. The teflon is necessary because of the high frequencies involved (standard G-10 epoxy printed circuit boards act like short circuits at frequencies above 3 GHz). Although teflon sounds exotic, it isn't, and it is readily available from the suppliers listed in the parts list.

Some people may not be familiar with strip-line circuitry. Any line that is etched on one side of a double-sided PC board will have inductance along its length and capacitance through the dielectric (the fiberglass, teflon, etc.) to the ground plane (the copper plating on the other side of the board). In a properly designed strip line, the inductance and capacitance cancel each other leaving the designer with just a resistive impedance to wor-

ry about. As it turns out, the width of the line and the thickness of the dielectric determine the resistive impedance.

In this particular case, it was determined that 50 ohms was the optimum impedance. After deciding which PC-board material would be best suited for this project, the following equation was used to determine the width of the strip line needed:

$$Z_o = (87/\sqrt{E_r + 1.41}) \times L_n[5.98H/(T + .8W)],$$

$Z_o$  = characteristic impedance (50 ohms)

$E_r$  = dielectric constant (2.48)

$L_n$  = natural logarithm

$H$  = thickness of dielectric (0.0156 inches)

$W$  = width of line (0.038 inches)


$T$  = thickness of copper cladding (0.0004 inches)

Once the width of the line is determined, all that's needed to finish the job is to determine the length of the line for the target frequency. (The oscillator is similar to a pipe organ where the length and diameter of a pipe determines the tone that is produced; the length of the strip line determines the resonant frequency.)

### Construction

Etch the circuit board using the pattern provided in PC Service; a ready-made board is also available. The transistor has four leads; two are connected to the emitter, and you must determine which they are. Use an ohmmeter if you are not sure. (The



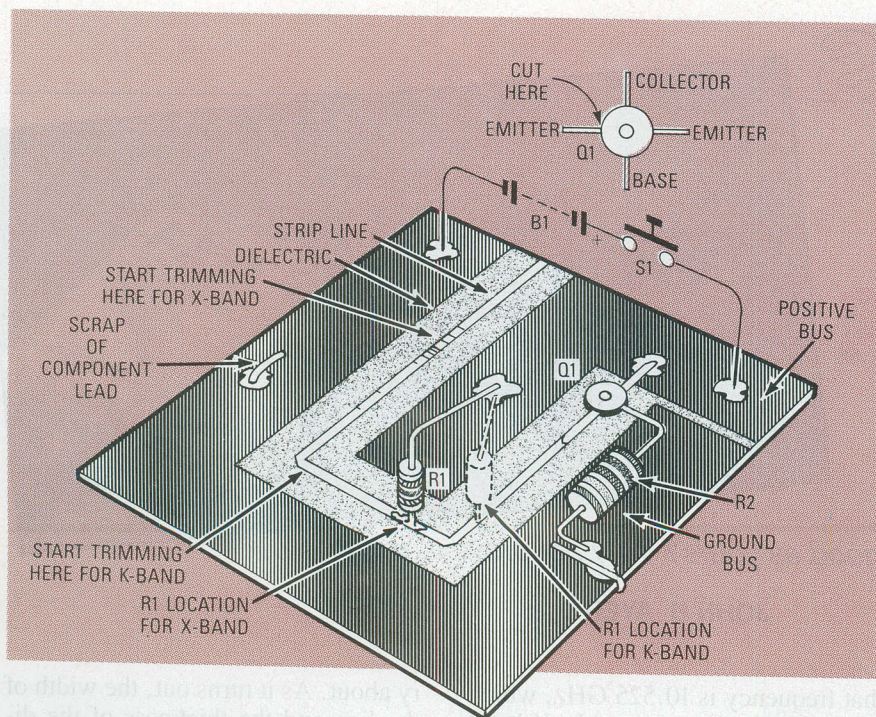

**FIG. 2—PARTS-PLACEMENT DIAGRAM.** Resistor R1 must be in a different location, depending on whether you're building an X- or K-band unit. Also, when aligning the unit, the strip line must be cut in a different location depending on the type of unit.

emitter leads are the only two that will exhibit a dead short from one to the other.) Cut off the left-hand emitter lead, as shown in Fig. 2.


After removing the extra lead, place the transistor in the hole on the board so that the base lead is on the strip line and the collector lead is on the positive bus, and solder them in place (see Fig. 2). Place R2 on the board and, keeping both leads as short as possible, solder one of its leads to the remaining emitter lead of Q1. The other resistor lead should go through the hole in the PC board, and soldered on both sides (a through hole, if you will). A scrap piece of component lead must go through the other hole on the left side of the board, and also soldered on both sides (another through hole).

Cut one lead of R1 so that it's  $\frac{1}{8}$ -inch long. Refer to Fig. 2 for proper placement of R1 for either the X or K band. Then solder the shortened lead of R1 to the strip line so that the resistor is standing on end. The longer lead of the resistor should then be soldered to the positive bus of the PC board (see Fig. 2).

Using a silicone adhesive, glue the PC board into the enclosure that you have selected. **DO NOT** use a metal enclosure. The microwaves need to escape from the box, and you will

defeat the entire project by using a metal box. Be sure to orient R1 so that it's closest to the front of the box, because most of the radiation is emitted from that point.

Attach the battery and switch as shown in Fig. 2, being careful not to reverse the polarity. Route wires away from the strip line and components, because stray wires can de-tune the oscillator. Construction is now complete and you are ready to tune the transmitter (see Fig. 3).

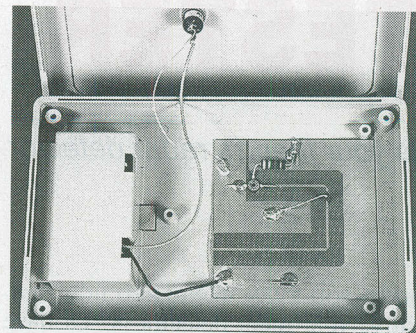

**FIG. 3—GLUE THE PC BOARD** into the plastic enclosure using a silicone-type adhesive.

### PARTS LIST

- R1—10,000 ohms,  $\frac{1}{4}$ -watt resistor
- R2—470 ohms,  $\frac{1}{2}$ -watt resistor
- Q1—MRF-901 Motorola transistor for X band, or NE68137 California Eastern Laboratories transistor for K band.
- B1—9-volt battery
- S1—push-button switch
- PC-board material—6 × 6-inch piece of 0.0158-inch thick teflon-fiberglass (Taconic Plastics, part number TLT-9-0150-C1/C1)

Plastic project case

**Note: A complete parts kit is available from MICROSERVE, 60 Thompson Street, Maynard, MA 01754. Besides the parts, the kit also includes a custom plastic enclosure with an integrated battery holder and decorative face plate. X-band kits are \$55, and K-band kits are \$65. Shipping and tax extra. Spare parts list available on request.**

**Motorola Semiconductor Products**

3102 N 56th St.  
Phoenix, AZ 85018  
602-952-3000 or 800-521-6274

**California Eastern Laboratories**

3260 Jay St.  
Santa Clara, CA 95054  
408-988-3500

**Taconic Plastics LTD.**  
Petersburg, NY 12138  
518-658-3202

### Alignment

To align the unit, you will need a radar detector and an X-acto knife with a fine blade. Turn on the radar detector and the tester. Now make an initial cut in the strip line starting at the point specified in Fig. 2 for either the X- or K-band unit. Be sure to cut all the way across and through the copper trace. If your detector does not sound an alarm, make another cut about  $\frac{1}{16}$ -inch closer to the transistor. At some point your detector will sound an alarm, and the tester will be properly tuned. Be careful not to cut too much at one time, because if you go too far you will have to carefully solder the line back together.

However, if you go just a *little* too far, you can save some work by cutting nicks in the remaining strip line (cuts that go part way across the strip line). That has the effect of making the strip line electrically longer.

If you find that your range is limited you may have tuned to the wrong harmonic resulting in low output. It will be necessary to experiment with different line lengths to achieve maximum range.

Your tester is now ready for use. Simply hold the unit near a detector and turn it on. The range of the X-band transmitter is about 12 feet, while the range for the K-band unit is about 5 to 10 feet.

R-E



# BUILD THIS

## ACOUSTIC FIELD GENERATOR

*Our AFG will turn any livingroom into a full-sized movie theater or concert hall.*

LAST TIME WE DISCUSSED THE AFG'S CIRCUITRY. So, by now, you must be anxious to experience its special sound effects. Without further ado, let's continue with complete construction details.

### Construction

All of the electronic components are mounted on a single PC board as shown in Fig. 9. The board can be made using the foil pattern provided in PC Service or purchased from the source mentioned in the parts list. Only the power transformer, the input and output jacks, and the function switches are mounted off-board.

The chassis shown is readily available, but it makes for a rather tight fit. If you plan to use a similar chassis, study the pictures of the prototype carefully before drilling. If you choose a different chassis, keep all the leads between jacks, switches, and the circuit board as short as possible. Locate the power transformer as far away from the circuit board as possible to avoid 60-Hz hum. If you must mount the transformer near the circuit board, wait until your unit is operational before you choose a final position for the transformer. Then, while listening, you can try the transformer in different positions until you find a location where no hum is coupled into the circuit.

Begin stuffing the board by mounting all of the fixed resistors and the small potentiometers. Note that R35 and R69 are mounted upright. Next mount the IC sockets. Position each socket's pin 1 identifier so that it matches the small dot indicating pin 1 on the circuit board (do not insert the IC's into their sockets at this time).

Next mount the capacitors. Please note where polyester and metal-film capacitors are called for in the parts list. *Do not* substitute ceramic capacitors; they perform poorly in audio circuits and their use will destroy the performance of the AFG. Also, don't substitute polarized electrolytic capacitors where bi-polar units are specified in the parts list.

Using some of the excess leads clipped from the capacitors, install bare jumpers where indicated, except for the six long jumpers. The two long jumpers in the audio power amplifier should be made from insulated heavy-gauge wire, as they carry relatively high current—no. 18 will do. The other four long jumpers in the decoder section should be made from lighter gauge insulated hookup wire.

Finish stuffing the circuit board by installing D1, D2, IC7-IC10, and the three large potentiometers, R77, R78, and R79. You can plug in the IC's now, but you should take static-electricity precautions with them.

Finish up the wiring between the PC-board pads and the switches, the input/output jack panel, the speaker terminal jacks, the power transformer, and the pilot LED. Use shielded cables for the leads to the input/output jacks. Try to keep all wiring as short and direct as possible to avoid crosstalk and hum. Use no. 18 or heavier wire for the speaker connections. To simplify construction, the prototype used inline fuse holders in the positive speaker leads and the power transformer primary circuit, as indicated in the schematics.

The power-supply regulator IC's are being operated very con-

servatively and thus do not require heat sinks. However, the LM1875T audio power amplifiers must *always* be operated with a heat sink. Failure to use a proper heat sink will cause the IC's to quickly overheat and possibly destroy themselves. Although they contain on-board circuitry to shut them down in case of overheating under normal operating conditions, it is best to leave fate untempted and refrain from operating the AFG until after the heat sink has been installed.

The heat sink used on the prototype was homemade from a 2- × 2- × 1/16-inch thick piece of aluminum angle stock cut 5 1/4-inches long and notched out in the front to fit over R77. If you use a commercially made heat sink, be sure that it provides about 8 to 10 square inches of surface area for each IC. Assuming that you are using a homemade heat sink like the one shown, temporarily position it so that the bottom edge is even with the bottom of the IC cases, or about 3/8" above the circuit board. Be sure that it does not touch D1. Mark the heat sink where the holes in the IC tabs fall and drill mounting holes at those points. In order to provide additional support, holes were also added at the top corners of the heat sink in line with the PC-board mounting holes. 3-inch screws with double sets of nuts were then used to mount the PC board as well as to hold the heat sink in place. Carefully examine the photographs that are shown in Fig. 10 to see how that was accomplished.

Because the metal tab of the LM1875T is not at ground potential,





## PARTS LIST

### All resistors 1/4-watt, 5%, except as noted.

R1—1500 ohms  
 R2, R3, R54—22,000 ohms  
 R4, R5, R32, R33—1000 ohms  
 R6, R7, R61, R62, R74—20,000 ohms  
 R8, R9—1 ohm, 1/2-watt, 5%  
 R10—R13, R19, R34, R35—47,000 ohms  
 R14—R17, R20—R25, R47—R49, R55, R56—100,000 ohms  
 R18, R57—330,000 ohms  
 R26—R31, R66, R70—150 ohms  
 R36—R43, R67—8060 ohms, 1%  
 R44—R46—16,000 ohms  
 R50, R51—5600 ohms  
 R52—2400 ohms  
 R53—8200 ohms  
 R58—R60, R63—R65, R71—R73—10,000 ohms  
 R68—9530 ohms, 1/4-watt, 1%  
 R69—102,000 ohms, 1/4-watt, 1%  
 R75, R80—100,000 ohms, potentiometer  
 R76—10,000 ohms, potentiometer  
 R77—50,000 ohms, PC-mount potentiometer  
 R78, R79—1000 ohms, PC-mount potentiometer

### Capacitors

C1—C4—2200  $\mu$ F, 25 volts, electrolytic  
 C5, C6—10  $\mu$ F, 35 volts, radial electrolytic  
 C7—C12, C19—C22, C27, C28, C30, C31, C45, C49, C58—0.1  $\mu$ F, 50 volts, metal film  
 C13, C14, C23, C24, C43—2.2  $\mu$ F, 50 volts, bi-polar radial electrolytic  
 C15, C16—22  $\mu$ F, 16 volts, bi-polar radial electrolytic  
 C17, C18—0.22  $\mu$ F, metal film  
 C25, C26—0.047  $\mu$ F, metal film  
 C32—C34—3300 pF, polyester  
 C36, C37—2700 pF, polyester  
 C38—C41—270 pF, 5% ceramic disc  
 C42, C47—0.47  $\mu$ F, metal film  
 C44—120 pF, 5% ceramic disc  
 C46—0.56  $\mu$ F, metal film

C48—0.039  $\mu$ F, metal film  
 C50—0.012  $\mu$ F, metal film  
 C51, C56—0.01  $\mu$ F, metal film  
 C52—1000 pF, 5% polyester  
 C53—C55—0.027  $\mu$ F, metal film  
 C57—5600 pF, 5% polyester  
 C58—4700 pF, 5% polyester  
 C59—470 pF, 5% ceramic disc

### Semiconductors

D1, D2—1N5400 50 PIV 3-amp diode  
 IC1—IC4—LF347 quad JFET  
 IC5—MN3008 2048-stage bucket brigade device  
 IC6—MN3101 2-phase clock  
 IC7—7812T +12-volt regulator  
 IC8—7912T -12-volt regulator  
 IC9, IC10—LM1875T audio amp  
 LED1—light emitting diode pilot lamp

### Other components

T1—Power Transformer 25.2 Volt Center Tapped 2 Amp.  
 F1—F3—1-amp fuse  
 J1—J8—8-pin RCA-style jack panel  
 J9—J12—4-position pushbutton speaker-terminal panel  
 S1, S2, S5—SPDT switch  
 S3, S4—DPDT switch

**Miscellaneous:** speakers of your choice, 5 14-pin IC sockets, 1 8-pin IC socket, 1 heat sink (2  $\times$  2  $\times$  5 1/4-inch aluminum angle stock), 2 T0-220 mica insulators with mounting hardware, silicone grease, 3 in-line fuse holders, 3 knobs, chassis, linecord, solder, etc.

**Note: The following items are available from T3 Research, Inc., 5329 N. Navajo Ave., Glendale, Wisconsin 53217-5036: An etched, drilled, and plated PC board, \$15.00; a basic parts kit consisting of all semiconductors, resistors, and capacitors, \$55.00; a piece of aluminum stock for the heat sink, \$3.00. Please include \$2.50 for postage and handling with your order. Wisconsin residents please include appropriate sales tax.**

## Setup and operation

Figure 11 shows one method of integrating the AFG into a home audio-video system. As mentioned earlier, a separate power amplifier is required for the subwoofer channel, in addition to the subwoofer speaker itself. In the setup in Fig. 11, the center channel is connected to the audio inputs of a monitor-style television receiver which has provisions for amplifying external line-level audio signals. If your TV set doesn't have audio in-


puts, or if you use the AFG in a music-only system, you'll have to provide a separate amplifier and speaker for the center channel as well. Please note that although the subwoofer-channel and center-channel speakers are a desirable part of any audio system, they are not absolutely necessary. The AFG may still be used as an excellent surround-channel decoder simply by adding a pair of small speakers for the surround channels.

The best place to patch the AFG into your system is between the pre-amplifier outputs and the power-amplifier inputs of your receiver or amplifier. Most component receiver/amplifiers allow for that connection by providing removable jumpers between the appropriate phono jacks on their rear panels. By placing the AFG in that loop, all the audio signals selected by the amplifier will also pass through the AFG. Furthermore, the volume and tone controls of the main amplifier will have control over all the levels in the system simultaneously; i.e. the subwoofer, surround speakers, and the center channel, as well as the regular left and right speakers. If your amplifier doesn't provide pre-amp out/main input jacks, you may still use the AFG by connecting it into a tape-monitor loop, or even more simply, to the audio output of a stereo VCR; but then you will have to adjust the levels of the subwoofer and surround channels independently of the main amplifier via the level controls on the AFG.

Calibration of the AFG is easy. Begin by setting, R75, R76, and R80 to their center positions. Now feed a mono signal into the AFG from some source in your system (an FM tuner switched to mono operation is a good choice). Set the balance control on your amplifier to its exact center mark. With the AFG switched to the matrix position (L-R), adjust R80 for the minimum output from the surround speakers. Now switch the receiver back to stereo and the AFG to concert (L+R). Adjust R76 for minimum distortion. R75 provides a means for matching the drive level of the AFG delay section to your system's normal audio levels. The BBD delay line has a maximum recommended input-signal level of 1.5 volts. To maximize the signal-to-noise ratio of the delay amplifier, the signal going into the delay line should be as high as possible without driving it

mica insulators and plastic shoulder washers must be used between the cases of the IC's and the heat sink. Use a small amount of silicone grease between the IC's and the heat sink to increase thermal conductivity. Make sure that the tabs of the IC's are actually insulated from the heat sink before operating the unit. Although adequate, the heat sink becomes moderately warm during operation, so be sure to provide good ventilation in your chassis.



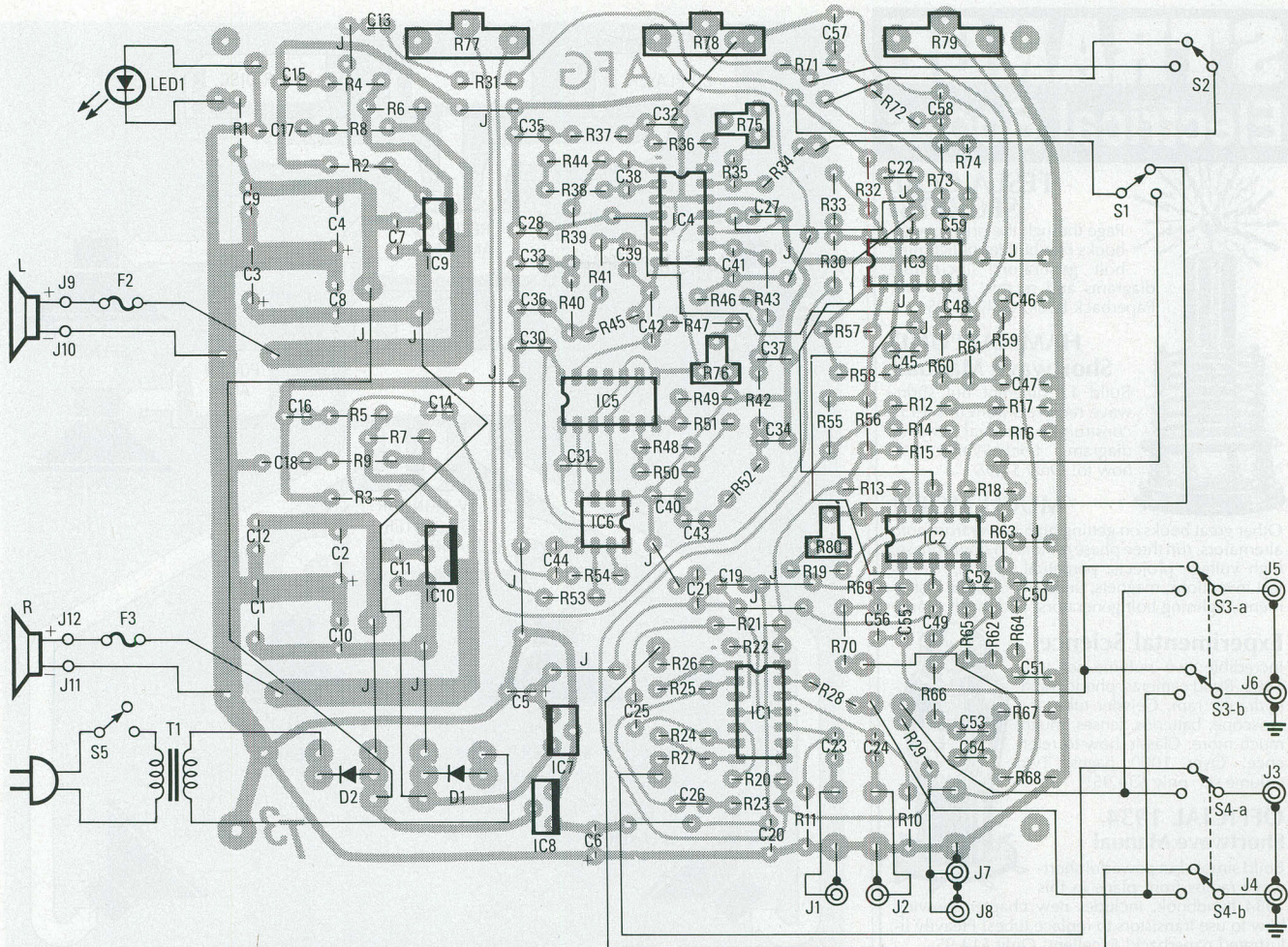

9—ALL OF THE COMPONENTS mount on a single PC board as shown.

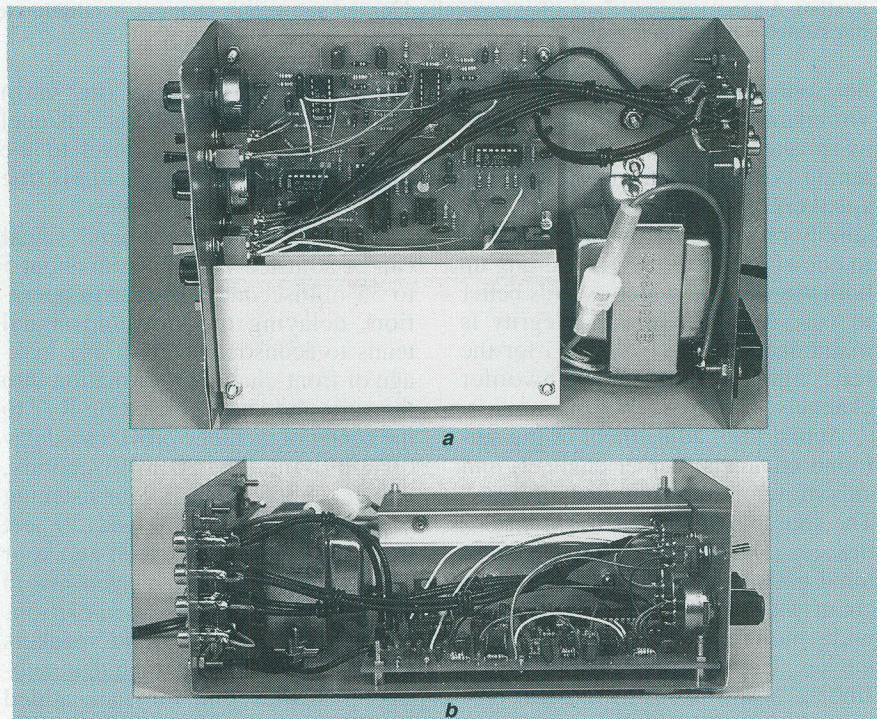



FIG. 10—THE HEAT SINK AND PC BOARD are installed as shown. Two 3-inch screws with double sets of nuts are used to mount the PC board on one side and hold the top of the heat sink in place (a). Two shorter screws hold down the other side of the board (b). Be sure to use spacers to prevent the board from touching the metal cabinet.

into distortion. While using the highest normal level you are likely to feed the AFG, adjust R75 to obtain the maximum level that does not cause distortion.

The speakers you choose for the surround channels don't have to match your front-channel speakers in sonic characteristics. The frequency response of the surround channel is limited at the time of encoding to a bandwidth from approximately 100 Hz to 7 kHz by the Dolby process. Small bookshelf-style speakers mounted toward the rear of the room at ear level or slightly above are adequate. Although it is customary to use two speakers for the surround channel, one placed to the right rear and one to the left rear of the listening position, the surround channel signal that feeds those speakers is really monaural. The internal power amplifiers in the AFG drive the signal to the two rear speakers 180 degrees out of phase. That tends to spread apart the sound field created between the rear speakers. However, that may or may



# STRANGE Electrical Books

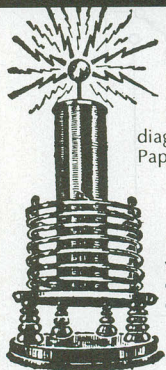

## TESLA COIL SECRETS!

Page through the private notebooks of a builder of lightning bolt generators! Incredible diagrams and secrets! Rare info! Paperback book. Only \$6.95

## HAMMARLUND Shortwave Manual!


Build 12 different hot short-wave receivers from this 1937 construction manual. Photos, diagrams, text! Wall-to-wall how to! Only \$4.95

## MUCH MORE!

Other great books on getting high power from auto alternators, run three phase motors on single phase, high voltage projects, perpetual motion, Tesla's lost inventions, magnets, unusual electrical instruments, lightning bolt generators, and much more!
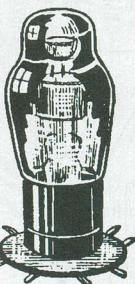
## Experimental Science

Incredible two volume set from 1906. Build cameras, phonograph, hydraulic ram, Geissler tube, microscope, batteries, lenses, much, much more. Classic how-to reference. Over 1000 pages. Two volume set only \$34.95!



## OFFICIAL 1934 Shortwave Manual

Build simple but powerful short-wave radios from plans in this 1934 handbook. Includes new chapter showing how to use transistors to replace tubes! Heavily illustrated paperback! Excellent! Only \$14.95

## MANY OTHERS:

Static Electricity \$5.95, Electrical Designs \$11.50, Experimental Physics \$23.95, Storage Batteries \$8.95, Power Inverter Technology \$4.00, Armature Winding & Motor Repair \$16.95, 50 Perpetual Motion Mechanisms \$3.75, more! See Catalog!




## ORDER FROM THIS AD TODAY!

Check, MO, Visa, MC. Handling: 75¢ first book, 25¢ each additional. Money-back guarantee.
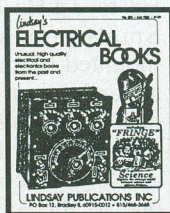
## OR WRITE FOR A CATALOG!

Write for your copy of Lindsay's unusual Electrical Books catalog and see for yourself what you've been missing! Send \$1.00 (US & Canada) or \$3.00 foreign airmail. We'll send your catalog immediately! Write today!



**Lindsay's Electrical Books**  
PO Box 12-WA7, Bradley IL 60915

☐ Send the books marked and a free catalog!

☐ Send just a catalog! \$1.00 enclosed...

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ St \_\_\_\_\_ Zip \_\_\_\_\_

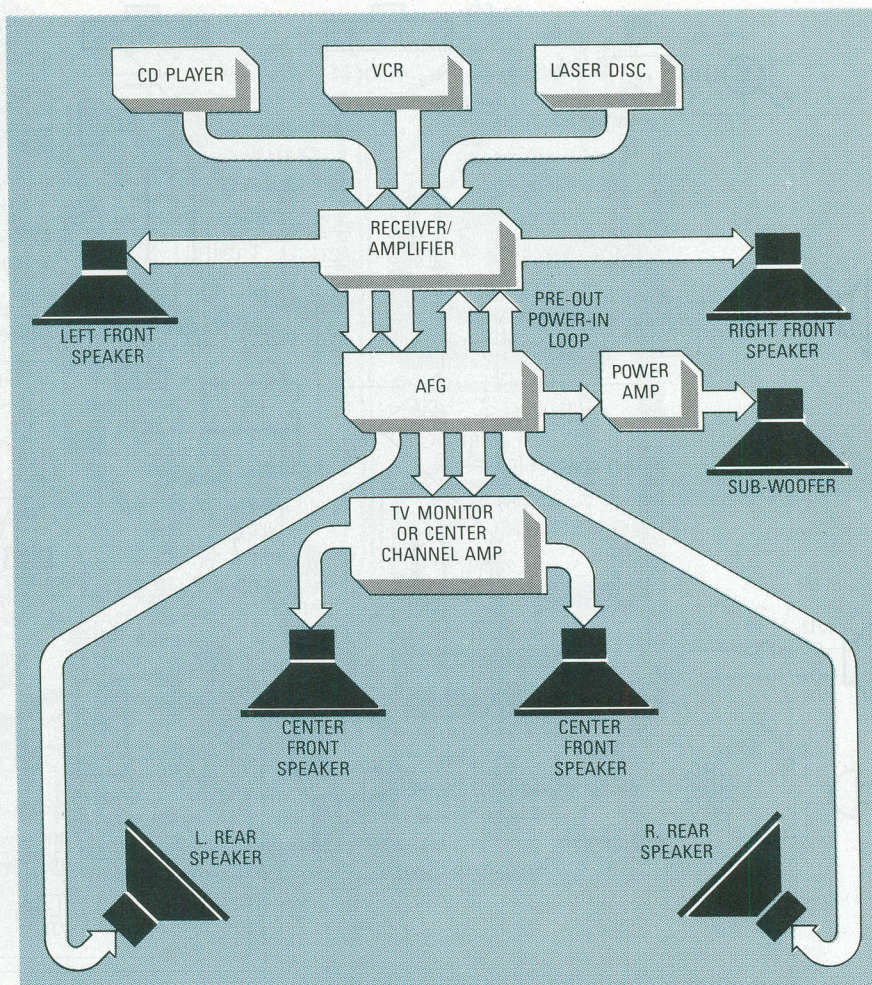


FIG. 11—HERE'S ONE METHOD OF INTEGRATING THE AFG into a home audio-video system. A separate power amplifier is required for the subwoofer channel, in addition to the subwoofer speaker itself.

not sound well in your listening environment, depending on such things as speaker placement and actual listening position. You may restore the speakers to in-phase operation by simply reversing the leads connected to one of the speakers. Try setting up both ways to find which sounds better to you. Note that phase integrity is maintained through the AFG for the left, right, center, and subwoofer channels.


Actual level adjustment of the surround channels, center channel, and subwoofer is a subjective process. The source material itself, the listening area, and personal preferences for tonal balance must be taken into account. Use the AFG in the matrix and wide modes for surround-encoded movies. Use the concert mode to add ambience and depth to musical performances. Generally speaking, don't set the level of the surround channel so high as to make it overwhelming. The surround signal is in-

tended to supplement the main channel, not to be a separate channel that is always equal in level to the front channel. That is particularly true for surround-encoded movies.

The delay of the surround signal can be adjusted via R77 from about 5 to 35 milliseconds. In matrix operation, delaying the surround signal tends to acoustically mask any leakage of front-channel information into the surround channel. Setting R77 to the center of its range provides a delay of approximately 20 milliseconds, which is about right if your listening position is between 10 and 20 feet from your television screen and your surround speakers are located just to the left and right of that position. However, if your surround speakers are located any farther than that, subtract 1 millisecond for each added foot. Likewise, add 1 millisecond for each foot less. For concert operation, adjust the delay for a pleasing ambience effect.

R-E



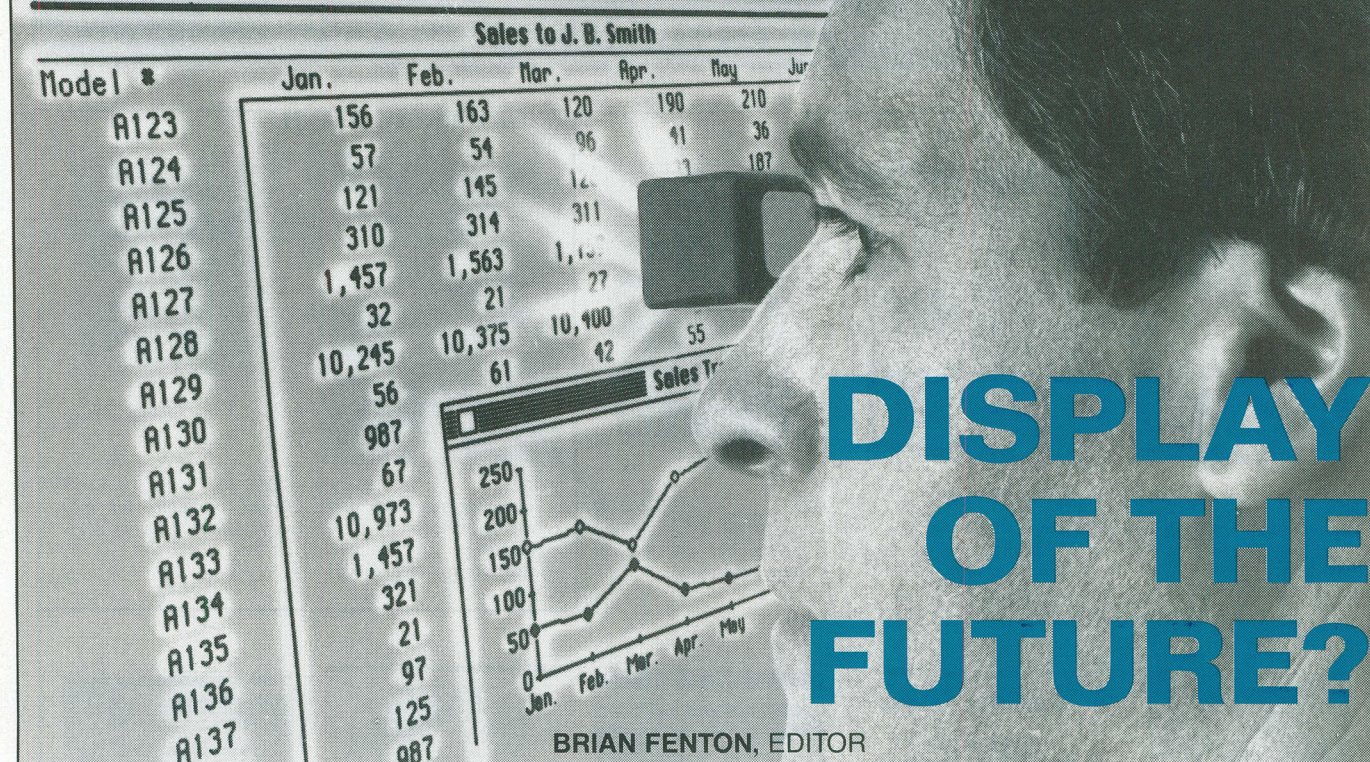

*Despite its size, you'll be seeing a lot of a new display called the Private Eye. It promises to change the way we look at portable computers, TV's, video games, and more.*

IF SOMEONE WERE TO SUGGEST REPLACING your computer monitor with a 1-inch display, you'd probably consider that person crazy. But that's exactly what Reflection Technology, a Waltham, Massachusetts-based company would like to do.

Actually, no one—including Reflection Technology—thinks that computer monitors will be replaced by their display called the *Private Eye*. But just as Sony's *Walkman* created an entire new category of stereo equipment, this "*Walkman* for the eye" promises to do the same for many other products. Pocket-sized computers are only the first to hit the market. But just imagine the advantages of an oscilloscope display that is worn in front of your eye. Or imagine what the next generation of portable video games—with a true three-dimensional image—will be like.

Although the *Private Eye* is innovative, the technology it uses is neither new nor dramatic. Instead, the display is a new combination of existing technologies. At its heart is a hybrid circuit consisting of a column of red LED's and driver circuitry, along with a magnifying lens and a mirror. While those components are certainly not exotic, the way they're used, and the results, are impressive nonetheless. The entire display measures slightly more than  $1 \times 1 \times 3\frac{1}{2}$  inches and weighs  $2\frac{1}{2}$  ounces. It can display text and graphics at a resolution of  $720 \times 280$  pixels, which is slightly better than a Hercules computer monitor. Total power consumption is just  $\frac{1}{2}$  watt.

The idea of peering at a 1-inch display might not seem too comfortable. However, the *Private Eye* is a virtual screen display that creates an image

larger than the screen itself—in this case 50 times larger. The user sees a completely readable, full-size, 12-inch screen by looking into a 1-inch window. The image appears to be floating in the air a few feet in front of the user. The result isn't as strange as the description sounds. The user isn't aware that the screen's plane of focus is a distance in front of him. Rather, he simply sees a perfectly readable screen that he doesn't have to strain to look at, despite the fact that it is only a couple of inches away from his eye.

#### It's all done with mirrors

As shown in Fig. 1, the main components of the display are a column of LED's, driver circuitry, a magnifying lens, a mirror, a counter weight, and a case.

At first glance, a column of LED's might not seem to be a logical way to create a display. The common question is, "Why not just use a matrix of LED's?" Unfortunately, while LED's are bright, efficient, fast, inexpensive, and easy to manufacture, current manufacturing technology is not ad-




Take any **3 BOOKS** for only **\$4<sup>95</sup>**

values to  
\$168.40

when you join the

**ELECTRONICS ENGINEERS & DESIGNERS BOOK CLUB®**


## COMPUTER SCIENCE

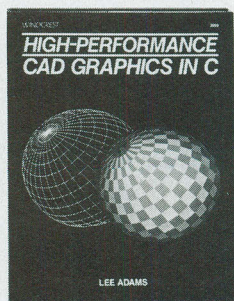

**3059** **\$34.95**  
Master the art of modeling, rendering, and animating on your IBM® PC.  
524 pp. *Counts as 2.*




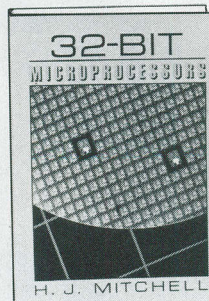**2809** **\$27.95**  
Reduce costly repair bills by troubleshooting and repairing your computer with this hands-on service manual. 416 pp.




**9829** **\$45.00**  
An inclusive overview for electronics engineers and computer scientists. 248 pp.


## ENGINEERING MATH

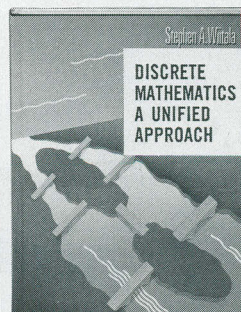

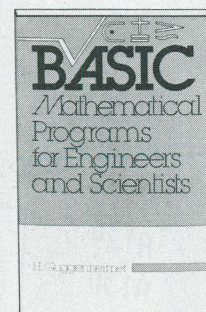
**9776** **\$36.95**  
A convenient guide to the power and practicality of discrete mathematics for computer science and math applications. 448 pp.



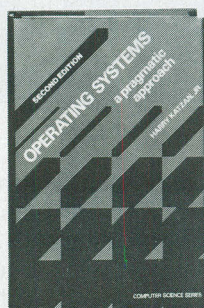**8225P** **\$29.95**  
Tested programs for most mathematical computing needs. 233 pp.



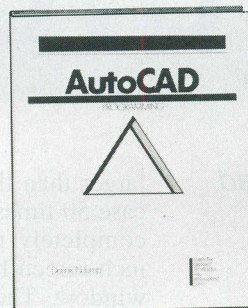
**9808** **\$34.95**  
For both micro and mainframe users, second edition of the all-time best selling guide. 449 pp.




**3093** **\$39.95**  
A tutorial and resource for extending the capability of AutoCAD Version 2.0.  
288 pp. *Counts as 2.*



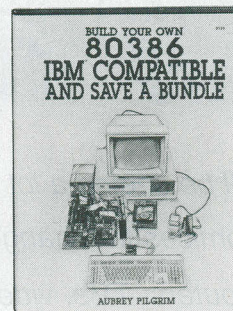**3147** **\$32.95**  
Implement PCs and streamline your process control schemes. 304 pp. *Counts as 2.*




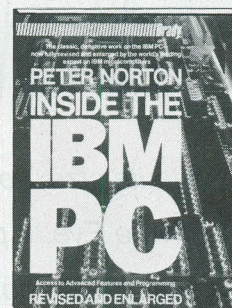**3131** **\$24.95**  
Assemble your own powerful microcomputer system... it's easy and inexpensive. 224 pp.




**9762P** **\$21.95**  
The classic definitive work on the IBM PC—fully revised and enlarged. 387 pp.


## ELECTRONIC CIRCUITS

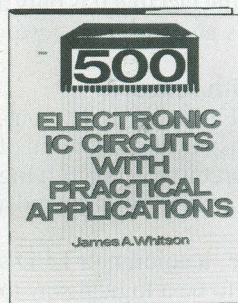

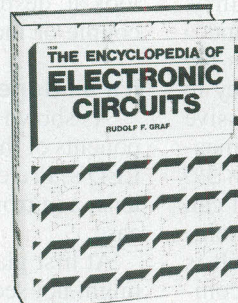
**2920P** **\$19.95**  
600 diagrams, schematics, and tables showing IC circuits. 352 pp.



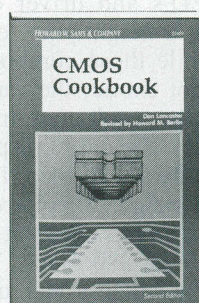**1938P** **\$29.95**  
Over 1,300 useful and versatile electronic circuit designs. 768 pp.



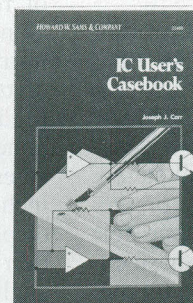**9244P** **\$18.95**  
This revised and updated edition is both a comprehensive, industry-wide reference, and a valuable collection of project ideas. 512 pp.



**9243P** **\$12.95**  
This book will eliminate guesswork in choosing the best circuit or tracking down malfunctions in a completed circuit. 282 pp.




**9825** **\$49.95**  
A comprehensive manual for soldering and cleaning printed circuit boards. 430 pp.






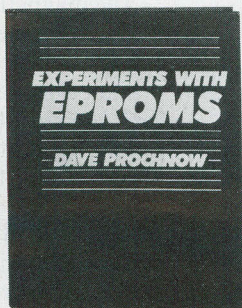
**9773** **\$44.95**  
Examines the significant advances in communications technology. 406 pp.



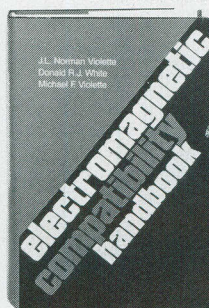
**2962P** **\$17.95**  
Complete schematic diagrams, parts lists, and photos for building a variety of projects. 296 pp.



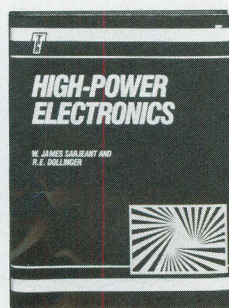**9781** **\$68.95**  
Designed to help deal effectively with today's fast-paced EMC technology. 707 pp.




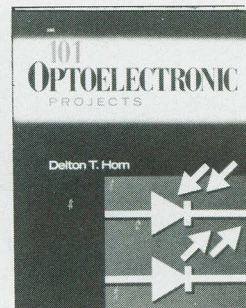**3094** **\$42.95**  
A new resource for those who design, develop, and install power systems. 400 pp.  
*Counts as 2.*




**3205** **\$24.95**  
Discover the broad range of practical applications for optoelectronic devices. 250 pp.

## ELECTRONIC COMPONENTS

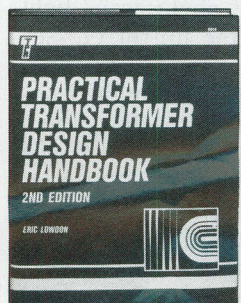

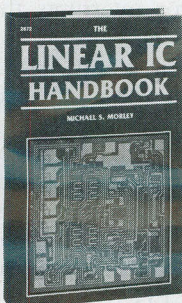
**3212** **\$34.95**

**3212** A no-nonsense guide on the designing, building, and applications of small ironcore transformers. 350 pp. *Counts as 2.*



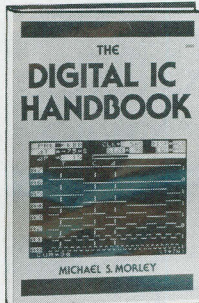
**2672** **\$49.50**

**2672** Linear integrated circuits—specifications, prices & data. 614 pp.



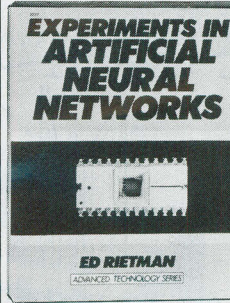
**3002** **\$49.50**

**3002** Fast, accurate information guaranteed to simplify your search for the right IC. 624 pp.



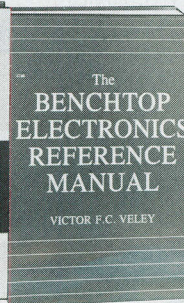
**3037** **\$24.95**

**3037** Build your own neural networking breadboards—systems that can store and retrieve information like the brain! 160 pp.



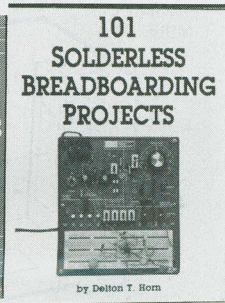**2785** **\$39.95**

**2785** Easy-to-use reference to 160 electronic principles: ac/dc, solid-state, oscillators, amplifiers and radio communications. 620 pp. *Counts as 2.*



**2985** **\$24.95**

**2985** This versatile project book reveals how you can design your own electronics circuits with solderless breadboarding. 218 pp.

## How the Club Works:

**YOUR BENEFITS:** You get 3 books for \$4.95 plus shipping & handling when you join. You keep on saving with discounts of up to 50% as a member.

**YOUR PROFESSIONAL BOOKSTORE BY MAIL:** Every 3-4 weeks, you will receive the EE&D Book Club News describing the Main Selection and Alternates, as well as bonus offers and special sales, with scores of titles to choose from.

**AUTOMATIC ORDER:** If you want the Main selection, do nothing and it will be sent to you automatically. If you prefer another selection, or no selection at all, simply indicate your choice on the reply form provided. As a member, you agree to purchase at least 3 books within the next 2 years and may resign at any time thereafter.

**BONUS BOOKS:** Starting immediately you will be eligible for our *Bonus Book Plan* with savings of up to 80% off publishers' prices.

**IRONCLAD NO-RISK GUARANTEE:** If not satisfied with your books, return them within 10 days without obligation!

**EXCEPTIONAL QUALITY:** All books are quality publishers' editions especially selected by our Editorial Board.

All books are hardcover unless number is followed by a "P" for paperback. (Publishers' Prices shown)  
©1990 EEDBC®, Blue Ridge Summit, PA 17294-0860



## ELECTRONICS ENGINEERS & DESIGNERS BOOK CLUB®

Blue Ridge Summit, PA 17294-0860

YES! Please accept my membership in the *Electronics Engineers & Designers Book Club®* and send my 3 volumes listed below billing me \$4.95 plus shipping and handling. If not satisfied, I may return the books within 10 days and have my membership cancelled. I agree to purchase 3 or more books at regular Club prices (plus shipping/handling) during the next 2 years, and may resign at any time thereafter.

--	--	--

Name

Address


City

State  Zip  Phone

Signature

Valid for new members only. Foreign applicants will receive special ordering instructions. Canada must remit in U.S. funds. This order is subject to acceptance by the *Electronics Engineers & Designers Book Club®*. DRE290



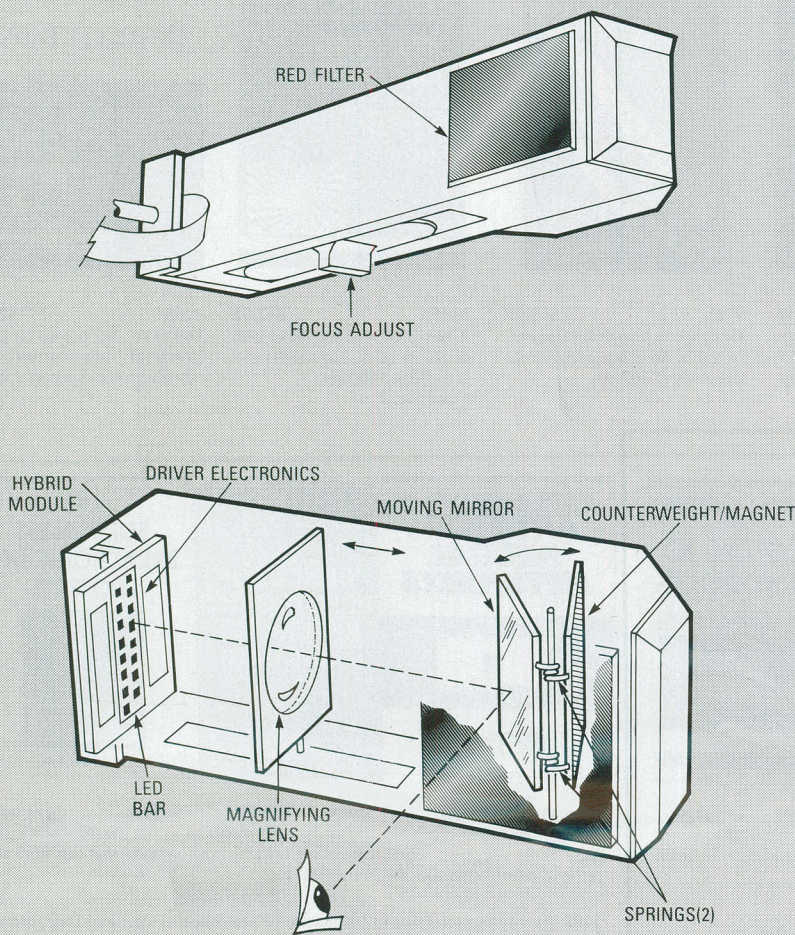

**FIG. 1—A HIGH-RESOLUTION DISPLAY** is packaged in a housing that measures about  $3.5 \times 1.2 \times 1.2$  inches (a). The heart of the display consists of an LED column, a magnifying lens, and a mirror (b).

vanced enough to produce a matrix that is dense enough.

An elegant solution was devised using a column of LED's, which can be manufactured reliably in long, dense arrays. Of course, a single column of LED's is not very useful as a computer display. But instead of trying to add dots (pixels) by brute force to make a matrix, the developers of the display combined the single LED column with a scanning mirror and magnified the result. One column of dots is shown at a time, and the mirror is moved to spread the single column across the full screen as the pattern on the column changes. As shown in Fig. 2, that makes it possible to create the perception of a full-screen display.

To improve the picture's resolution, two columns are used instead of one. They are laid out as a staggered, or zig-zag, array. The individual LED's (pixels) alternate between the columns. To create a single image, each

LED column is illuminated at a slightly different time to allow the mirror's movement to combine the columns, making the pixels appear to touch each other, top-to-bottom. The image that results from this "hardware interlacing" is a solid field without any of the blank interrupt lines that are normally seen on a CRT.

Apparent brightness is achieved not by overpowering ambient light, as in most other displays, but by putting the display in a light-tight enclosure. The image appears as vibrant, high-contrast red characters on a deep black background.


While the LED column is important to the success of the display, the scanning mirror completes the picture. The mirror is hinged and supported by springs at one end. As shown in Fig. 3, a small voice coil, similar to that of a speaker, is attached to the back of the mirror and pushes against a magnetic counterweight.

The magnetic counterweight is also spring-mounted. The resonant frequency of the counterweight system is designed to be the same as the mirror's, so essentially the entire mirror/counterweight/coil mechanism acts like a tuning fork. Not only does it consume very little power—only  $\frac{1}{100}$  watt is needed to keep it going—but most of the vibration that would be created by the oscillation of the mirror alone is canceled out. The resonant system is also relatively immune to external shocks and vibration.

Synchronizing the movement of the mirror is achieved by using a photodetector sensor. As shown in Fig. 4, a tab mounted to the back of the mirror interrupts the photosensor light beam circuit as the mirror crosses maximum deflection. At that time, power is applied to maintain resonance. The advantage of this system is that the exact frequency of the vibration is not important.


The photosensor signal also provides the information to determine the right time to start turning on the LED's for each screen. Due to the sinusoidally varying speed of the mirror throughout its cycle (it slows down to a stop at each end), a timing correction must be applied to make the columns appear in the right locations.

The spring mounts for the resonant system act as frictionless pivots for

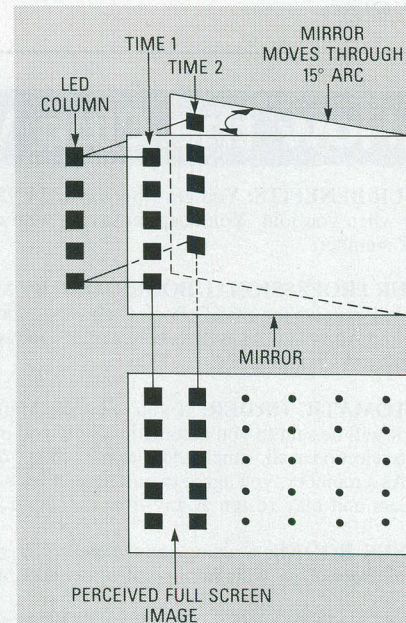


**FIG. 2—THE MOVEMENT OF THE MIRROR** forms a horizontal "raster" as the pattern on the LED column changes. In the actual display, the LED column is made up of two offset bars, which are blended together by the mirror's movement.



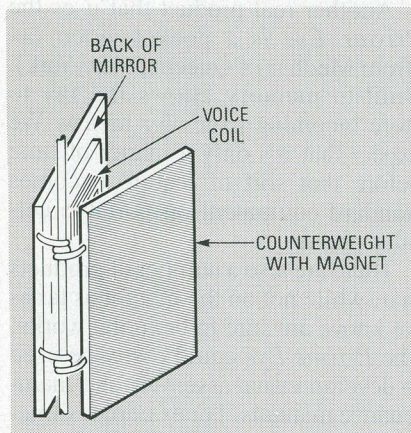

**FIG. 3—THE SCANNING MOTOR.** The mirror is set into motion by a small voice coil that is mounted on back of the mirror; the voice coil pushes against a magnetic counterweight.

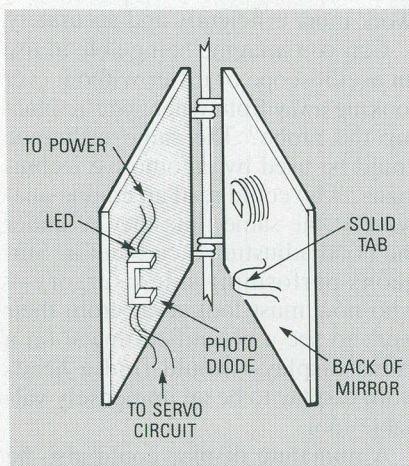

**FIG. 4—ACCURATE TIMING** is essential to keeping the pattern of the LED column in sync with the movement of the mirror. A photosensor assembly makes the job easy. When the mirror reaches the end of its travel, the photodetector sends a signal to the servo circuit, which gives the mirror a "kick" back.

the mechanism and create minimal power loss. And, because the motions required are small (the mirror travels only 15 degrees), the springs are stressed to a small fraction of their fatigue life. In addition, because of a resonant system's tendency to resist any disturbance to the system (such as rapid movement or outside vibration), the image is not only extremely stable and clear, but remains so under a broad range of conditions.

The magnifying lens that sits between the mirror and the LED array allows the user to adjust the optics so that the displayed image appears to be at a point in space anywhere between 9 inches and infinity. An image can therefore be located on the same plane

as other objects in the user's field of view. Because the optics are adjustable, users do not suffer from eye strain and do not need to refocus their eyes when shifting their gaze from the display to other objects surrounding them.

### Other features

If a portable display is to be successful, its power consumption must be kept to a minimum. We've already seen how the LED's and resonant vibrating mirror are very efficient. Additional power reduction is achieved by being able to use a low refresh rate of 50 Hz. Other displays that refresh at that rate, such as TV's in Europe, suffer from very noticeable flickering, particularly when viewed with peripheral vision. The *Private Eye* is flicker-free because it has high contrast and is seen through the central portion of the eye, which is relatively insensitive to flicker.

The *Private Eye* runs asynchronously from the host device. The display has an internal control chip and screen buffer memory. The control chip takes bit-map data transmitted as serial data up the cable to the internal memory. It then takes the bit map and places it into shift registers. The display is automatically and continuously refreshed with the current image until new data is sent by the host device.

### Future developments

The technology we've described is still only in its infancy. In fact, the development kit that we examined when preparing this article used technology that is already outdated. For example, the development kit, which is used with a PC, requires two plug-in cards. One card contains logic circuitry, while the other contains the servo circuitry to control the mirror's motion. Most of that circuitry has been incorporated inside the display package for future versions. At the same time, the display has been made lighter and easier to manufacture, and the slight vibration of the development unit has been reduced to be even less noticeable. We wouldn't be at all surprised if future displays use a wireless radio-data link to receive their images.

Other improvements have been successfully demonstrated in the laboratory, but will have to wait for refinements in LED manufacturing be-

fore they become a commercial reality. Reflection Technology's five-year target is to produce a megapixel (1000- × 1000-pixel) full-color display in an even smaller, but substantial package. Before that goal—essentially HDTV in a matchbox—is reached, a number of smaller advances are planned.

First will be the addition of gray scale or, in the case of the *Private Eye*, "red scale." Showing brightness levels merely requires redesigning the electronics to vary the light cycles of the LED's according to the desired brightness.

Resolution will increase continuously from model to model. Moderate increases within the existing packaging technology (perhaps to 640 × 480) will occur, and then larger increases as denser packaging becomes available. Only current wire-bonding manufacturing practices limit the development of higher-density displays. Integrating the components onto a single substrate and using conductive paths between them will certainly provide the leap that is needed for megapixel resolution.

Color can be attained when green and blue LED's become available in arrays similar to those used for red LED's today. The scanning mirror will combine the red, green, and blue pixels from individual LED arrays to visually superimpose the pixels and produce colors (in much the same way that it now combines the staggered red LED columns). Blue and green LED arrays are still a few years from commercial availability.

The price for the display can also be expected to drop. The only costly component is the LED hybrid, which, like other semiconductor components, will lower in price as production volume increases and new manufacturing techniques are used.

### Potential applications

If you've ever used a laptop computer with an LCD screen, you're well aware of the need for improvements. Even the highest-resolution and easily read laptop screen has the disadvantage of having to be large enough to see. The *Private Eye* will dramatically shrink the minimum size of laptops. In fact, by the time you read this article, at least one company (Cyberspace of Norcross, Georgia) will have introduced a pocket PC about the size of a video cassette.



# Radio-Electronics REPRINT BOOKSTORE

- |   |  |
|---|--|
| <input type="checkbox"/> 126 Radio-Electronics Annual 1986 ..... \$6.00     | <input type="checkbox"/> SP8 Special Projects #8 ..... \$6.00          |
| <input type="checkbox"/> 125 Radio-Electronics Annual 1985 ..... \$6.00     | <input type="checkbox"/> SP6 Special Projects #6 ..... \$6.00          |
| <input type="checkbox"/> 109 Radio-Electronics (1989 back issues) .. \$3.50 | <input type="checkbox"/> SP5 Special Projects #5 ..... \$6.00          |
| Write in issues desired _____   | <input type="checkbox"/> SP4 Special Projects #4 ..... \$6.00          |
| <input type="checkbox"/> 108 Radio-Electronics (1988 back issues) .. \$3.75 | <input type="checkbox"/> SP1 Special Projects #1 ..... \$7.00          |
| Write in issues desired _____   | <input type="checkbox"/> EH87 Experimenters Handbook (1987) ... \$5.00 |
| <input type="checkbox"/> 107 Radio-Electronics (1987 back issues) .. \$4.00 | <input type="checkbox"/> EH88 Experimenters Handbook (1988-89) \$4.50  |
| Write in issues desired _____   |  |
| <input type="checkbox"/> 106 Radio-Electronics (1986 back issues) .. \$4.25 |  |
| Write in issues desired _____   |  |
| <input type="checkbox"/> 105 Radio-Electronics (1985 back issues) .. \$4.75 |  |
| (January not available)   |  |
| Write in issues desired _____   |  |
| <input type="checkbox"/> 104 Radio-Electronics (1984 back issues) .. \$5.75 |  |
| (December not available)  |  |
| Write in issues desired _____   |  |
| <input type="checkbox"/> 119 Popular Electronics (1989 back issues) \$3.50  |  |
| Write in issues desired _____   |  |
| <input type="checkbox"/> 118 Hands-On Electronics (1988 back issues)\$3.75  |  |
| Write in issues desired _____   |  |
| <input type="checkbox"/> 117 Hands-On Electronics (1987 back issues)\$4.00  |  |
| Write in issues desired _____   |  |
| <input type="checkbox"/> 116 Hands-On Electronics (1986 back issues)\$4.50  |  |
| Write in issues desired _____   |  |
| <input type="checkbox"/> 115A Hands-On Electronics #6 ..... \$5.50          |  |
| <input type="checkbox"/> 115 Hands-On Electronics #5 ..... \$5.50           |  |
| <input type="checkbox"/> 114 Hands-On Electronics #4 ..... \$5.50           |  |
| <input type="checkbox"/> 113 Hands-On Electronics #3 ..... \$5.50           |  |
| <input type="checkbox"/> 112 Hands-On Electronics #2 ..... \$5.50           |  |
| <input type="checkbox"/> 111 Hands-On Electronics #1 ..... \$6.00           |  |
| <input type="checkbox"/> SP10 Special Projects #10 ..... \$6.00             |  |
| <input type="checkbox"/> SP9 Special Projects #9 ..... \$6.00               |  |

## REPRINTS REPRINTS

- |  |
|--|
| <input type="checkbox"/> 169 Think Tank (133 Circuits) ..... \$3.50  |
| <input type="checkbox"/> 169A Think Tank Vol. 2 ..... \$3.00   |
| <input type="checkbox"/> 168 Fact Cards (#34-66) ..... \$3.50  |
| <input type="checkbox"/> 168B Fact Cards (#67-99) ..... \$3.50   |
| <input type="checkbox"/> 168C Fact Cards (#100-132) ..... \$3.50   |
| <input type="checkbox"/> 167 Designing With IC's ..... \$4.00  |
| <input type="checkbox"/> 166 Collected Works of Mohammed Ulyses Fips<br>(62 pages, April Fools Collection)..... \$7.50 |
| <input type="checkbox"/> 165 How to Repair CD Disc Players ..... \$5.00  |
| <input type="checkbox"/> 164 Modern Electrics (April 1908) ..... \$3.00  |
| <input type="checkbox"/> 163 Receiving Satellite TV ..... \$5.00   |
| <input type="checkbox"/> 162 Build Your Own Satellite TV Receiver \$5.00   |
| <input type="checkbox"/> 161 Descrambling (Feb., 1984) ..... \$3.00  |
| <input type="checkbox"/> 160 New Ideas - 42 Circuits ..... \$3.50  |
| <input type="checkbox"/> 159 Low Frequency Receiving Techniques<br>Building and using VLF Antennas ..... \$5.00        |
| <input type="checkbox"/> 158 Electro Importing Co. Catalog<br>(Circa 1918) ..... \$5.95                                |
| <input type="checkbox"/> 157 All About Kits ..... \$2.00   |
| <input type="checkbox"/> 156 How To Make PC Boards ..... \$2.00  |
| <input type="checkbox"/> 155 IBM Typewriter To Computer ..... \$2.00   |
| <input type="checkbox"/> 154 How To Repair VCR's ..... \$3.50  |

To order any of the items indicated above, check off the ones you want. Complete the order form below, **include your payment**, check or money order (DO NOT SEND CASH), and mail to **Radio-Electronics**, Reprint Department, P.O. Box 4079, Farmingdale, NY 11735. Please allow 4-6 weeks for delivery.

If you need a copy of an article that is in an issue we indicate is unavailable you can order it directly from us. We charge 50¢ per page. Indicate the issue (month & year), pages and article desired. Include payment in full, plus shipping and handling charge. Make checks payable to Gernsback Publications, Inc.

ARTICLE \_\_\_\_\_

PAGES \_\_\_\_\_

MONTH \_\_\_\_\_

YEAR \_\_\_\_\_

TOTAL PAGES \_\_\_\_\_

@50¢ each

TOTAL PRICE \_\_\_\_\_

MAIL TO: **Radio-Electronics**

Reprint Bookstore, P.O. Box 4079, Farmingdale NY 11735

SHIPPING CHARGES IN USA & CANADA

\$0.01 to \$5.00 ..... \$1.25	\$30.01 to 40.00 ..... \$5.00
\$5.01 to \$10.00 ..... \$2.00	\$40.01 to 50.00 ..... \$6.00
\$10.01 to 20.00 ..... \$3.00	\$50.01 and above ..... \$7.50
\$20.01 to 30.00 ..... \$4.00	

Total price of merchandise ..... \$ \_\_\_\_\_

Sales Tax (New York State Residents only) ..... \$ \_\_\_\_\_

Shipping Charge (see chart) ..... \$ \_\_\_\_\_

Name \_\_\_\_\_

Total Enclosed ..... \$ \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

R-290

All payments must be in U.S. funds

**SORRY** — We only ship to USA & Canada

Another real product that uses the *Private Eye* is a pocket video fax (from Medbar of Queens, New York). Built-in memory allows the fax to store incoming pages for review. We expect that it's only a matter of time before that sort of feature becomes standard equipment on portable cellular phones.

There are also a number of products that, while not on the market as far as we know, are sure to be in the works. The *Private Eye* could easily be used to develop visual assembly and maintenance manuals. For example, someone testing an electronic product at the end of an assembly line could see a picture that would show where to place a probe. Because the technician would not have to look away from the task at hand, he could presumably work more efficiently and accurately.

Can you imagine being able to use an oscilloscope or meter without ever looking away from where you're placing the probe? The same technique could be used by automotive technicians, who could read an engine analyzer at the same time they're under the hood adjusting a carburetor. Surgeons performing microsurgery—who now must look away from their work to see a magnified image on a video display—would find a head-worn display to be an immensely valuable tool.

A miniature display could also be incorporated into radio pagers or other mobile data displays. Potential users might include field engineers needing technical documentation, salespeople wanting access to product documentation during a sales call, drivers needing maps to their destination, or subscribers to public service such as news, sports, or stock-market information.

Another application that you can bet on is videogames. We can imagine goggle-like headsets with one display mounted in front of each eye. That would allow for completely portable, very exciting, true three-dimensional games.

In short, the *Private Eye* will be used wherever the information content and clarity of desktop screens can be used—from pocket PC's, to electronic instrumentation, from pocket fax receivers to ISDN telephone displays, from educational devices to toys and games. Even more exciting are the applications that haven't yet been thought of.

R-E



# BUILD THIS

ED BATHGATE

THE MAJORITY OF PROBLEMS THAT OCCUR in a VCR are mechanical in nature. Problems caused by dirty heads, worn idlers, stretched belts, and jammed gears are perhaps most common, but VCR's also have their share of electrical problems. Such problems may be bad end sensors, burned out motors, power-supply problems, etc.

A good oscilloscope and a digital voltmeter can get you through the majority of VCR problems quickly and easily. However, problems involving the video heads, rotary transformer, head pre-amps, and head-switching circuits can be tough to troubleshoot. There are low-cost (\$60) video-head testers, but they won't indicate if a head is contaminated or if the gap is clogged; in either case the output will seriously be degraded.

You could replace the video head in question, but that requires that you have a spare head for every make and model of VCR you service. Changing heads is time consuming, and keeping lots of heads in stock is expensive. What's really needed is an instrument that can generate a known-to-be-good video-head playback signal, and one inexpensive source for such a signal is another VCR. A VCR creates that signal whenever it plays a tape, so a working VCR can be used to troubleshoot a broken VCR (see Fig. 1).

If you are repairing VCR's as part of a service business, you probably have more than one working VCR in the shop at any given time. What's needed is a video jumper cable to take the signal from the source VCR and inject it into the VCR being repaired. This project makes it possible to do just that, with no modifications to either VCR.

## VCR operation

There are several signals that a video head generates during playback. The luminance and sync is a signal from 3.4 to 4.4 MHz, frequency-modulated by video luminance and sync information. The chroma, or color information, is a 629.371-kHz signal recorded by amplitude modulating the 3.4 MHz FM carrier. The



## VCR HEAD AMP TESTER

*This inexpensive piece of equipment can turn a second VCR into a valuable troubleshooting tool.*

combined signals are usually referred to as video-head RF or RF envelope.

Two video heads are needed to "read" the information from a standard VHS videocassette (see Fig. 2). The two heads are mounted 180 degrees apart on a polished aluminum cylinder that spins counter-clockwise at 30 rpm. When one head completes a scan of the tape, the other head is ready to start its scan. In one scan, one video head generates a "field," a full top-to-bottom picture on the TV screen. The second video head also

generates a field, but it is interlaced with the field from the first head. The two interlaced fields make one frame.

A standard four-head VCR uses only two heads at a time, one pair for "SP" (two-hour standard play), and one pair for "EP" (six-hour extended play). If one of the video heads is bad, the VCR will send a full-size picture to the TV, but with only half the picture information, with every other field composed of "snow."

Each head has its own pre-amp, and the output of each one goes to an


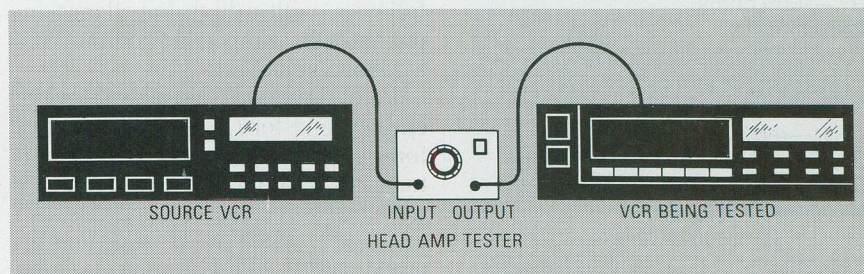


FIG. 1—THE VIDEO HEAD-AMP TESTER enables you to use a good signal from a working VCR to test a VCR with possible head problems.

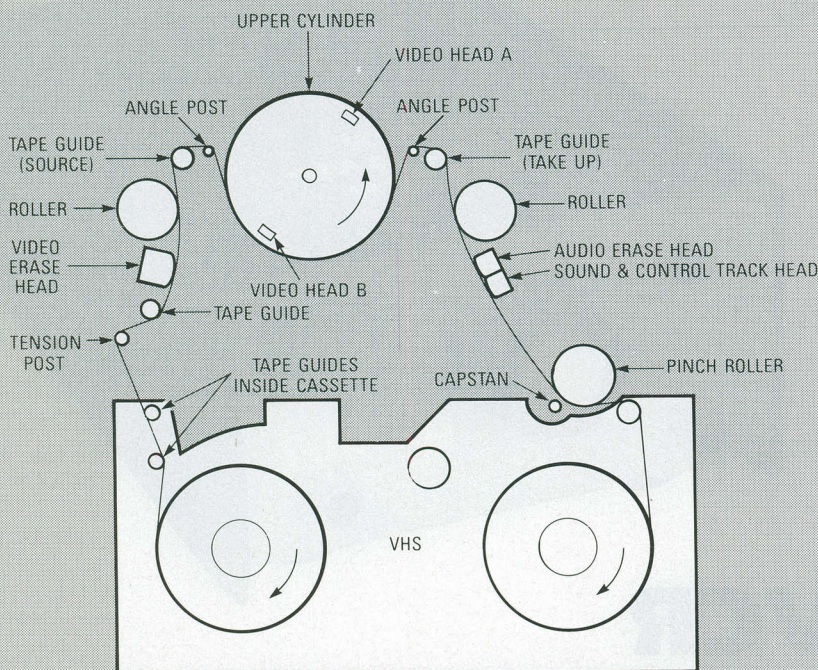



**FIG. 2—VHS BASIC MECHANISM.** Two video heads are needed to generate the standard VHS format. The two heads are mounted 180 degrees apart on a polished aluminum cylinder that spins counter-clockwise at 30 rpm.

electronic head switch (see Fig. 3). The head-switching circuit combines the outputs from each head pre-amp, by switching to the head which is in contact with the tape at that time. The head-switching control pulse is a 30-Hz square wave derived from the rotation of the head-cylinder motor. The output envelope (waveform *d*) is the

sum of the two individual head pre-amp envelopes (waveforms *a* and *b*).

If the head-switching pulse is not present, or if it's distorted or inverted in phase, the symptoms will be similar to bad heads or a bad pre-amp. Some examples of bad waveforms are shown in Fig. 4. Waveforms *a* to *d* are caused by mechanical misalignment of the tape guides, and the waveforms in *e* and *f* indicate proper alignment, but show a problem with the video heads, pre-amps, or head switcher.

### Head-amp tester circuitry

The schematic for the tester is shown in Fig. 5. The input is an RF envelope from a working VCR, applied to Q1 through coupling-capacitor C1. Q1 is connected as an emitter follower, with a high-impedance input and a low-impedance output, and a voltage gain of 1.

Potentiometer R3 is used as the emitter load for Q1 and level control for the signal applied to Q2. Capacitor C2 is for improving the frequency response of R3. Transistor Q2 is also a 2N2222, wired in the same configuration as Q1, but with a lower output impedance in order to drive circuits in the VCR under test. The circuit draws

only 12 mA, so a 9-volt battery is well suited for the project.


### Construction

The circuit should be built on a PC board, because RF as high as 4.5 MHz will be present. A single-sided board was used in the author's prototype with no problems. The board layout is very simple and can be drawn by hand directly on the copper with an etch-resist pen. See Fig. 6 for a parts-placement diagram; a foil pattern is provided in PC Service.

The assembled circuit should be mounted in a shielded box and coaxial leads should be used for input and output. Keep the lead length as short as possible (2-foot leads were used on the prototype with no problems).

### Checkout

After assembly, check the voltages on Q1 and Q2, and the current draw, to verify proper circuit operation. Connect the VCR to be used as the signal

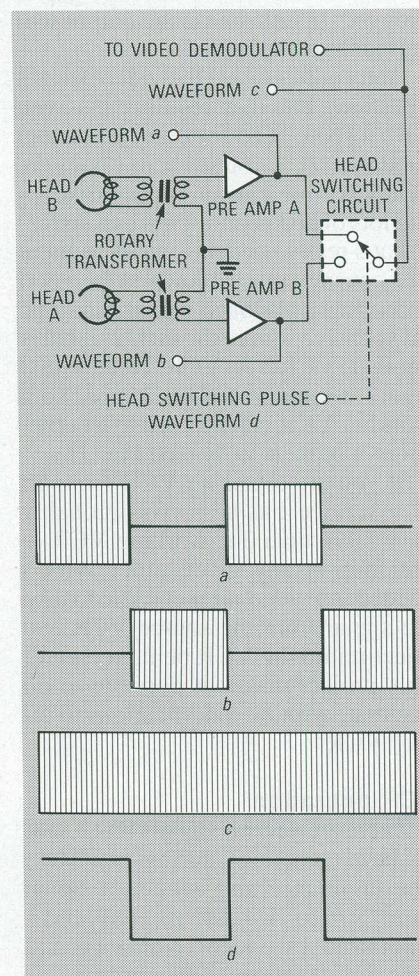

**FIG. 3—EACH HEAD HAS ITS OWN PRE-amp, and the output of each one goes to an electronic switch that combines the outputs from each head pre-amp.**

### PARTS LIST

**All resistors are 1/4-watt, 5%, unless otherwise indicated.**

R1, R4—100,000 ohms

R2—220,000 ohms

R3—10,000 ohms, audio-taper potentiometer

R5—150,000 ohms

R6—2200 ohms

R7—1000 ohms

#### Capacitors

C1, C3, C4—0.001  $\mu$ F, ceramic disc

C2—39 pF, ceramic disc

#### Semiconductors

LED1—red light-emitting diode

Q1, Q2—2N2222 NPN transistor


#### Other components

J1, J2—RCA-type jack


S1—SPST on/off switch

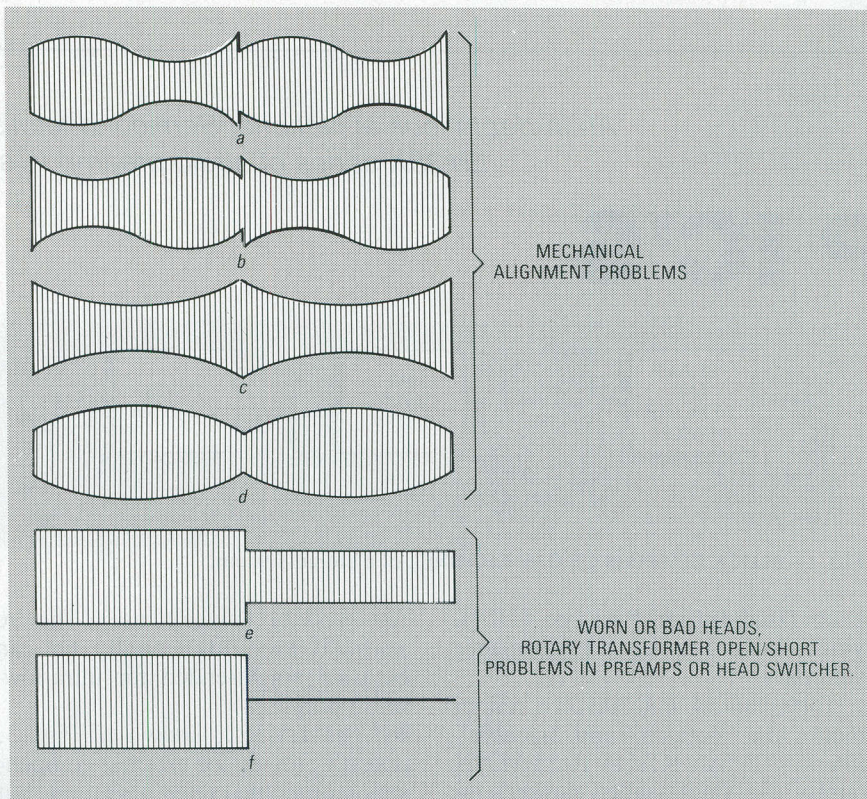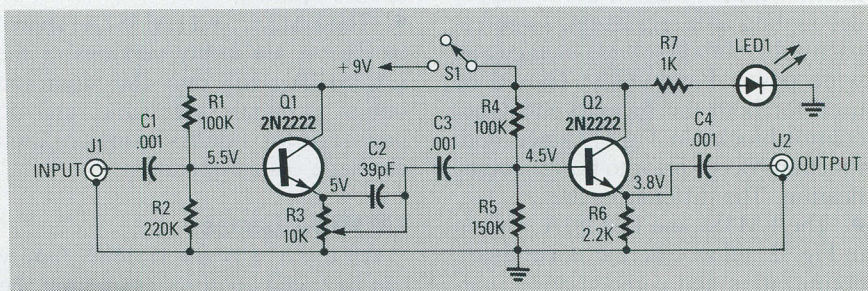**Miscellaneous:** Coaxial cable, PC board, metal case, solder, etc.

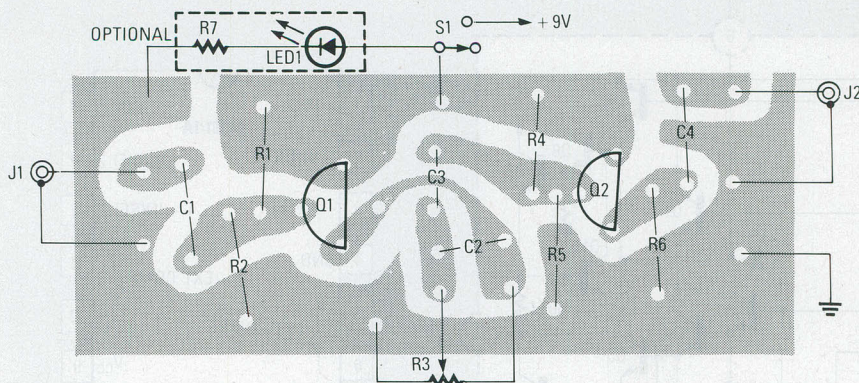




**FIG. 4—IMPROPER WAVEFORMS.** Waveforms *a-d* are caused by mechanical misalignment of the tape guides. The waveforms in *e* and *f* indicate proper alignment, but show that there's a problem with either the video heads, pre-amps, or head switcher.



**FIG. 5—THE SCHEMATIC** for the head-amp tester.



**FIG. 6—PARTS-PLACEMENT DIAGRAM.** Use the foil pattern provided in PC Service to make your own board.

source to a TV or monitor, and play a tape to use as the test signal; it can be a test pattern, or a home-made record-

ing of the news or some other show. Use an oscilloscope to check out the head RF envelope (Fig. 3-c), from the

source VCR for proper flatness. The RF envelope should be between 100- and 500-mV p-p in most VCR's.

Now turn on and connect the head-amp tester to the source VCR at the same point in the circuit that you measured the RF envelope (Fig. 3-c) with the oscilloscope. There may be a slight amount of signal degradation but if the entire picture disappears, it is loading down the source and the output signal will be unusable.

Check the output signal of the head-amp tester with the oscilloscope; it should be the same amplitude as the input signal with the level control at maximum. The output should be 0-V with the level control at minimum.

### Using the tester

To substitute a signal in place of bad or questionable video heads, first put the source VCR into play, connect the head-amp tester, and adjust the output for 5-10-mV p-p. Put the VCR to be tested into play with a blank tape, and connect the output of the tester to the input of one of the head amps. That may be done at the connector end of the cable between the rotary transformer and the head amps. You can also capacitively inject the signal by clipping the output lead over the insulation of a non-shielded wire (no electrical connection), and increasing the output level to about  $\frac{1}{2}$  to  $\frac{3}{4}$  of maximum. Signals can also be injected into the input and output of the head switcher. The output level should be high and direct electrical connections should be made.

The rotary transformer (one that can couple a signal from a rotating drum to the rest of the circuitry) can be tested with the VCR under test in "stop" mode, but the source VCR must be in "play" to supply a signal. Connect the output lead directly across one head at a time, and measure the output at the pre-amp input connector. You should disconnect the pre-amp connector from the pre-amps if possible. The signal from the rotary transformer should be equal or greater in voltage than the applied signal voltage. Test each head and the corresponding transformer winding.

The head-amp tester is not going to replace any major test equipment, but it does help you to troubleshoot some problems. And, after all, why wouldn't you want all the help you can get?

**R-E**



# CIRCUITS

## AUDIO PRE AMP IC'S

An in-depth look at National Semiconductor's LM38X series of audio preamp IC's.

RAY M. MARSTON

ONE OF THE MOST VERSATILE SERIES of linear preamp IC's is the LM38X versions from National Semiconductor. They're extremely useful for audio and tone-control applications, and have excellent ripple rejection, low signal distortion, wide bandwidth, and low noise. You'll find them in virtually any modern piece of audio gear. This discussion will investigate how they work, and look at several useful applications.

### The LM38X IC's

Figure 1 shows a representative block diagram of a conventional stereo system channel with both volume and tone control. National Semiconductor produces five low-noise dual preamps in the LM38X series, the LM381, LM381A, LM382, LM387, and LM387A; the "A" denotes versions with superior noise figure performance. Figures 2-4 show the configurations of the three different versions for one of the two amplifiers in

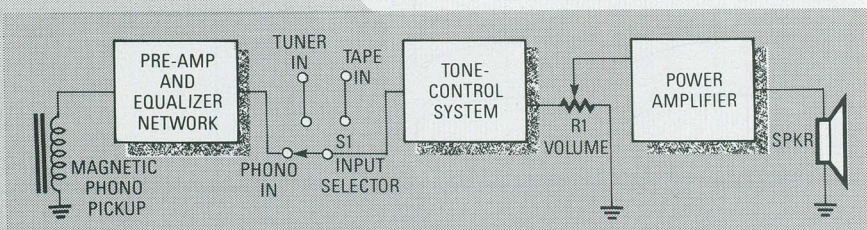


FIG. 1—BLOCK DIAGRAM OF ONE CHANNEL of a stereo system.

each *Dual-Inline Package* (DIP), while Table 1 gives a performance summary.

Tone control may involve refinements like "scratch" and "rumble" filters. All five IC's in the LM38X family use single-ended power supplies, and have the same basic amplifier circuitry, but differ in internal details and pinouts. Also, all five have internal compensation, power-supply decoupling and regulation, large capacity for output-voltage swing, and wide power bandwidth. They'd be used for both the preamp and tone-control blocks in Fig. 1, since both functions occur prior to power amplification. The differences are:

- The LM381 and LM381A, shown in Fig. 2, allow external noise figure optimization and compensation (nar-

row-band or low-gain use). They're normally used differentially, but can be used single-ended for ultra-low-noise purposes.

- The LM382, shown in Fig. 3, doesn't provide for external compensation or single-ended operation, but has a built-in resistor matrix to let the user select from among several closed-loop gain and frequency-response options.

- The LM387 and LM387A, shown in Fig. 4, are utility versions of the LM381/1A, with only the input and output terminals accessible, and no provision for external compensation or single-ended operation.

### LM381/1A basics

All the IC's in the LM38X family can be understood by examining the


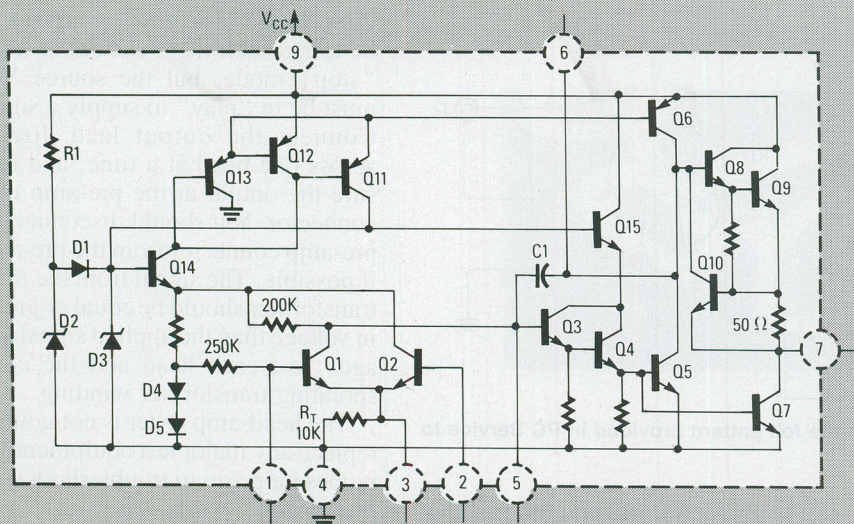


FIG. 2—THE LM381/1A DUAL LOW-NOISE PREAMP.

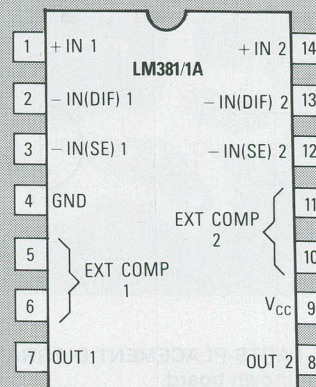




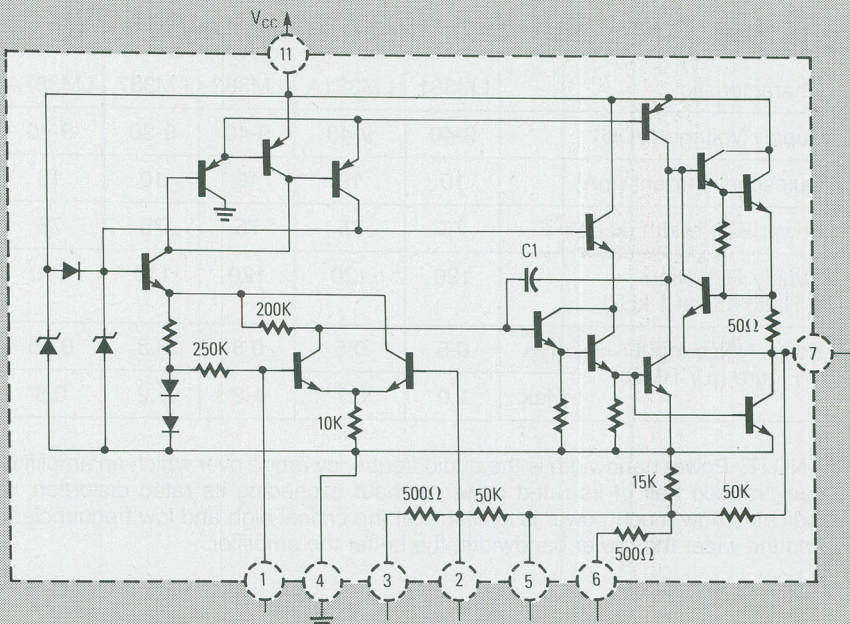


FIG. 3—THE LM382 DUAL LOW-NOISE PREAMP.

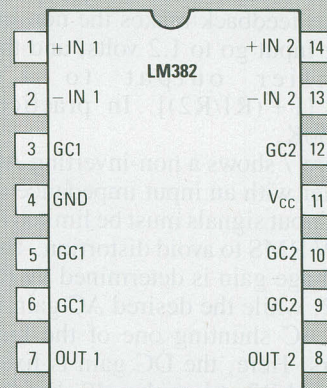

NOTE:  
GC = GAIN CONTROL


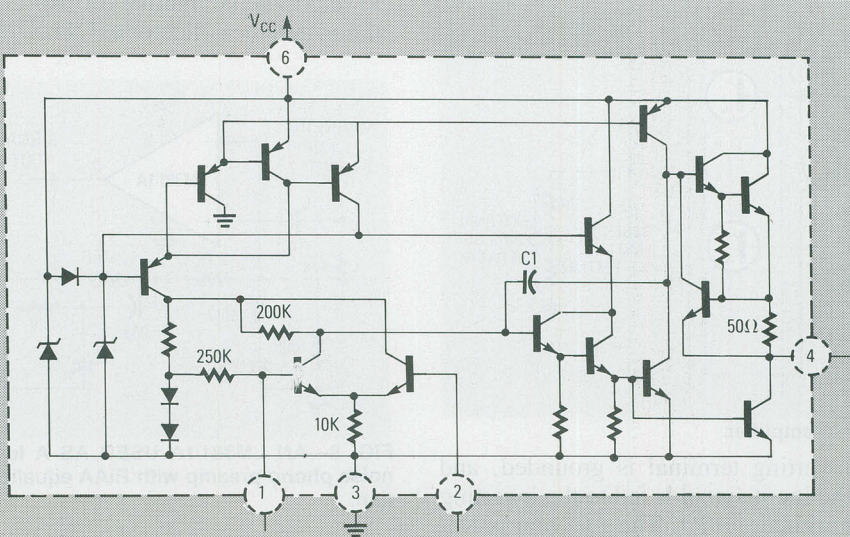


FIG. 4—THE LM387/7A DUAL LOW-NOISE PREAMP.

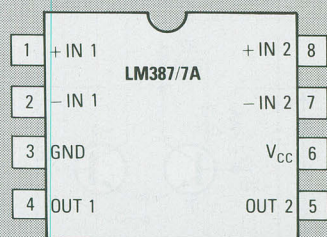

LM381/1A shown in Fig. 2. It has a first stage (Q1 and Q2), second stage (Q3-Q6), output stage (Q7-Q10), and bias network (Q11-Q15); Fig. 5 shows a simplified equivalent. The first stage is biased at 1.2 volts via R1, and can be operated either differentially or single-ended, although differential operation generates 41% more noise.

In differential use, the first stage has to be balanced by externally biasing the base of Q2 at 1.2 volts. In single-ended mode, Q2 has to be turned off by grounding its base, and Q1 has to be balanced by externally biasing the emitter of Q2 at 600 milli-

volts. The first stage has a differential voltage gain of 80, or 160 when used single-ended.

The second stage uses common-emitter Q5 and constant-current load Q6, and is driven by Q1 via Darlington emitter follower Q3-Q4. Its voltage gain is 2000, and it's internally compensated via C1 for unity gain at 15 MHz, giving stability at closed-loop gains of 10 or more. At lower gains, an external capacitor can go in parallel with C1 for compensation purposes.

The output stage uses Darlington emitter follower Q8-Q9, with active current sink Q7. Then, Q10 provides

short-circuit protection by limiting output current to 12 mA. The bias network gives 120 dB of supply-signal rejection, and includes the high-impedance constant-current generator Q11-Q12-Q13, which generates ripple-free reference voltage across D3. That reference voltage operates the first two stages via Q14 and Q15, and biases the base of Q1 internally.

### Differential operation

In differential mode, the IC output is given a positive quiescent value independent of supply-voltage variations, by connecting divider R1-R2 as a DC negative-feedback loop, as



shown in Fig. 6. The inverting input is biased internally at 1.2 volts. When R1 and R2 are used as in Fig. 6, DC negative feedback makes the non-inverting input go to 1.2 volts, and the amplifier output to  $1.2 \text{ volts} \times [1 + (R1/R2)]$ . In practice:  $R2 < 250K$ .

Figure 7 shows a non-inverting AC amplifier with an input impedance of 250K; input signals must be limited to 300 mV RMS to avoid distortion. The DC voltage gain is determined by R1 and R2, while the desired AC gain is set by AC shunting one of the bias resistors. Here, the DC gain is fixed by R1 and R2 at less than 10, but the AC gain is fixed by R1 and R3 at 100.

That shunting technique can be expanded for frequency-dependent AC gain in various filter applications. Fig-

TABLE 1—PERFORMANCE OF THE LM381/1A/2/7/7A LINEAR IC'S

Characteristic	LM381	LM381A	LM382	LM387	LM387A
Supply Voltage (VDC)	9-40	9-40	9-40	9-30	9-40
Quiescent Current (mA)	10	10	10	10	10
Power Bandwidth (kHz)*	75	75	75	75	75
Supply Rejection Ratio (dB at 1 kHz)	120	120	120	110	110
Equiv. Noise Input Figure ( $\mu\text{V RMS}$ )	Typ.	0.5	0.5	0.8	0.65
	Max.	1.0	0.7	1.2	0.9

\* NOTE: Power bandwidth is the audio frequency range over which an amplifier can produce half of its rated power, without exceeding its rated distortion. It indicates how much power is available at the critical high and low frequencies, and the wider the power bandwidth, the better the amplifier.

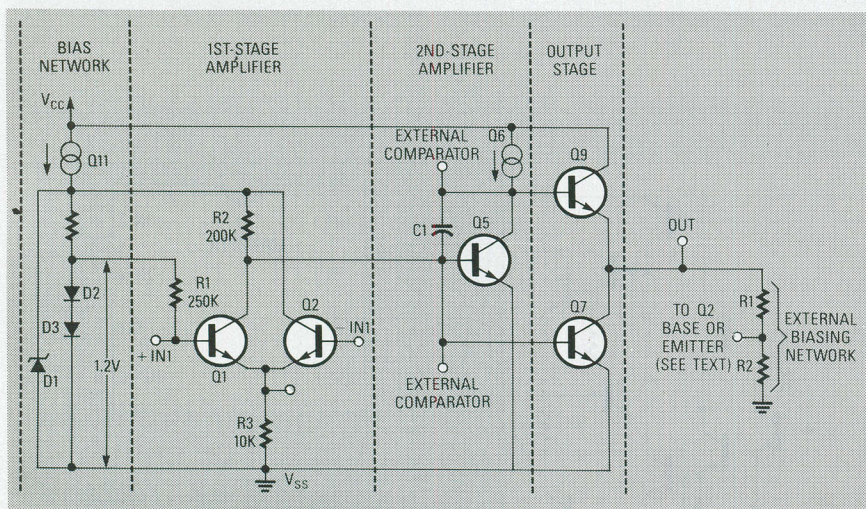


FIG. 5—EQUIVALENT CIRCUIT OF THE LM381/1A amplifier.

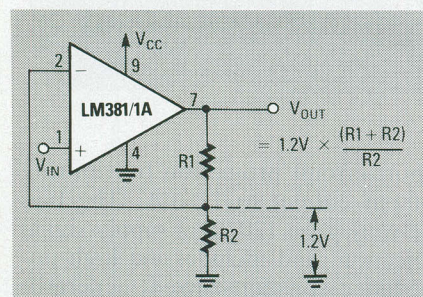


FIG. 6—DIFFERENTIAL BIASING OF THE LM381/1A.

ure 8 shows the same amplifier configuration used as a low-noise phono preamp with Recording Industries Association of America (RIAA) equalization, while Fig. 9 shows a similar tape-playback amplifier with National Association of Broadcasters (NAB) equalization. Figure 10 shows an inverting AC amplifier; here, the non-

inverting terminal is grounded, and the input signal is fed to the inverting terminal via R1. The AC gain is  $R3/R2 = 10$ , the quiescent output is +12 volts, and the input impedance is about R1. Figure 11 shows a unity-gain, 4-input audio mixer.

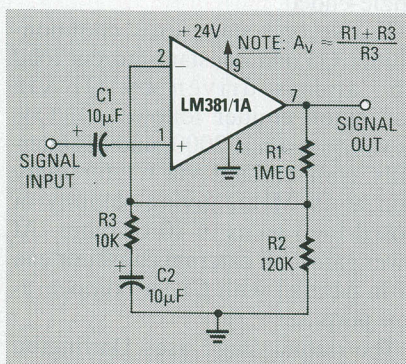


FIG. 7—A LOW-NOISE LM381/1A non-inverting amplifier, with a gain of 100.

### Single-ended operation

The differential first stage of an LM381 composed of Q1-Q2 is powered via the internal 5.6-volt regulator, and the collector of Q1 is fed to

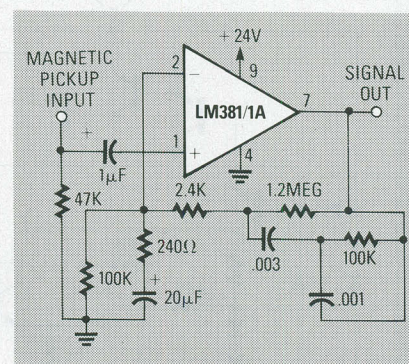


FIG. 8—AN LM381/1A USED AS A low-noise phono preamp with RIAA equalization.

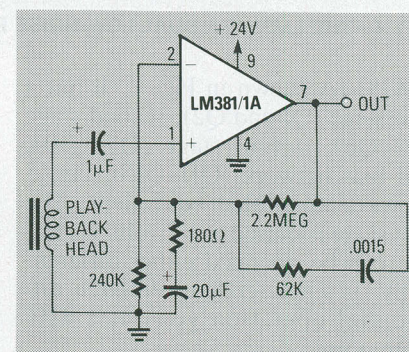


FIG. 9—AN LM381/1A used as a tape playback amplifier with NAB equalization.

the output via a DC amplifier. The IC can be operated in single-ended mode by grounding the base of (and disabling) Q2, but it needs to be biased



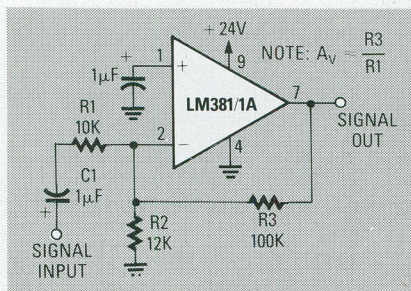


FIG. 10—THIS LM381A low-distortion (less than 0.05%) inverting amplifier has a gain of 10.

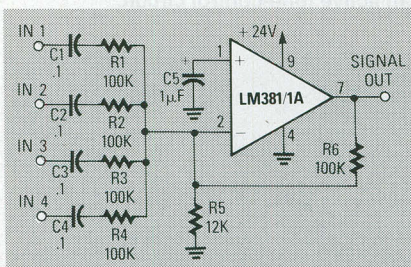


FIG. 11—THE LM381/1A is used here as a 4-input unity-gain audio mixer.

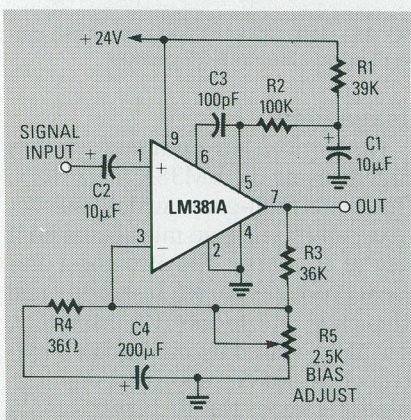


FIG. 12—THIS LM381A ultra-low-noise preamp has a gain of 1000.

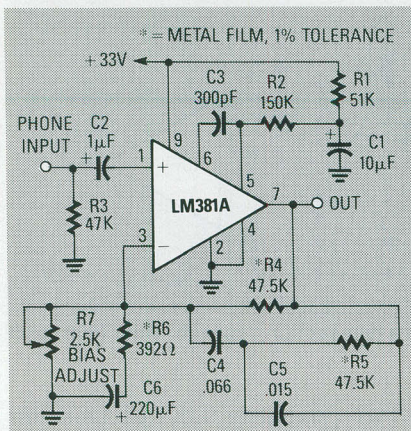


FIG. 13—LM381A ULTRA-LOW-NOISE magnetic phono preamp that includes RIAA equalization.

using emitter feedback.

Suitable DC biasing is obtained by connecting a voltage divider that ap-

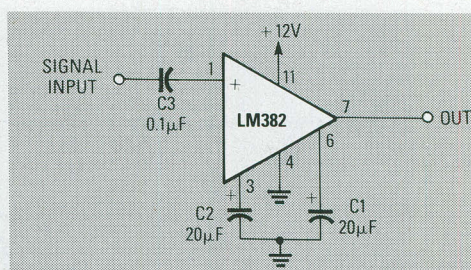


FIG. 14—AN LM382 FIXED-GAIN non-inverting amplifier with a 12-volt power supply.

GAIN	REQUIRED CAPACITOR
40dB	C1 ONLY
55dB	C2 ONLY
80dB	C1 AND C2

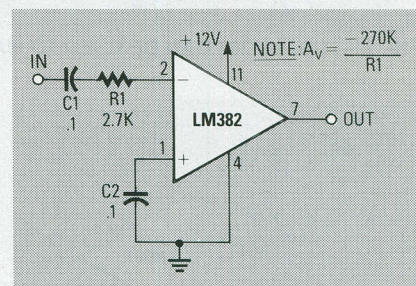


FIG. 15—THE LM382 is used here to make a 40-dB inverting amplifier.

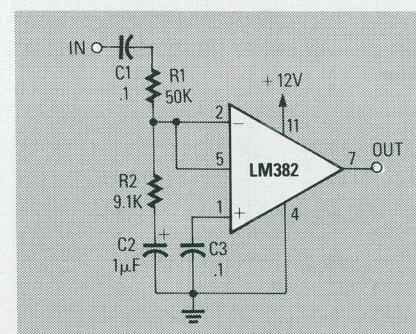


FIG. 16—SHOWN HERE IS AN LM382 unity-gain inverter.

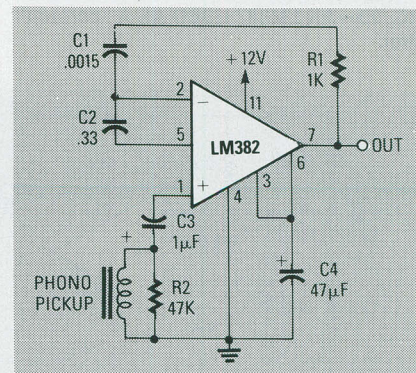


FIG. 17—LM382 phono preamp with RIAA equalization.

plies 600 millivolts to pin 3 when the IC output is at the desired DC level. If a quiescent +12-volt output is needed, the divider needs a DC voltage gain of 20.

In practice, the noise from the input transistor varies with collector current, and is minimized at 170 μA.

A single-ended LM381 is intended

for non-inverting use only, with a typical input impedance of 10K. Ideally, input signals should have source impedances below 2K, and all resistors should be of the low-noise, metal-film variety. Figure 12 is an ultra-low-noise version with a gain of 1000, where C3 limits the upper 3-dB frequency response to 10 kHz, and R5 adjusts the DC output voltage to half-supply value. Figure 13 is a magnetic phono preamp circuit that uses RIAA equalization, with the DC output voltage set by R7.

## LM382 circuits

The internal circuitry of each half of a LM382 is identical to a LM381, except for a 5-resistor matrix and elimination of certain terminal connections. Eliminating those terminals means that an LM382 can't be used single-ended or externally compensated. The resistor matrix greatly simplifies bias- and filter-network design. The matrix is specifically intended for applications where the IC is powered from a +12-volt supply. Figures 14–17 show various ways to use the LM382 with a +12-volt supply. Figure 14 shows a non-inverting amplifier with 40, 55 or 80 dB of AC gain. Figure 15 shows an inverting amplifier with 40 dB gain, Fig. 16 shows a unity-gain inverting amplifier, and Fig. 17 shows a phono preamp with RIAA equalization.

## LM387 circuits

The internal circuitry of each half of a LM387/7A is identical to an LM381, except for eliminating certain terminal connections, letting the IC be used differentially without external compensation. The IC is nevertheless quite versatile, and Figs. 18–24 show some practical applications. Figure 18 shows how to connect an LM387 as a non-inverting amplifier with an AC gain of 52 dB. The DC gain and quiescent output voltage of the amplifier circuit are determined



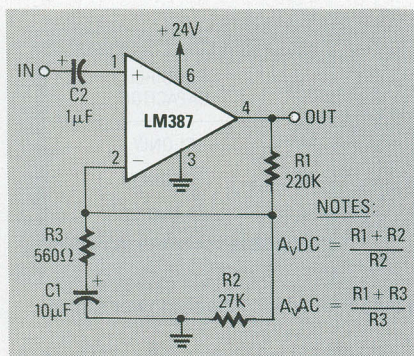


FIG. 18—LM387 NON-INVERTING AC amplifier with a gain of 52 dB.

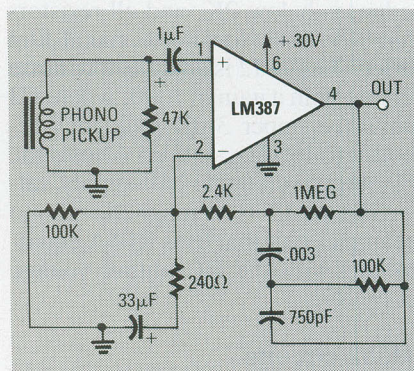


FIG. 19—LM387 PHONO PREAMP with RIAA equalization.

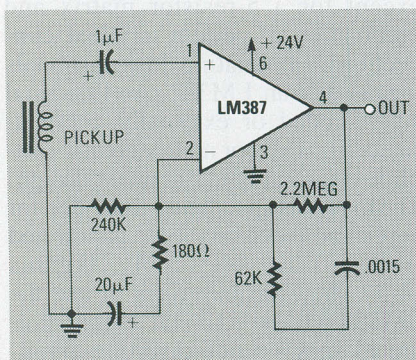


FIG. 20—AN LM387 USED AS a tape playback amplifier (NAB).

by R1 and R2, and the AC gain by R1 and R3. Figure 19 shows an LM387 used as a phono preamp with RIAA equalization, while Fig. 20 shows how it can be used as a NAB tape playback amplifier for use in all kinds of devices ranging from cassette players to telephone-answering machines.

Figure 21 shows an active tone control giving unity gain with its controls in the "flat" position, or 20 dB of boost or rejection with the controls fully rotated. The "rumble" filter of Fig. 22 is a 2nd-order high-pass active filter that rejects signals below 50 Hz at 12 dB/octave. Figures 23 and 24 show various ways of using an LM387 in inverting mode in active filters. The

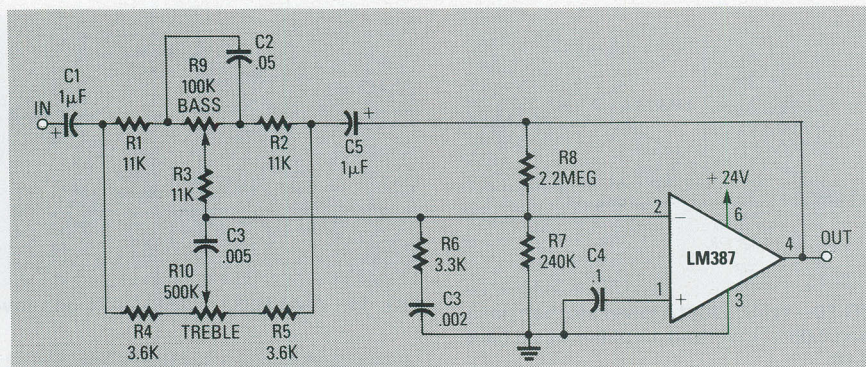


FIG. 21—THE LM387 CAN BE USED TO MAKE an active tone-control circuit.

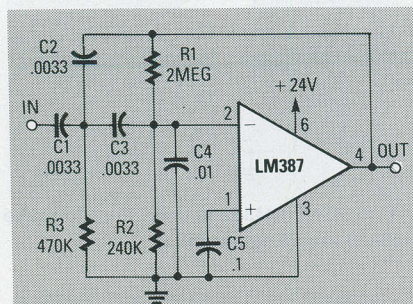


FIG. 22—AN LM387 USED AS A "rumble" filter.

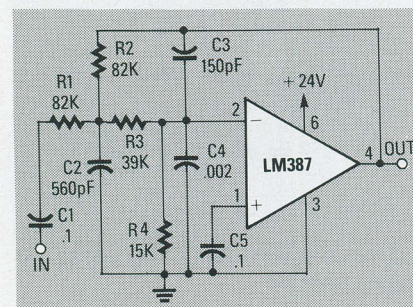


FIG. 23—AN LM387 USED AS A "scratch" filter.

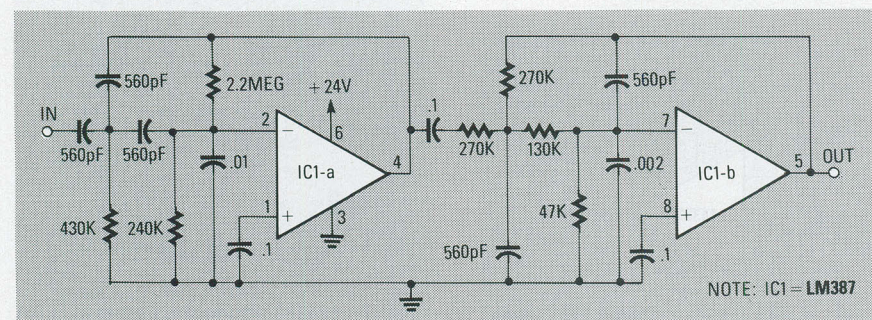


FIG. 24—BOTH HALVES OF AN LM387 make up a two-section "speech" filter (300 Hz–3 kHz).

"scratch" filter of Fig. 23 is a 2nd-order low-pass filter that rejects signals above 10 kHz. The "speech" filter of Fig. 24 consists of a 2nd-order high-pass and a 2nd-order low-pass filter in series, to give 12 dB/octave rejection to signals outside 300 Hz–3 kHz.

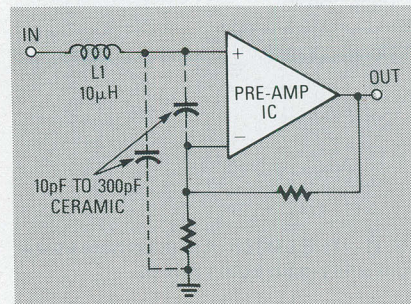


FIG. 25—THE CIRCUIT SHOWN HERE can be used to eliminate RF pickup.

### Usage hints


This article has examined various circuits using the LM38X linear IC's. These are high-gain, wide-band devices, and some care must be taken if they're to work. The two most frequent problems are RF instability and RF pickup. The former, RF instability, is usually caused by inadequate high-frequency power supply decoupling. In all preamps, the IC power supply has to be RF-decoupled by wiring a

0.1 μF ceramic or 0.001 μF tantalum capacitor across the IC power pins. The latter, RF pickup, manifests itself as AM demodulation. It can usually be eliminated with a 10-μH RF choke in series with an IC's input terminals, or by also decoupling the input with a capacitor, as in Fig. 25.

R-E






# PC SERVICE

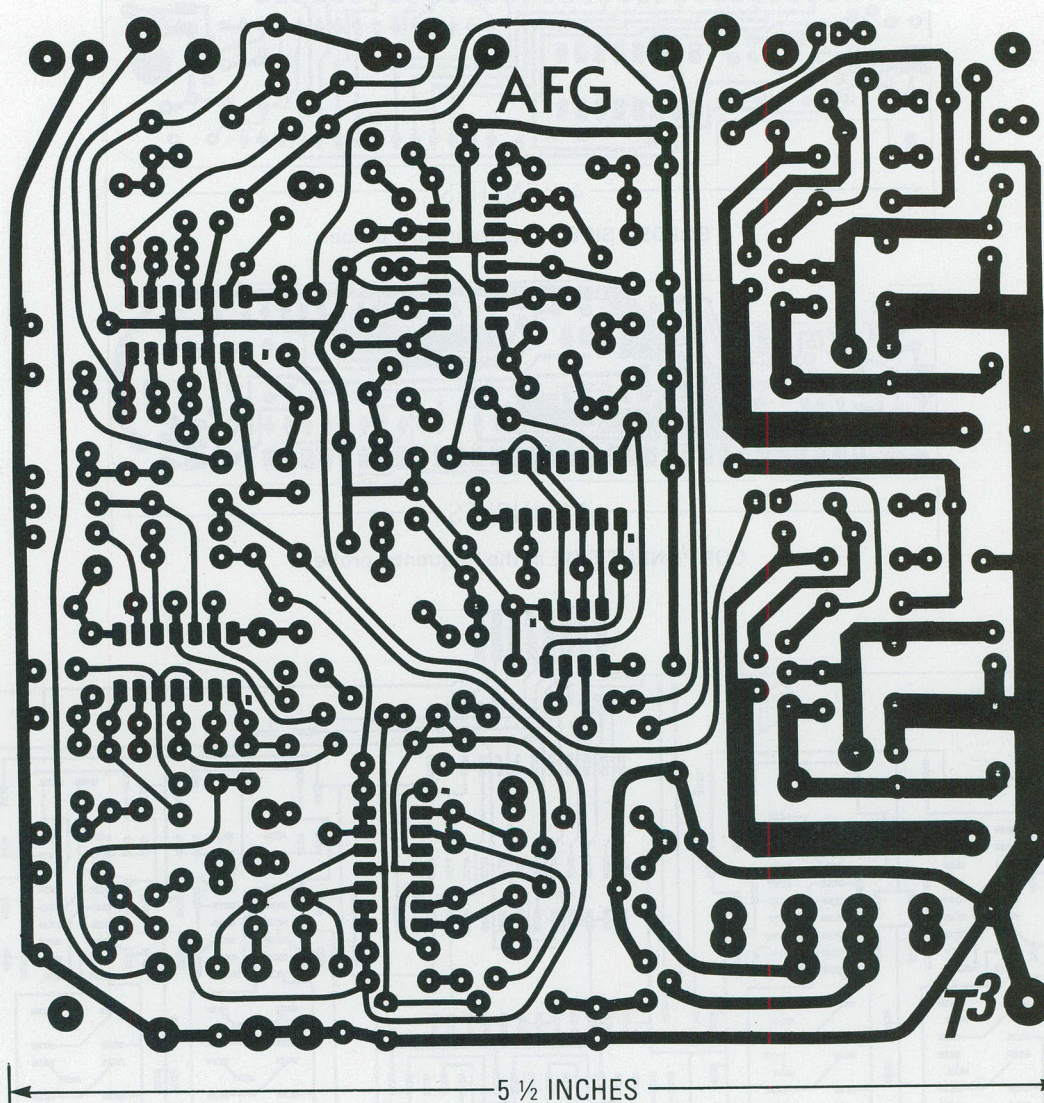


ACOUSTIC FIELD GENERATOR foil pattern.




# PC SERVICE

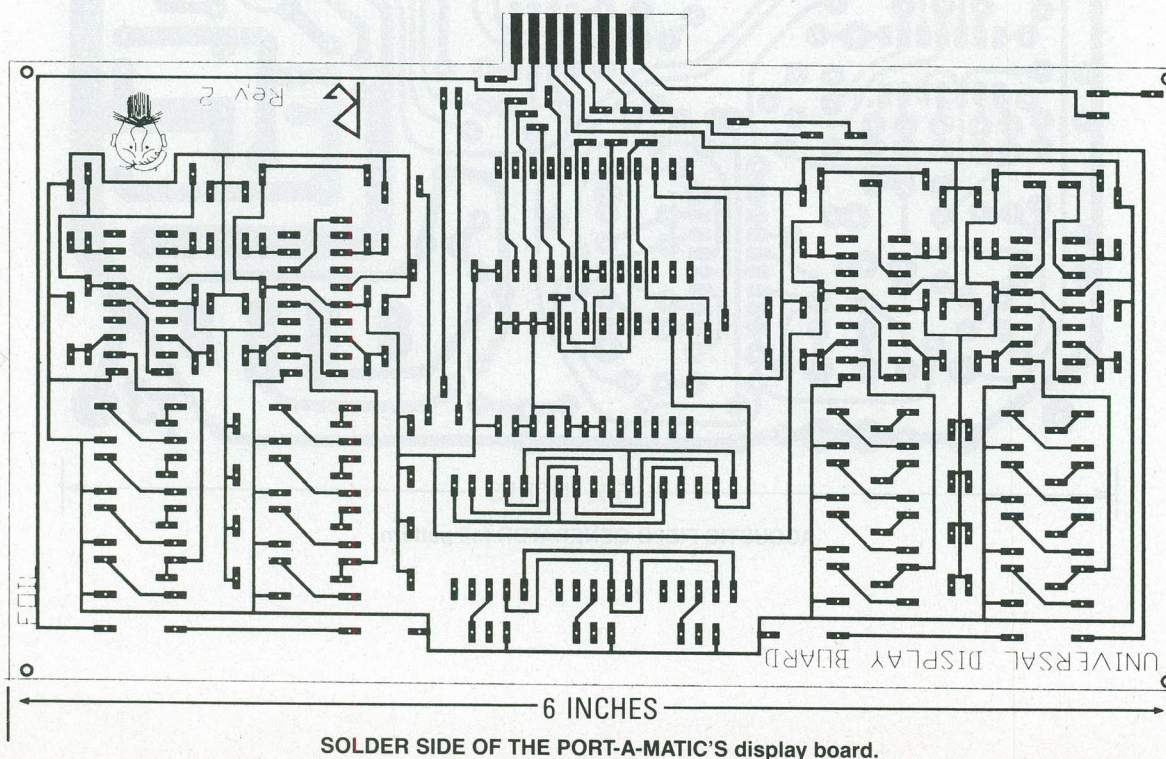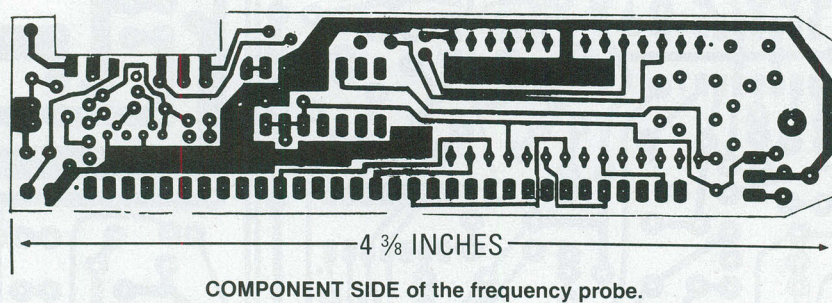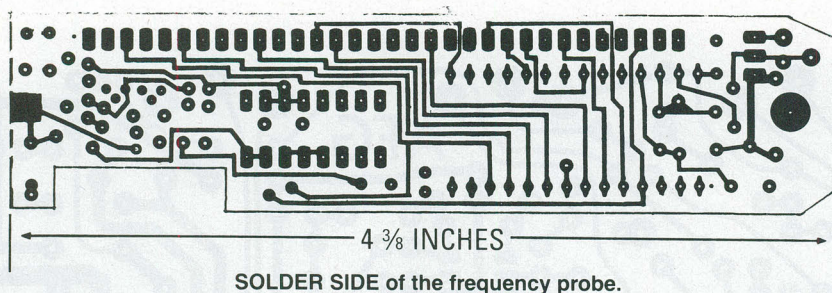



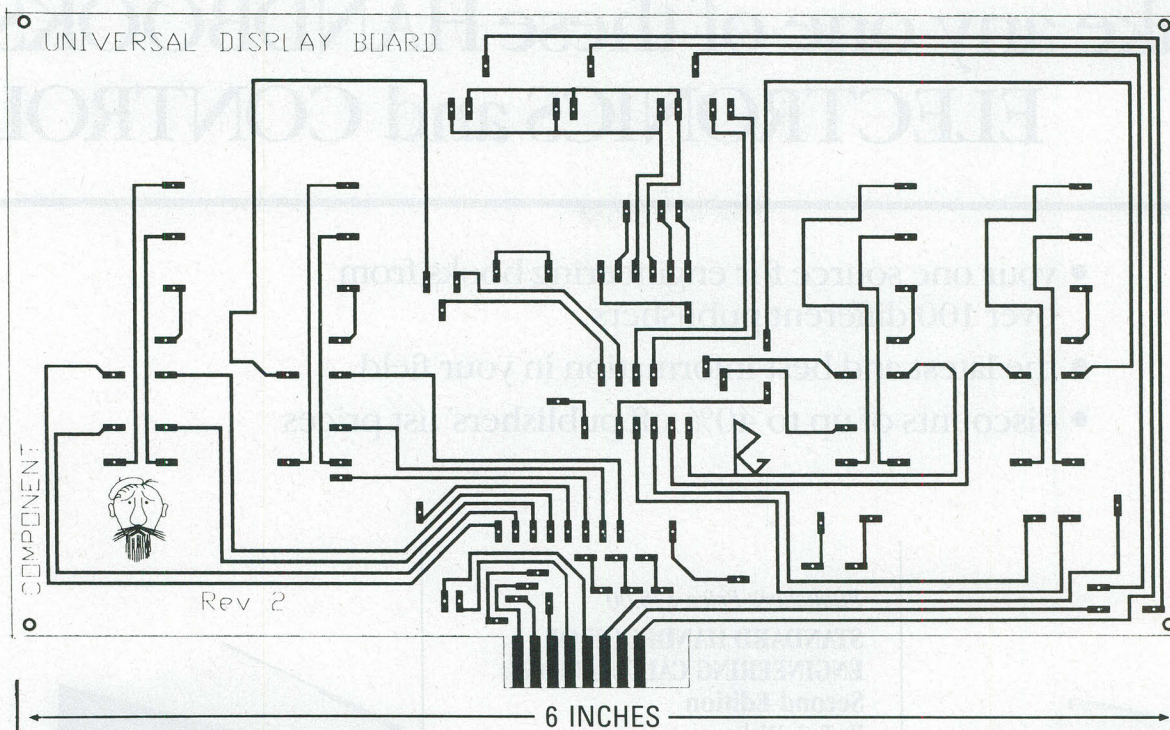

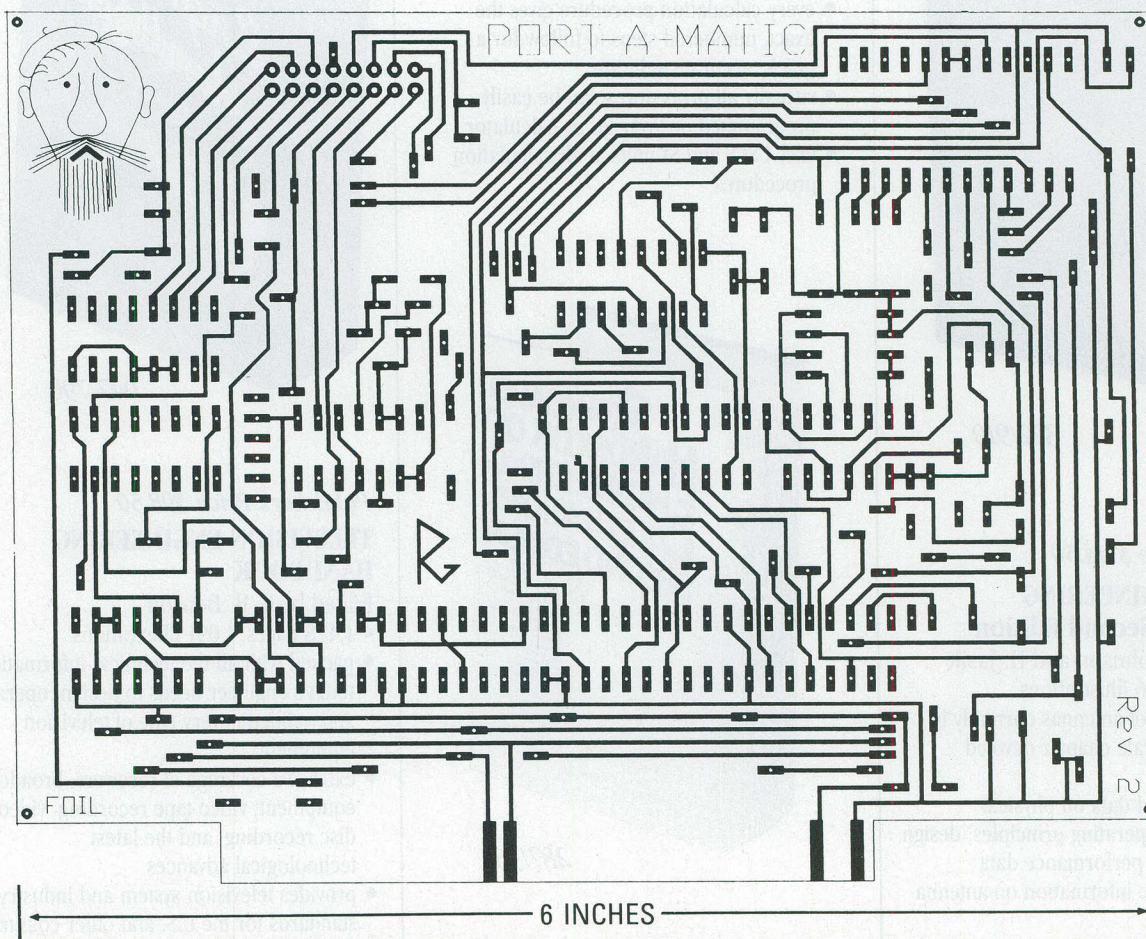COMPONENT SIDE OF THE PORT-A-MATIC'S display board.




SOLDER SIDE OF THE PORT-A-MATIC'S bus-interface board.


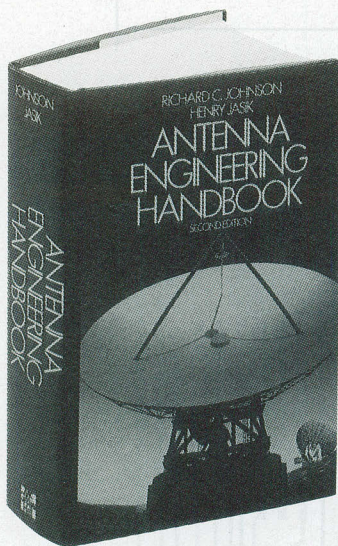
# Take any one of these HANDBOOKS ELECTRONICS and CONTROL

- your one source for engineering books from over 100 different publishers
- the latest and best information in your field
- discounts of up to 40% off publishers' list prices



322/910

*Publisher's Price \$114.50*

## **ANTENNA ENGINEERING HANDBOOK, Second Edition**

Edited by R. C. Johnson and H. Jasik


- 1,408 pages, 946 illustrations
- covers all types of antennas currently in use with a separate chapter devoted to each
- provides detailed data on physical fundamentals, operating principles, design techniques, and performance data
- up-to-the-minute information on antenna applications
- a must for those involved in any phase of antenna engineering

*Publisher's Price \$75.00*

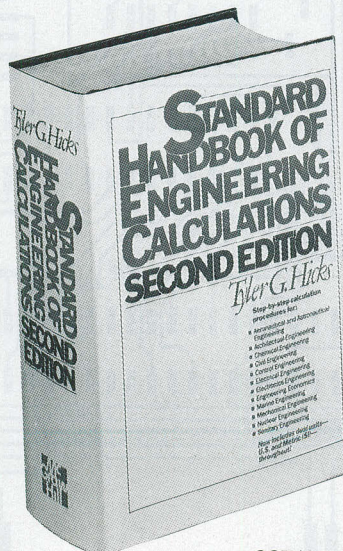
## **STANDARD HANDBOOK OF ENGINEERING CALCULATIONS, Second Edition**

By T. G. Hicks

- 1,468 pages, 793 illustrations, 499 tables
- puts more than 1,100 specific calculation procedures at your fingertips
- every calculation procedure gives the exact, numbered steps to follow for a quick, accurate solution
- virtually all procedures can be easily programmed on your PC or calculator
- uses USCS and SI units in all calculation procedures



287/35X

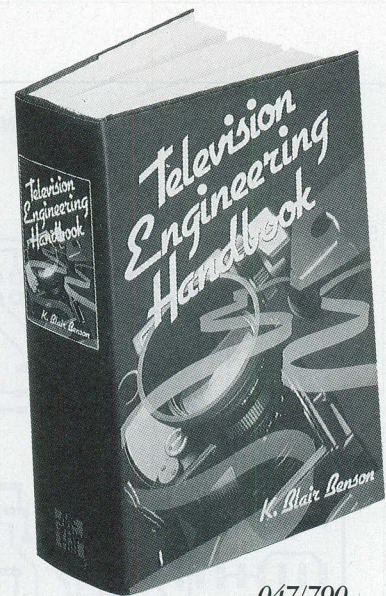

047/790

*Publisher's Price \$98.50*


## **TELEVISION ENGINEERING HANDBOOK**

Edited by K. B. Benson

- 1,478 pages, 1,091 illustrations
- packed with all the technical information today's engineer needs to design, operate, and maintain every type of television equipment
- extensive coverage of receivers, broadcast equipment, video tape recording, video disc recording, and the latest technological advances
- provides television system and industry standards for the U.S. and other countries
- the most comprehensive book on the subject of television engineering


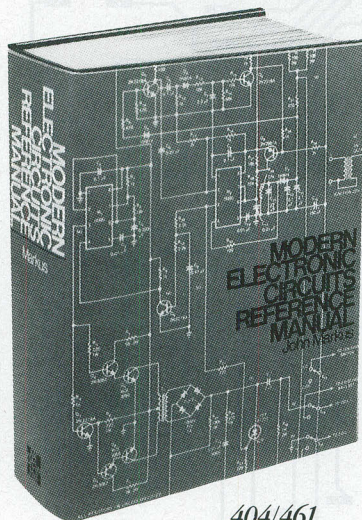
# for only \$14.95 — when you join the ENGINEERS' BOOK CLUB



404/461

*Publisher's Price \$89.95*

## MODERN ELECTRONIC CIRCUITS REFERENCE MANUAL

By J. T. Markus

- 1,264 pages, 3,666 circuit diagrams
- a handy, desktop reference with 103 chapters organized by "family" grouping
- filled with predesigned and use-tested circuits to save you production time and money
- includes concise summaries of all the recent applications notes, journal articles, and reports on each circuit, efficiently organized and indexed for the practicing engineer

values up to  
\$114.50



## 4 reasons to join today!

**1. Best and newest books from ALL publishers!** Books are selected from a wide range of publishers by expert editors and consultants to give you continuing access to the best and latest books in your field.

**2. Big savings!** Build your library and save money, too! Savings range up to 40% off publishers' list prices.

**3. Bonus books!** You will automatically be eligible to participate in our Bonus Book Plan that allows you savings up to 70% off the publishers' prices of many professional and general interest books!

**4. Convenience!** 14-16 times a year (about once every 3-4 weeks) you receive the Club Bulletin FREE. It fully describes the Main Selection and alternate selections. A dated Reply Card is included. If you want the Main Selection, you simply do nothing — it will be shipped automatically. If you want an alternate selection — or no book at all — you simply indicate it on the Reply Card and return it by the date specified. You will have at least 10 days to decide. If, because of late delivery of the Bulletin you receive a Main Selection you do not want, you may return it for credit at the Club's expense.


As a Club member you agree only to the purchase of two additional books during your first year of membership. Membership may be discontinued by either you or the Club at any time after you have purchased the two additional books.

*Publisher's Price \$92.00*
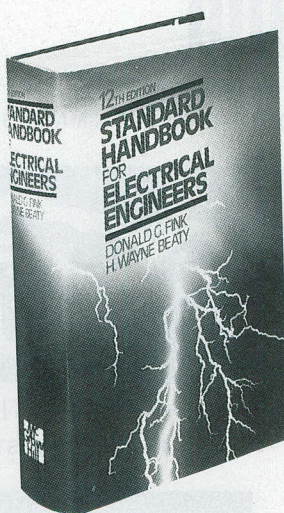
## STANDARD HANDBOOK FOR ELECTRICAL ENGINEERS, Twelfth Edition

Edited by D.G. Fink and H.W. Beaty

- 2,416 pages, 1,388 illustrations, 430 tables
- the essential reference for all electrical engineers
- ranges from basic circuits and measurements to advanced topics, such as power distribution and telecommunications
- fully updated to cover all recent advances and developments
- written and compiled by 115 contributors — all experts in their fields



209/758

FOR FASTER SERVICE IN ENROLLING CALL TOLL FREE 1-800-2-MCGRAW

**McGraw-Hill Book Clubs**  
**Electronics and Control Engineers' Book Club®**  
**P.O. Box 582**  
**Hightstown, NJ 08520-9959**

Please enroll me as a member of the Electronics and Control Engineers' Book Club® and send me the book I have chosen for only \$14.95 plus local tax, postage and handling. I agree to purchase a minimum of two additional books during my first year as outlined under the Club plan described in this ad. Membership in the club is cancellable by me or McGraw-Hill any time after the two book purchase requirement has been fulfilled. A shipping and handling charge is added to all shipments.

I wish to order the following book:

- ☐ ANTENNA ENGINEERING HANDBOOK (322/910)
- ☐ MODERN ELECTRONIC CIRCUITS REFERENCE MANUAL (404/461)
- ☐ STANDARD HANDBOOK FOR ELECTRICAL ENGINEERS, 12/e (209/758)
- ☐ TELEVISION ENGINEERING HANDBOOK (047/790)
- ☐ STANDARD HANDBOOK OF ENGINEERING CALCULATIONS (287/35X)

Signature \_\_\_\_\_

Name \_\_\_\_\_


Address/Apt. # \_\_\_\_\_

City/State/Zip \_\_\_\_\_

This order subject to acceptance by McGraw-Hill. Offer good only to new members. Foreign member acceptance subject to special conditions.

ECGA-025




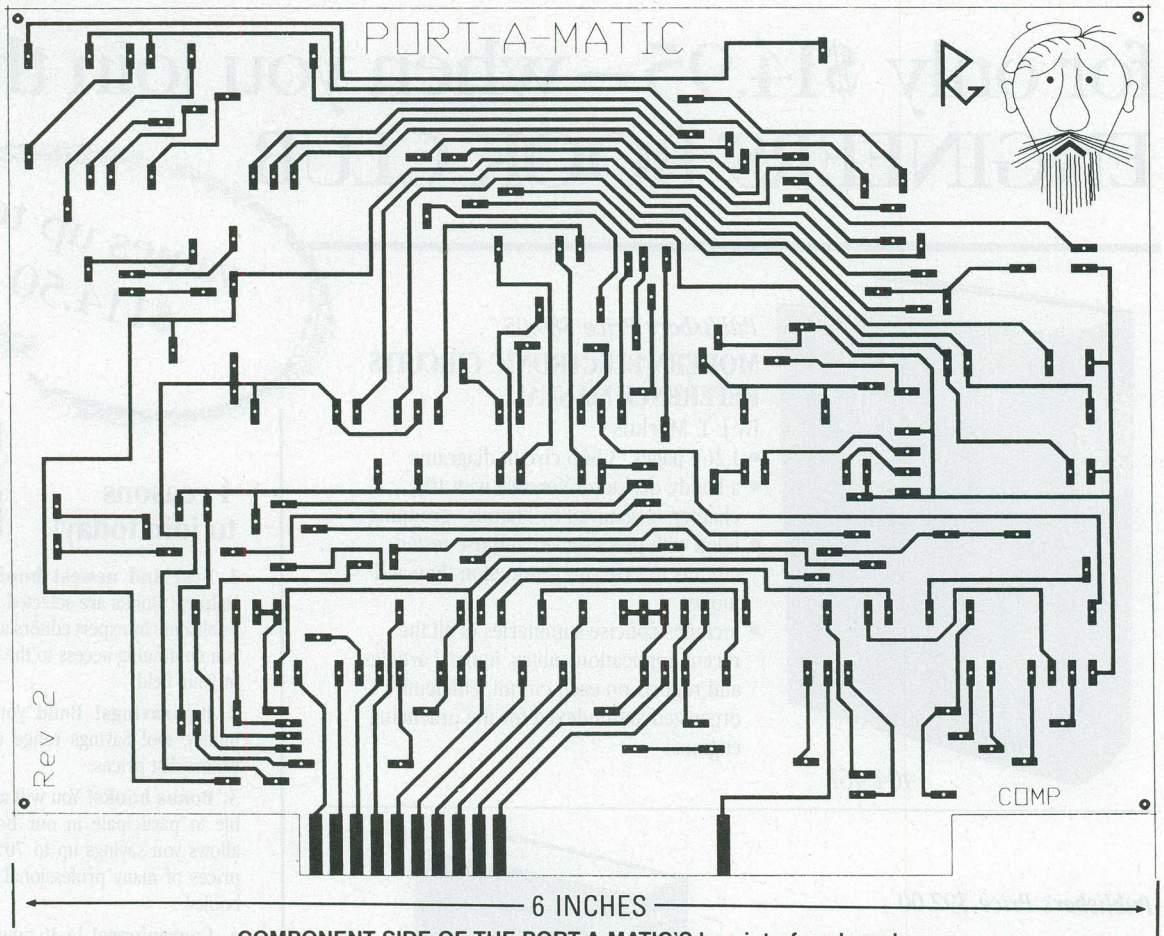

COMPONENT SIDE OF THE PORT-A-MATIC'S bus-interface board.



HEAD-AMP TESTER foil pattern.

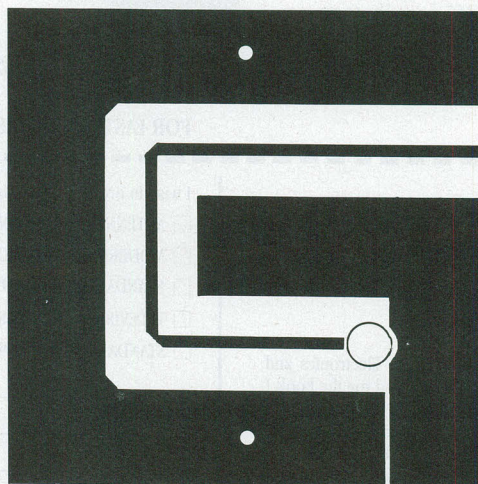

RADAR-DETECTOR TESTER foil pattern.



# HARDWARE HACKER

## Cold-fusion papers and kits

THERE'S LOTS OF EXCITING NEWS THIS month, including cold-fusion kits, an update on the direct-toner printed-circuit process, a major new hacker magazine, and some details on unusual dew-sensor components. So, let's just jump right on in...

### Cold fusion kits

There seems to be lots of good news on the cold-fusion front these days. At a recent conference, several more independent researchers confirmed those excess heat production effects, verified expected nuclear by-products, and made lots of similar supporting observations.

See the October 27th, 1989 *Science* on page 449 for a good summary. The key sentence: "The experimental evidence for cold fusion, or at least some unknown nuclear phenomenon, is too great to ignore."

At the same time, many of those earlier measurements and experiments have been made far more precise, and many possible error sources seem to have been eliminated. In particular, tighter control experiments involving non-deuterium and non-reacting cells have been carried out to the satisfaction of several prominent skeptics. The general feeling seems to be that something really is happening here. And the most reasonable explanation for that something is that cold fusion is actually taking place, or else some previously unknown nuclear reaction seems to be occurring.

On the other hand, the exces-

sive energy production is still very erratic, rather low, and highly unpredictable. Tremendous quantities of time and effort are usually required under extremely careful conditions to get any observable results at all.

There's been two major cold-fusion developments this month that should be of major hardware hacking interest. The first is that all of the key fusion papers are now readily available, and the second is that you can now get your own low-cost (\$27) experimental cold-fusion kit.

By the time you read this, over a hundred key cold-fusion papers should be available by way of that *Dialog Information Service* that you will find through your local library. Figure 1 should get you started. I've listed two dozen earlier papers, gotten through the *INSPEC* service within *Dialog*.

The costs of generating your own complete and up-to-date cold-fusion abstract listing should be around \$35, and should take twenty minutes.

As a reminder, the best sources for current info on cold fusion are in the *News and Comments* section found in *Science* magazine, and the *Technology* section that is

### NEED HELP?

Phone or write your **Hardware Hacker** questions to:  
Don Lancaster  
**Synergetics**  
Box 809-RE  
Thatcher, AZ 85552  
(602) 428-4073

Dew sensor circuits  
Direct toner pc update  
Hacker cold fusion kits  
Midnight Engineering mag  
Alarm & security resources

DON LANCASTER

usually found on page B-4 of your *Wall Street Journal*.

On to those kits: Guy Wicker is a name-brand hardware hacker and a well-known energy researcher. By a special arrangement, Guy has offered to put together several cold-fusion mini-kits for all you **Radio-Electronics** hackers. The kits cost only \$25, plus \$2 shipping and handling.

As Fig. 2 shows us, the kit consists of a small test tube full of a 0.1-molar deuterium and lithium hydroxide solution, a short piece of 50-mil palladium rod, and a small loop of nickel wire. Nickel is used instead of platinum for the anode.

A classic cold-fusion cell is built up something like what you see in Fig. 3. Use a coiled nickel-wire anode, and a nickel suspended palladium-rod cathode. You apply a DC current in the 4 to 20 milliamperes range, with positive to the nickel anode and negative to your palladium cathode.

Be sure to carefully monitor your temperatures at several locations. If possible, also monitor for radiation. A "charging" time of several hours or a few days seems normal for that size palladium rod. Look for both a very low level and a separate "burst mode" excessive heat production effects.

Some sort of a continuous temperature recorder, possibly based on a personal computer, is probably a very good idea. You'll want to work inside of a styrofoam block which itself sits inside a picnic cooler or other well-insulated box.

Guy reports that very small cells like that one are far more likely to



produce a low-level tritium radiation than excess heat production. Getting both to happen at once when someone is watching is usually frustratingly difficult. It is also the Holy Grail of cold-fusion research.

Some warnings here. Your cell is extremely small and the excess heat production, if any, is likely to be correspondingly tiny. Opportunities of cell contamination are very great. Your odds of your cold-fusion cell working at all are only something like one in ten, and the odds of your being able to observe that operation when and as it occurs is also estimated as around one in ten or so. Thus, your estimated odds are only one in one hundred that you will be able to prove your cell actually works.

So, what we have here appears to be a crap shoot.

On the other hand, here you have a sure fire winner for a science fair entry, show-and-tell, or school report. And the "touchy-feely" and "See what I've got!" as-

## NEW FROM DON LANCASTER

### HANDS-ON BOOKS

Hardware Hacker Reprints II	24.50
Ask The Guru Reprints I or II	24.50
CMOS Cookbook	18.50
TTL Cookbook	16.50
Active Filter Cookbook	15.50
Micro Cookbook vol I or II	16.50
Enhancing your Apple I or II	17.50
AppleWriter Cookbook	19.50
Apple Assembly Cookbook	21.50
Incredible Secret Money Machine	10.50
LaserWriter Reference (Apple)	19.50
PostScript Cookbook (Adobe)	16.50
PostScript Ref. Man. (Adobe)	22.50
PostScript Prog. Design (Adobe)	22.50
Real World Postscript (Roth)	22.50

### UNLOCKED SOFTWARE

LaserWriter Corner (Ile/Mac/PC)	29.50
PostScript Show & Tell	39.50
Intro to PostScript VHS Video	39.50
PostScript Beginner Stuff	39.50
PostScript Perspective Draw	39.50
PostScript Technical Illustrations	39.50
PostScript Work in Progress	39.50
PostScript BBS stuff	19.50
Absolute Reset Ile & Iic	19.50
AppleWriter/Laserwriter Utilities	49.50
Enhance I or II Companion Disk	19.50
AppleWriter CB or Assy CB Disk	24.50

FREE VOICE HELPLINE

VISA/MC

**SYNERGETICS**

Box 809-RE  
Thatcher, AZ 85552  
(602) 428-4073

CIRCLE 83 ON FREE INFORMATION CARD

**Triple collision reaction of deuterons as a possible explanation of cold fusion**  
E. Becker, *Naturwissenschaften* (W. Germany), May 1989, Vol 76 #5, pp 214.

#### Cold fusion in metals

J. Kondo, *Journal of the Physical Society of Japan*, June 89, Vol 58 #56, pp 1869-1870.

#### Deuterium nuclear fusion in metals at room temperature

P. Tomas, *Fizika* (Yugoslavia), vol 21 #2, 1989, pp 209-214.

#### Exact upper bound on barrier penetration probabilities for cold fusion

A. Lettitt, *Physics Review Letters*, (USA), Vol 63 #2, 10 July 89, pp 191-194.

#### Cold fusion: how close can deuterium atoms come inside palladium?

Z. Sun, *Physics Review Letters* (USA), Vol 63 #1, 3 July 89, pp 59-61

#### Search for fusion reactions between deuterium atoms implanted into titanium

R. Behrisch, *Nuclear Fusion* (Australia), Vol 29 #7, July 89, pp 1187-1190.

#### Can solid-state effects enhance the cold-fusion rate?

A. Leggett, *Nature*, (UK), Vol 340 #6228, 6 July 89, pp 45-46.

#### Upper limits on neutron and gamma ray emission from cold fusion

M. Gai, *Nature* (UK), Vol 340 #6228 6 July 89, pp 29-34.

#### Calculated fusion rates in isotopic hydrogen molecules

S. Koonin, *Nature* (UK), Vol 339 #6227, 29 June 89, pp 690-691.

#### Search for neutrons during heavy water electrolysis on palladium electrodes

S. Blagus, *Physics of the atomic nuclei* (Germany), Vol 333 #3, 1989, pp 321-322.

#### Search for neutrons from cold nuclear fusion

D. Alber, *Physics of the atomic nuclei* (Germany), Vol 333 #3, 1989, pp 319-320.

#### Screening corrections in cold deuterium fusion rates

K. Langanke, *Physics of the atomic nuclei* (Germany), Vol 333 #3, 1989, pp 317-318.

#### Cold fusion in the solid state?

J. Goedkoop, *Energiespectrum* (Netherlands), Vol 13 #6, June 89, pp 156-162.

#### Nuclear fusion

P. Bullo, *Elettrificazione* (Italy), #5, May 89, pp 57-61.

#### Neutron emission under particular nonequilibrium conditions

P. Perfetti, *Nuovo Cimento D* (Italy), Vol 11D ser. 1 #6, June 89, pp 921-926.

#### Theoretical considerations on the cold nuclear fusion in condensed matter

F. Parmigiani, *Nuovo Cimento D* (Italy), Vol 11D ser. 1 #6, June 89, pp 913-919.

#### Chemical forces associated with deuterium confinement in palladium

J. Mintmire, *Physics Letters A* (Netherlands), Vol 138 #1-2, 12 June 89, pp 51-54.

#### Cold fusion in condensed matter: is a theoretical description possible?

W. Schommers, *Modern Physics Letters B* (Singapore), Vol 3 #8, 20 May 89, pp 597-604.

#### Doubts grow as many attempts at cold fusion fail

B. Levi, *Physics Today* (USA), Vol 42 #6, June 89, pp 17-19.

#### Muon catalyzed fusion

C. Petitjean, *Fusion Engineering Design* (Netherlands), Vol 11 #1-2, June 89, pp 255-264.

#### Opening possibility of deuteron-catalyzed cascade fusion channel

A. Takahashi, *J. Nuclear Science Technology* (Japan), Vol 26 #5, May 89, pp 558-560.

#### Computation of the cold fusion rate

P. Dong, *New Physics* (South Korea), Vol 29 #2, April 89, pp 233-234.

#### The observation of 2.2 MeV gamma-ray in electrochemical cell

Y. Park, *New Physics* (South Korea), Vol 29 #2, April 89, pp 231-232.

#### First steps toward an understanding of "cold" nuclear fusion

T. Bressani, *Nuovo Cimento A* (Italy), Vol 101A ser. 2 #5, May 89, pp 845-849.

#### Emission of neutrons as a consequence of titanium-deuterium interaction

A. De Ninno, *Nuovo Cimento A* (Italy), Vol 101A ser. 2 #5, May 89, pp 841-844.

#### Fermi gas like hypothesis for Fleischmann-Pons experiment

O. Rossler, *Z. Nat. Phys. Chem. Kosmophys* (W Germany), Vol 44A #4, April 89, pp 329.

#### Observation of cold nuclear fusion in condensed matter

S. Jones, *Nature* (UK), Vol 338 #6218, 27 April 89, pp 737-740.

#### Electrochemically induced nuclear fusion of deuterium

M. Fleischmann, *Jour. Electroan. Chem.* (Switzerland), Vol 261 #2A, 10 April 89, pp 301.

#### Cold nuclear fusion

A. Rusu, *Energetica* (Romania), Vol 3 #6, June 88, pp 258-261.

#### On the practical use of the cold fusion (problems and prospects)

Y. Petrov, *Muon Catalyzed Fusion* (Switzerland), Vol 3 #1-4, 1988, pp 525-535.

#### Observation of enhanced low-energy charged-particles in cold fusion

U. Gollerthan, *Physics Letters B* (Netherlands), Vol 201 #2, 4 Feb 88, pp 206-210.


**FIG. 1—SOME KEY COLD-FUSION PAPERS.** For a complete and up-to-date list, use the Dialog Information Service at your local library. Start with their INSPEC resource data base. Fleischmann's paper started it all.

pects of all those kits are completely off scale.

Golly gee, Mr. Science.

Guy also offers fancier cold fusion kits and other products for serious researchers. Contact him



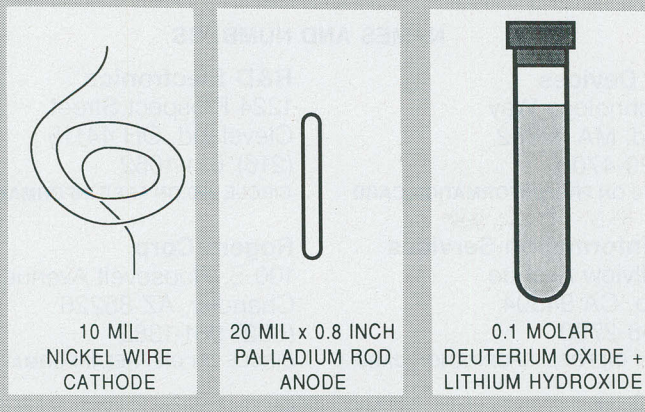

**FIG. 2—LOW-COST HACKER FUSION KITS** consist of a small test tube filled with heavy water, a short palladium-rod anode, and a nickel-wire cathode. While the odds of positive results are rather low, this is a great show-and-tell item.

directly for more information on those kits.

Needless to say, be sure to let us know the outcomes of all your test experiments. That is a wide open field with mind-boggling hacker potential.

#### Midnight engineering

There's a brand new magazine out called *Midnight Engineering*. It is specifically aimed at you hard-

ware hackers and software developers who are trying to market their high-tech products on a small-scale or startup basis. Its shoot-from-the-hip style is very much cast in the same mold as my *Incredible Secret Money Machine*. Emphasis is on real-world solutions and new hacker opportunities. Free sample copies are available to you. It really is a "must have."

#### ALARM & SECURITY SYSTEMS RESOURCES

##### ADEMCO

165 Eileen Way  
Syosset, NY 11791  
(800) 645-7492

CIRCLE 200 ON FREE INFORMATION CARD

##### Alarm Installer & Dealer

2512 Artesia Boulevard  
Redondo Beach, CA 90278  
(213) 376-8788

CIRCLE 201 ON FREE INFORMATION CARD

##### ARIUS

959 Concord Street  
Framingham, MA 01701  
(800) 241-3278

CIRCLE 202 ON FREE INFORMATION CARD

##### Cain Security Systems

2593 Wexford Bayne Rd, S301  
Sewickley, PA 15143  
(412) 934-1000

CIRCLE 203 ON FREE INFORMATION CARD

##### Jensen Tools

7815 South 46th Street  
Phoenix, AZ 85044  
(602) 968-6231

CIRCLE 204 ON FREE INFORMATION CARD

##### King Alarm

145 English Street  
Hackensack, NJ 07601  
(800) 526-0162

CIRCLE 205 ON FREE INFORMATION CARD

##### Security Dealer

210 Crossways Park Drive  
Woodbury, NY 11797  
(516) 496-8000

CIRCLE 206 ON FREE INFORMATION CARD

##### Security Distributing

1350 E Touhy Avenue  
Des Plaines, IL 60017  
(312) 390-2117

CIRCLE 207 ON FREE INFORMATION CARD

##### TechniTool

5 Apollo Road  
Plymouth Meeting, PA 19462  
(215) 825-4990

CIRCLE 208 ON FREE INFORMATION CARD


##### Valley Security

PO Drawer J  
Thatcher, AZ 85552  
(602) 428-2142

CIRCLE 209 ON FREE INFORMATION CARD

#### Printed-circuit update

There sure were a lot of helpline calls and letters over our PostScript direct toner prototype printed-circuit breakthrough in the December issue. I thought I would summarize some of your hacker suggestions to date. They appear in Fig. 4.

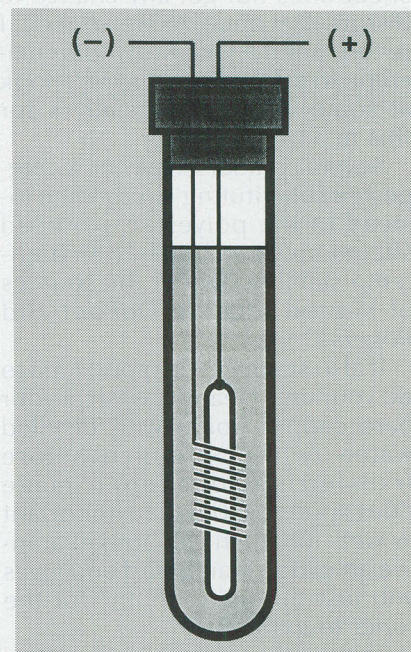

**FIG. 3—A TYPICAL COLD-FUSION test setup.** Apply a DC current around 10 mA. The anode and cathode should not contact. You measure for excess temperature, neutrons, and tritium.

Many of you totally and completely underestimated just how crucially important the PostScript language is to that breakthrough process. Among its many other advantages, PostScript lets you exactly trim your final image size to precisely 1:1; it is totally output-independent, meaning that you can use either a desktop laser printer or a more precise phototypesetter; it easily lets you work 1X, 2X, 4X, forward or backward, normal or reversed, to as many as eight layers at once; it has no upper size or any complexity limit; it is totally host-independent, which allows you to use any old-world processor on any old personal computer; it simply lets you pass layouts over any BBS system in the world as a plain old textfile; and is compatible with virtually all of the existing CAD/CAM programs, either through a direct



PostScript driver or by a PostScript HPGL emulator.

Similarly, using the heated-roller method works far better than an iron. The obvious reasons for that are the far more uniform pressure and temperature. You also gain bunches in dimensional stability, since the Mylar transfer sheet does not get any chance to distort all at once. As we've seen, I recommend a fake *Kroy Kolor* machine to do the transfer. We'll look at some cheaper alternatives for that in a future issue.

Several readers have now suggested substituting *Kapton* film instead of the polyester overhead sheets since it has better high-temp stability. Two of the sources of Kapton include *DuPont* and *Rogers Corp.*

It also seems a very good idea to do your final cleaning wash of your bare copper board with distilled water. A brief pre-etch before transferring your toner image does appear to be quite important as well. The etch will both guarantee an extra-clean board and gives you just the right "tooth" for the toner to grab onto.

Some other suggestions: Pre-heat the copper board as much as you dare before doing the transfer. The idea is to keep the copper from acting as a giant heat sink. Something around 150 degrees Fahrenheit should work. Note that gloves are an absolute must at that temperature.

And run an ice cube on the back of the transfer sheet before separating it from the PC board. That seems to improve the transfer process bunches.

Be sure to send in your own tips and techniques for getting perfect 1:1 toner transfers. When all of the dust settles, we'll try to separate the black magic from the reality and standardize on a useful direct-toner process.

### Alarm and security resources

To continue our ongoing series of resource sidebars, this month we'll look at what you need to know to pick up insider information on burglar alarms and security systems. Those magic names and numbers appear in that *Alarm and Security Resources* sidebar.

As with any field at all, your best

### NAMES AND NUMBERS

#### Analog Devices

One Technology Way  
Norwood, MA 02062  
(617) 329-4700

CIRCLE 210 ON FREE INFORMATION CARD

#### Dialog Information Services

3460 Hillview Avenue  
Palo Alto, CA 94304  
(415) 858-2700

CIRCLE 211 ON FREE INFORMATION CARD

#### DuPont

1007 Market Street  
Wilmington, DE 19898  
(302) 774-1000

CIRCLE 212 ON FREE INFORMATION CARD

#### IGLIDE/IGUS Bearings

PO Box 4349  
Rumford, RI 02914  
(800) 521-2747

CIRCLE 213 ON FREE INFORMATION CARD

#### Kroy Kolor

14555 North Hayden Road  
Scottsdale, AZ 85260  
(800) 521-4997

CIRCLE 214 ON FREE INFORMATION CARD

#### Lehman Scientific RD1 Box 580

Wrightsville, PA 17368

CIRCLE 215 ON FREE INFORMATION CARD

#### Midnight Engineering

PO Box 7041  
Fort Collins, CO 80525  
(303) 491-9092

CIRCLE 216 ON FREE INFORMATION CARD

#### Ming Engineering

977 S. Meridian Avenue  
Alhambra, CA 91803  
(818) 570-0058

CIRCLE 217 ON FREE INFORMATION CARD

#### muRata/Erie

2200 Lake Park Drive  
Smyrna, GA 30080  
(404) 436-1300

CIRCLE 218 ON FREE INFORMATION CARD

#### Panasonic

50 Meadowland Pkwy.  
Secaucus, NJ 07094  
(201) 348-7000

CIRCLE 219 ON FREE INFORMATION CARD

#### R&D Electronics

1224 Prospect Street  
Cleveland, OH 44115  
(216) 621-1052

CIRCLE 220 ON FREE INFORMATION CARD

#### Rogers Corp

100 S. Roosevelt Avenue  
Chandler, AZ 85226  
(602) 961-1382

CIRCLE 221 ON FREE INFORMATION CARD

#### Samsung

3725 N 1st Street  
San Jose, CA 95134  
(408) 434-5400

CIRCLE 222 ON FREE INFORMATION CARD

#### Science/AAAS

1333 H Street NW  
Washington, DC 20005  
(202) 326-6400

CIRCLE 223 ON FREE INFORMATION CARD

#### Synergetics

Box 809  
Thatcher, AZ 85552  
(602) 428-4073

CIRCLE 224 ON FREE INFORMATION CARD

#### Taiyo Yuden

714 W Algonquin Road  
Arlington Heights, IL 60005  
(312) 364-6104

CIRCLE 225 ON FREE INFORMATION CARD

#### Thompson Nyliner

Shore Road & Channel Drive  
Port Washington, NY 11050  
(516) 883-8000

CIRCLE 226 ON FREE INFORMATION CARD

#### Toshiba

1220 Midas Way  
Sunnyvale, CA 94086  
(408) 739-0560

CIRCLE 227 ON FREE INFORMATION CARD

#### Wall Street Journal

420 Lexington Avenue, 14th Fl.  
New York City, NY 10170  
(212) 808-6960

CIRCLE 228 ON FREE INFORMATION CARD

#### Guy Wicker

30437 Fairfax  
Southfield, MI 48076  
(313) 647-1820

CIRCLE 229 ON FREE INFORMATION CARD

bet is to start with the trade journals. A complete list of all trade

journals is available as *Uhlrichts Periodicals Dictionary* on the ref-



1. The PostScript language is essential to the direct toner process. Its totally overwhelming advantages include precise scaling to 1:1, total format flexibility, host and printer independence, easy BBS downloads, and the ability to use nothing but a word processor.
2. Heated roller transfer methods work much better than an iron. Use a fake *Kroy Kolor* machine or its equivalent. The reasons include better stability and tighter temperature control.
3. Use a "dry" (silicon oil free) fuser wiper pad for several copies before your transfer sheet is run.
4. For extreme dimensional stability, try using a *Kapton* film, rather than polyester or mylar.
5. Do your final washing of your cleaned copper board with distilled water.
6. A brief etch before your final washing step is essential to give the proper "tooth" for toner transfer.
7. Preheat the copper to 150 degrees or so before the transfer to minimize any heat sinking effects.
8. Rub an ice cube over the back of the transfer sheet before separating it from the pc board.

FIG. 4—HERE'S AN UPDATE on the direct-toner printed-circuit prototypes we first looked at in the December 89 issue.

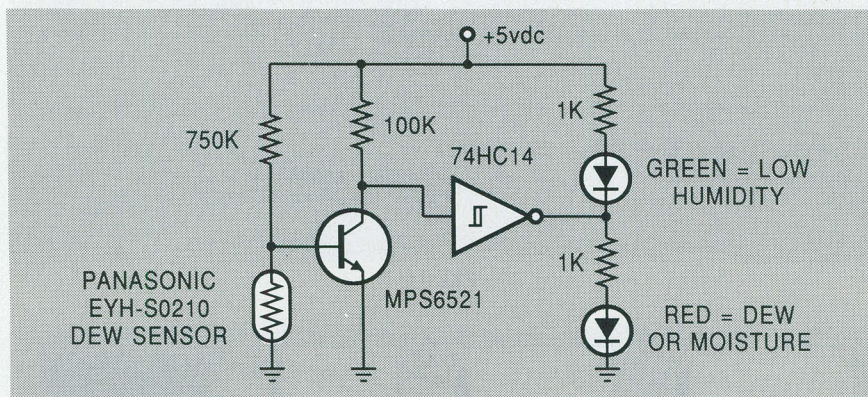


FIG. 5—A DEW-SENSOR TEST CIRCUIT. The red LED lights when the humidity exceeds 100 percent; the green one turns on in the absence of dew.

erence shelf at your neighborhood library. A second source that is almost as good is the *International Standard Periodicals Dictionary* on the same shelf.

Typical trade journals for the field include *Security Dealer*, the *Security Distributing and Marketing*, and the *Alarm Installer and Dealer*.

Trade shows play an important part of the alarm industry. A pair of the largest are the *International Security Conference and Exposition*, and *The Security Show*. They do move around from town to town. Check any of the trade journals for the show dates.

There are a number of specialty wholesale distributors that cater to the alarm trade. You'll find lots of ads for them in all the trade journals and their directories. Three

larger examples are *King Alarm*, *Arius*, and *Ademco*.

Two sources of general installation tools and test instruments include *Jensen Tools* and *TechniTool*. Sadly, both of those yuppieized outfits are rather pricey. But all of their products happen to be both first-rate and top-quality.

There are now hundreds of security consultants that will be glad to help you for a sane and reasonable fee. Two examples here are Wyatt Palmer (no relation) of *Valley Security*, and Jeff Lancaster (my widdle brudder) of his *Cain Security Systems*.

Please let me know if you know of any other similar kinds of resources that you think should be added to the list.

*continued on page 74*

Get A Complete Course In

## ELECTRONIC ENGINEERING

8 volumes, over 2000 pages, including all necessary math and physics. 29 examinations to help you gauge your personal progress. A truly great learning experience.

Prepare now to take advantage of the growing demand for people able to work at the engineering level.

Ask for our brochure giving complete details of content. Use your free information card number, or write us directly. **\$99.95**, Postage Included. Satisfaction guaranteed or money refunded.



**Banner  
Technical  
Books, Inc.**

1203 Grant Ave.  
Rockford, IL 61103

CIRCLE 67 ON FREE INFORMATION CARD

## 33 Ways to Help You Qualify for the Job You Want

Free Facts about Career  
Diplomas and Degrees

Now at home in your spare time, without any previous experience, you can train for a money-making career...even get a Specialized Associate Degree. Call or send for free information on the career field that interests you most and how to train for it.

CALL  
TOLL-  
FREE

**1-800-228-5300** Dept. DES10

CALL ANYTIME—24 hours a day, 7 days a week  
No cost. No obligation. No salesman will visit.  
OR MAIL COUPON TODAY

**ICS**  
SINCE 1890

**International Correspondence Schools**

Dept. DES10, 925 Oak Street, Scranton, PA 18515

Send free facts on how I can study at home for the career I have chosen. No obligation. No salesman will visit. **CHECK ONE BOX ONLY.**

**ASSOCIATE IN SPECIALIZED BUSINESS DEGREE PROGRAMS**

- ☐ Business Management
- ☐ Accounting
- ☐ Business Management with option in Marketing
- ☐ Business Management with option in Finance

**ASSOCIATE IN SPECIALIZED TECHNOLOGY DEGREE PROGRAMS**

- ☐ Mechanical Engineering Technology
- ☐ Civil Engineering Technology
- ☐ Electrical Engineering Technology
- ☐ Electronics Technology

**CAREER DIPLOMA PROGRAMS**

- ☐ Computer Programming
- ☐ Personal Computer Specialist
- ☐ High School
- ☐ Catering/Gourmet Cooking
- ☐ Microcomputer Repair
- ☐ Auto Mechanics
- ☐ Bookkeeping
- ☐ Hotel/Restaurant Management
- ☐ Drafting
- ☐ Air Conditioning & Refrigeration
- ☐ Electronics
- ☐ Electrician
- ☐ Police Sciences
- ☐ Art
- ☐ Small Business Management
- ☐ Wildlife/Forestry Conservation
- ☐ Diesel Mechanics
- ☐ Gun Repair
- ☐ Motorcycle Repair
- ☐ Surveying & Mapping
- ☐ TV/VCR Repair
- ☐ Veterinary Assistant
- ☐ Travel Agent
- ☐ Photography
- ☐ Journalism/Short Story Writing

Name \_\_\_\_\_ Age \_\_\_\_\_  
Address \_\_\_\_\_ Apt. # \_\_\_\_\_  
City/State \_\_\_\_\_ Zip \_\_\_\_\_  
Phone( ) \_\_\_\_\_

A Subsidiary of National Education Corporation

CIRCLE 185 ON FREE INFORMATION CARD



# DRAWING BOARD



ROBERT GROSSBLATT,  
CIRCUITS EDITOR

## A crystal-controlled video timing generator.

WHEN YOU START FOOLING AROUND with video circuitry, there are three things you always have to keep in mind: timing, timing, and, above all else, timing. The key to designing video circuits is making sure that the right voltages show up at the right time. The values can be slightly off, but if they don't show up exactly when they're supposed to, they might just as well not show up at all.

Since video is fairly complex, everyone has his or her own ideas about the best way to get into it. Theory is important; after all, the video waveform is an agreed-upon standard, and you have to understand its component parts before you can design hardware to produce it. But the best way to learn is to do, and the easiest way to pick up theory is by having it demonstrated; so let's see what's involved in designing basic hardware.

### Hardware basics

The waveform in Fig. 1 is one line of National Television Standards Committee (NTSC) standard horizontal color video. We've already discussed its component parts, but this time I've included all the timing. There are several basic frequencies to be generated, and the pulse width is strictly defined. National Semiconductor, and other manufacturers, make IC's that can take a basic clock frequency in at one end, and put out all needed video frequencies at the other end. They are good chips for designing real-world circuitry, and we'll look at some later; but first let's re-invent the wheel so we know how it works.

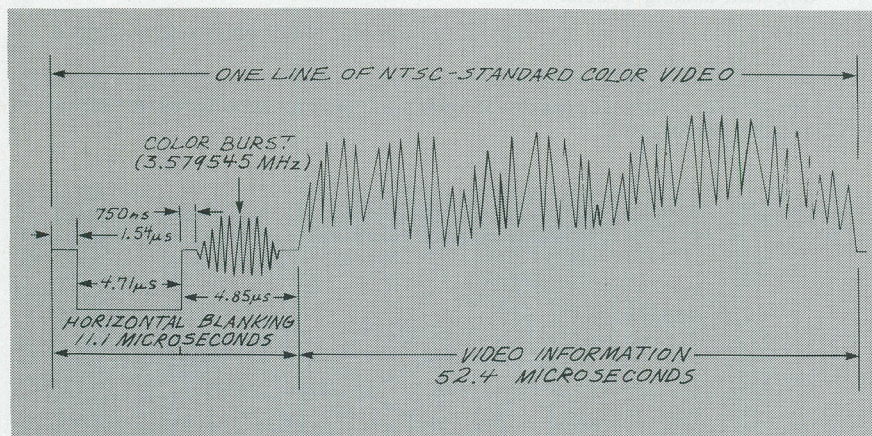


FIG. 1

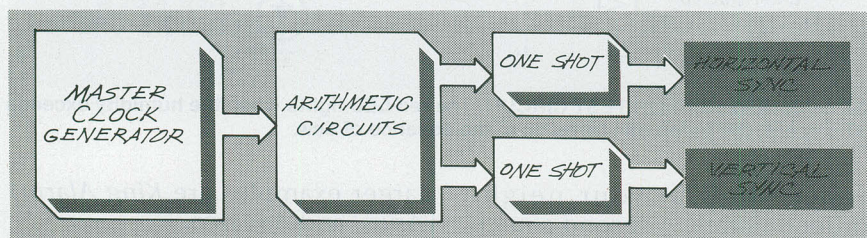


FIG. 2

Designing a video sync generator is an exercise in pure logic and arithmetic. We need clock generators to control production of the needed frequencies, and one-shots to produce pulses of the right width. Since the most basic signal needed is horizontal sync, that's the place to start.

The block diagram in Fig. 2 gives a good overview of the circuit to be designed. There's a master clock generator, whose frequency is divided down to produce horizontal and vertical sync clocks. They will trigger pulse generators to output the actual sync pulses. By deriving everything from a master clock, the generated sync sig-

nals maintain constant timing with regard to one another, an absolute must for video. The sync-generator accuracy will depend completely on that of the master clock, so we have to use a crystal-based circuit. That creates certain problems, but it's the best way to go.

### The master clock

Crystal oscillators used to be exotic and expensive, but are now cheap and easy to build. The issue now is what frequency to use, and what chip will produce it. Everyone has his or her own preferences, but one that's often overlooked is the 8284 shown in Fig. 3, in an appropriate oscillator



circuit. It was originally designed by Intel as the basic clock for the 808X microprocessors, and any 808X-based computer will have one on the motherboard. Its frequencies and duty cycles are really geared to Intel's microprocessors, but it's a handy general-purpose clock generator, also.

Most of the 8284 control pins like  $\overline{\text{AEN1}}$  (pin 3),  $\overline{\text{AEN2}}$  (pin 7),  $\text{RDY1}$  (pin 4),  $\text{RDY2}$  (pin 6),  $\text{READY}$  (pin 5), and  $\text{CSYNC}$  (pin 1) are used only when you're using the chip in a computer; we won't use them here. They have to be tied either high or low to make the chip work for our purposes.

All we want the 8284 to do is to act as a stable oscillator. That's easy to set up, and the 8284 has several free extras. The pins used here are crystal inputs  $\text{X1}$  (pin 17) and  $\text{X2}$  (pin 16), and clock outputs  $\text{OSC}$  (pin 12),  $\text{CLK}$  (pin 8), and  $\text{PCLK}$  (pin 2).

In Fig. 3, the 8284 takes the crystal and provides three different output clocks. The  $\text{OSC}$  output (pin 12) is a buffered version of the crystal frequency, the  $\text{CLK}$  output (pin 8) is  $\frac{1}{3}$  the crystal frequency at a 33% duty cycle, and  $\text{PCLK}$  (pin 2) is half the  $\text{CLK}$  frequency with a 50% duty cycle. The  $\text{CLK}$  output has an unusual duty cycle for use with an Intel microprocessor.

Also, note the  $\text{F/C}$  (Frequency or Crystal) input on pin 13. Since the chip is a collection of flip-flops and buffers, it needs an input frequency divided down internally to provide the output clocks. The state of  $\text{F/C}$  determines the origin of the input clock. If  $\text{F/C}$  is tied low, the 8284 will look at its internal oscillator, the frequency of which depends on the crystal hanging off inputs  $\text{X1}$  and  $\text{X2}$ . If  $\text{F/C}$  is high, the 8284 will look at the clock being fed to  $\text{EFI}$  (External Frequency In) input at pin 14.

That means that you can change the output clocks simply by changing the logic level on  $\text{F/C}$  (pin 13). Most two-speed IBM-XT clones use that feature to switch from "normal" to "turbo" speed. By trapping a scan code from the keyboard and using it to toggle a flip-flop, they change the level of  $\text{F/C}$ , and switch the master clock speed of the microprocessor, giving a two-speed computer.

Now that we have a circuit to

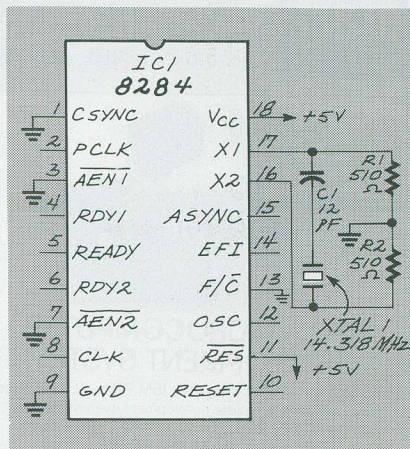



FIG. 3

produce our clock, we have to decide on what clock to produce. It would be really nice if all the frequencies needed were derivable from one easily available crystal frequency, but they're not. There's just no easy number to provide everything we need. For reasons that'll become apparent when we are farther along in our design, 14.318 MHz is a good choice. One obvious reason is that division-by-four will give 3.579545 MHz, the colorburst frequency. Getting a horizontal frequency of 15734 kHz, however, will take a little more work than that.

The 12-pF capacitor in series with the crystal helps start the 8284's internal oscillator. Since it's similar to an amplifier, the resistance of the crystal network has to be kept as low as possible. If it's too high, the gain drops; and if it's too low, it won't oscillate. The two resistors reduce the effects of stray board capacitance and voltage fluctuations on the frequency. A breadboard is a good choice for construction, but there's considerable capacitance between rows. Since the crystal frequency is pretty high, that stray capacitance can wreak havoc, so the two resistors will keep the oscillator frequency fairly stable.

If your oscillator frequency is outside the 14.3–14.4 MHz range, there's a problem on the breadboard. The easiest way to fix it is to accept the breadboard-induced error as unavoidable, and correct the frequency by varying the capacitor value over 4.7–47 pF. If you're really ambitious, replace it with a small trimmer capacitor. R-E
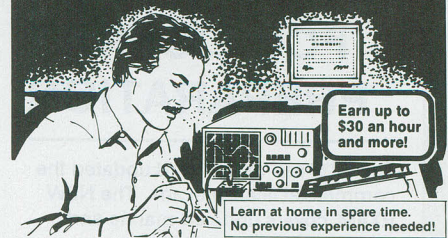
# Be an FCC LICENSED ELECTRONIC TECHNICIAN!



No costly School. No commuting to class. The Original Home-Study course prepares you for the "FCC Commercial Radiotelephone License". This valuable license is your "ticket" to thousands of exciting jobs in Communications, Radio-TV, Microwave, Computers, Radar, Avionics and more! You don't need a college degree to qualify, but you do need an FCC License.

## No Need to Quit Your Job or Go To School

This proven course is easy, fast and low cost! **GUARANTEED PASS**— You get your FCC License or money refunded. **Send for FREE facts now. MAIL COUPON TODAY!**

### COMIMAND PRODUCTIONS

FCC LICENSE TRAINING, Dept. 90  
P.O. Box 2824, San Francisco, CA 94126

Please rush FREE details immediately!

NAME \_\_\_\_\_  
ADDRESS \_\_\_\_\_  
CITY \_\_\_\_\_ STATE \_\_\_\_\_ ZIP \_\_\_\_\_

## NEW SUPER LONG PLAY TAPE RECORDERS

12 Hour Model — \$119.00\*  
USES D-120 TAPE

Modified Panasonic Slimline, high quality, AC-DC Recorders provide 6 continuous hours of quality recording & playback on each side of cassette for a total of 12 hours. Built-in features include: • Voice level control, • Digital counter, etc. TDK DC 120 Cassette Furnished.



## PHONE RECORDING ADAPTER

Records calls automatically. All Solid state connects to your telephone jack and tape recorder. Starts recording when phone is lifted. Stops when you hang up. **\$28.50\*** FCC APPROVED



## VOX VOICE ACTIVATED CONTROL SWITCH

Solid state. Self contained. Adjustable sensitivity. Voices or other sounds automatically activate and control recorder. Uses either recorder or remote mike. **\$28.50\***



\*Add for ship & hdg. Phone Adapter & Vox \$1.50 ea. Records \$4.00 ea. Cal. Res. add tax. Mail order, VISA, M/C, COD's OK. Money Back Guarantee. Qty. disc. avail., Dealer Inquiries invited, Free data. **AMC SALES INC. Dept. A9335 Lubec St., Box 928, Downey, CA 90241 Phone (213) 869-8519**



# R-E Engineering Admart


Rates: Ads are 2 1/4" x 2 7/8". One insertion \$950. Six insertions \$925. each. Twelve insertions \$895. each. Closing date same as regular rate card. Send order with remittance to **Engineering Admart**, Radio Electronics Magazine, 500-B Bi-County Blvd., Farmingdale, NY 11735. Direct telephone inquiries to Arline Fishman, area code-516-293-3000. **Only 100% Engineering ads are accepted for this Admart.**

## FCC LICENSE PREPARATION

The FCC has revised and updated the commercial license exam. The **NEW EXAM** covers updated marine and aviation rules and regulations, transistor and digital circuitry. **THE GENERAL RADIOTELEPHONE OPERATOR LICENSE - STUDY GUIDE** contains vital information. **VIDEO SEMINAR KITS ARE NOW AVAILABLE.**

WPT PUBLICATION  
979 Young Street, Suite A  
Woodburn, Oregon 97071  
Phone (503) 981-5159

CIRCLE 181 ON FREE INFORMATION CARD

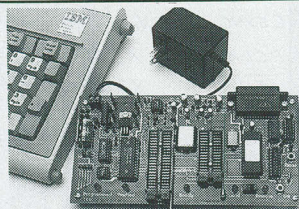

## 6805 MICROCOMPUTER DEVELOPMENT SYSTEM

The MCPM-1 system allows the IBM PC and compatibles to be used as a complete development system for the Motorola MC68705P3, P5, U3, U5, R3 and R5 single chip microcomputers. The system includes a cross assembler program, a simulator/debugger program and a programming board that connects to a serial port. Price—\$449.00 VISA and MASTERCARD accepted.


**TECI** THE ENGINEERS COLLABORATIVE, INC.

RR#3, BOX 8C Barton, Vermont 05822  
Phone (802) 525-3458 FAX (802) 525-3451

CIRCLE 193 ON FREE INFORMATION CARD

## Surface Mount Chip Component Prototyping Kits—

Only \$49<sup>95</sup>

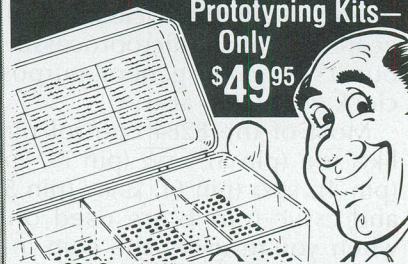

CC-1 Capacitor Kit contains 365 pieces, 5 ea. of every 10% value from 1pf to .33µf. CR-1 Resistor Kit contains 1540 pieces; 10 ea. of every 5% value from 10Ω to 10 megΩ. Sizes are 0805 and 1206. Each kit is ONLY \$49.95 and available for Immediate One Day Delivery!

Order by toll-free phone, FAX, or mail. We accept VISA, MC, AMEX, COD, or Pre-paid orders. Company P.O.'s accepted with approved credit. Call for free detailed brochure.

**COMMUNICATIONS SPECIALISTS, INC.**  
426 West Taft Ave. • Orange, CA 92665-4296  
Local (714) 998-3021 • FAX (714) 974-3420

Entire USA 1-800-854-0547

CIRCLE 182 ON FREE INFORMATION CARD

## HARDWARE HACKER

continued from page 71

### Dew sensors

We've looked at humidity sensors in several earlier columns. One unique and low-cost humidity detector is called a *dew sensor*. They cost only a dollar each and are intended to protect moisture-sensitive VCR drums.

Three typical part numbers would be the *Murata* HOS 101-100, the *Taiyo Yuden* TD-P-100, or that *Panasonic* EYH-S0210.

At a 100 percent humidity, the air retains all of the moisture it possibly can. Beyond that, the moisture in the air will condense out, forming a rain or a dew coating.

A special moisture-sensing paint dramatically raises its resistance well beyond 1 Megohm whenever it gets wet. Thus, your sensor is typically at 10K when dry and 1 Megohm when wet. A good decision point is to split up the difference on a log basis, and do your tripping at a 100K level.

Figure 5 shows you one possible sensing circuit. Because you have to keep the total system power under two milliwatts, the maximum DC voltage that you are allowed to apply is only 0.8 volts. The sensor acts as a current-robber. At low humidities, the sensor's resistance is

around 10K and steals so much current, that the NPN transistor remains off. When wet, the sensor impedance goes above 1 megohm, and conventional current flows into the base of the NPN transistor, turning it on.

That inverting CMOS *Schmitt* trigger gives you an on-off snap action. Your red light-emitting diode lights when wet and the green when dry.

Tellyawhat. For this month's contest, just tell me about a new or unique use for dew sensors. There will be all of those usual *Incredible Secret Money Machine* book prizes going to the best dozen or so entries, with an all expense paid (FOB Thatcher, AZ) *tinaja quest* for two for the best of all.

As usual, all entries must be written and should be sent directly to me here at *Synergetics*, rather than to the editor of *Radio-Electronics*. Show me what you can come up with.

### New tech literature

Data books this month include the *Data Conversion Products Databook* from *Analog Devices*, and an absolutely astounding new *Semiconductor Product Guide* from *Samsung*. That latter gem is chock full of new hacker integrated circuits for use as scientific calculators, speech synthesis, melody chips, cassette recorders,

watches, for alarm clocks, and bunches more.

Two surplus catalogs are available from *R&D Electronics*, and *Lehman* has weather radiosonde transducers that include humidity, pressure, and temperature sensing for only \$3.50. Stock number is MC-1019-MOD.

Some surprisingly cheap and high-quality digital voice recording and playback modules are available from *Ming Engineering*. The single-quantity prices start at \$49. They are all fully EPROM-programmable. They apparently use that new *Toshiba* TC8830F speech synthesis chip.

Turning to mechanical stuff, low-cost nylon bearings and a free calculator are available from *Thompson Nyliner*, while the *IGUS* folks offer all sorts of the self-lubricating plastic bearings. Prices for them start at fifteen cents in quantity.

A reminder here that I am book-on-demand publishing a complete set of the edited, indexed, and updated reprints of everything you've seen here in these columns since day one. Ask for my *Hardware Hacker*, volume II, now available through *Synergetics*.


For those of you who are not yet into PostScript, I also stock an *Intro to PostScript* VHS video that shows you what you need in order

continued on page 88



# COMPUTER DIGEST

## BUILD THE PORT-A-MATIC

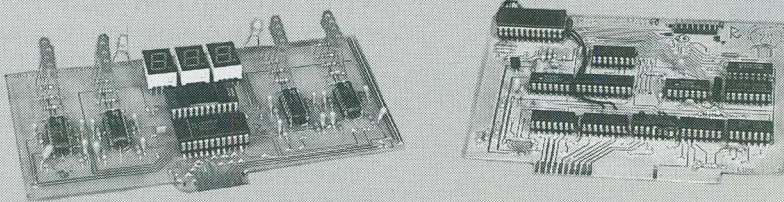

*Building the Port-A-Matic*

ROBERT GROSSBLATT

**T**he Port-A-Matic is a fairly complex circuit that depends on tight signal timing. Although you could wirewrap it on perf board, you're better off using a PC board; patterns are shown in PC Service and a supplier is listed in the "ordering information" box.

The Port-A-Matic was designed to be built on two PC boards; an internal bus interface (that installs in any 8- or 16-bit PC-compatible expansion slot) and an external display board. The two boards are connected by ribbon cable, and the pins are arranged in the same order on both boards so you can use a straight-through ribbon-cable connection.

Sixteen conductors are required, but you'll probably want to use 20-conductor cables, because they're easy to obtain (and inexpensive) because they're used as data cables connecting controller cards and hard-disk drives in PC compatibles.

To install the components, use the diagrams shown in Fig. 1 and


Fig. 2. Of course, be sure to observe the polarity of diodes, transistors, electrolytic capacitors, and IC's. None of the IC's on the board are rare or expensive, but you should still be careful when you're handling them since blown IC's look an awful lot like good ones.

Since you'll probably make occasional changes to the look-up table in the EPROM, you'll want to install it in an IC socket. In fact, all IC's should be socketed because there is no absolutely safe way to desolder a suspect IC. If you suspect that an IC is fried, desoldering it to check it may make your suspicion a reality if you don't know what you're doing!

Although you can put parts on the board in any order you want, assembly is easier if you start with the IC sockets, then go through the passive components (resistors and capacitors), and finally the active components (diodes and transistors). That's a good order to follow because

*continued on page 78*

## EDITOR'S WORK- BENCH

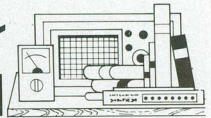

### Announcement

**M**ario Maniscalco's \$100 challenge to Computer Digest readers to crack the secret message published in the April 1988 issue has gone unanswered, so he will now send the key to anyone who sends an SASE to P.O. Box 110082, Cleveland, OH 44111. (The address published in the October 1989 issue is incorrect.) Mario also plans a newsletter on the encryption program; write to him at that address for more information.

### Modular IC programming system

**I**t wasn't so long ago when EPROM's were novelties, and 2716's (2K bytes) were considered high density. Now 64K EPROM's are common, 128K EPROM's are becoming economical, and there are several other types of programmable devices, including PAL's, EEPROM's, standard bipolar PROM's, and more. You can spend thousands of dollars for a universal programmer for different types of devices. Or you can latch onto JDR's modular system, let your PC provide the intelligence, and buy only the modules you need when you need them.

Several modules are available. I



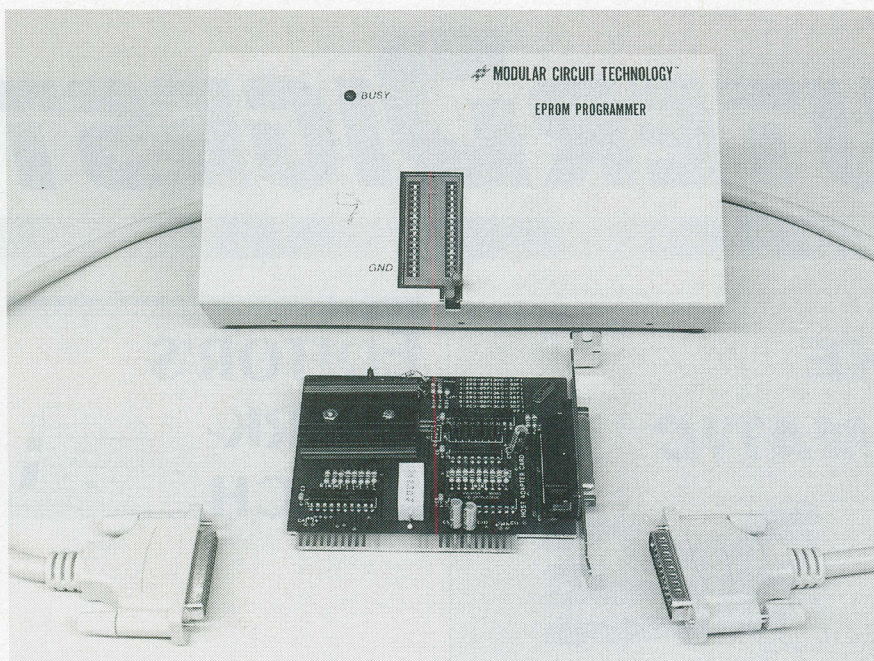


FIG. 1

```

MCT  E(E)PROM PROGRAMMER  V1.0  * MFG.: DON'T CARE  * ZIP.: 1 socket
MODEL : MCT-MEP  (C) SEP 1988  * TYP.: 27C256  * PROG.: intelligent
By Modular Circuit Technology  # Vpp.: 12.5V  # VCC.: 6.0V
MAIN MENU :
=====
1. DIR
2. LOAD OBJ FILE TO MEMORY BUFFER
3. SAVE MEMORY BUFFER TO DISK
4. DEBUG MEMORY BUFFER
5. GANG SIZE
6. PROGRAMMING ALGORITHM
7. SET MEMORY BUFFER SIZE
M. MANUFACTURER
T. TYPE
B. BLANK CHECK
P. PROGRAM      A. AUTO
R. READ         V. VERIFY
C. COMPARE      D. DISPLAY & EDIT
Q. QUIT

SELECT WHICH NUMBER ?

```

FIG. 2

tested the EPROM/EEPROM module (shown in Fig. 1), which lists for about \$120; 4-, 8-, and 16-socket versions are available for volume production. Other programmers include one for PAL's (\$250), one for micro-processors (\$180), and one for bipolar PROM's (\$260). An IC tester20 is also available for \$130, and PAL development software for \$100. Each module includes a ZIF (Zero Insertion Force) socket

(or several, for the multi-gang models).

If you're planning to buy two or more modules, you'd probably be better off going with the Universal Module, which lists for about \$500, and can perform all functions of the individual modules.

Whichever module(s) you choose, you'll need a \$30 host adapter/cable. The adapter is a short card that fits in any 8- or 16-bit expansion slot. The cable

is a quality molded 25-conductor job with 25-pin D connectors on both ends. Unfortunately, the connector on the card is identical to a standard PC printer connector; make sure you don't connect a printer cable to that port—a high-voltage pulse could have the misfortune of frying your printer instantly!

Installing the card requires setting a couple of jumpers that determine the card's I/O address. Installing the software consists of copying the contents of a 360K disk to a subdirectory on your hard disk, and then running a setup program in which you specify your computer type and speed. Neither my computer type nor its speed were listed, but I picked the closest match and had no trouble.

The module can program all common and several uncommon EPROM's that you might want to use ranging from the 2716 to the 27010, CMOS versions thereof, and 2816, 2817, and 2864 EEPROM's. However, it can't program paged EPROM's, such as the 27011.

The software is menu-driven, as shown in Fig. 2. You can list a directory and load a file into a memory buffer. You can then modify the contents of that buffer using either the software's built-in editor or DEBUG.COM, which

#### ITEMS DISCUSSED

- 75C188N driver, 75C189N receiver (\$0.75/M), Texas Instruments, Literature Center, P.O. Box 809066, Dallas, TX 75380-9066.

CIRCLE 48 ON FREE INFORMATION CARD

- The XT-AT Handbook (\$9.95), John Choisser and John Foster, Annabooks, 12145 Alta Carmel Court, Suite 250-262, San Diego, CA 92128. (619) 271-9526.

CIRCLE 47 ON FREE INFORMATION CARD

- (E)EPROM Programmer (MOD-MEP, \$119.95) and host adapter (MOD-MAC, \$29.95), JDR Microdevices, 2233 Branham Lane, San Jose, CA 95124.

CIRCLE 46 ON FREE INFORMATION CARD



# R-E Computer Admart

**Rates:** Ads are 2 1/4" x 2 7/8". **One** insertion \$950. **Six** insertions \$925 each. **Twelve** insertions \$895 each. Closing date same as regular rate card. Send order with remittance to **Computer Admart**, Radio Electronics Magazine, 500-B Bi-County Blvd., Farmingdale, NY 11735. Direct telephone inquiries to Arline Fishman, area code-516-293-3000. **Only 100% Computer ads are accepted for this Admart.**

## GETTING THE MOST FROM YOUR PRINTER

Getting The Most From Your Printer



**BP181**—It is probable that 80% of dot-matrix printer users only ever use 20% of the features offered by their printers. This book will help you unlock the special features and capabilities that you probably don't even know exist. To order your copy **send \$6.95 plus \$1.50 for shipping** in the U.S. to **Electronic Technology Today Inc., P.O. Box 240, Massapequa Park, NY 11762-0240.**

## SECRETS OF THE COMMODORE 64

Secrets of the COMMODORE 64



**BP135**—A beginners guide to the Commodore 64 presents masses of useful data and programming tips, as well as describing how to get the best from the powerful sound and graphics facilities. We look at how the memory is organized, random numbers and ways of generating them, graphics-color and simple animation, and even a chapter on machine code. Get your copy today. **Send \$5.00 plus \$1.25 for shipping** in the U.S. to **Electronic Technology Today Inc., P.O. Box 240, Massapequa Park, NY 11762-0240.**

## ICs PROMPT DELIVERY!!!

SAME DAY SHIPPING (USUALLY)  
QUANTITY ONE PRICES SHOWN FOR OCT. 22, 1989  
OUTSIDE OKLAHOMA: NO SALES TAX

DYNAMIC RAM			
SIMM	AST Prem386/33Mhz		\$300.00
SIMM	(1) 256Kx36	80 ns	300.00
SIMM	(1) 1Mx9	80 ns	122.00
SIMM	(2) 256Kx9	100 ns	35.00
1Mbit	1Mx1	100 ns	11.25
41256	256Kx1	60 ns	4.95
41256	256Kx1	80 ns	3.95
41256	256Kx1	100 ns	2.80
41256	256Kx1	120 ns	2.65
4464	64Kx4	120 ns	3.75
41264 (3)	64Kx4	100 ns	7.95
EPROM			
27C1000	128Kx8	200 ns	\$20.75
27S12	64Kx8	200 ns	7.80
27256	32Kx8	150 ns	6.50
27128	16Kx8	250 ns	4.25
STATIC RAM			
62256P-10	32Kx8	100 ns	\$12.95
6264P-12	8Kx8	120 ns	4.85
6116AP-12	2Kx8	120 ns	4.50

OPEN 6 1/2 DAYS, 7:30 AM-10 PM. SHIP VIA FED-EX ON SAT.  
SAT DELIVERY INCLUDED ON FED-EX ORDERS  
RECEIVED BY: MICROPROCESSORS UNLIMITED, INC.  
24,000 S. Peoria Ave., BEGGS, OK 74421  
Tel: 52 \$6.25 4 B (918) 267-4961  
Pr: A1 \$14.25 1 B  
No minimum order. Please note: prices subject to change!  
Shipping, insurance extra, up to \$1 for packing materials.

CIRCLE 61 ON FREE INFORMATION CARD

the software will load for you when you choose item 4 from the menu. The built-in editor is rather weak, but by using DEBUG you can search the memory buffer, fill it with a constant, assemble code into it, etc. You can also save all of the contents of the memory buffer to disk if you like.

Other functions allow you to set up the programming parameters, including (E)EPROM manufacturer, type, and programming algorithm. Not all manufacturers are represented, however, so you may have to do some research (or experimentation) to determine the proper programming voltage and algorithm for some types of EPROM's. I had no trouble burning Intel EPROM's, but I burned up several junk-box varieties of EPROM'S that the programmer didn't support. Also, the software doesn't allow you to set the programming voltage independently of the programming algorithm.

Other functions allow you to verify that an (E)EPROM is erased, to read the contents of an (E)EPROM into the memory buffer, to program an (E)EPROM, and to verify programming by comparing buffer contents to (E)EPROM contents. You can

specify starting and stopping addresses for all activities. A separate utility is provided with the package that converts hex format files output by some assemblers and compilers to binary image format.

A short user's guide explains how to use the programmer, and outlines several programming algorithms, but it sorely lacks technical information on (E)EPROM pinouts, programming algorithms, and programming voltages.

My only other complaint is that it is possible to crash out of the program by pressing Ctrl-C at the wrong time. If you did so while the programming pulse was being applied, you could fry a chip. So the software should take control of the DOS interrupt 1Bh handler.


Otherwise, the product performed flawlessly. At \$150, it's an excellent buy for anyone who needs that kind of equipment.

CD
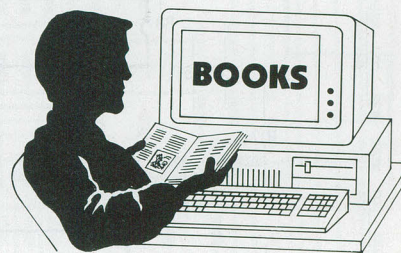
### TI's new RS-232 interfaces

**T**exas Instruments recently introduced an RS-232 line driv-

er and a line receiver, both of which are pin-compatible with the 1488 and 1489 standards. Overall power consumption of the new devices is reduced by a factor of about 2000, compared with standard IC's. In addition, the new drivers contain on-chip slew-rate limiters that eliminate the need for external capacitors. The 75C188N and the 75C189N are priced at \$0.75 in quantities of 1000. CD



### The XT-AT Handbook

**T**his 70-page booklet fits in your shirt pocket and modestly proclaims that it consists of "a collection of hardware and software facts and data on continued on page 82

FEBRUARY 1990



## PORT-A-MATIC

*continued from page 75*

there are lots of holes on the board and mounting the IC sockets first gives you reference points for locating the other components. Also, several components are mounted on pads by feedthroughs, so be sure not to install a component in the wrong pad!

Speaking of feedthroughs, both Port-A-Matic boards are double-sided, and several connections "jump" from one side of the board to the other by means of feedthroughs. The pattern was designed to make most of those jumps at component mounting holes, but there were several places where that wasn't possible. In each of those places you'll have to solder a piece of hookup wire to both the foil and the com-

ponent sides of the board. (Of course, that applies only if you make your own boards. If you use plated-through boards, the connections will be made automatically by soldering one side.)

Several of the jumps are done on the legs of the IC's, and that can be a problem if you use standard low-profile IC sockets. You can get around the problem by using machined-pin sockets with long legs. Mount the socket slightly above the board so that you can solder the legs to both sides of it. A better solution is to use socket strips, which are single strips of machined socket pins. They're similar to Molex pins, but they have the advantage of being mounted in pieces of plastic. Wirewrap sockets are not recommended because their legs are too fat.


The three FND-500 digits on the display board have rows of pins that are spaced 0.6-inches

apart. You can make a socket for them by doing a bit of surgery on a 40-pin socket. There's a space of 0.2 inches between each digit, so you really need a 38-pin socket. Make one by removing the unwanted pins from a 40-pin socket; you'll find that there's more than enough room at the sides of the digits to fit a 40-pin socket on the board.

### Lookup tables

The Port-A-Matic needs two programmed EPROM's to work. Listing 1 shows the binary file for the character generator; Fig. 3 shows how the characters look. You can change them any way you want; just beware that it's difficult to distinguish between 6 and b. In our design, the 6 has a "tail" on the top segment, but it's still easy to mistake one for the other.

The Port-A-Matic won't work without a port-select EPROM in-

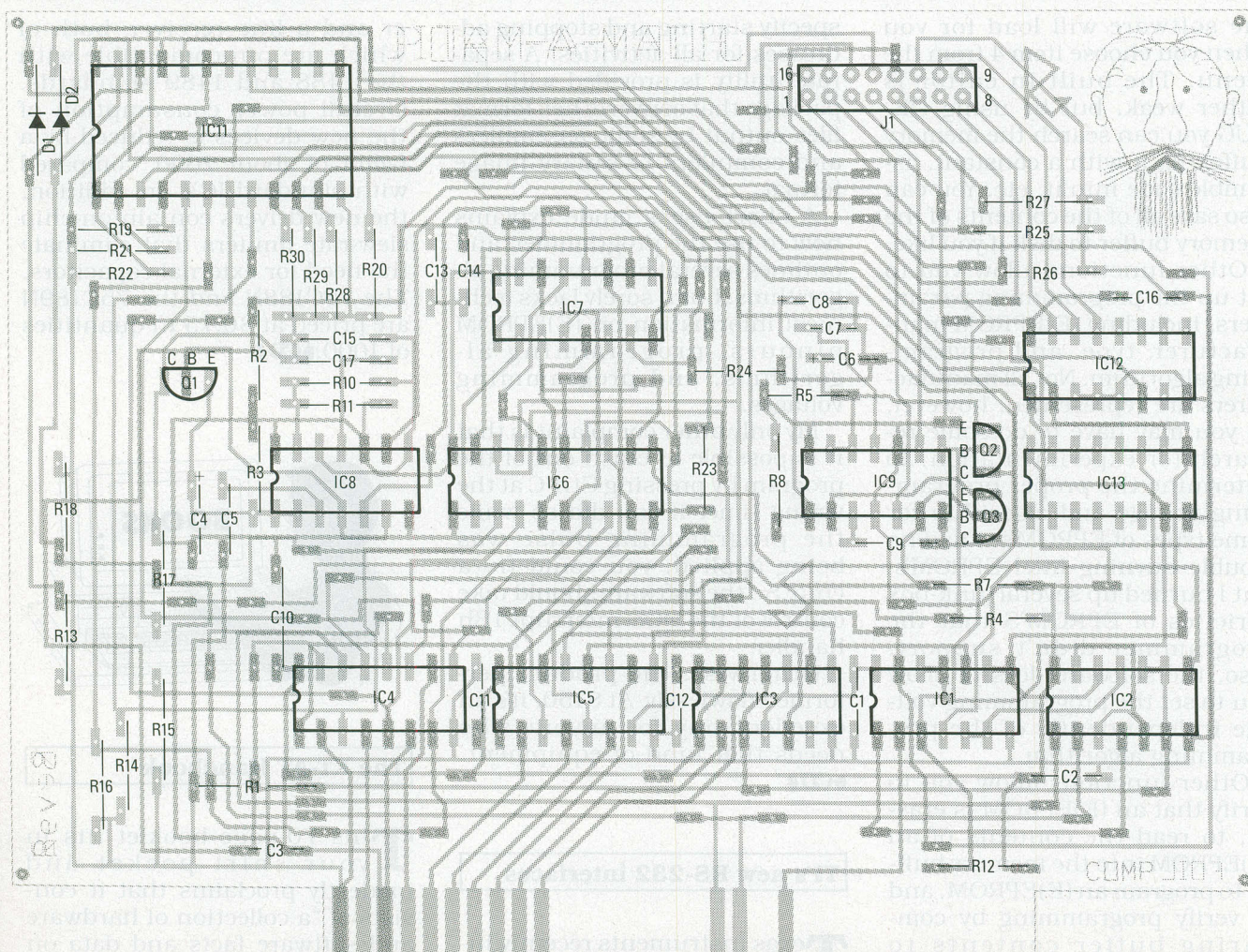

**Fig. 1** BUS INTERFACE BOARD PARTS PLACEMENT DIAGRAM.



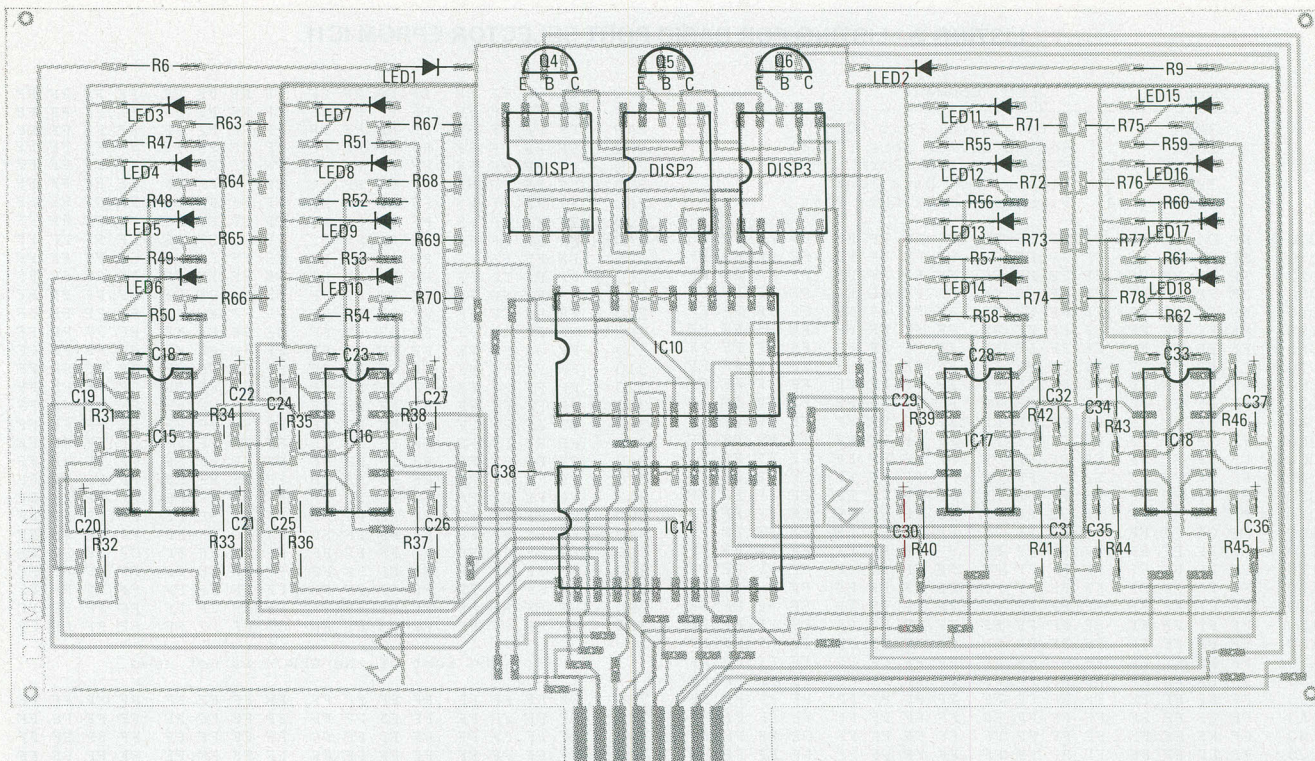


Fig. 2 DISPLAY BOARD PARTS PLACEMENT DIAGRAM.

stalled, and a blank EPROM produces the same effect as no EPROM. Listing 2 shows one possible port-decoding table. When your Port-A-Matic is up and working, you can alter the table to decode any addresses you want, but for the purposes of testing, go with the default. That table decodes the five most commonly used port addresses: COM1, COM2, LPT1, floppy disk, and joystick 1.

#### Oh no—it doesn't work!

If you build the Port-A-Matic on PC boards, you shouldn't have much trouble getting it to work. If you do have trouble, most likely you've made some sort of assembly error. Before you start any heavy-duty troubleshooting, check for solder bridges and cold solder joints.

Before we discuss troubleshooting, remember that the Port-A-Matic is sitting in an ex-

pansion slot, and even the best designed motherboards are noisy places, electronically speaking. Putting a scope probe on an expansion-slot pin is a real eye-opener; you'll find so much ringing, noise, and hash that you'll be amazed the computer can work at all.

Realize that the Port-A-Matic processes high-frequency signals, and there's no way you're going to be able to troubleshoot complex problems without an oscilloscope. Too much is happening too fast to be able to use logic probes and multimeters. However, as we go through the troubleshooting procedure, we'll try to provide alternatives for signal monitoring.

If the computer hangs up with the Port-A-Matic in a slot, but it works fine when the board is removed, you've probably got a short between two of the lines on the board that are connected directly to the bus. The cure for that is a strong light, a magnifier, and careful inspection.

Assuming that your computer works with the Port-A-Matic installed in a slot and that you have installed a suitably programmed port-selector EPROM in the Port-

#### LISTING 1—CONTENTS OF CHARACTER-GENERATOR EPROM IC10

```

000 - 3F 06 5B 4F 66 6D 7D 07 7F 6F 77 7C 39 5E 79 71
010 - FF FF FF FF FF FF FF FF FF FF FF FF FF FF FF
020 - FF FF FF FF FF FF FF FF FF FF FF FF FF FF FF
030 - FF FF FF FF FF FF FF FF FF FF FF FF FF FF FF
040 - FF FF FF FF FF FF FF FF FF FF FF FF FF FF FF
050 - FF FF FF FF FF FF FF FF FF FF FF FF FF FF FF
060 - FF FF FF FF FF FF FF FF FF FF FF FF FF FF FF

```

The rest of the EPROM is not used

```

770 - FF FF FF FF FF FF FF FF FF FF FF FF FF FF FF
780 - FF FF FF FF FF FF FF FF FF FF FF FF FF FF FF
790 - FF FF FF FF FF FF FF FF FF FF FF FF FF FF FF
7A0 - FF FF FF FF FF FF FF FF FF FF FF FF FF FF FF
7B0 - FF FF FF FF FF FF FF FF FF FF FF FF FF FF FF
7C0 - FF FF FF FF FF FF FF FF FF FF FF FF FF FF FF
7D0 - FF FF FF FF FF FF FF FF FF FF FF FF FF FF FF
7E0 - FF FF FF FF FF FF FF FF FF FF FF FF FF FF FF
7F0 - FF FF FF FF FF FF FF FF FF FF FF FF FF FF FF

```



### LISTING 2—LISTING FOR BASIC PORT SELECTOR EPROM IC11

[illegible]

**Fig. 3** THE PORTAMATIC'S CHARACTER SET. You can modify any or all by programming the character-generator EPROM (IC10).

A-Matic, here's a step-by-step procedure you can follow to troubleshoot the circuit.

Load BASIC and type in the simple program shown in Listing 3. That may not be the world's most elegant program, but it will repeatedly access a port that the Port-A-Matic is set to decode. The alternating reads and writes to the port will test both halves of IC9 (shown in Fig. 3 of the January 1990 installment) and the delay loop will cause a visible

change on the activity LED's on the display board. You'll have to adjust the length of the delay loop to match the speed of your computer, but the number in the listing is a good starting point

The key to the operation of the circuit is pin 6 of IC2-b, which is where the master-enable signal is generated. If you have a scope you should see a series of negative-going pulses there. The frequency of the pulses will depend on the speed of your computer, but a

12-MHz AT will access the port at a rate of about 1 kHz, so set the scope's sweep speed accordingly. If the signal is there, you'll see a trace similar to the one in Fig. 4-*a*. You may have a hard time locking the scope to that signal because the time between pulses isn't constant. However, regularity isn't important, since all you want to do is make sure it's there. If you don't have a scope, you can use a logic probe, but it will be hard to tell whether the signal is actually present or you're just detecting noise. The presence or absence of the MASTER ENABLE signal determines what troubleshooting route to follow next.

## With the master enable

If the signal is present, you've got a problem farther down the line. The most logical places to check are the outputs of the timers, since those are the signals that enable the displays. You should see something similar to the trace shown in Fig. 4-*b* at the output of IC8-a. The reason that signal doesn't swing closer to the




supply rails is that the timer is retrigged so often that the output is driven high before it has a chance to go low.

The test program causes the outputs of IC9 to swing alternately high and low. The frequency will depend on the number in the delay loop and on the speed of your computer, but you should be able to see that activity with just about any test equipment there is; a scope, logic probe, even a multimeter.

If you're getting activity at the timer outputs, your problem is probably on the display board. Check the cable and make sure that you have the correct orientation on the connectors. If that's correct and the board is generating the MASTER ENABLE signal, you've narrowed the problem to the timer circuits, which are so simple that the problem should now be easy to find. Chances are you've got one of the assembly errors discussed earlier, such as poor soldering.

The presence of the MASTER ENABLE signal means that the majority of the Port-A-Matic is happy. Aside from the timers, there are several other places on the board that can help you locate the problem. Some of these points can be tested with logic probes and multimeters, but once again you should look at them with a scope. As with the other test points, the frequency will depend on your computer, but the exact number isn't important.

1. The Q2 output of IC7, the data multiplexer, should look like the trace in Fig. 4-c. If there's nothing there, check IC8-b, IC13, and the reset logic made up of

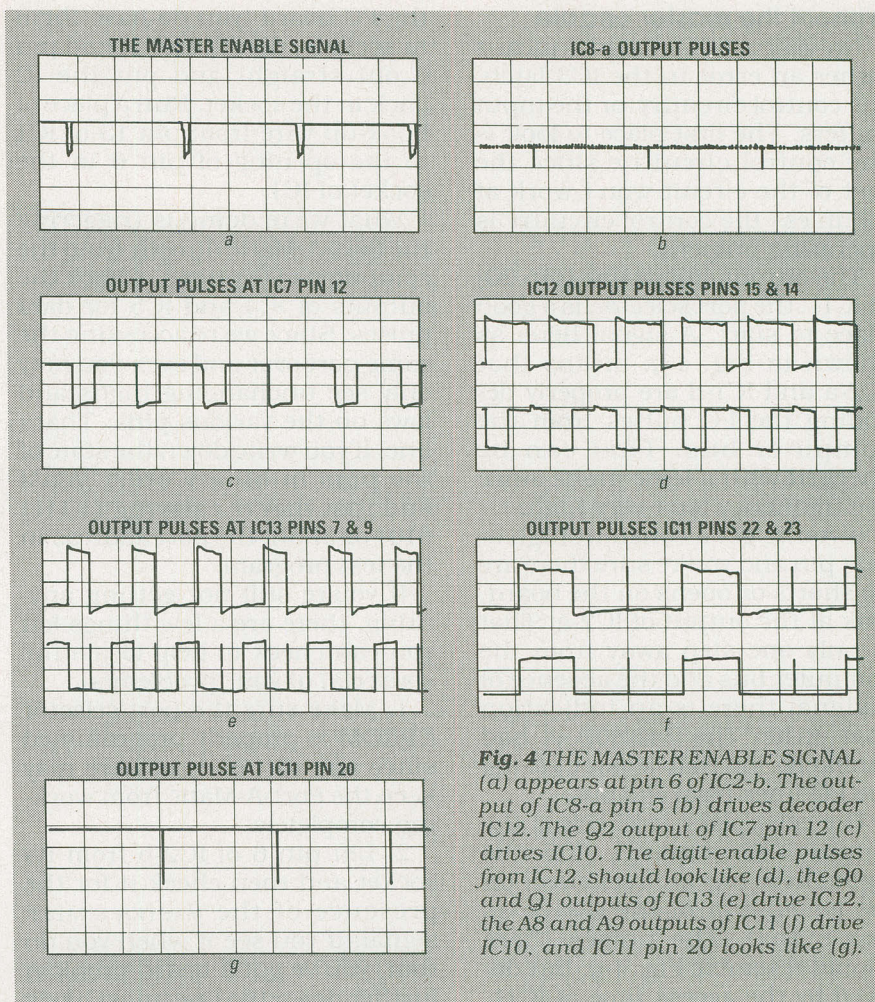

**Fig. 4** THE MASTER ENABLE SIGNAL (a) appears at pin 6 of IC2-b. The output of IC8-a pin 5 (b) drives decoder IC12. The Q2 output of IC7 pin 12 (c) drives IC10. The digit-enable pulses from IC12, should look like (d), the Q0 and Q1 outputs of IC13 (e) drive IC12, the A8 and A9 outputs of IC11 (f) drive IC10, and IC11 pin 20 looks like (g).

IC2-d and IC1-b.

2. You should see square waves similar to Fig. 4-d at the outputs of IC12, the digit multiplexer. Look at IC8-a and IC13, as well as Q4-Q6 on the display board. If the waveform appears when you disconnect the ribbon cable, you've got a short somewhere on the display board.

3. The two least-significant outputs of IC13, Q0 and Q1 (pins 7 and 9), should have square

waves like the ones in Fig. 4-e. A problem here can be caused by a constant high on the reset line (pin 11), or by the absence of input clock pulses on pin 10. Check IC2-b, IC1-b, and IC8-b.

4. The waveform in Fig. 4-f should be present on IC11, which is the port-select EPROM, at pins 22 and 23. Also make sure that you check IC1-c, diodes D1 and D2, IC5 pins 11 and 13, and the outputs of IC3.

#### LISTING 3—TEST PROGRAM

```
=====
4 REM *****
5 REM *   Exercise the Port-A-Matic *
6 REM *   by reading and writing    *
7 REM *   to Port 3F5h              *
8 REM *                               *
9 REM *****
10 REM
10 X=INP(1013):FOR N = 1 TO 500:NEXT
20 OUT 1013,X:FOR N = 1 TO 500:NEXT
30 GOTO 10
40 END
```

#### ORDERING INFORMATION

A set of two double-sided printed circuit boards is available for \$38.95 from Systems 80 Instruments Ltd., c/o CF Liebert, Inc., P.O. Box L, Blaine, WA 98230. The two programmed EPROMs (2716-1, 350 ns) as described in the article are also available from Systems 80 for \$19.95. All prices include shipping and handling.



### Without the master enable

NO MASTER ENABLE signal means either an error in the IC3 latch, the control circuitry, or the input buffers. The first place to look is the control circuitry, since the rest of the circuit won't work at all unless the control circuitry is operating properly.

The output enable line (pin 20) of IC11, the port selector, is a good place to start. A signal here, as shown in Fig. 4-g, means that IC2-a and IC1-d are properly decoding the I/O pulses from the computer bus. That can be checked with a logic probe since the frequency isn't very high.

If you've got a constant high at that pin and you're sure there are no shorts or opens on the board, look at the output of IC2-a. That is only one step away from the computer bus and the absence of a signal there is an indication that either the 74LS00 is bad (unlikely), or that it isn't seeing the I/O lines from the bus.

The next place to check is the output of IC1-a (pin 1), since the signal here has a direct effect on the generation of the MASTER ENABLE signal. The pulses there should resemble Fig. 4-g, but delayed by the access time of IC11. You can catch them with any good logic probe but a scope is better. The general appearance of all the control-circuit signals will be the same; very narrow, irregularly spaced, positive- or negative-going spikes.

The input buffers (IC4 and IC5), are more difficult to check since nothing will happen there unless the MASTER ENABLE signal is being produced by the control circuitry. There is one trick you can use, but it's probably going to cost you an IC. Remove IC2 from

the PC board (you do have them in sockets, don't you?), bend pin 6 out straight and put the IC back in the socket. Run a piece of hook-up wire from pin 13 of IC1 to the opening of pin 6 in the socket of IC1.

What we're doing is triggering the Port-A-Matic directly from the computer's I/O pulses. Check the outputs of IC4 and IC5 for data pulses. Since we're accessing the same port over and over, you may only see unchanging highs and lows on the various pins. That's fine. If you write down the state of the pins in binary order you'll find that they're carrying 11 1111 0101 or 3F5h, the port address in the test program.

If you're still not getting anything, there are a few things left you can check to help locate the source(s) of your problem(s).

1. Make sure the port-selector EPROM is properly programmed since any sort of error here may keep the Port-A-Matic from working completely.

2. Lift pin 6 of IC2-b from its socket and then check it for the presence of the MASTER ENABLE signal. If you see it when you do that, you've got a board problem further down the line (most likely a solder short).

3. Check the values of R1 and R12.

4. Check the value of C3. The Port-A-Matic will work with a value less than 0.001  $\mu$ F (although operation may be flaky), but a larger value will stop the Port-A-Matic completely. If you substitute a 0.01  $\mu$ F capacitor for C3, it will completely swallow the narrow MASTER ENABLE pulses, so the circuit won't work. There are several systems used to mark capacitor values, so let's just state for

the record that a marking of 104 is 0.1  $\mu$ F, 103 is 0.01  $\mu$ F, and 102 is 0.001  $\mu$ F.

### Putting the Port-A-Matic to work

Although the Port-A-Matic was originally intended to be a diagnostic tool for hardware, it's also a terrific aid in debugging software. A standard troubleshooting technique in program development is to use a PRINT statement in BASIC (or the equivalent in whatever language you use) to track program flow.

The Port-A-Matic can decode sixteen different port addresses (or thirty two if you distinguish I/O reads and writes), so you could program some unused port addresses into IC11 and replace PRINT statements with INP and OUT arguments.

The operation of the Port-A-Matic is totally transparent to the computer and that makes it especially valuable for those times when you're doing graphics programming and PRINT statements can't easily be seen on the screen.

There's no reason why you can't use the Port-A-Matic to control a variety of external devices. Remember that accessing a valid port will result in a unique half-second pulse. Although they're being used to light LED's, there's no reason why they can't turn external hardware on or off, as well.

The Port-A-Matic is a valuable addition to any PC and the number of uses it has is limited only by your imagination. Even if all you need is something that tells you if that new I/O card is properly set up or not, the amount of time it will save you may very well be worth having one in your computer. ♦CD♦

### WORKBENCH

*continued from page 77*

the PC-compatible family and its operating system." That's the truth, but it's not the whole truth.

*The XT/AT Handbook* contains in summary form darned near everything a systems integrator,

technician, or designer needs to know about the PC family, including bus pin-outs, memory maps, cable connections, card dimensions, programmable registers in the DMA20 and other system controllers, interrupts, BIOS entry points, switch settings, keyboard scan codes, the hard-to-locate diagnostic error codes, DOS commands, and

more. I'd like to see a complete listing of the DOS interrupt (21h) services, and printer codes for the IBM/Epson and HAP LaserJet families. But, as it is, the book can replace a foot of fancy (and expensive) documentation. At less than ten dollars, the price is criminally low. The company also sells some really neat software—stay tuned for details. ♦CD♦



# MARKET CENTER

## FOR SALE

**PHOTOFACT** folders, under #1400 \$4.00. Others \$6.00. Postpaid. **LOEB**, 414 Chestnut Lane, East Meadow, NY 11554.

**GREAT buys!** Surplus prices, ICs, linears, transformers, PS, stepping motors, vacuum pump, phototransistor, meters, LSASE, **FERTIK'S**, 5400 Ella, Phila., PA 19120.

**DESCRAMBLERS.** All brands. Special: Combo Jerrold 400 and SB3 \$165. Complete cable descrambler kit \$39. Complete satellite descrambler kit \$45. Free catalog. **MJM INDUSTRY**, Box 531, Bronx, NY 10461-0531.

**T.V. notch filters**, surveillance equipment, brochure \$1.00. **D.K. VIDEO**, Box 63/6025, Margate, FL 33063. (305) 752-9202.

**SURPLUS ELECTRONICS.** New giant wholesale catalog. Hundreds of amazing bargains. \$2. Box 840, Champlain, NY 12919.

**TUBES:** "oldest," "latest." Parts and schematics. **SASE** for lists. **STEINMETZ**, 7519 Maplewood, RE, Hammond, IN 46324.

## FREE CATALOG

**FAMOUS "FIRESTIK" BRAND CB ANTENNAS AND ACCESSORIES. QUALITY PRODUCTS FOR THE SERIOUS CB'er. SINCE 1962**  
**FIRESTIK ANTENNA COMPANY**  
2614 EAST ADAMS  
PHOENIX, ARIZONA 85034

**LASER Listener II**, other projects. Surveillance, descrambling, false identification, information. Plans, kits, other strange stuff. Informational package \$3.00 refundable. **DIRIJO/BOND ELECTRONICS**, Box 212, Lowell, NC 28098.

**ENGINEERING** software, PC/MSDOS. Hobbyists — students — engineers. Circuit design \$59.00, FFT analysis \$69.00, Mathematics \$49.00, Logic Simulation \$49.00, Circuit Analysis \$29.00. Free catalog, (614) 491-0832, **BSOFT SOFTWARE**, 444 Colton Rd., Columbus, OH 43207.

**RESTRICTED technical information:** Electronic surveillance, schematics, locksmithing, covert sciences, hacking, etc. **Huge selection. Free brochures.** **MENTOR-Z**, Drawer 1549, Asbury Park, NJ 07712.

## CB RADIO OWNERS!

We specialize in a wide variety of technical information, parts and services for CB radios. 10-Meter and FM conversion kits, repair books, plans, high-performance accessories. Thousands of satisfied customer since 1976! Catalog \$2.

### CBC INTERNATIONAL

P.O. BOX 31500RE, PHOENIX, AZ 85046

**TEST** equipment pre-owned now at affordable prices. Signal generators from \$50.00. Oscilloscopes from \$50.00. Other equipment, including manuals available. Send for Catalog. **J.B. ELECTRONICS**, 3446 Dempster, Skokie, IL 60076. (312) 982-1973.

**COMMUNICATIONS.** Electronic equipment, sales, service, FCC licensed, free catalog. **RAYS**, PO Box 14862, Fort Worth, TX 76117-0862.

**CABLE TV converters:** Jerrold, Oak, Scientific Atlantic, Zenith and many others. "New MTS" stereo add-on: mute & volume. Ideal for 400 and 450 owners! 1 (800) 826-7623, Amex, Visa, M/C accepted. **B & B INC.**, 4030 Beau-D-Rue Drive, Eagan, MN 55122.

**DESCRAMBLERS.** Lowest prices on top name brands. Tocom, Zenith, Oak, Jerrold, SA, Pioneer, Hamlin. Examples: RTC 56 \$150.00 — 10 @ 130 each. Tri-Bi @ \$79.00 in lots of 10. COD ok same day shipping. **MOUNT HOOD ELECTRONICS**, (206) 896-6837.

**ELECTRONIC** test equipment, laboratory equipment, — surplus and priced to go! Catalog \$1.00. **LEHMAN**, R.D. 1 Box 580, Wrightsville, PA 17368.

## MICROWAVE TV RECEIVERS 1.9 to 2.7 GHz



2 CH Compact Dish System - \$77.95  
5 CH Dish System - \$93.95  
12 CH Yagi (Rod) System - \$123.95  
30 CH Dish System - \$163.90 Yagi - \$183.90  
**SUN MICROWAVE INT'L. INC.** Send \$1.00 for  
P.O. BOX 34522 catalog on these  
PHOENIX, AZ 85067 and other fine  
(602) 230-0640 video products.  
**QUANTITY DISCOUNTS LIFETIME WARRANTY**

**SURPLUS CATV** converters and descramblers at wholesale prices. Unmodified units only. Oak M35B \$30. Jerrold 400 DIC w/remote \$80. (415) 566-9815.

**STEPPER** motor drive & control with **Commodore 64**. Affordable hardware, interface, & software. Send for detailed literature & prices to: **MASE**, R.D. #2 Box 166, Mohrsville, PA 19541.

**FEB 87** Triparts \$59.00. Feb 84 SB parts \$49.00. \$3.50 shipping. **OCTE**, Box 276, Alburg, VT 05440. (514) 739-9328.

**RENTAL movie stabilizer.** Connect between VCRs or to monitor. Satisfaction guaranteed. \$69.95, \$4.00 handling. 1 (800) 367-7909.

**PARABOLIC** reflectors. 18" spun metal dish focuses RF, light, sound. \$25.00; **PJC**, 2981 Tess Ave., Granger, Utah 84119.

**MINIATURE** electronics like James Bond. Catalog \$3.00, refundable. **F & P ENTERPRISES**, Box 51272, Palo Alto, CA 94303-L.

**CABLE** boxes, all types in stock, lowest prices, guaranteed, COD ok, same day shipment, Tocom, Tocom, Tocom. **G.D. ELECTRONICS**, (602) 829-9441.

**TUBES**, new, up to 90% off, **SASE**, **KIRBY**, 298 West Carmel Drive, Carmel, IN 46032.

**BOARDS** for Radio-Electronics and Popular Electronics projects. Inexpensive! **Free sample!** **INDUSTRIAL MICRO** Box 596, Logan, Utah 84321. 1 (800) 359-0466.

**TOCOM** 5503 V.I.P. descrambler "Turnon." All channels; formats. New easy hookup; parts included! Manual and remote tuning. Free "detailed" schematic. \$39.00. **MIKE**, Box 743, Oldsmar, FL 34677.

## ANTIQUE RADIO CLASSIFIED

Free Sample!

Antique Radio's  
Largest Circulation Monthly.  
Articles, Ads & Classifieds.

6-Month Trial: \$11. 1-Yr: \$20 (\$30-1st Class).  
A.R.C., P.O. Box 802-L4, Carlisle, MA 01741

**LASERS** from \$35, for free catalog write **MWK INDUSTRIES**, 1440 South State College Building 3B-R, Anaheim, CA 92806 or call (714) 956-8497.

**ENGINEERING** development tools, IBM PC extender boards, timing software. **DETROIT DATACOMM**, 1409 W. 14 Mile, Mid Hgts, MI 48071.

**CABLE** converters and descramblers, wholesale prices, full warranties, RTC-56 w/r \$150.00, MLD-1200 \$45.00, Pioneer 125, Jerrold-400 w/r \$125.00. These are just examples, all makes in stock, new this month only, Tocom w/r \$199.00. **S.A.C.**, Orders 1 (800) 622-3799. Information (702) 647-3799.

**CABLE TV converters and descramblers.** We sell only the best. Low prices. **SB-3 \$79.00.** We ship **C.O.D.** Free catalog. **ACE PRODUCTS**, PO Box 582, Dept. E, Saco, ME 04072. (207) 967-0726.

**TEST** equipment reconditioned (guaranteed). Terrific prices, NBS calibration available. Visa, M/C, Amex, COD. **ELECTRONIC SURPLUS, INC.**, 4350 Town Plaza, Suite 203, Houston, TX 77045. (713) 728-9718.

**SAMS** closeout sale. #2 to #2600 \$6.00 each postpaid. MC/Visa. Call 1 (800) 888-1328. 9-5 CST.

**MEMORY** chips, Simms and Sippis: 4164-100 \$2.50, 41256-100 \$3.50, 41464-100 \$4.60. Call **ED/DATAFIX**, (201) 322-7666.

**COMPUTERIZED** linecard system for IBM compatibles. Fast. Easy. Just \$24.95. **NORTHSTAR**, 2924 Stark, Eugene, OR 97404.

**CABLE TV** converters/descramblers. All major brands. Are you tired of ordering cable TV equipment and receiving inferior merchandise, **not at K.D. Video.** We are a well established company that will offer you the best quality, service and prices. **Our units have worked where others have failed.** Call Toll free 1 (800) 327-3407. **K.D. VIDEO INC.**, PO Box 29538, MLPS., MN 55429.

**JOB?** Top electronic firms addresses and PH's. \$2.00. **ENGINEERING**, 6611 Edgemont, Huntington Beach, CA 92647.

**TUBES** Sylvania 6LQ6 6L6GC 20LF6 etc. Huge discounts. **ARLEN SUPPLY**, 7409 West Chester Pike, Upper Darby, PA 19082. 1 (800) 458-1301.

## AMAZING SCIENTIFIC & ELECTRONIC PRODUCTS

PARTS ARE IN STOCK	GRA1 — ANTI GRAVITY GENERATOR	\$10.00
	LC7 — 40 WATT BURNING CUTTING LASER	\$20.00
	RUB4 — HI POWER PULSED DRILLING LASER	\$20.00
	BTCS — 1 MILLION VOLT TESLA COIL	\$20.00
	MCP1 — HI VELOCITY COIL GUN	\$15.00
	LLS1 — LASER LIGHT SHOW 3 METHODS	\$20.00
	EH1 — ELECTRONIC HYPNOTISM TECHNIQUES	\$8.00
	EML1 — LOWER POWERED COIL GUN LAUNCHER	\$8.00
	JL3 — JACOB LADDER 3 MODELS	\$10.00
	SD5 — SEE IN THE DARK	\$10.00
PLANS IN STOCK	LEV1 — LEVITATION DEVICE	\$10.00
	FMV1K — 3 MILE FM VOICE TRANSMITTER	\$34.50
	PFS1K — HAND CONTROLLED PLASMA FIRE SABER	\$49.50
	NIG7K — HI FLUX NEGATIVE ION GENERATOR	\$34.50
	PG5K — PLASMA LIGHTNING GLOBE	\$49.50
	LHC2K — VISIBLE SIMULATED 3 COLOR LASER	\$44.50
	HOD1K — HOMING/TRACKING BEEPER TRANSMITTER	\$44.50
	LGU6K — 2.5 MW HAND-HELD VISIBLE LASER GUN	\$249.50
	BTC3K — 250,000 VOLT TABLE TOP TESLA COIL	\$249.50
	IOG2K — ION RAY GUN, project energy without wires	\$129.95
ASSISTANCE KITS PROGRAM AVAILABLE	TKE1K — TELEKINETIC ENHANCER/ELECTRIC MAN	\$79.50
	VWPM7K — 3 MILE AUTO TELEPHONE TRANSMITTER	\$49.50
	ASSEMBLED IN OUR LABS	
	LIST10 — INFINITY XMTR Listen in via phone lines	\$199.50
	IPG70 — INVISIBLE PAIN FIELD BLAST WAVE GENERATOR	\$74.50
	ITM10 — 100,000 VOLT INTIMIDATOR UP TO 20'	\$99.50
	TAT30 — AUTOMATIC TELEPHONE RECORDING DEVICE	\$24.50
	PSP40 — PHASOR SONIC BLAST WAVE PISTOL	\$89.50
	DNE10 — ALL NEW 26" VIVID COLORED NEON STICK	\$74.50
	LGU20 — 5 TO 1MW VISIBLE RED HEAT LASER GUN	\$199.50
ASSEMBLED	BLS10 — 100,000 WATT BLASTER DEFENSE WAND	\$89.50

**EASY ORDERING PROCEDURE:** TOLL FREE 1-800-221-1705 or 24 HRS ON 1-603-673-4730 or FAX IT TO 1-603-672-5406  
VISA, MC, CHECK, MO IN US FUNDS. INCLUDE 10% SHIPPING. ORDERS \$100.00 & UP ONLY ADD \$10.00. CATALOG \$1.00 OR FREE WITH ORDER.

**INFORMATION UNLIMITED**  
P.O. BOX 716, DEPT. R2, AMHERST, NH 03031



## A collage of various cable TV converters and equipment. At the top left is a small, dark, rectangular remote control with many buttons. To its right is the text "CABLE TV CONVERTERS &amp; EQUIPMENT" in a bold, sans-serif font. Further right is a long, thin, black rectangular device, possibly a converter or a component of a system. Below these are several larger pieces of equipment. On the left is a large, dark, rectangular set-top box with a control panel featuring many buttons and a small display. To its right is another large, dark, rectangular set-top box, also with a control panel. Below the large set-top box on the left is a smaller, dark, rectangular device with a circular logo on the front. To its right is a dark, rectangular set-top box with a control panel. At the bottom left is a small, dark, rectangular power supply unit with a coiled cable. To its right is a dark, rectangular set-top box with a control panel.

# VIDEO-LINK

## Enterprises, Inc.

**IMPORTANT:** Have make and model # of the equipment used in your area.

CIRCLE 64 ON FREE INFORMATION CARD

## Be a TV/VCR Repair Specialist

**MAIL COUPON TODAY**

## PLANS AND KITS

**INVESTIGATORS**, experimenters — Quality new plans. Hard to find micro and restricted devices. Free catalog. Self addressed stamped envelope to **KELLEY SECURITY INC.**, Suite 90, 2531 Sawtelle Blvd., Los Angeles, CA 90064.

84



85



## ASSEMBLE YOUR OWN COMPUTER FOR LESS

### 10 MHz 8088 Compatible Kit .....\$379

- 4.77/10 MHz 8088 Motherboard
- 256KB RAM (640KB max)
- 150W Power Supply
- Floppy Disk Controller
- One 5 1/4" 360KB Drive
- MonoGraphics Card w/ P
- 101 Key Keyboard
- Case (3LED, 2Button, Key)
- 12" Amber Mono Monitor
- Installation Guide & Manual



### 12 MHz 80286 Compatible Kit .....\$669

- 12 MHz 80286 Motherboard
- 512 KB RAM (4 MB max)
- 200W Power Supply
- Floppy Disk Controller
- One 5 1/4" 1.2 MB Drive
- MonoGraphics Card w/ P
- 101 Key Keyboard
- Case (3LED, 2Button, Key)
- 12" Amber Mono Monitor
- Installation Guide & Manual



### 20 MHz 80386 Compatible Kit .....\$1399

All Components Fully Tested Before Ship  
One Year Warranty on All Parts  
Installation Available at No Extra Charge !!!  
VISA & M/C add 3% Amex add 4%  
Price & Quantity subject to change without prior notice  
15% Restocking Fee on All Non-Defective Items

## JINCO COMPUTERS INC.

5122 WALNUT GROVE AVE.  
SAN GABRIEL, CA 91776

Tel: (818) 309-1108  
Fax: (818) 309-1107

CIRCLE 178 ON FREE INFORMATION CARD

## NUTS & VOLTS

P.O. Box 1111-E  
Placentia, CA 92670  
714-632-7721

GIVE YOURSELF A BREAK—A PRICE BREAK!  
NUTS & VOLTS WILL **Save** YOU MONEY  
ON ELECTRONIC PARTS & EQUIPMENT  
Plus SHOW YOU WHERE TO FIND UNIQUE,  
UNUSUAL AND HARD-TO-FIND ITEMS.  
SUBSCRIBE TODAY!

A National Publication For The Buying And Selling Of Electronic Equipment

Subscription Rates  
U.S. FUNDS REQUIRED  
3rd Class Mail-USA  
ONE YEAR \$12.00  
TWO YEARS \$21.00  
LIFETIME \$60.00  
1st Class Mail  
ONE YEAR USA \$20.00  
CANADA/MEXICO \$22.00  
AIR MAIL  
FOREIGN 1 Yr. \$55.00

## EDUCATION & INSTRUCTION

**MAGIC!** Four illustrated lessons plus inside information shows you how. We provide almost 50 tricks including equipment for four professional effects. You get a binder to keep the materials in, and a one-year membership in the International Performing Magicians with a plastic membership card that has your name gold-embossed. You get a one-year subscription to our quarterly newsletter "IT'S MAGIC!" Order now! \$29.95 for each course + \$3.50 postage and handling. (New York residents add applicable state and local sales tax). **THE MAGIC COURSE**, 500-B BiCounty Boulevard, Farmingdale, NY 11735.

**LEARN IBM PC assembly language.** 80 sample programs. Disk \$5. Book \$18. **ZIPFAST**, Box 12238, Lexington, KY 40581-2238.

**COLOR TV repairs made easy! Fastest color TV repairs anyone can do.** \$2 brings sample. **CHECKMATE COMMUNICATIONS**, PO Box 11-0808, Brooklyn, NY 11211.

## MULTI CHANNEL MICROWAVE ANTENNAS

- CRYSTAL CONTROLLED MICROWAVE ANTENNAS FOR OVER THE AIR CABLE SYSTEMS (WIRELESS CABLE)
  - CAPABLE OF RECEIVING 30 CHANNELS
  - CONVERTERS AVAILABLE FOR ZENITH SYSTEMS
- CATALOG & INFO: (203) 975-7543

## VIDEO-LINK ENTERPRISES

520 GLENBROOK RD., SUITE 202, STAMFORD CT 06906

## WANTED

**INVENTIONS/new products/ideas wanted:** Call TLCI for free information 1 (800) 468-7200 24 hours/day - USA/Canada.

**INVENTORS! Confused? Need help?** Call IMPAC for Free information package. In US and Canada: 1 (800) 225-5800.

**SEISMOMETER** wanted to measure earthquakes. Pay cash. **D. HUTCHINSON**, 4000 Little Timber, Edmond, OK 73034. (405) 341-9615.

## DESCRAMBLER MODULE

**LATEST** technology alternative to Jerrold SB-3 or Radio-Electronics Feb. 1984 project. Featuring electronic tuning, AGC, auto-on/off, AC/DC power, mini-size, A&T, and more. For literature — **SOUTH-TECH DISTRIBUTING**, (813) 527-2190.

## BUSINESS OPPORTUNITIES

**EASY** work! Excellent pay! Assemble products at home. Call for information. (504) 641-8003 Ext. 5192.

**MAKE** \$50/hr working evenings or weekends in your own electronics business. Send for free facts. **INDUSTRY**, Box 531, Bronx, NY 10461.

**YOUR own radio station!** AM, FM, TV, cable. Licensed/unlicensed. **BROADCASTING**, Box 130-F2, Paradise, CA 95967.

**INVENTIONS**, ideas, technology wanted for presentation to industry/exhibition at national innovation exposition. Call 1 (800) 288-IDEA.

**LET** the government finance your small business. Grants/loans to \$500,000. Free recorded message: (707) 449-8600. (KS1).

**LEARN** gold, silver, platinum scrap recycling business. Free information. Write: **RECYCLING**, Box 11216RT, Reno, NV 89510-1216.

**BURGLAR** alarms-booming business. Get started now. Information \$2.00. **DYNAMIC SECURITY**, PO Box 1456, Grand Rapids, MI 49501.



EMINENCE



1-800-338-0531

### 3-WAY 100W CROSSOVER

12 dB/octave rolloff.  
800Hz, 8000Hz  
crossover points. 8  
ohm. 100 watts RMS.



#260-210 \$12.50 \$9.95  
(1-9) (10-up)

### SPEAKER CONTROL PANEL

Panel with 50 watt L-pads  
for tweeter and midrange  
and built-in LED power  
meter. 5" x 2 1/2" 100  
watt version available



#260-235 \$14.50 \$12.90  
(1-5) (6-up)

### 12" POLY WOOFER


Super duty, 40 oz. magnet.  
100 watts RMS, 145 watts  
max. 4 and 8 ohm compat-  
ible (6 ohm). 2" voice coil.  
fs = 25 Hz. QTS = .166,  
VAS = 10.8 cu. ft.  
Response: 25-1500 Hz. Net  
weight: 9 lbs. Pioneer  
#A30GU40-51D



#290-125 \$36.80 \$34.50  
(1-3) (4-up)
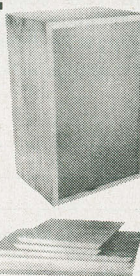
### WALNUT SPEAKER CABINET KIT

Super quality,  
genuine walnut  
veneer cabinet. Kit  
includes: routed and  
mitred top, sides,  
and bottom in  
unfinished 3/4"  
walnut veneer. Cut  
your own custom  
holes in the front  
and rear to match  
your drivers. 15" x  
24" x 11". Volume:  
1.9 cubic feet.



#260-350 \$22.50 \$19.95  
(1-3) (4-up)

### PIONEER HORN TWEETER

Mylar dome. 2.93 oz.  
barium ferrite magnet. 8  
ohm. Response: 1800-  
20000 Hz. 35W RMS,  
50W max. fs = 2000 Hz,  
SPL = 106 dB. Pioneer  
#AHE60-51F



#270-050 \$6.50 \$5.90  
(1-9) (10-up)

### 12" SUB WOOFER

Dual voice coil sub woofer.  
30 oz. magnet, 2" voice  
coils. 100 watts RMS, 145  
watts max. fs = 25 Hz. 6 ohm  
(4 and 8 ohm compatible).  
SPL = 89 dB 1W/1M.  
Response: 25-700 Hz.  
QTS = .31, VAS = 10.3 cu. ft.  
Pioneer #A30GU30-85D.  
Net weight: 6 lbs.



#290-145 \$39.80 \$36.80  
(1-3) (4-up)

### 15" THRUSTER WOOFER

Thruster by Eminence.  
Made in USA. Poly foam  
surround, 56 oz. magnet.  
2-1/2", 2 layer voice coil.  
150 watts RMS, 210 watts  
max. 4 ohm. fs = 23.5  
Hz, QTS = .33, VAS = 17.9  
cu. ft. SPL = 94.8 dB 1W/  
1M. Net weight: 15 lbs.



#290-180 \$43.50 \$39.80  
(1-3) (4-up)

### GRILL FRAME KIT

With this kit you  
can make speaker  
grill frames up to  
30" x 40". Kit  
includes 4 corner  
pieces, 2 "T"  
brackets, and 7  
frame bars. Grill  
mounting kit  
included.



#260-333 \$8.50 \$7.80  
(1-9) (10-up)

### 18" EMINENCE WOOFER

MADE IN USA  
100 oz. magnet, 3" voice  
coil. 250 watts RMS, 350  
watts max. 8 ohm, 30 Hz  
resonant frequency. 22-  
2700 Hz response.  
Efficiency: 95 dB 1W/1M.  
Paper cone, treated  
accordian surround. Net  
weight: 29 lbs.



#290-200 \$98.90 \$89.50  
(1-3) (4-up)

### TITANIUM COMPOSITE TWEETER

Titanium is deposited on a polymer  
dome to combine the advantages of  
both hard and soft dome  
technologies. 8 ohm. Ferro fluid  
cooled voice coil. fs = 1200 Hz,  
SPL = 90 dB 1W/1M. 50 watts RMS,  
70 watts max. 4" round. Polydax  
part #DTW100T12S.



#270-047 \$27.50 \$24.80  
(1-9) (10-up)





**WHOLESALE** adaptors. RF, video, audio. Why pay top dollar? Deal with importer. Connectors too. Free catalog. **C&D INTERNATIONAL**, PO Box 4333A, L.I.C., NY 11104.

## CABLE RENTERS STOP!

If your currently renting your cable equipment it's time to look into owning your own. You can save up to \$100 plus every year. Satisfaction Guaranteed.

We carry all the major brands of Converters, Remote controls and Descramblers. JERROLD, OAK, ZENITH, EAGLE, HAMLIN, SCIENTIFIC ATLANTA, Many more. Fast courteous service.

Call today 512-250-8816 or write for your Free catalog.

VISA M/C Order C.O.D. Toll Free **1-800-228-7404**

Nu-Tek Electronic 5114 Balcones Woods dr. Suite#307 Dept.298R Austin, Tx 78759

## DIGITAL CAR DASHBOARDS

**BUILD** yourself complete electronic dashboards. Information package: \$2.00 (refundable). **MODERN LABS**, 2900-F Ruisseau, Saint-Elizabeth, QC, J0K 2J0, Canada.

## PROJECT CABINETS/ ENCLOSURES

**RIGID** 1/16 aluminum shell, hardwood trim, contemporary styling. Several sizes and styles available. \$10.99 — \$26.99, free brochures. **PYRAMID ELECTRONIC PRODUCTS**, 15020 LaGrange Road, Suite 2100, Orland Park, IL 60462.

## CABLE TV DESCRAMBLER LIQUIDATION!

- Major Makes & Models!
- Will match or beat anyone's prices!
- Dealer discounts at 5 units!
- Examples:  
HAMLIN COMBOS \$44 ea. (Min. 5)  
OAK ADD/ON \$40 ea. (Min. 5)  
OAK M35B \$60 ea. (Min. 5)

**WEST COAST ELECTRONICS**  
For Information: 818-709-1758  
Catalogs & Orders: 800-628-9656

## INVENTORS

**INVENTORS!** Can you patent and profit from your idea? Call **AMERICAN INVENTORS CORPORATION** for free information. Over a decade of service 1 (800) 338-5656. In Massachusetts or Canada call (413) 568-3753.

## COMPUTER BOOKS

**DISCOUNT computer books.** All titles available, including recent releases. Please call or write for our latest catalog. **BOOKWARE**, 147 Campville Road, Northfield, CT 06778. 1 (800) 288-5662.

## SOFTWARE

**FREE software** for IBM and compatible computers! Info \$1.00. **BLUE CHIP ENGINEERING**, Dept. 33, PO Box 1100, Walnut, CA 91789.

## CABLE TV DESCRAMBLERS

JERROLD™ Tri-Bi Mode.....	\$105.00	10 Lot \$85.00
JERROLD™ SB-3 OR 2.....	\$89.00	\$65.00
Hamlin MLD-1200.....	\$99.95	\$62.00
Oak N-12 W/V.S.....	\$99.95	\$62.00
Oak M-35-B W/V.S.....	\$99.00	\$78.00
OAK E-13.....	\$99.95	\$58.00
Zenith SSAVL.....	\$185.00	\$145.00
Eagle PD-3.....	\$120.00	\$85.00
Scientific Atlanta.....	\$129.95	\$105.00
SA-Combo's.....	CALL	\$Call
Tocom.....	\$350.00	\$295.00
Oak N-12 W/ Auto.....	\$140.00	\$105.00
Jerrold Starcom CSV.....	\$139.95	Call

**M.D. ELECTRONICS**  
**WILL MATCH ANY**  
**ADVERTISED PRICE**  
**IN THIS MAGAZINE**

## \*NEW STARGATE 2000 CABLE CONVERTER



1-\$89.00 10-\$69.00 100-Call

Last channel recall-Favorite channel select-75 channel-Channel scan-Manual fine tune-One year warranty-surge protection-HRC & Standard switchable- and much more. Call Today!

**INFORMATION(402)554-0417**

Orders Call Toll Free  
**1-800-624-1150**

**M.D. ELECTRONICS**  
**115 NEW YORK MALL**  
**SUITE 133E**  
**OMAHA, NE. 68114**

**M.C.**  
**VISA**  
**C.O.D.**

**CIRCLE 53 ON FREE INFORMATION CARD**

## MARK V NEW FREE CATALOG IS NOW AVAILABLE!

▲ indicates the level of difficulty in the assembling of our Products. ▲ Beginner ▲▲ Intermediate ▲▲▲ Advanced ★ Fully Assembled

**NEW LOW PRICE!**

**T1 T2**

**FC-1000A**

### AMPLIFIERS

MODEL	DESCRIPTION	KIT	ASSEMBLED
TA-001	1 W Mini-Amplifier▲	\$ 5.07	
TA-006	6W Mini-Amplifier▲	6.90	
TA-007	12W Mini-Amplifier▲	11.20	
TA-10	Stereo Pre-Amp. w/magnetic mic. amp▲	8.20	
TA-28MK2	Digital Voice Recorder▲▲	30.00	\$ 40.00
TA-50A/B	Multi-Purpose Melody Generator▲	11.84	16.58
TA-50C	Multi-Purpose Melody Generator▲	12.65	17.71
TA-120MK2	Class "A" Main Power Mono Amp▲	27.16	38.81
TA-300	30W Multi-Purpose Single Channel Amp▲	20.00	
TA-302	60W Stereo Power Booster▲★	50.00	70.00
TA-3221	50W + 50W IC Stereo Amp. w/led level display▲	35.50	
TA-323A	HQ 30W + 30W Stereo Amp▲	29.50	
TA-377A	FET Stereo Pre-Amp▲▲	59.95	75.00
TA-400	40W Solid State Mono Amp▲	28.00	
TA-477	120W Mostet Power Mono Amp▲	68.00	
TA-800	80W + 80W DC Pre-Main & Power Amp.▲▲	60.92	
TA-802	80W + 80W DC Stereo Main Power Amp.▲	45.94	
TA-820A	60W + 60W OCL DC Pre-Main Stereo Amp.▲▲	40.39	49.37
TA-1000A	100W Class "A" Main Power Mono Amp▲	59.69	80.58
TA-1500	100W x2 Class "A" DC Stereo Pre-Main Amp▲▲	73.70	95.81
TA-2200	DC FET Super Class "A" Pre-Amp.▲	47.70	58.24
TA-2400A	Electronic Echo & Revelation Amp▲▲★	93.30	116.80
TA-2500	HQ Pre-Amp. w/10 band graphic equalizer★		90.80
TA-2800	Hi-Fi Bi-Fet Pre-Amp. w/3 way tone control▲	48.90	
TA-3000	Stereo Simulator▲	30.20	41.38
TA-3600	300W HQ Hi-Fi Power Mono Amp.▲▲	79.00	103.00

### MISCELLANEOUS

MODEL	DESCRIPTION	KIT	ASSEMBLED
TY-23B	3 Channel Color Light Controller▲▲▲★	\$ 56.04	\$74.50
TY-25	Stereo Loudspeaker Protector▲	12.65	
TY-35	FM Wireless Microphone▲	9.22	
TY-36	AC/DC Quartz Digital Clock▲	18.00	
TY-38	Sound/Touch Control Switch▲	12.00	
TY-41 MK111	Infrared Remote Control Unit▲▲	15.00	25.00
TY-41 MKV	Infrared Remote Control Unit▲▲	20.00	35.00
TY-42	Bar/Dot Level Meter▲	24.15	
TY-43	3 1/2 Digital Panel Meter▲	33.00	46.20
TY-45	20 Steps Bar/Dot Audio Level Display▲	38.45	
TY-47	Superior Electronic Roulette▲	19.46	
SM-328	4 Channel Professional Color Light Controller▲		150.00
SM-333	Audio/Video Surround Sound Processor▲▲★	62.00	83.00
SM-666	Dynamic Noise Reduction▲	26.00	34.00
T-1	LCD Thermometer Clock w/in-outdoor sensor★		15.40
T-2	LCD Thermometer Clock w/F & C measurement★		14.40

### POWER SUPPLIES

MODEL	DESCRIPTION	KIT	ASSEMBLED
TR-100A	O-15V 2A Regulated DC Power Supply	59.50	69.50
TR-355A	O-15V 5A Regulated DC Power Supply	14.55	20.76
TR-355B	O-30V 3A Regulated DC Power Supply	14.55	20.76
TR-503	O-50V 3A Regulated DC Power Supply	15.75	22.65

### INSTRUMENTS

MODEL	DESCRIPTION	KIT	ASSEMBLED
SM-43	3 1/2 Multi-Functional Led D.P.M.	34.50	43.00
SM-48	4 1/2 Hi-Precision D.P.M.	38.00	48.00
SM-49	3 1/2 Multi-Functional LCD D.P.M. (w/hold function)	36.00	44.50
SM-48A	4 1/2 Hi-Precision D.P.M. w/stdnd case	41.20	52.00
SM-100	150 MC Digital Frequency Counter	79.00	90.00
FC1000A	1 GHz Frequency Counter		179.00

— WE ACCEPT MAJOR CREDIT CARDS, MONEY ORDERS AND CHECKS — BUSINESS & SHOWROOM HOURS: (PACIFIC TIME) MON. - FRI. 9:30 A.M. - 5:00 P.M. SAT. 10:00 A.M. - 5:00 P.M. TERMS: \$10.00 MIN. ORDER \* \$20 MIN. CHARGE CARD ORDER \* WE SHIP UPS GROUND \* ADD 10% OF TOTAL ORDER (MIN. \$3.00) FOR SHIPPING OUTSIDE USA. ADD 20% (MIN. \$5.00) TRANSIT INSURANCE. ADD 5% OF TOTAL (OUTSIDE USA ONLY). CA RESIDENTS ADD SALES TAX \* ALL MERCHANDISE SUBJECT TO PRIOR SALE \* PRICES ARE SUBJECT TO CHANGE WITHOUT NOTICE \* WE ARE NOT RESPONSIBLE FOR TYPOGRAPHICAL ERRORS.

**MARK V ELECTRONICS, INC. — 8019 E. Slauson Ave., Montebello, CA 90640**


**CIRCLE 93 ON FREE INFORMATION CARD**




## THE ELECTRONIC GOLDMINE
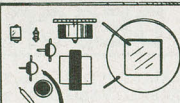
### INFRARED DETECTOR KIT

Uses sensitive sensor and electronic circuitry to respond to all types of infrared TV, VCR, etc. remote controllers and LEDs by producing sound and lighting a bright red LED. Great for testing and verification of infrared output - sees what you can not see. Small size: 2.5" x 1.4". Operates on 9V battery (not included). Kit comes with all parts and PC board.



C6441 \$59.95

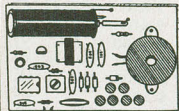

### MINI GEIGER COUNTER KIT

This useful kit lets you detect the radiation that you are being exposed to! Use it to detect radium dials on old watches, camping lantern mantles, radioactive minerals, background radiation, etc. Kit detects alpha, beta, gamma and X-ray radiation and features sensitive alpha-window GM tube with IC Circuit. Limits clicks in proportion to intensity of radiation! Size only 1.9" x 3". Operates from one 9V battery (not included). With all parts and PC board.

C6430 \$59.95

### PARTIAL LISTING OF OVER 130 UNIQUE KITS

All of our kits come with an etched and drilled PC board and all parts - you provide the battery and case (if desired). Kits that operate from 120VAC should be built by knowledgeable builders only due to AC safety concerns.

Lightning Bolt Strobe Kit (120VAC)	C6431	\$34.95
3 Channel Color Organ Kit (120VAC)	C4530	\$12.98
10 Channel Light Sequencer Kit (120VAC)	C4725	\$28.95
Battery Operated Blacklight Kit (6VDC)	C6356	\$13.95
Wheel of Fortune Kit (9VDC)	C3806	\$14.98
Logic Probe Kit (5VDC)	C6384	\$12.00
Ultrasonic Pest Repeller Kit (9VDC)	C6350	\$ 9.00
Burglar Alarm Kit (6VDC)	C6280	\$ 8.75
Jungle Bird Kit (9VDC)	C6374	\$ 6.25
Electronic Intercom Kit (9VDC)	C4743	\$12.49
Micro Xenon Tube Flasher Kit (1.5VDC)	C6268	\$14.95
Simulated Laser Kit (9VDC)	C6394	\$ 8.00
Battery Tester Kit (Tests all Types)(9VDC)	C6414	\$ 6.95

Ultra-brilliant clear jumbo case red led. Output 300mcd.	SUPER BRIGHT LED	A1012	3/\$1.00
			100/\$25.00

### SURFACE MOUNT CHIP COMPONENTS

CAPS		RESISTORS	
2pf	10	220	1.5K
3pf	39	270	1.8K
47	47	390	2.2K
10pf	56	470	3.3K
12pf	82	560	8.2K
22pf	120	680	12K
100pf	180	1.2K	15K

### INVERTER TRANSFORMER

Tiny 4 lead xformer for use with 555 IC to convert 12VDC to over 250V for strobes, fluorescent tubes, etc. Simple schematic included. \$7.95 \$2.00 each 100 for \$170

### 4KV TRIGGER COIL

3 lead trigger coil to fire most xenon flashlamps. \$17.00 \$1.25 each 100 for \$80

MINIMUM ORDER \$10.00 plus 3.00 shipping and handling. We accept M/C, Visa and money orders. COD is \$5.00 in addition to 3.00 shipping charge.

SEND ORDERS TO: The Electronic Goldmine

P.O. Box 5408 Scottsdale, AZ 85261

PHONE ORDERS: (602) 451-7454

CIRCLE 176 ON FREE INFORMATION CARD

## HARDWARE HACKER

continued from page 74

to get started with that outstanding graphics language.

I also have a new and free mailer for you that includes dozens of insider and top secret sources for all hardware hacking.

As always, this is your column and you can get technical help and off-the-wall networking per that *Need Help?* box. The best calling times are weekdays 8-5 in Mountain Standard Time. R-E

\*\*\*\*\*PRESENTING\*\*\*\*\*

## CABLE TV DESCRAMBLERS

\*\*\*\*\*STARRING\*\*\*\*\*  
JERROLD, HAMLIN, OAK  
AND OTHER FAMOUS MANUFACTURERS


- FINEST WARRANTY PROGRAM AVAILABLE
  - LOWEST RETAIL/WHOLESALE PRICES IN U.S.
  - ORDERS SHIPPED FROM STOCK WITHIN 24 HOURS
- FOR FREE CATALOG ONLY 1-800-345-8927  
FOR ALL INFORMATION 1-818-716-5914



PACIFIC CABLE CO. INC.  
7325 1/2 RESEDA BLVD., DEPT. RET 89  
RESEDA, CA 91355


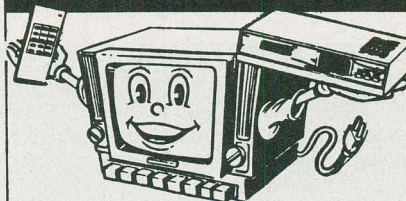
## CABLE T.V. CONVERTERS WHY PAY A HIGH MONTHLY FEE?



All Jerrold, Oak, Hamlin, Zenith, Scientific Atlanta, Magnavox and all specialized cable equipment available for shipment within 24 hours. For fast service MC / VISA or C.O.D. telephone orders accepted (800) 648-3030 60 Day Guarantee (Quantity Discounts) 8 A.M. to 5 P.M. C.S.T. CLOSED WEEK-ENDS. Send self-addressed Stamped envelope (60¢ postage) for Catalog.

MIDWEST ELECTRONICS INC.

P.O. Box 5000  
Suite 311 (R)  
Carpentersville, IL 60110

No Illinois Orders Accepted.

## TELEPHONE CALL SCREENING

REAL telephone call screening! Protect telephones, Fax, computer, hearing impaired, day sleepers. Eliminate wrong numbers, prank and sales calls. Plugin unit provides variable ring cadence signaling. True unlisted number on any touchtone private line. Automatic call routing. Send \$13.95 for complete theory and construction manual. ELECTRONIC CONTROL SYSTEMS, R.D. 2 Box 3308, Wernersville, PA 19565.

## But What Do All These Good Ideas Mean? Lower Prices!

For the past few months we have been telling you, among other things, that because we ask for a \$35 a year Membership Fee we do not force our customers to subsidize the cost of sending hundreds of thousands of Catalogs every few months to everyone on our Mailing List, and because our Catalog is actually a 2-inch three ring binder we don't waste money in sending the same old stuff to our customers over and over again. So what do all these cost saving ideas mean? Much lower prices than anywhere else on more than 10,000 items of electronic components. The following is a sample listing of some of these low prices:

- \* 1/4 Watt, 5%, Carbon Film Resistors: \$0.77/100, \$4.76/1000
- \* 74HC00, 74HCT00, 74LS00 Integrated Circuits: \$0.18/1, \$144.00/1000
- \* 78xx Positive Voltage Regulators (TO-220): \$0.38/1, \$30.80/100
- \* Cambion Low Profile 14-Pin Solder-Tab Sockets: \$0.10/1, \$73.92/1000
- \* Panasonic ECQ-V 0.1µF, 50V Bypass Capacitors: \$0.93/10, \$64.53/1000
- \* Package of 50, 3.0" Overall Length Wire-Wrap Wire: \$0.60/1
- \* 1N4001 Rectifier Diodes: \$0.42/10, \$28.52/1000
- \* 2N2222A Transistors: \$0.32/1, \$22.20/100, \$185/1000
- \* Howard W. Sams and Hayden Books: 34% Off Cover Price
- \* 1/4 Watt, 1%, Metal Film Resistors: \$0.32/10, \$1.16/100, \$8.25/1000
- \* LM741 Operational Amplifiers: \$2.00/10, \$165.24/1000
- \* 79xx Negative Voltage Regulators (TO-220): \$0.48/1, \$39.60/100
- \* Panasonic 15-Turn Rectangular Trim Pots: \$1.10/1, \$632.00/1000
- \* Panasonic Dipped Tantalum 10µF, 25V Capacitors: \$5.11/10, \$354.67/1000
- \* AP Products (Associated Electronics/3M): 20% Off List
- \* 1N4148 Switching Diodes: \$0.28/10, \$19.44/1000
- \* 2N3906 Transistors: \$7.20/100, \$60.00/1000
- \* Hammond Manufacturing Cases: 20% to 30% Off List

### 12 Months Saving Guarantee

We will refund the first year Membership Fee of any member who has purchased \$300 or more worth of products from Electronic Buyers Club and has not saved an amount greater than the first year Membership Fee, if buying the same items elsewhere.

These are not just a select number of items that we have chosen as 'Loss Leaders'. In fact we have been selling these items for the same (or lower) prices for the past 4 years! There are no grouping or volume purchase requirements to obtain these prices either! Become a Member today so you can start saving on all of the more than 10,000 items that we stock.

### 30 Days Money Back Guarantee

We will refund the full Membership Fee of any new member of Electronic Buyers Club who within 30 Days after receiving the Membership Binder, returns the Binder to EBC and asks for the cancellation of Membership.

**Electronic  
Buyers  
Club**

A Division of International Components Corporation

1803 N.W. Lincoln Way • Toledo, OR 97391  
PHONE (All 50 States & Canada): 1-800-325-0101  
FAX: (503) 336-4400 • Hours: 6:00 AM - 6:00 PM PST






# ANNOUNCING ...

## WORLD'S FIRST
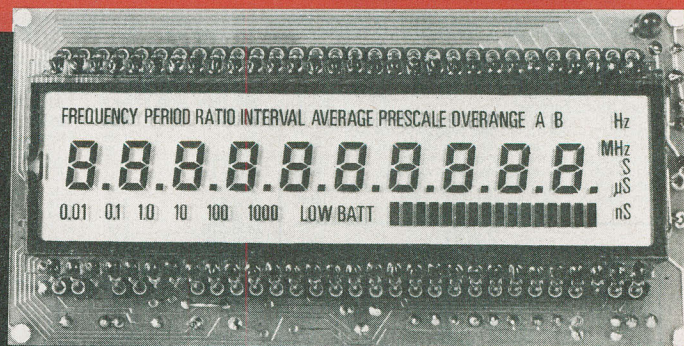
### High Performance Universal Counter Timer Module/Panel Meter



ACTUAL SIZE

#### INTRODUCTORY PRICING

Quantity	Price
1-10	189.00
11-99	159.00
100+	129.00

ENGINEERING EVALUATION KIT \$250.00

### OPTOELECTRONICS INC.

5821 N.E. 14th Avenue • Fort Lauderdale, Florida 33334  
(800) 327-5912 • FL (305) 771-2050 • FAX (305) 771-2052

CIRCLE 187 ON FREE INFORMATION CARD

- 10 Digit (120 Segment) LCD Display with Gate, Function, and Input Annunciators.
- .1 Hz to Over 150 MHz Direct Count (1 Hz resolution in 1 Sec).
- Single Shot Time Interval 100 ns, .1 ns averaged.
- Functions Include: Frequency, Period, Ratio, and Time Interval and Average.
- 16 Segment Analog Input Bargraph is driven by an 8 Bit A to D and Can Be Used for Signal Level Display.
- Low Power (250 mw) with Single 5v Supply.
- High Accuracy, 1 ppm 10 MHz Crystal Time Base with Cal Adjust on Board.
- Economical to Use in Custom OEM Applications.

## DESCRAMBLERS

"The Empire Strikes Back"



"We Cut Prices To The Bare Essentials"  
There Is NO Competition ANYWHERE !

## 10% UNDER ANYONES

Quoted or Advertised Prices...Even The WholeSale  
For Ordering & Info. (402)331-3228 Kings!  
Please Call.....

SALES REGULATED BY FEDERAL & STATE LAW ANYONE IMPLYING THEFT OF  
SERVICES WILL BE DENIED PURCHASE.

Cable Network Co., 5078 S. 108th St., Ste. 121, Omaha, NE 68137

CIRCLE 194 ON FREE INFORMATION CARD

JERROLD™  
TB-3

SCIENTIFIC  
ATLANTA  
SA-3

HAMLIN  
MLD 1200

OAK  
M35B  
W/ VARI-SYNC

INTELESTAR  
CONVERTERS

DF-3/2  
FILTERS

FULL  
WARRANTY

## CONSOLIDATED ELECTRONICS



COMPLETE WITH  
NEW PRICE LIST!

CONSUMER & INDUSTRIAL ELECTRONICS CATALOG • 37TH EDITION

## THE ULTIMATE ELECTRONICS CATALOG

Order your 260 page catalog and price list with over 14,000 money saving electronic parts and equipment! Send \$3.00 in a check or money order, or call 1-800-543-3568 today and use your Mastercard or Visa. Consolidated Electronics, Incorporated  
705 Watervliet Ave., Dayton, Ohio 45420-2599

Name \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

CIRCLE 70 ON FREE INFORMATION CARD



# Mail-Order Electronics

## 24 Hour Order Hotline

### 415-592-8097

### SIP & SIMM MODULES

Part No.	Function	Price
512KIT*	IBM PS/2 100ns 256K x 9 SIMM (2 each)	119.95
2MEGKIT*	IBM PS/2 100ns 1MEG x 9 SIMM (2 each)	469.95
41256A9A-10	282 144x9 100ns 256K x 9 SIMM (Has Leads)	49.95
41256A9B-80	282 144x9 80ns 256K x 9 SIMM	64.95
42100A8B-10	1,048 576x8 100ns 1MEG x 8 SIMM	164.95
42100A9A-80	1,048 576x9 80ns 1MEG x 9 SIMM (Has Leads)	169.95
42100A9B-80	1,048 576x9 80ns 1MEG x 9 SIMM	169.95

\*Upgrade for Models 30, 502 and 60

### 7400

Part No.	1-9	10+	Part No.	1-9	10+
7400	29	19	7474	39	29
7402	29	19	7475	49	39
7404	29	19	7476	45	35
7405	35	25	7483	59	49
7406	39	29	7485	65	55
7407	39	29	7486	45	35
7408	35	25	7489	2.25	2.15
7410	29	19	7490	49	39
7411	39	29	7493	45	35
7414	49	39	7495	59	49
7416	35	25	74107	29	19
7417	35	25	74121	39	29
7420	29	19	74123	49	39
7427	29	19	74125	49	39
7430	49	39	74174	1.99	1.89
7432	39	29	74150	1.35	1.25
7438	39	29	74151	39	29
7442	49	39	74154	1.35	1.25
7445	75	65	74161	69	59
7446	89	79	74174	59	49
7447	89	79	74177	59	49
7473	39	29	74193	79	69

### 74LS

74LS00	26	16	74LS139	49	39
74LS02	28	18	74LS151	49	39
74LS03	28	18	74LS153	49	39
74LS04	28	18	74LS154	1.29	1.19
74LS05	28	18	74LS157	45	35
74LS06	59	49	74LS161	49	39
74LS07	59	49	74LS163	49	39
74LS08	28	18	74LS164	59	49
74LS09	28	18	74LS165	75	65
74LS10	26	16	74LS166	89	79
74LS11	29	19	74LS173	45	35
74LS14	49	39	74LS174	39	29
74LS20	28	18	74LS175	39	29
74LS21	29	19	74LS191	59	49
74LS27	35	25	74LS192	69	59
74LS30	28	18	74LS193	69	59
74LS32	28	18	74LS194	69	59
74LS38	35	25	74LS221	69	59
74LS42	49	39	74LS240	59	49
74LS47	85	75	74LS241	59	49
74LS73	39	29	74LS244	59	49
74LS74	35	25	74LS245	79	69
74LS75	39	29	74LS257	49	39
74LS76	39	29	74LS259	99	89
74LS83	55	45	74LS273	89	79
74LS85	55	45	74LS279	49	39
74LS86	29	19	74LS367	49	39
74LS90	49	39	74LS373	79	69
74LS93	49	39	74LS374	79	69
74LS123	49	39	74LS393	89	79
74LS125	49	39	74LS541	1.29	1.19
74LS132	49	39	74LS590	5.95	5.85
74LS138	49	39	74LS688	2.39	2.29

### 74S/PROMS\*

74S00	25	74S188*	1.49
74S04	25	74S189	1.49
74S32	25	74S240	1.39
74S74	25	74S244	.99
74S112	25	74S287*	1.49
74S124	1.25	74S288*	1.49
74S138	49	74S373	.99
74S153	49	74S374	.99
74S163	75	74S387*	1.29
74S174	29	74S472*	2.95
74S175	39	74S571*	2.49

### CD-CMOS

CD4001	19	CD4051	59
CD4002	19	CD4052	59
CD4007	19	CD4053	59
CD4011	19	CD4060	65
CD4012	25	CD4066	65
CD4013	29	CD4069	25
CD4015	29	CD4070	19
CD4016	29	CD4071	19
CD4017	29	CD4072	19
CD4018	29	CD4073	19
CD4020	59	CD4081	19
CD4021	49	CD4093	35
CD4024	45	CD4094	35
CD4027	45	CD4503	69
CD4028	49	CD4504	69
CD4029	69	CD4518	75
CD4030	69	CD4520	69
CD4040	65	CD4522	75
CD4042	49	CD4528	69
CD4043	59	CD4538	79
CD4046	65	CD4543	79
CD4047	29	CD4584	49
CD4049	29	CD4585	69

### NEC V20 & V30 CHIPS

Replace the 8086 or 8088 in Your IBM PC and Increase Its Speed by up to 30%

Part No.	Function	Price
UPD70108-5	(5MHz) V20 Chip	5.25
UPD70108-8	(8MHz) V20 Chip	6.95
UPD70108-10	(10MHz) V20 Chip	10.95
UPD70116-8	(8MHz) V30 Chip	7.95
UPD70116-10	(10MHz) V30 Chip	13.49

### MICROPROCESSOR COMPONENTS

Z80, Z80A, Z80B, SERIES		8000 SERIES Continued		8000 SERIES Continued	
Part No.	Price	Part No.	Price	Part No.	Price
Z80	1.25	8155-2	3.75	8286	2.29
Z80A	1.29	81C55	4.25	8741	9.49
Z80A-CTC	1.65	8205	9.95	8742	14.95
Z80A-DART	4.95	82C11	6.95	8748 (25V)	7.95
Z80A-PIO	1.89	8212	1.99	8748H (HMOS)(21V)	9.95
Z80A-SIO/O	3.95	8216	1.39	8749	9.95
Z80B	2.75	8224	1.49	8751H (3.5-12MHz)	34.95
Z80B-CTC	3.95	8228	1.49	8755	13.95
Z80B-PIO	3.95	8237-5	4.25	ADC0808CN	5.49
Z8400H-B1 CPU-BM1	3.95	8249	1.95	ADC0809CN	5.49
8000 SERIES		8250A	4.95	80287-3 (5MHz)	109.95
8031	3.95	8250B (For IBM)	5.95	80287-8 (8MHz)	209.95
80C31	8.95	8251A	1.95	80386-16 PGA	259.95
8035	1.25	8251B	1.89	80387-16 (16MHz)	349.95
8039	1.59	8253-5	1.95	80387-20 (20MHz)	399.95
8052AH-BASIC	24.95	82C53-5	3.95	80387-25 (25MHz)	499.95
8080A	1.95	8254	4.95	82284 (8MHz)	5.49
8085A	1.95	8255A-5	2.95	82288 (8MHz)	6.95
8085A-2	3.59	82C55A-5	4.49	DATA ACQUISITION	
8086	3.95	8256	11.95	ADC0804LCN	3.25
8087 (5MHz)	89.95	8259-5	2.25	ADC0808CN	5.49
8087-1 (10MHz)	169.95	8272	3.75	ADC0809CN	5.49
8087-2 (8MHz)	129.95	8274	4.75	ADC1205CJ-1	19.95
8088 (5MHz)	4.95	8279-5	2.95	DAC0808LCN	1.49
8088-2 (8MHz)	6.95	8282	2.95	AY-3-10150	4.95
8155	2.49	8284A	1.95	AY-5-1013A	2.95

### STATIC RAMS

Part No.	Function	Price
2016-12	2048x8 120ns	2.95
2102	1024x1 350ns	.89
2112	256x4 450ns MOS	2.49
2114N	1024x4 450ns	2.49
2114N-2L	1024x4 200ns Low Power	1.49
21C14	1024x4 200ns (CMOS)	1.49
5101	256x4 450ns (CMOS)	1.95
6116P-1	2048x8 150ns (16K) CMOS	3.19
6116P-3	2048x8 150ns (16K) CMOS	2.79
6116LP-1	2048x8 100ns (16K) LP CMOS	3.59
6116LP-3	2048x8 150ns (16K) LP CMOS	3.09
6264P-10	8192x8 100ns (64K) CMOS	6.75
6264P-15	8192x8 150ns (64K) CMOS	6.29
6264LP-10	8192x8 100ns (64K) LP CMOS	6.95
6264LP-12	8192x8 120ns (64K) LP CMOS	6.75
6264LP-15	8192x8 150ns (64K) LP CMOS	6.49
6514	1024x4 350ns CMOS	1.75
43256-10L	32,768x8 100ns (256K) Low Power	10.95
43256-15L	32,768x8 150ns (256K) Low Power	9.95
62256LP-10	32,768x8 100ns (256K) LP CMOS	11.95
62256LP-12	32,768x8 120ns (256K) LP CMOS	11.25
62256LP-15	32,768x8 150ns (256K) LP CMOS	10.95

### DYNAMIC RAMS

TMS4416-12	16,384x4 120ns	5.95
TMS4416-15	16,384x4 150ns	5.49
4116-15	16,384x4 150ns (MMS290N-2)	4.49
4128-15	31,072x1 150ns (Piggyback)	4.49
4164-100	65,536x1 100ns	2.75
4164-120	65,536x1 120ns	2.39
4164-150	65,536x1 150ns	2.15
41256-60	262,144x1 60ns	6.95
41256-80	262,144x1 80ns	6.95
41256-100	262,144x1 100ns	3.95
41256-120	262,144x1 120ns	3.69
41256-150	262,144x1 150ns	3.25
41264-12	64Kx4 120ns Video RAM	10.95
41464-80	65,536x4 80ns	5.95
41464-12	65,536x4 120ns	4.49
41464-15	65,536x4 150ns	4.25
51258-10	262,144x1 100ns Static Column	8.95
51100P-80	1,048,576x1 80ns (1 Meg)	13.95
51100P-10	1,048,576x1 100ns (1 Meg)	12.95
514256P-10	262,144x4 100ns (1 Meg)	14.49
514258-10	262,144x4 100ns Static Column	26.95

### EPROMS

TMS2516	2048x8 450ns (25V)	4.95
TMS2532	4096x8 450ns (25V)	5.95
TMS2532A	4096x8 450ns (12.5V)	5.95
TMS2564	8192x8 450ns (25V)	6.95
TMS2716	2048x8 450ns (-5V, +5V, +12V)	6.49
1702A	256x8 2K (1µs)	4.25
2708	1024x8 450ns	4.95
2716	2048x8 450ns (25V)	5.49
2716-1	2048x8 350ns (25V)	3.95
27C16	2048x8 450ns (25V) CMOS	4.25
2732	4096x8 450ns (25V)	3.95
2732A-20	4096x8 200ns (21V)	3.95
27C32	4096x8 450ns (25V) CMOS	4.25
2764-25	8192x8 250ns (12.5V)	4.19
2764A-25	8192x8 250ns (12.5V)	3.49
27C64-15	8192x8 150ns (12.5V) CMOS	4.95
27128-20	16,384x8 200ns (21V)	5.95
27128-25	16,384x8 250ns (21V)	5.25
27128A-15	16,384x8 150ns (12.5V)	6.95
27C256-25	32,768x8 250ns (12.5V) CMOS	4.75
27C128-25	16,384x8 250ns (21V) CMOS	7.25
27526-15	32,768x8 150ns (12.5V)	8.49
27526-20	32,768x8 200ns (12.5V)	5.49
27526-25	32,768x8 250ns (12.5V) CMOS	4.95
27C256-15	32,768x8 150ns (12.5V) CMOS	7.25
27C256-20	32,768x8 200ns (12.5V) CMOS	5.49
27512-25	65,536x8 250ns (12.5V)	7.95
27C512-15	65,536x8 150ns (12.5V) CMOS	9.95
27C512-25	65,536x8 250ns (12.5V) CMOS	7.49
27C010-15	131,072x8 150ns (12.5V) CMOS (1 Meg)	19.95
68764	8192x8 64K 450ns (25V) (Chip Enable)	14.95
68766-35	8192x8 64K 350ns (25V) (Output Enable)	15.95

### EEPROMS

2816A-25	2048x8 250ns (9V-15V) 5V Read/Write	5.49
2817A	2048x8 350ns 5V Read/Write	6.95
2864A	8192x8 250ns 5V Read/Write (Pin 1, No R/W) 10.95	10.95
2865A	8192x8 250ns 5V Read/Write	10.95

### MISC. COMPONENTS

TANTALUM CAPACITORS				
TM.1	.1µf @ 35V.....	19	TM4.7	4.7µf @ 35V... .45
TM1	1µf @ 35V.....	19	TM6.8	6.8µf @ 35V... .59
TM2.2	2.2µf @ 35V... .25		TM10	10µf @ 35V... .69



# Now Available...Jameco's NEW 1990 Catalog with 80 pages of Computer Peripherals, Components & More!

## Oscilloscope Probes


- Attenuation: x1 / x10
- Capacitance (LF180): 180pF / 22pF; (LF210): 40pF / 17pF



- LF180** 40MHz Oscilloscope Probe ..... \$19.95  
**LF210** 100MHz Oscilloscope Probe ..... \$29.95

## TEST EQUIPMENT

**GoldStar 20MHz Oscilloscope and 1GHz Frequency Counter**

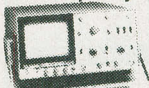

GS7020

- Large 6" rectangular display • High sensitivity: 1 mV/div

**GS7020** Oscilloscope.....\$399.95

- Wide measuring range • Measured value hold function

**FC7102** Frequency Counter \$299.95

## Prometheus 9600 Baud Modem



**9600E** External 9600 Baud.... \$749.95

**1200B** Internal 1200 Baud ..... \$49.95

**2400B** Internal 2400 Baud ..... \$99.95

## Metex Digital Multimeters

### Metex General Specs:

- Handheld, high accuracy
- AC/DC Voltage, AC/DC Current, Resistance, Diodes, Continuity, Transistor hFE
- Manual ranging w/overload protection

M4650

**M3650, 3650B & M4650 only:**

- Also measure frequency and capacitance

**M4650 only:** • Data Hold Switch • 4.5 Digit

**M3610** 3.5 Digit Multimeter .....\$49.95


**M3650** 3.5 Digit Multimeter w/Frequency & Capacitance .....\$69.95

**M3650B** Same as M3650 w/Bargraph.....\$79.95

**M4650** 4.5 Digit w/Frequency, Capacitance and Data Hold Switch.....\$99.95

## PROTOTYPING PRODUCTS

### Jameco Solderless Breadboards

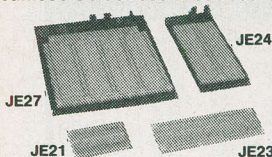

Part No.	Dim. L" x W"	Contact Points	Binding Posts	Price
JE21	3.25 x 2.125	400	0	\$4.95
JE23	6.5 x 2.125	830	0	\$6.95
JE24	6.5 x 3.125	1,360	2	\$12.95
JE25	6.5 x 4.25	1,660	3	\$17.95
JE26	6.875 x 5.75	2,390	4	\$22.95
JE27	7.25 x 7.5	3,220	4	\$32.95

## Prototype Design Stations

WM2


- WM1 & WM2 Features:** • Removable solderless breadboard • Variable and fixed DC power supply • Multi-frequency signal generator • Analog multimeter • 8 bicolor LEDs (red & green) • 8 logic switches • Logic probe • Lighted power switch • Fuse overload protected • Sturdy ruggedized case

- WM1 Special Features:** • 4 potentiometers • Built-in speaker

- WM2 Special Features:** • Pulse Generator • Binary coded decimal (BCD) to 7-segment decoder/driver • DB25 connector • Frequency counter (1Hz to 1MHz)

**WM1** Analog Prototype Station .... \$199.95

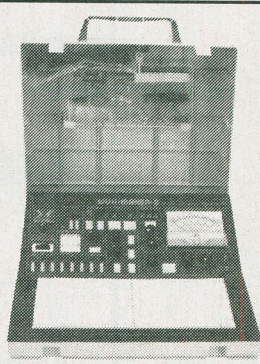**WM2** Digital Prototype Station .... \$249.95



## IBM Compatible Cases and Power Supplies

JE2012



JE1030

**JE1010** Flip-Top Standard PC/XT Case..... \$39.95

**JE1011** Slide Standard PC/XT Case..... \$39.95

**JE1018** Slide Baby AT Case ..... \$59.95

**JE1030** 150 watt PC/XT Power Supply ..... \$59.95

**JE1032** 200 watt Baby AT Power Supply ..... \$89.95


**JE2011** Vertical Case w/300W Pwr. Supply..... \$279.95

**JE2012** Mini-Vertical Case w/200W Pwr. Supply..... \$149.95

**JE2014** Flip-Top Baby XT Turbo Case ..... \$69.95

**JE2019** Flip-Top Baby AT Case ..... \$69.95

## Jameco IBM PC/XT/AT Compatible Keyboards

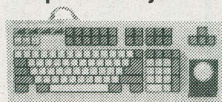

JE2017

**JE2015** 84-Key Standard AT Style Layout .....\$59.95

**JE1016** 101-Key Enhanced Layout with 12 Function Keys .....\$69.95

**JE2016** 111-Key Enhanced with Solar Powered Calculator.....\$79.95

**JE2017** 104-Key Enhanced with Trackball (Microsoft Compatible) .... \$99.95

## 3.5" and 5.25" Floppy Disk Drives



MPF11 Pictured

### Sony

**MPF11** 3.5" 720Kb Internal Drive.... \$69.95

**SMK** 5.25" Installation Kit w/Faceplate .. \$14.95

### Toshiba

**356KU** 3.5" 1.44Mb Internal Drive \$109.95

### TEAC

**FD55B** 5.25" 360Kb Half Ht. .... \$99.95

**FD55G** 5.25" 1.2Mb Half Ht. .... \$119.95

### Jameco

**JE1020** 5.25" 360Kb Half Ht. Black \$89.95


**JE1021** 5.25" 360Kb Half Ht. Gray \$89.95

**JE1022** 5.25" 1.2Mb Half Ht. Gray \$99.95

## SPECIALS



JE1061

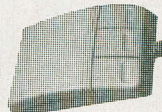

DMS200S

**DMS200S** Mouse w/Driver & Graph Stwr. & Pad ... \$49.95

**JE1045** Hard Disk/Floppy Controller (AT) ..... \$129.95

**JE1061** RS232 half card (XT) ..... \$24.95

**JE1079A** Multi I/O & 360 Kb Controller (XT) ..... \$59.95

**JE1198** Universal Printer Stand ..... \$7.95

**JE2010** Vertical Case w/250W Power Supply.. \$249.95

**SCAN200** Logitech 200DPI Scanner ..... \$159.95

**SMGC** Monochrome Graphics Card ..... \$34.95

**2012WR** Mini Vertical Case w/200W Supply .... \$129.95

## Display Monitors and Packages

**AMBER** 12" Amber Monochrome ..... \$99.95

**HD55H** 14" RGB 640 x 240 ..... \$249.95

**M9070S** 16" Multiscan Monitor 1280 x 800..... \$1099.95

**TM5154** 14" EGA 720 x 350 ..... \$369.95


**JE1059** TM5154 EGA Monitor & EGA Card..... \$459.95

**TM5156** 14" VGA 720 x 480 ..... \$399.95

**JE2060** TM5156 VGA Monitor & VGA Card..... \$529.95


**TM5157** 14" Multiscan 800 x 600..... \$469.95

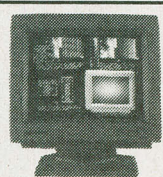**JE2057** TM5157 Multiscan Monitor & EGA Card ... \$559.95



M9070S

## A.R.T. EPROM Programmer

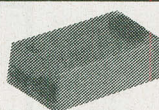

- Programs all current EPROMs in the 2716 to 27512 range plus the X2864 EEPROM • May be operated by any RS232 port w/terminal emulation • Fully intelligent • ASCII command driven • Menu driven software included

**EPP**.....\$179.95

## UVP EPROM Eraser



- Erases all EPROM's • Erases 1 chip in 15 Min. and 8 chips in 21 min. • Maintains constant exposure distance of 1" • Special conductive foam liner eliminates static build-up • Built-in safety lock • UV intensity: 6800 UW/CM<sup>2</sup>

**DE4**.....\$69.95

## Soldering and Desoldering Stations



XY1683



XY999

**60 Watt Digital Display Soldering Station • Electronic temperature control from 200° to 878°F**

• Temperature displayed on easy to read .560" H 3-digit LED readout • Nichrome heating element

**XY960** ..... \$99.95

**60 Watt Analog Display Soldering Station • Electronic temperature control from 200° to 878°F**

• Cartridge heating element for a longer life of the soldering tip

**XY1683** ..... \$59.95

**60 Watt Analog Display Soldering Station • Electronic temperature control from 200° to 878°F**

• Ceramic heating element for a steady temperature and long life

**XY2660** ..... \$89.95

**30 Watt Electronic Temperature Controlled Desoldering Station • Electronic temperature control from 212° to 842°F • Self-contained high rotary vacuum pump**

**XY999** ..... \$279.95

## Hard & Hard/Floppy Disk Controller Cards

Computer Type	MFM Hard		RLL Hard		MFM Hard/Floppy		RLL Hard/Floppy	
	Part No. / Price		Part No. / Price		Part No. / Price		Part No. / Price	
8088 (PC/XT) @ 3:1 Interleave	XTGEN/\$79.95		1004A27X/\$89.95		JE1044/\$109.95		.....	
80286 (AT)/386 @ 2:1 Interleave	1003VMM1/\$129.95		1003VSR1/\$149.95		1003VMM2/\$149.95		1003VSR2/\$169.95	
80286 (AT)/386 @ 1:1 Interleave	1006VMM1/\$149.95		1006VSR1/\$169.95		1006VMM2/\$169.95		1006VSR2/\$189.95	

1355 Shoreway Road  
Belmont, CA 94002  
24 Hour Order Hotline (415) 592-8097  
FAX's (415) 592-2503 or (415) 595-2664  
Telex 176043 - Ans. Back: Jameco Blmt  
Data Sheets - 50¢ each  
Send \$2.00 Postage for a FREE 80-Page Catalog  
© 1990 Jameco Electronics 2/90  
IBM is a registered trademark of International Business Machines



\$25.00 Minimum Order - U.S. Funds Only  
CA Residents Add 6%, 6.5% or 7.5% Sales Tax  
Shipping - Add 5% plus \$1.50 Insurance  
(May vary according to weight and shipping method)  
Terms: Prices subject to change without notice.  
We are not responsible for typographical errors.  
We reserve the right to substitute manufacturers.  
Items subject to availability and prior sale.  
Products pictured may only be representative.  
Complete list of terms/warranties is available upon request.

24-Hour Order Hotline (415) 592-8097 • The Following Services Are Also Available Through (415) 592-8097 From 7AM - 5PM P.S.T.:  
• Customer Service • Technical Assistance • Credit Department • All Other Inquiries

CIRCLE 114 ON FREE INFORMATION CARD



# 1-800-345-5399

AK, Puerto Rico - 218-681-6674 FAX - 218-681-3380

TWX - 910350892 DIGI KEY CORP

INTEGRATED CIRCUITS				INTEGRATED CIRCUITS				SILICON TRANSISTORS				PANASONIC® SU SERIES				DISC CAPACITORS						
7400 TTL				7400 CMOS				1 AMP SILICON RECTIFIERS				Miniature Aluminum Electrolytic Capacitors										
Part No.	Price	Part No.	Price	Part No.	Price	Part No.	Price	Part No.	Price	Part No.	Price	Part No.	Price	Part No.	Price	Part No.	Price					
7400	35	74LS00	35	7401	35	74LS01	35	PN4565	37	PN153	26	PN153B	27	6.3/10.00	PN317	1.62	P4129	1200/1K	2.25	P4307	047/125	1.61
7401	35	74LS01	35	7402	35	74LS02	35	PN4566	37	PN153B	26	PN153B	27	6.3/12.00	PN317	1.62	P4130	1500/1K	2.25	P4311	147/125	1.61
7402	35	74LS02	35	7403	35	74LS03	35	PN4567	37	PN153B	26	PN153B	27	6.3/15.00	PN317	1.62	P4131	1800/1K	2.25	P4312	180/125	1.61
7403	35	74LS03	35	7404	35	74LS04	35	PN4568	37	PN153B	26	PN153B	27	6.3/20.00	PN317	1.62	P4132	2000/1K	2.23	P4313	1500/150	1.75
7404	35	74LS04	35	7405	35	74LS05	35	PN4569	37	PN153B	26	PN153B	27	6.3/25.00	PN317	1.62	P4133	2200/1K	2.93	P4314	2200/250	1.75
7405	35	74LS05	35	7406	35	74LS06	35	PN4570	37	PN153B	26	PN153B	27	6.3/30.00	PN317	1.62	P4134	2400/1K	2.93	P4315	2400/500	1.75
7406	35	74LS06	35	7407	35	74LS07	35	PN4571	37	PN153B	26	PN153B	27	6.3/35.00	PN317	1.62	P4135	2600/1K	4.36	P4316	2600/750	1.75
7407	35	74LS07	35	7408	35	74LS08	35	PN4572	37	PN153B	26	PN153B	27	6.3/40.00	PN317	1.62	P4136	2800/1K	4.36	P4317	2800/1000	1.75
7408	35	74LS08	35	7409	35	74LS09	35	PN4573	37	PN153B	26	PN153B	27	6.3/45.00	PN317	1.62	P4137	3000/1K	5.36	P4318	3000/1500	1.75
7409	35	74LS09	35	7410	35	74LS10	35	PN4574	37	PN153B	26	PN153B	27	6.3/50.00	PN317	1.62	P4138	3200/1K	8.44	P4319	3200/2500	1.75
7410	35	74LS10	35	7411	35	74LS11	35	PN4575	37	PN153B	26	PN153B	27	6.3/55.00	PN317	1.62	P4139	3400/1K	8.44	P4320	3400/5000	1.75
7411	35	74LS11	35	7412	35	74LS12	35	PN4576	37	PN153B	26	PN153B	27	6.3/60.00	PN317	1.62	P4140	3600/1K	8.44	P4321	3600/7500	1.75
7412	35	74LS12	35	7413	35	74LS13	35	PN4577	37	PN153B	26	PN153B	27	6.3/65.00	PN317	1.62	P4141	3800/1K	8.44	P4322	3800/10000	1.75
7413	35	74LS13	35	7414	35	74LS14	35	PN4578	37	PN153B	26	PN153B	27	6.3/70.00	PN317	1.62	P4142	4000/1K	8.44	P4323	4000/15000	1.75
7414	35	74LS14	35	7415	35	74LS15	35	PN4579	37	PN153B	26	PN153B	27	6.3/75.00	PN317	1.62	P4143	4200/1K	8.44	P4324	4200/20000	1.75
7415	35	74LS15	35	7416	35	74LS16	35	PN4580	37	PN153B	26	PN153B	27	6.3/80.00	PN317	1.62	P4144	4400/1K	8.44	P4325	4400/25000	1.75
7416	35	74LS16	35	7417	35	74LS17	35	PN4581	37	PN153B	26	PN153B	27	6.3/85.00	PN317	1.62	P4145	4600/1K	8.44	P4326	4600/30000	1.75
7417	35	74LS17	35	7418	35	74LS18	35	PN4582	37	PN153B	26	PN153B	27	6.3/90.00	PN317	1.62	P4146	4800/1K	8.44	P4327	4800/35000	1.75
7418	35	74LS18	35	7419	35	74LS19	35	PN4583	37	PN153B	26	PN153B	27	6.3/95.00	PN317	1.62	P4147	5000/1K	8.44	P4328	5000/40000	1.75
7419	35	74LS19	35	7420	35	74LS20	35	PN4584	37	PN153B	26	PN153B	27	6.3/100.00	PN317	1.62	P4148	5200/1K	8.44	P4329	5200/45000	1.75
7420	35	74LS20	35	7421	35	74LS21	35	PN4585	37	PN153B	26	PN153B	27	6.3/105.00	PN317	1.62	P4149	5400/1K	8.44	P4330	5400/50000	1.75
7421	35	74LS21	35	7422	35	74LS22	35	PN4586	37	PN153B	26	PN153B	27	6.3/110.00	PN317	1.62	P4150	5600/1K	8.44	P4331	5600/55000	1.75
7422	35	74LS22	35	7423	35	74LS23	35	PN4587	37	PN153B	26	PN153B	27	6.3/115.00	PN317	1.62	P4151	5800/1K	8.44	P4332	5800/60000	1.75
7423	35	74LS23	35	7424	35	74LS24	35	PN4588	37	PN153B	26	PN153B	27	6.3/120.00	PN317	1.62	P4152	6000/1K	8.44	P4333	6000/65000	1.75
7424	35	74LS24	35	7425	35	74LS25	35	PN4589	37	PN153B	26	PN153B	27	6.3/125.00	PN317	1.62	P4153	6200/1K	8.44	P4334	6200/70000	1.75
7425	35	74LS25	35	7426	35	74LS26	35	PN4590	37	PN153B	26	PN153B	27	6.3/130.00	PN317	1.62	P4154	6400/1K	8.44	P4335	6400/75000	1.75
7426	35	74LS26	35	7427	35	74LS27	35	PN4591	37	PN153B	26	PN153B	27	6.3/135.00	PN317	1.62	P4155	6600/1K	8.44	P4336	6600/80000	1.75
7427	35	74LS27	35	7428	35	74LS28	35	PN4592	37	PN153B	26	PN153B	27	6.3/140.00	PN317	1.62	P4156	6800/1K	8.44	P4337	6800/85000	1.75
7428	35	74LS28	35	7429	35	74LS29	35	PN4593	37	PN153B	26	PN153B	27	6.3/145.00	PN317	1.62	P4157	7000/1K	8.44	P4338	7000/90000	1.75
7429	35	74LS29	35	7430	35	74LS30	35	PN4594	37	PN153B	26	PN153B	27	6.3/150.00	PN317	1.62	P4158	7200/1K	8.44	P4339	7200/95000	1.75
7430	35	74LS30	35	7431	35	74LS31	35	PN4595	37	PN153B	26	PN153B	27	6.3/155.00	PN317	1.62	P4159	7400/1K	8.44	P4340	7400/100000	1.75
7431	35	74LS31	35	7432	35	74LS32	35	PN4596	37	PN153B	26	PN153B	27	6.3/160.00	PN317	1.62	P4160	7600/1K	8.44	P4341	7600/105000	1.75
7432	35	74LS32	35	7433	35	74LS33	35	PN4597	37	PN153B	26	PN153B	27	6.3/165.00	PN317	1.62	P4161	7800/1K	8.44	P4342	7800/110000	1.75
7433	35	74LS33	35	7434	35	74LS34	35	PN4598	37	PN153B	26	PN153B	27	6.3/170.00	PN317	1.62	P4162	8000/1K	8.44	P4343	8000/115000	1.75
7434	35	74LS34	35	7435	35	74LS35	35	PN4599	37	PN153B	26	PN153B	27	6.3/175.00	PN317	1.62	P4163	8200/1K	8.44	P4344	8200/120000	1.75
7435	35	74LS35	35	7436	35	74LS36	35	PN4600	37	PN153B	26	PN153B	27	6.3/180.00	PN317	1.62	P4164	8400/1K	8.44	P4345	8400/125000	1.75
7436	35	74LS36	35	7437	35	74LS37	35	PN4601	37	PN153B	26	PN153B	27	6.3/185.00	PN317	1.62	P4165	8600/1K	8.44	P4346	8600/130000	1.75
7437	35	74LS37	35	7438	35	74LS38	35	PN4602	37	PN153B	26	PN153B	27	6.3/190.00	PN317	1.62	P4166	8800/1K	8.44	P4347	8800/135000	1.75
7438	35	74LS38	35	7439	35	74LS39	35	PN4603	37	PN153B	26	PN153B	27	6.3/195.00	PN317	1.62	P4167	9000/1K	8.44	P4348	9000/140000	1.75
7439	35	74LS39	35	7440	35	74LS40	35	PN4604	37	PN153B	26	PN153B	27	6.3/200.00	PN317	1.62	P4168	9200/1K	8.44	P4349	9200/145000	1.75
7440	35	74LS40	35	7441	35	74LS41	35	PN4605	37	PN153B	26	PN153B	27	6.3/205.00	PN317	1.62	P4169	9400/1K	8.44	P4350	9400/150000	1.75
7441	35	74LS41	35	7442	35	74LS42	35	PN4606	37	PN153B	26	PN153B	27	6.3/210.00	PN317	1.62	P4170	9600/1K	8.44	P4351	9600/155000	1.75
7442	35	74LS42	35	7443	35	74LS43	35	PN4607	37	PN153B	26	PN153B	27	6.3/215.00	PN317	1.62	P4171	9800/1K	8.44	P4352	9800/160000	1.75
7443	35	74LS43	35	7444	35	74LS44	35	PN4608	37	PN153B	26	PN153B	27	6.3/220.00	PN317	1.62	P4172	10000/1K	8.44	P4353	10000/165000	1.75
7444	35	74LS44	35	7445	35	74LS45	35	PN4609	37	PN153B	26	PN153B	27	6.3/225.00	PN317	1.62	P4173	10200/1K	8.44	P4354	10200/170000	1.75
7445	35	74LS45	35	7446	35	74LS46	35	PN4610	37	PN153B	26	PN153B	27	6.3/230.00	PN317	1.62	P4174	10400/1K	8.44	P4355	10400/175000	1.75
7446	35	74LS46	35	7447	35	74LS47	35	PN4611	37	PN153B	26	PN153B	27	6.3/235.00	PN317	1.62	P4175	10600				




★QUALITY PARTS ★DISCOUNT PRICES ★FAST SHIPPING

# ALL ELECTRONICS CORP.
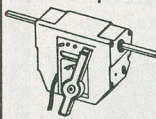
## 3 to 6 Vdc MOTOR with GEARBOX

Probably designed for child's toy. Lever selects 2 forward and one reverse speed. 1st gear approx.

120 rpm/6vdc,  
2nd gear approx.  
300 rpm/6vdc,  
Reverse approx.  
120 rpm/6vdc.



3.35" X 1.75" X 3.25"  
CAT# DCM-10 \$6.00

## 4 AA BATTERY PACK (USED)

Four AA nickel cadmium batteries connected in series to make a 4.8 volt pack. Batteries are in a 2 X 2 configuration with a 2 pin connector attached. The four batteries can be separated into single AA size solder tab nickel cadmium batteries or resoldered into other configurations.



SPECIAL SALE PRICE - WERE-  
\$4.00 per pack NOW \$3.00 per pack  
CAT# NCB-41AAU

## STEPPER MOTOR

Airpax# A82743-M4  
Brand new 12 volt  
dc stepper motor.




35 ohm coil.  
7.5 degrees per  
step. 2.25" diameter,  
0.93" long excluding shaft.  
0.22" diameter shaft is 0.75" long. 2  
hole mounting flange, 2.675" mounting  
centers. 6 wire leads.

CAT# SMT-5  
\$10.00 each

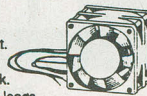
## 12 VOLT DC MINI FAN

Howard Industries#  
3-15-810. Operates on  
12 Vdc, 0.10 amp, 1.0 watt.  
Compact plastic housing,  
0.35" square X 1.275" thick,  
9 blade fan. Two 9" pigtail leads.  
CAT# CF-121 \$9.00 each


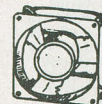
## 115 VAC COOLING FAN

STANDARD SIZE  
COOLING FAN.  
Features die cast metal housing  
for strength and durability.  
IMPEDANCE PROTECTED  
4 1/16" square X 1 1/2" deep.  
Factory new 120 Vac fans. CF1-N \$9.50 each



## WALL TRANSFORMERS

ALL PLUG DIRECTLY INTO 120 VAC OUTLET



6 Vdc @ 200 ma. CAT# DCTX-620 \$2.25  
9 Vdc @ 250 ma. CAT# DCTX-925 \$2.50  
18 Vac @ 1 amp. CAT# ACTX-1885 \$3.50  
24 Vac @ 625 ma. CAT# ACTX-2482 \$3.25

## SWITCHES

### ITT PUSH BUTTON

ITT MDPL series. 3/4" X  
1/2" gray rectangular  
key cap. S.P.S.T. N.O.  
Push to close. RATED: 0.1 amp switching, 0.25  
amp carry current. P.C. mount. CAT# PB-8  
65¢ each • 10 for \$6.00 • 100 for \$50.00



### 10 POSITION MINI-ROTARY

Grayhill# 56P36-01-1-10N-C  
Mini rotary switch. Non-shorting.  
1 deck, 10 positions. .125" dia  
shaft X .375" long. .377" behind  
the panel depth. P.C. pins.  
CAT# MRS-10 WAS \$2.50 NOW \$1.50 each



### SPDT PUSHBUTTON

Marquardt# 1843  
Rated 6 amps @ 125/250 Vac.  
Black plastic pushbutton.  
Switch body: .92" X .94" X .65".  
CAT# PB-18 \$1.65 each • 10 for \$1.50 each



### PUSHBUTTON SWITCH

GC/Thornsen# 35-420  
S.P.S.T., normally open momentary push-  
button switch. Red plastic actuator .57" dia.  
Chrome bezel .68" diameter. Threaded  
bushing mounts in .50" diam. chassis hole.  
Rated 3 amp @ 250 Vac. Solder loop terminals.  
CAT# PB-20 \$1.00 each



## LOOK WHAT \$1.00 WILL BUY

### 200 ASSORTED

1/4 WATT RESISTORS  
Bent leads, carbon comp. and carbon film.  
CAT# GRES \$1.00 per assortment

### 200 ASSORTED

1/2 WATT RESISTORS  
Bent leads, carbon comp. and carbon film.  
CAT# GRABRC \$1.00 per assortment

### 50 ASSORTED

DISC CAPACITORS  
Most are cut (p.c. leads). Some to 500 volts  
CAT# GRABDC \$1.00 per assortment

### 15 VALUES OF

ELECTROLYTICS  
Contains both axial and radial styles from 1 mfd.  
CAT# GRABCP \$1.00 per assortment

## LED'S

STANDARD JUMBO

DIFFUSED T-1 3/4 size

RED CAT# LED-1

10 for \$1.50 • 100 for \$13.00

GREEN CAT# LED-2

10 for \$2.00 • 100 for \$17.00

YELLOW CAT# LED-3

10 for \$2.00 • 100 for \$17.00

### FLASHING LED

with built in flashing circuit

operates on 5 volts...

RED \$1.00 each

CAT# LED-4 10 for \$9.50

GREEN \$1.00 each

CAT# LED-4G 10 for \$9.50

### BI-POLAR LED

Lights RED one direction,

GREEN the other. Two leads.

CAT# LED-6 2 for \$1.70

### LED HOLDER

Two piece holder.

CAT# HLED 10 for 65¢

## RELAYS

### 12 VOLT D.C. COIL S.P.D.T.

Omron# G2E-184P 4 Amp contacts

335 ohm coil.

Sugar cube size.

.61" X .42" X .44" high.

P.C. mount with pins on DIP spacing.

CAT# RLY-787 \$1.50 each



### 5-6 VDC SIP REED RELAY

Electrol

"Blue Boy" #

BBS1A05A10

5-6 Vdc, 500 ohm coil.

S.P.S.T. normally open reed relay.

0.5 amp contacts. SIP configuration.

1" X .375" X .3".

CAT# RRLY-SIP5

\$1.10 each • 10 for \$10.00



## 10 AMP SOLID STATE RELAY

ELECTROL# S2181

CONTROL:

Rated 5.5 to 10 Vdc

(will operate on 3-32 Vdc).

LOAD: 10 amp @ 240 Vac

2 1/4" X 1 3/4" X 7/8"

CAT# SSRLY-10B \$9.50 each

QUANTITY DISCOUNT

10 for \$85.00 • 25 for \$175.00

50 for \$300.00 • 100 for \$500.00



## XENON TUBE

1" long flashtube prepped with

3 1/2" red and black leads. Ideal for

electronic flash or strobe projects.

CAT# FLT-3 2 for \$1.00



## PHOTO FLASH CAPACITOR

Rubycon# FKX


200 mfd, 330 volts.

0.79" diameter X 1.11" high

Solder loop terminals.

CAT# PPC-200 \$3.25 each

10 for \$30.00 • 100 for \$275.00

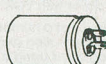

## 22/44 PIN CONNECTOR



.156" pin spacing, 0.200" between double  
rows, gold contacts, P.C. mounting.

SPECIAL Same as AMP# 2-530655-6.

CAT# EBC-1G \$1.00 each • 10 for \$8.00

## 0-30 MINUTE AUTO-SHUTOFF TIMER

Sankey Seiko Mfg.# TMCF35MYB9

120 Vac 60 Hz. 10 amp contacts.

UL rated. Turn shaft to turn on

lights or other electrical devices.

Bell rings and circuit breaks after specified amount

of time. Ideal for any device that needs to shut off

automatically. 2.92" X 1.9" X 2.54" behind face

plate. 1/4" half-round shaft.

CAT# TMC-30 \$3.00 each



## LED CHASER KIT

Build this variable

speed led chaser.

10 leds flash

sequentially

at whatever

speed you set

them for. Easy to build kit includes pc board, parts

and instructions. Operates on 3 to 9 volts. PC

board is 5" X 2.25". A great one hour project.

CAT# AEC \$6.50 each



## 1/4 WATT RESISTOR KIT

Ideal for the workshop, this

1/4 watt resistor kit contains 10

pieces each of 42 of the most

popular values (420 pieces to

total). Includes a divided box and

a parts locator.

VALUES in this kit are:

1 ohm, 10 ohm, 39 ohm,

47 ohm, 51 ohm, 68 ohm, 100 ohm, 130 ohm,

150 ohm, 180 ohm, 220 ohm, 330 ohm, 470 ohm,

560 ohm, 680 ohm, 1K, 1.2K, 1.5K, 2K, 2.2K, 2.7K,


3K, 4.7K, 5.1K, 5.6K, 10K, 15K, 22K, 30K, 33K, 39K,

47K, 56K, 68K, 100K, 120K, 150K, 220K, 470K,

1 MEG, 5.1 MEG, 10 MEG

The resistors alone would sell for \$21.00.

Complete kit • CAT# REKIT-14 \$17.00

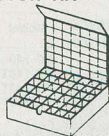

## PIEZO WARNING DEVICE



Murata Erie # PKB9-4A0

High pitched audible alarm. Operates on 3 - 20 Vdc @ 20 ma. 1"

high x 7/8" dia. P.C. board mount.

CAT# PBZ-84 \$1.75 each

## NICKEL-CAD BATTERIES (RECHARGEABLE)

SPECIAL!! AAA SIZE

Panasonic# P-18AAA

1.2 volt @ 180 Mah

CAT# NCB-AAAX \$1.50 each

10 for \$13.50 • 100 for \$125.00



AA SIZE \$2.00 each

1.25 volts 500 mAh

CAT# NCB-AA

AA SIZE \$2.20 each

WITH SOLDER TABS

CAT# NCB-SAA

C SIZE \$4.25 EACH

1.2 volts 1200 mAh

CAT# NCB-C

D SIZE \$4.50 each

1.2 volts 1200 mAh

CAT# NCB-D



## TRANSISTORS

ORDER BY PART #

PN2222 NPN

TO-92 5 for 75¢

PN2907 PNP

TO-92 5 for 75¢

2N3055 NPN

TO-3 \$1.00 each

MJ2955 PNP

TO-3 \$1.50 each

MJE2955T PNP

TO-220 75¢ each

MJE3055T NPN

TO-220 75¢ each

TIP31 NPN

TO-220 75¢ each

TIP32 PNP

TO-220 75¢ each

TIP121 NPN

TO-220 75¢ each

TIP126 PNP

TO-220 75¢ each

## TIL-99 PHOTO TRANSISTOR

TO-18 case with window. For wide-angle viewing

applications. Spectrally and mechanically compat-

ible with TIL-31B. CAT# TIL-99

\$1.00 each • 10 for \$9.00



## TIL-31B PHOTO DIODE

TO-18 case with window. Infrared emitting photo

diode. CAT# TIL-31B \$1.00 ea. • 10 for \$9.50

LARGE QUANTITY AVAILABLE

## N-CHANNEL MOSFET

IRF-511 TO-220 case

CAT# IRF 511

\$1.00 each • 10 for \$9.00



## L.E.D. FLASHER KIT

Two L.E.D.'s flash in

unison when a 9 volt

battery is attached.

This kit includes a

p.c. board, all the

parts and instructions to make a simple flasher cir-

cuit. A quick and easy project for anyone with basic

soldering skills. CAT# LEDKIT \$1.75 per kit



## TELEPHONE COUPLING TRANSFORMER

Multi Products International# A19N-HO-1D/1


Primary 600 ohm

Secondary: 600/600 ohm

.77" X .61" X .63" high.

6 p.c. pins on



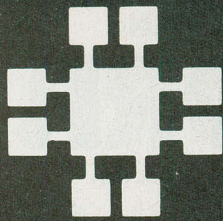

# JDR Microdevices®

**MMC**  
MICROCOMPUTER  
MARKETING COUNCIL  
of the Direct Marketing Association, Inc.

30 DAY MONEY BACK GUARANTEE • 1 YEAR WARRANTY ON ALL PRODUCTS • TOLL-FREE TECHNICAL SUPPORT

## DYNAMIC RAMS

PART#	SIZE	SPEED	PINS	PRICE
4164-150	65536x1	150ns	16	2.49
4164-120	65536x1	120ns	16	2.89
4164-100	65536x1	100ns	16	3.39
TMS4464-15	65536x4	150ns	16	3.59
TMS4464-12	65536x4	120ns	16	3.95
TMS4464-10	65536x4	100ns	16	4.95
41256-150	262144x1	150ns	16	2.59
41256-120	262144x1	120ns	16	2.95
41256-100	262144x1	100ns	16	3.15
41256-80	262144x1	80ns	16	3.75
41256-60	262144x1	60ns	16	5.25
414256-100	262144x4	100ns	20	12.95
414256-80	262144x4	80ns	20	13.45
1 MB-120	1048576x1	120ns	18	11.95
1 MB-100	1048576x1	100ns	18	12.35
1 MB-80	1048576x1	80ns	18	12.95

## SIMM/SIP MODULES

PART#	SIZE	SPEED	TYPE	PRICE
41256A9B-12	256K x 9	120ns	SIMM/PC	36.95
41256A9B-80	256K x 9	80ns	SIMM/PC	49.95
421000A9B-10	1MB x 8	100ns	SIMM/MAC	109.95
421000A9B-10	1MB x 9	100ns	SIMM/PC	113.95
421000A9B-80	1MB x 9	80ns	SIMM/PC	119.95
256KX9SIP-80	256K x 9	80ns	SIP/PC	54.95
256KX9SIP-60	256K x 9	60ns	SIP/PC	64.95
1MBX9SIP-80	1MB x 9	80ns	SIP/PC	124.95

## STATIC RAMS

PART#	SIZE	SPEED	PINS	PRICE
HM6116LP-2	2048x8	120ns	24	5.49
HM6264LP-15	8192x8	150ns	28	4.95
HM6264LP-12	8192x8	120ns	28	6.49
HM43256LP-12	32768x8	120ns	28	14.95
HM43256LP-10	32768x8	100ns	28	15.95

## MATH COPROCESSORS

## 8-BIT COPROCESSORS

8087	5 MHz	89.95
8087-2	8 MHz	129.95
8087-1	10 MHz	169.95

## 16-BIT COPROCESSORS

80287	6 MHz	139.95
80287-8	8 MHz	209.95
80287-10	10 MHz	239.95
80C287	12 MHz	299.95

## 32-BIT COPROCESSORS

80387-16	16 MHz	359.95
80387-SX	16 MHz	319.95
80387-20	20 MHz	399.95
80387-25	25 MHz	499.95
80387-33	33MHz	649.95

A photograph showing an Intel 80387 coprocessor chip and its retail box. The box is white with the Intel logo and text that reads "Coprocessor 387 32-bit floating point". The chip is a small, square integrated circuit with pins. The background is dark and out of focus.

Intel Inside

INTEL CORPORATION

2000 N. BURNING BUSH BLVD. SANTA CLARA, CA 95051

TEL: (415) 354-2200 FAX: (415) 354-2201

© 1989 INTEL CORPORATION. ALL RIGHTS RESERVED.

INTEL, THE INTEL LOGO, AND "INTEL INSIDE" ARE REGISTERED TRADEMARKS OF INTEL CORPORATION.

80387, 80287, 8087, AND COPROCESSOR 387 ARE REGISTERED TRADEMARKS OF INTEL CORPORATION.

80387-SX, 80387-20, 80387-25, 80387-33, AND 80C287 ARE TRADEMARKS OF INTEL CORPORATION.

8087-1, 8087-2, AND 80C287 ARE TRADEMARKS OF INTEL CORPORATION.

8087 IS A TRADEMARK OF INTEL CORPORATION.

80287 IS A TRADEMARK OF INTEL CORPORATION.

8087 IS A TRADEMARK OF INTEL CORPORATION.

80387 IS A TRADEMARK OF INTEL CORPORATION.

80287 IS A TRADEMARK OF INTEL CORPORATION.

8087 IS A TRADEMARK OF INTEL CORPORATION.

80387 IS A TRADEMARK OF INTEL CORPORATION.

80287 IS A TRADEMARK OF INTEL CORPORATION.

8087 IS A TRADEMARK OF INTEL CORPORATION.

80387 IS A TRADEMARK OF INTEL CORPORATION.

80287 IS A TRADEMARK OF INTEL CORPORATION.

8087 IS A TRADEMARK OF INTEL CORPORATION.

80387 IS A TRADEMARK OF INTEL CORPORATION.

80287 IS A TRADEMARK OF INTEL CORPORATION.

INCLUDES MANUAL  
& SOFTWARE GUIDE

## 74 SERIES LOGIC

7400	.19	74LS32	.18	74LS245	.79
74LS00	.16	74LS73	.29	74LS273	.79
74LS02	.17	7474	.33	74LS288	1.69
7404	.19	74LS74	.24	74LS322	3.95
74LS04	.16	74S74	.49	74LS367	.39
74S04	.29	74LS138	.39	74LS373	.79
7406	.29	74LS155	.59	74LS374	.79
7408	.24	74LS163	.39	74LS393	.79
74LS08	.18	74LS240	.69	74LS682	3.20
7432	.29	74LS244	.69	74LS688	2.40

## C.P.U.'s

8000	
8052AH	
BASIC	34.95
8088	5.99
8250	6.95
8251A	1.69
8253-5	1.95
8254	9.95
8255-5	2.49
8741	9.95
8748	7.95
8749	9.95
8755	14.95
6500	
65C02*	7.95
6522	2.95
V-20	
V20	6.95
V20-8	8.95
V20-10	11.95
V30	13.95

## MISC

DAC0800	3.29
1793	9.95
COM8116	8.95
MC146818	5.95
MM58167	9.95
INS8250	6.95
NS16450	10.95
LM317T	.69
NE555	.29
LM741	.29
7805T	.49
7812T	.49
75150	1.95
75154	1.95
14411	9.95

## PALS

16L8	2.95
16R4	2.95
16R6	2.95
16R8	2.95
20L8	4.95
20R4A	4.95
20R6	4.95
20R8	4.95
20X8	4.95

## PAL KIT

AN ENTRY-LEVEL  
COMPLETE PAL  
DEVELOPMENT  
KIT FROM CUPL.  
FULL SUPPORT  
FOR 16L8, 16R4,  
16R6, 16R8, 20L8,  
20R4, 20R6, 20R8,  
AND 20X8.  
MOD-MPL-SOFT  
\$99.95

## CRYSTAL OSCILLATORS

1.0MHz	5.95
1.8432	5.95
20.0	4.95
24.0	4.95

## Derick's HIGH-TECH SPOTLIGHT



Call our BBS: (408) 559-0253 for more info in SIG file "Hitech"

I stopped recommending CGA display systems to my friends about 4 years ago. Then, the cost per pixel was lower for CGA than EGA, and my suggestion was frequently ignored. Now, however, VGA has a lower cost per pixel than either CGA or EGA. In fact, expect to get about 60% more resolution for your dollar with VGA as compared to CGA.

This isn't just a numbers game. Operator comfort and display presentation are the real key issues. With more and more programs using a GUI (graphical user interface), the need for high resolution color increases.

Reading text on a CGA display is not particularly easy for any length of time. The lines seem to run together and during scrolling the first few lines on the screen flicker.

With VGA, and to some extent EGA, those complaints disappear. They are replaced with comments about the smooth line edges, realistic shading, rapid screen updates, and lifelike colors. In 256 color mode, from a palette of 256 thousand colors, the ability of a VGA display to render near photographic images must be seen to be appreciated.

If the move to full color VGA isn't in your pocketbook, please let me suggest a monochrome VGA system as an alternate choice. With 16 or 64 levels of gray scale, it is particularly useful for desktop publishing where your printer doesn't do color anyway.

Derick Moore, Director of Engineering

## EPROMS

PART#	SIZE	SPEED	Vpp	PINS	PRICE
2716-1	2048x8	350ns	25V	24	3.95
2732A	4096x8	250ns	21V	24	3.95
2764	8192x8	450ns	12.5V	28	3.49
2764-250	8192x8	250ns	12.5V	28	3.69
2764-200	8192x8	200ns	12.5V	28	4.25
27C64	8192x8	250ns	12.5V	28	4.95
27128	16384x8	250ns	12.5V	28	4.25
27128A-200	16384x8	200ns	12.5V	28	5.95
27256	32768x8	250ns	12.5V	28	4.95
27256-200	32768x8	200ns	12.5V	28	5.95
27C256	32768x8	250ns	12.5V	28	5.95
27512	65536x8	250ns	12.5V	28	7.95
27C512	65536x8	250ns	12.5V	28	8.95
27C101-20	131072x8	200ns	12.5V	32	24.95

## EPROM ERASERS

DATASE II \$39.95

- SHIRT POCKET SIZE!
- ALL SIZES UP TO 4 AT A TIME
- ERASES MOST EPROMS IN 3 MINUTES

DATASE II

SPECTRONICS  
CORPORATION

Model	Timer	# of Chips	Intensity (uW/Cm²)	Unit Cost
PE-140	NO	9	8,000	\$89.95
PE-140T	YES	9	8,000	\$139.95
PE-240T	YES	12	9,600	\$189.95
PL-265T	YES	30	9,600	\$255.95

## POWER SUPPLIES

### 135 WATT

- XT-COMPATIBLE • UL APPROVED • 110-220V SWITCH
- +5V @ 15A, +12V @ 7A, -5V @ .5A, -12V @ .5A

PS-135 ..... \$59.95

PS-150 150W SUPPLY ..... \$69.95

PS-200X 200W SUPPLY ..... \$89.95

### 200 WATT

- AT-COMPATIBLE • UL APPROVED • 110-220V SWITCH
- +5V @ 20A, +12V @ 7A, -5V @ .5A, -12V @ .5A

PS-200 ..... \$89.95

PS-250 250W SUPPLY ..... \$129.95

## PROTOTYPE CARDS

FR-4 EPOXY GLASS LAMINATE WITH GOLD PLATED  
EDGE CARD FINGERS AND SILK SCREENED LEGENDS



### FOR XT

JDR-PR1	WITH +5V AND GROUND PLANE	27.95
JDR-PR2	ABOVE WITH I/O DECODING LAYOUT	29.95
JDR-PR2-PK	PARTS KIT FOR JDR-PR2 ABOVE	8.95

### FOR AT

JDR-PR10	BIT WITH I/O DECODING LAYOUT	34.95
JDR-PR10-PK	PARTS KIT FOR JDR-PR10 ABOVE	12.95

### FOR PS/2

JDR-PR32	32 BIT PROTOTYPE CARD	69.95
JDR-PR16	16 BIT WITH I/O DECODING LAYOUT	49.95
JDR-PR16-PK	PARTS KIT FOR JDR-PR16 ABOVE	15.95
JDR-PR16V	16 BIT FOR VIDEO APPLICATIONS	39.95

### EXTENDER CARDS

SIMPLIFY PROTOTYPING AND TESTING

EXT-8088	8-BIT FOR 8088 MOTHERBOARDS	29.95
EXT-80286	16-BIT FOR 286/386 MOTHERBOARDS	39.95
EXT-16	MICROCHANNEL 16-BIT	69.95
EXT-32	MICROCHANNEL 32-BIT	99.95

## PC BREADBOARD-ON-A-CARD



- 62 BUS LINES
- USE UP TO 24 14-PIN ICs
- 1940 TIE POINTS
- DB25 D-SUB CONNECT.
- PDS-604 ..... \$49.95

## SOLDER STATION



- UL APPROVED
- ADJUSTABLE HEAT SETTING
- TIP TEMPERATURE READOUT
- REPLACEMENT TIPS @ \$2.95
- 168-3C ..... \$59.95

## IC SOCKETS/DIP CONNECTORS

SOLDERTAIL	WIREWRAP	ZIF SOCKETS
8 PIN ST .11	8 PIN WW .59	ZIF-14 5.95
14 PIN ST .11	14 PIN WW .69	ZIF-16 5.95
16 PIN ST .12	16 PIN WW .69	ZIF-20 6.95
18 PIN ST .15	18 PIN WW .99	ZIF-24 7.95
20 PIN ST .18	20 PIN WW 1.09	ZIF-28 7.95
24 PIN ST .20	24 PIN WW 1.49	ZIF-40 10.95
28 PIN ST .22	28 PIN WW 1.69	
40 PIN ST .30	40 PIN WW 1.99	

VOLUME  
DISCOUNTS  
CALL!

## SOLDER-CUP D-SUBS

MALE	FEMALE	IDC'S
DB09P .45	DB09S .49	IDE20 .55
DB15P .59	DB15S .69	IDE34 .89
HDB15P 1.49	HDB15S 1.59	IDS20 .65
DB19P .69	DB19S .75	IDS34 .75
DB25P .69	DB25S .75	IDB09P 1.39
DB37P 1.35	DB37S 1.39	IDB09S 1.45
DB50P 1.85	DB50S 2.29	IDB25P 2.25
		IDB25S 2.35

## CABLES AND GENDER CHANGERS

MOLDED; GOLD-PLATED CONTACTS; 100% SHIELDED

CBL-PRNTR	6 FT. PC PRINTER CABLE	9.95
CBL-PRNTR-25	25 FT. PC PRINTER CABLE	15.95
CBL-PRNTR-RA	RIGHT ANGLE PRINTER CABLE	15.95
CBL-DB25-MM	DB25 MALE-DB25 MALE 6 FT.	9.95
CBL-DB25-MF	DB25 FEMALE-DB25 MALE 6 FT.	9.95
CBL-9-SERIAL	9-PIN SERIAL CABLE	7.95
CBL-KBD-EXT	5 FT. KEYBOARD EXTENSION	7.95
CBL-CNT-MM	36-PIN CENTRONICS-MM	14.95
CBL-FDC-EXT	37-PIN EXT. FLOPPY CABLE	9.95
CBL-MNT-9	9-PIN MONITOR EXTENSION	6.95
CBL-MNT-15	15-PIN MONITOR EXTENSION CABLE	9.95
CBL-MODEM	MODEM-DB25-DB25 FEMALE	6.95
GENDER-VGA	DB9-DB15 ADAPTOR	4.95
GENDER-9-25	DB9-DB25 SERIAL ADAPTOR	4.95

**PARTIAL LISTINGS ONLY—CALL FOR FREE 100-PG CATALOG!**

COPYRIGHT 1989 JDR MICRODEVICES

JDR MICRODEVICES AND THE JDR MICRODEVICES LOGO ARE REGISTERED TRADEMARKS OF JDR MICRODEVICES. IBM, AT, PS/2 ARE TRADEMARKS OF INTERNATIONAL BUSINESS MACHINES.


CIRCLE 113 ON FREE INFORMATION CARD  
DEALERS CIRCLE 170 ON FREE INFORMATION CARD



## 4800/2400 BAUD FAX/DATA MODEM \$119<sup>95</sup>

- FAX TRANSMISSION ONLY
- 4800 BAUD FAX CAPABILITY TO ANY GROUP III FAX
- 2400 BAUD V.22BIX DATA MODEM
- XT/AT COMPATIBLE HALF CARD
- MENU-DRIVEN SOFTWARE
- MULTIPLE FAX TRANSMISSIONS TO GROUPED ADDRESSES

MCT-FAXM

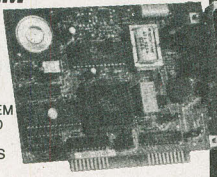


## 2400 BAUD MODEM \$89<sup>95</sup>

- 2400/1200/300 BAUD
- FULL Hayes COMPATIBILITY
- CONFIGURE AS COM1, COM2, COM3 OR COM4
- BUILT-IN SPEAKER • AUTO WAIT-FOR-DIAL TONE AND AUTO-REDIAL • PROCOMM COMMUNICATIONS SOFTWARE • MADE IN THE USA

MCT-241

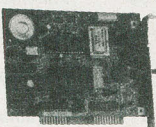
MCT-121 1200 BAUD INTERNAL MODEM ..... \$59.95



## MINI UPRIGHT CASE \$199<sup>95</sup>

- SMALL FOOTPRINT MINI-UPRIGHT FOR 8088 OR MINI 286/386 MOTHERBOARDS
- ROOM FOR 6 EXPANSION CARDS
- HOLDS 3 5-1/4" & 1 3-1/2" DRIVES (1/2 HT)
- 200 WATT POWER SUPPLY
- 2-DIGIT LED SPEED DISPLAY
- 12" H X 16" L X 8" W

CASE-120

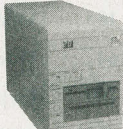

## UPRIGHT CASE \$249<sup>95</sup>

- SPACE SAVING DESIGN HOLDS ALL SIZES OF MOTHERBOARDS AND INCLUDES: • 250W POWER SUPPLY
- MOUNTS FOR 3 FLOPPY & 4 HARD DRIVES
- TURBO & RESET SWITCH • LED SPEED DISPLAY • POWER & DISK LED'S
- ALL HARDWARE, FACEPLATES & SPEAKER

CASE-100

- CASE-FLIP FOR 8088 MB'S ..... \$39.95
- CASE-SLIDE FOR 8088 MB'S ..... \$39.95
- CASE-70 FOR 286 MB'S ..... \$89.95
- CASE-50 FOR MINI 286 MB'S ..... \$59.95
- CASE-JR MINI-286 W/150W PS \$149.95




## MODULAR PROGRAMMING SYSTEM

MODULES USE A COMMON HOST ADAPTOR CARD-- 1 SLOT PROGRAMS EPROMS, PROMS, PALS, MORE!
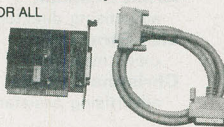
### HOST ADAPTOR CARD \$29.95

- UNIVERSAL INTERFACE FOR ALL PROGRAMMING MODULES!
- SELECTABLE ADDRESSES PREVENTS CONFLICTS
- MOLDED CABLE
- MOD-MAC



### UNIVERSAL MODULE \$499.95

- PROGRAMS EPROMS, EEPROMS, PALS, BI-POLAR PROMS, 8748 & 8751 SERIES DEVICES; 16V8 AND 20V8 GAL'S (GENERIC ARRAY LOGIC) FROM LATTICE, NS, SGS • TESTS TTL CMOS, DYNAMIC & STATIC RAMS • LOAD DISK, SAVE, DISK, EDIT, BLANK CHECK, PROGRAM, AUTO, READ MASTER, VERIFY AND COMPARE • TEXT TOOL SOCKET FOR 3" - 6" W. IC'S (8-40 PINS)

MOD-MUP

### EPROM MODULE \$119.95

- PROGRAMS 24-32 PIN EPROMS, CMOS EPROMS & EEPROMS FROM 16K TO 1024K • HEX TO OBJ CONVERTER • AUTO, BLANK CHECK/PROGRAM/VERIFY • VPP 5, 12.5, 12.75, 13, 21 & 25 VOLTS • NORMAL, INTELLIGENT, INTERACTIVE & QUICK PULSE PROGRAMMING ALGORITHMS

MOD-MEP

- MOD-MEP-4 4-EPROM PROGRAMMER ..... \$169.95
- MOD-MEP-8 8-EPROM PROGRAMMER ..... \$259.95
- MOD-MEP-16 16-EPROM PROGRAMMER ..... \$499.95

### OTHER MODULES

- MOD-MPL PAL MODULE ..... \$249.95
- MOD-MIC DIGITAL TESTER MODULE ..... \$129.95
- MOD-MBP BI-POLAR PROGRAMMING MODULE ..... \$259.95
- MOD-MMP MICROPROCESSOR PROG. MODULE ..... \$179.95
- MOD-MPL-SOFT CUPL SOFTWARE ..... \$99.95

## VGA COMPATIBLE PACKAGE

\$499<sup>95</sup>

- 720 X 540 MAX RESOLUTION, 640 X 480 IN 16 COLORS, 528 X 480 RESOLUTION IN 256 COLORS • IBM STYLE MONITOR
- VGA, EGA, CGA, AND MGA COMPATIBLE

VGA-PKG (INCLUDES VGA CARD AND MONITOR)

### VGA MONITOR \$359.95

- 14" ANALOG VGA • GLARE RESISTANT SCREEN • 720 X 480 TILT/SWIVEL BASE • FRONT MOUNTED POWER SWITCH


### RELISYS MULTISYNCH \$429.95

- FULL FEATURED MULTISCAN MONITOR WITH UNLIMITED COLORS • 1024 X 768 RESOLUTION, 14" NON-GLARE DISPLAY
- AUTO SWITCHING • TTL/ANALOG VIDEO INPUT

JDR-MULTI

EGA SPECIAL! CARD & MONITOR--JUST \$479

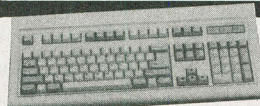- EGA-MONITOR 14" RGB MONITOR ..... \$339.95
- NEC-MULTI-3D DIGITAL 1024X768 RESOLUTION ..... \$649.95
- JDR-MONO 12" TTL MONOCHROME- GREEN ..... \$69.95
- JDR-AMBER 12" TTL MONOCHROME-AMBER ..... \$69.95



### STANDARD KEYBOARDS:

- BTC-5060 AUTONSENSE FOR XT/AT ..... \$59.95
- MAX-5060 WITH TACTILE FEEDBACK ..... \$64.95

### ENHANCED KEYBOARDS:

- BTC-5339 AUTONSENSE FOR XT/ AT, AUTOREPEAT .. \$69.95
- K103-A AUDIBLE "CLICK" STYLE ..... \$84.95
- MAX-5339 MAXI-SWITCH W/TACTILE FEEDBACK ..... \$84.95

## QUALITY KEYBOARDS

## MODULAR CIRCUIT TECHNOLOGY

### DRIVE CONTROLLERS:

- MCT-FDC FLOPPY DISK CONTROLLER ..... \$29.95
- MCT-FDC-HD 1.44MB FLOPPY CONTROLLER ..... \$49.95
- MCT-HDC HARD DISK CONTROLLER ..... \$79.95
- MCT-RLL RLL CONTROLLER ..... \$89.95
- MCT-FH FLOPPY/HARD CONTROLLER ..... \$139.95
- MCT-AFH 286/386 FLOPPY/HARD ..... \$149.95
- MCT-AFH-RLL 286/386 RLL CONTROLLER ..... \$199.95

### DISPLAY ADAPTOR CARDS:

- MCT-MGP MONOCHROME GRAPHICS ..... \$49.95
- MCT-CG COLOR GRAPHICS ADAPTOR ..... \$44.95
- MCT-EGA ENHANCED GRAPHICS ADAPTOR ..... \$149.95
- MCT-VGA-8 8-BIT VGA, ANALOG OUTPUT ..... \$169.95
- MCT-VGA-16 16-BIT VGA, ANALOG OUTPUT ..... \$199.95
- MCT-MGMO MONOGRAPHS MULTI I/O ..... \$119.75
- MCT-MGAIO 286/386 MONOGRAPHS I/O ..... \$99.95

### MULTIFUNCTION CARDS:

- MCT-MIO MULTI I/O FLOPPY CONTROLLER ..... \$79.95
- MCT-IO MULTI I/O CARD ..... \$59.95
- MCT-AMF 286/386 MULTIFUNCTION ..... \$139.95
- MCT-AIO 286/386 MULTI I/O CARD ..... \$59.95


### MEMORY CARDS:

- MCT-RAM 576K RAM CARD ..... \$49.95
- MCT-EMS EXPANDED MEMORY CARD ..... \$99.95
- MCT-AEMS 286/386 EMS CARD ..... \$129.95

## GeniScan 400 DPI \$199<sup>95</sup>

- UP TO 400 DPI • 32 LEVELS OF GRAY SCALE • SPEED OVERRUN WARNING LIGHT
- INCLUDES SCANNED IT AND DR. GENIUS SOFTWARE


GS-4500

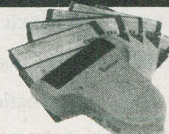

## EPROM PROGRAMMER \$129.95

- PROGRAMS 27XX AND 27XXX EPROMS UP TO 27512
- SUPPORTS VARIOUS PROGRAMMING FORMATS & VOLTAGES
- SPLIT OR COMBINE CONTENTS OF SEVERAL EPROMS OF DIFFERENT SIZES
- READ, WRITE, COPY, BLANK CHECK & VERIFY
- SOFTWARE FOR HEX AND INTEL HEX FORMATS

MOD-EPROM

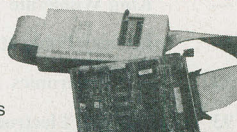

## HARD DISKS KITS

- 21.4 MB \$199 21.4 MB \$249
- 32.7 MB \$219 32.1 MB \$279
- 42.8 MB \$339
- 65.5 MB \$389
- 80.2 MB \$569




SIZE	MODEL	AVG. SPEED	FORM DRIVE	ONLY KIT	XT KIT	AT F/H KIT
21.4MB	ST-225	65 MS	5-1/4"	\$199	\$249	\$309
32.7MB RLL	ST-238	65 MS	5-1/4"	\$219	\$279	\$379
42.8MB	ST-251-1	28 MS	5-1/4"	\$339	\$389	\$449
65.5MB RLL	ST-277-1	28 MS	5-1/4"	\$389	\$449	\$549
80.2MB	ST-4096	28 MS	5-1/4"	\$569	—	\$679
122.7MB RLL	ST-4144A	28 MS	5-1/4"	\$699	\$759	\$859
21.4MB	ST-125	40 MS	3-1/2"	\$259	\$299	\$373
32.1MB RLL	ST-138	40 MS	3-1/2"	\$289	\$339	\$429

## 157.5MB ESDI DRIVE KIT \$1049<sup>95</sup>

- 5-1/4" HARD DISK, FLOPPY/HARD CONTROLLER, CABLES, MOUNTING HARDWARE & SOFTWARE. 1355-PKG
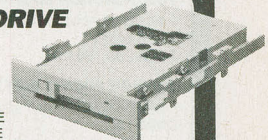
## 1.44MB 3-1/2" DRIVE \$99<sup>95</sup>

- ULTRA HIGH DENSITY
- READ/WRITE 720K DISKS, TOO
- FDD-1.44X BLACK FACEPLATE
- FDD-1.44A BEIGE FACEPLATE
- FDD-1.44 SOFT SOFTWARE DRIVER \$19.95



### 1/2 HEIGHT FLOPPY DISK DRIVES:

- FD-55B 5-1/4" TEAC DS/DD 360K ..... \$99.95
- FD-55G 5-1/4" TEAC DS/HD 1.2M ..... \$129.95
- FDD-360 5-1/4" DS/DD 360K ..... \$69.95
- FDD-1.2 5-1/4" DS/HD 1.2M ..... \$95.95

## MOTHERBOARDS

### 20MHZ 386 \$629<sup>95</sup> UPGRADE!

- 16/20 MHZ
- 16 MB RAM CAPACITY - 8MB ON BOARD(OK), 8 MB RAM CARD
- USES 256K OR 1MB SIP RAMS
- 8 SLOTS: 1X32-BIT RAM 2X 8-BIT & 5X 16-BIT
- MEMORY INTERLEAVING
- AMI BIOS • XT-SIZE BOARD



- MCT-M386-20 25MHZ MINI 386 W/CACHE ..... \$1199.00
- MCT-C386-25 8MB RAM CARD (OK) ..... \$99.95
- MCT-M386-M4 10/20MHZ 386 ..... \$799.00
- MCT-386MB20 10/25MHZ 386 ..... \$999.00

### 10MHZ MINI-286 \$189<sup>95</sup>

- AT COMPATIBLE • KEYBOARD SELECTABLE 6/10MHZ
- EXPANDABLE TO 4MB ON-BOARD WITH 1MB DRAMS (OK)
- SIX 16-BIT, TWO 8-BIT SLOTS • AMI BIOS • LED SUPPORT

- MCT-M286-10 8/12MHZ MINI-286 ..... \$199.95
- MCT-M286-12 8/16MHZ 286 ..... \$289.95
- MCT-M286-16N 10/20MHZ 286 ..... \$389.95
- MCT-M286-20N STANDARD 4.77MHZ 8088 ..... \$87.95
- MCT-XMB 4.77/8MHZ 8088 ..... \$89.95
- MCT-TURBO 4.77/10MHZ SINGLE CHIP 8088 ..... \$99.95

## LOGITECH MICE

- THREE-BUTTON SERIES 9
- LOGITECH • 320 DPI RESOLUTION
- SERIAL PS/2 COMPATIBLE.

- LOGC9 SERIAL MOUSE ..... \$98.95
- LOGC9-C SERIAL (NOT PS/2 COMPATIBLE) ..... \$79.95
- LOGC9-PC SERIAL MOUSE WITH PAINTSHOW ..... \$109.95
- LOGC9-PC SERIAL MOUSE WITH PAINT/CAD ..... \$154.95
- LOGB9 BUS MOUSE ..... \$89.95
- LOGB9-PC BUS MOUSE WITH PAINTSHOW ..... \$104.95
- LOGB9-PC BUS MOUSE WITH PAINT/CAD ..... \$149.95



JDR MICRODEVICES, 2233 BRANHAM LANE, SAN JOSE 95124  
LOCAL (408) 559-1200 FAX (408) 559-0250 TELEX 171-110

RETAIL STORE: 1256 S. BASCOM AVE., SAN JOSE, CA  
(408) 947-8881 HOURS: M-F 9-7 SAT. 9-5 SUN. 12-4


# ORDER TOLL FREE 800-538-5000

CUSTOMER SERVICE TOLL-FREE 800-538-5001 • TECHNICAL SUPPORT TOLL-FREE 800-538-5002

CIRCLE 113 ON FREE INFORMATION CARD  
DEALERS CIRCLE 170 ON FREE INFORMATION CARD


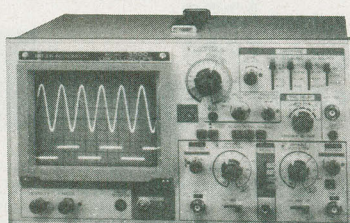
## VALUE-PRICED TEST EQUIPMENT ALL WITH A 2 YEAR WARRANTY!



**35 MHZ DUAL TRACE OSCILLOSCOPE** **\$499.95**  
• WIDE BAND WIDTH • VARIABLE HOLDOFF  
MODEL-3500 (SHOWN)

**20 MHZ DUAL TRACE OSCILLOSCOPE** **\$389.95**  
• TV SYNC FILTER • COMPONENTS TESTER  
MODEL 2000

**THE ULTIMATE 3.5 DIGIT DMM** **\$79.95**  
• BASIC DC ACCURACY  $\pm 0.25\%$   
• 34 RANGES  
• TEMP, TRANSISTOR & RESISTANCE FEATURES  
DMM-300 (SHOWN)



**3.5 DIGIT FULL FUNCTION DMM** **\$49.95**  
• BASIC DC ACCURACY  $\pm 0.25\%$   
• 22 RANGES  
DMM-200 \$49.95

**3.5 DIGIT POCKET SIZE DMM** **\$29.95**  
• BASIC DC ACCURACY  $\pm 0.5\%$  • 14 RANGES  
DMM-100

**3.5 DIGIT PROBE TYPE DMM** **\$54.95**  
• AUTORANGING  
• AC/DC 2V - 500V  
• RESISTANCE: 2K-2M  
DPM-1000 (SHOWN)



**HIGH/LOW LOGIC PROBE** **\$17.95**  
• DETECTS TTL/CMOS LOGIC STATES  
• MEMORY FUNCTION FREEZES DATA FOR LATER USE  
LP-2800

**PULSER PROBE FOR QUICK DEBUGGING** **\$19.95**  
• INJECTS PULSE INTO TEST CIRCUIT-VARIABLE WIDTH  
• TTL, DTL, TRL, HTL, HINIL, MOS, & CMOS COMPATIBLE  
LP-540



Jim Wharton  
JDR's VP Sales

## JIM'S BARGAIN HUNTERS CORNER

**REFURBISHED FULL SIZE AT MOTHERBOARD** **\$99.95**

WAS \$299.95

SAVE 66% OFF THE ORIGINAL PRICE OF THIS FACTORY REFURBISHED 8MHZ AT-COMPATIBLE MOTHERBOARD!

- 6/8MHZ KEYBOARD SELECTABLE SPEEDS
- 256K TO 1MB ON-BOARD RAM CAPACITY (OK INSTALLED)
- 8 EXPANSION SLOTS (SIX 16-BIT & TWO 8-BIT)
- BATTERY BACKED CLOCK/CALENDAR
- SET-UP ROUTINES BUILT IN TO BIOS
- JUMPER FOR RESET SWITCH, SPEED INDICATORS AND KEYLOCK

R/MCT-286

EXPIRES 2/15/90



**JDR Microdevices**  
• 2233 BRANHAM LANE, SAN JOSE, CA 95124

**ORDER TOLL-FREE**  
**800-538-5000**

LOCAL (408) 559-1200 CUSTOMER SERVICE 800-538-5001  
TECH SUPPORT 800-538-5002 FAX (408) 559-0250

CIRCLE 113 ON FREE INFORMATION CARD  
Dealers Circle 170 on information card

## ADVERTISING INDEX

RADIO-ELECTRONICS does not assume any responsibility for errors that may appear in the index below.

Free Information Number		Page			
108	AMC Sales	73	56	Parts Express	86
75	Ace Products	30	78	Radio Shack	5
107	All Electronics	93	—	RE Bookstore	50
—	Amazing Concepts	83	179	Sequoia Publishing	30
77	B&K Precision	CV4	188,189	Sencore	CV3, 23
67	Banner Technical Books	71	—	Star Circuits	22
109	C & S Sales	13	83	Synergetics	68
70	CEI	89	193	TECI	74
—	CIE	3, 11	183	Video Repair School	30
194	Cable Network Co.	89	64	Video-Link	84, 86
50	Caig Laboratories	21	180	Viejo Publications	16
190	Chenesko Products	30	181	WPT Publications	74
—	Command Productions	73			
182	Communications Specialists	74			
58	Cook's Institute	25			
—	Damark International	16			
127	Deco Industries	30			
82	Digi-Key	92			
176	Electronic Goldmine	88			
—	Electronics Book Club	44			
—	Electronics Tech Today	82			
192	Emulation Associates	30			
121	Fluke Manufacturing	CV2			
184	Global Specialties	7			
—	Grantham College	14			
86	Heathkit	19			
185	ICS Computer Training	71			
177	International Components Corp.	88			
113,170	JDR Microdevices	94, 96			
114	Jameco	90			
104	Jan Crystals	25			
178	Jinco Computers	86			
—	King Wholesale	21			
—	Lindsay Publications	42			
53	MD Electronics	87			
93	Mark V. Electronics	87			
—	McGraw Hill Book Club	62			
61	Microprocessors Unltd.	82			
191	Movie Time	12			
—	NRI Schools	26			
186,187	Optoelectronics	15, 89			
—	Pacific Cable	85, 88			

**Gernsback Publications, Inc.**  
500-B Bi-County Blvd.  
Farmingdale, NY 11735  
1-516-293-3000  
Fax 1-516-293-3115  
President: **Larry Steckler**  
Vice President: **Cathy Steckler**

**For Advertising ONLY**  
1-516-293-3000  
Fax 1-516-293-3115  
**Larry Steckler**  
publisher  
**Arline Fishman**  
advertising director  
**Lisa Strassman**  
credit manager  
**Christina Estrada**  
advertising assistant

**SALES OFFICES**

**EAST/SOUTHEAST**  
**Stanley Levitan**  
Eastern Sales Manager  
Radio-Electronics  
259-23 57th Avenue  
Little Neck, NY 11362  
1-718-428-6037, 1-516-293-3000

**MIDWEST/Texas/Arkansas/  
Okla.**  
**Ralph Bergen**  
Midwest Sales Manager  
Radio-Electronics  
540 Frontage Road—Suite 339  
Northfield, IL 60093  
1-312-446-1444  
Fax 1-312-446-8451

**PACIFIC COAST/ Mountain  
States**  
**Marvin Green**  
Pacific Sales Manager  
Radio-Electronics  
5430 Van Nuys Blvd. Suite 316  
Van Nuys, CA 91401  
1-818-986-2001  
Fax 1-818-986-2009

**Gernsback Publications, Inc.**  
500-B Bi-County Blvd.  
Farmingdale, NY 11735  
1-516-293-3000  
Fax 1-516-293-3115  
President: Larry Steckler  
Vice President: Cathy Steckler

**For Advertising ONLY**  
1-516-293-3000  
Fax 1-516-293-3115  
**Larry Steckler**  
publisher

**Arline Fishman**  
advertising director  
**Lisa Strassman**  
credit manager  
**Christina Estrada**  
advertising assistant

### SALES OFFICES

**EAST/SOUTHEAST**  
**Stanley Levitan**  
Eastern Sales Manager  
Radio-Electronics  
259-23 57th Avenue  
Little Neck, NY 11362  
1-718-428-6037, 1-516-293-3000

**MIDWEST/Texas/Arkansas/Okla.**  
**Ralph Bergen**  
Midwest Sales Manager  
Radio-Electronics  
540 Frontage Road—Suite 339  
Northfield, IL 60093  
1-312-446-1444  
Fax 1-312-446-8451

**PACIFIC COAST/ Mountain States**  
**Marvin Green**  
Pacific Sales Manager  
Radio-Electronics  
5430 Van Nuys Blvd. Suite 316  
Van Nuys, CA 91401  
1-818-986-2001  
Fax 1-818-986-2009



# FOR FREE INFORMATION USE THESE POST-PAID CARDS

1 Print your name, address and Zip Code on one of the attached postage-paid cards.


2 Circle the number (or numbers) on the card that matches the number at the bottom of each ad or editorial item that you want information on. Advertisers' free information numbers also appear in the ad index on the facing page.

3 Mail the card. It's Postage-Paid.

The free information cards are BUSINESS/PROFESSIONAL CARDS. Please complete the spaces for Company Name, Title, and Phone Number if applicable.
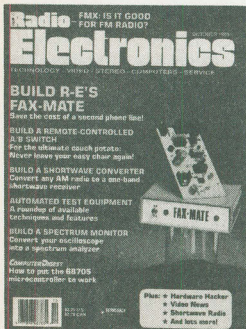
## NOTE:

Use the postcard address for Free Product Information only. Address all editorial inquiries to Editor, Radio-Electronics®, 500-B Bi-County Blvd., Farmingdale, NY 11735



**Radio-Electronics.**

Your favorite electronics magazine and still getting better

## BUSINESS/PROFESSIONAL FREE INFO CARD

If information requested is for business use, please complete all applicable spaces.

**Radio-Electronics.**

4-290

Name \_\_\_\_\_ Title \_\_\_\_\_  
Company \_\_\_\_\_  
Dept./MS \_\_\_\_\_  
Daytime Business Phone \_\_\_\_\_  
Company Address \_\_\_\_\_  
City \_\_\_\_\_ State \_\_\_\_\_ Zip + 4 \_\_\_\_\_

Unclear or incomplete mailing info will prevent our processing this request.

2 ☐ Please send me 12 issues of RADIO-ELECTRONICS® for \$17.97 and bill me. (Canada \$23.97 - US Funds only)  
4 ☐ Please send me 12 issues (1 year) of POPULAR ELECTRONICS® for \$18.95 and bill me. (Canada \$23.95- US Funds only)

19 37 55 73 91 109 127 145 163 181 199 217 235 253 271  
20 38 56 74 92 110 128 146 164 182 200 218 236 254 272  
21 39 57 75 93 111 129 147 165 183 201 219 237 255 273  
22 40 58 76 94 112 130 148 166 184 202 220 238 256 274  
23 41 59 77 95 113 131 149 167 185 203 221 239 257 275  
24 42 60 78 96 114 132 150 168 186 204 222 240 258 276  
25 43 61 79 97 115 133 151 169 187 205 223 241 259 277  
26 44 62 80 98 116 134 152 170 188 206 224 242 260 278  
9 27 45 63 81 99 117 135 153 171 189 207 225 243 261 279  
10 28 46 64 82 100 118 136 154 172 190 208 226 244 262 280  
11 29 47 65 83 101 119 137 155 173 191 209 227 245 263 281  
12 30 48 66 84 102 120 138 156 174 192 210 228 246 264 282  
13 31 49 67 85 103 121 139 157 175 193 211 229 247 265 283  
14 32 50 68 86 104 122 140 158 176 194 212 230 248 266 284  
15 33 51 69 87 105 123 141 159 177 195 213 231 249 267 285  
16 34 52 70 88 106 124 142 160 178 196 214 232 250 268 286  
17 35 53 71 89 107 125 143 161 179 197 215 233 251 269 287  
18 36 54 72 90 108 126 144 162 180 198 216 234 252 270 288

## FREE INFORMATION CARD

VOID after April 30, 1990  
Allow 6-8 weeks for delivery of first issue

## BUSINESS PROFESSIONAL FREE INFO CARD

If information requested is for business use, please complete all applicable spaces.

**Radio-Electronics.**

3-290

Name \_\_\_\_\_ Title \_\_\_\_\_  
Company \_\_\_\_\_  
Dept./MS \_\_\_\_\_  
Daytime Business Phone \_\_\_\_\_  
Company Address \_\_\_\_\_  
City \_\_\_\_\_ State \_\_\_\_\_ Zip + 4 \_\_\_\_\_

Unclear or incomplete mailing info will prevent our processing this request.

2 ☐ Please send me 12 issues of RADIO-ELECTRONICS® for \$17.97 and bill me. (Canada \$23.97 - US Funds only)  
4 ☐ Please send me 12 issues (1 year) of POPULAR ELECTRONICS® for \$18.95 and bill me. (Canada \$23.95- US Funds only)

19 37 55 73 91 109 127 145 163 181 199 217 235 253 271  
20 38 56 74 92 110 128 146 164 182 200 218 236 254 272  
21 39 57 75 93 111 129 147 165 183 201 219 237 255 273  
22 40 58 76 94 112 130 148 166 184 202 220 238 256 274  
23 41 59 77 95 113 131 149 167 185 203 221 239 257 275  
24 42 60 78 96 114 132 150 168 186 204 222 240 258 276  
25 43 61 79 97 115 133 151 169 187 205 223 241 259 277  
26 44 62 80 98 116 134 152 170 188 206 224 242 260 278  
9 27 45 63 81 99 117 135 153 171 189 207 225 243 261 279  
10 28 46 64 82 100 118 136 154 172 190 208 226 244 262 280  
11 29 47 65 83 101 119 137 155 173 191 209 227 245 263 281  
12 30 48 66 84 102 120 138 156 174 192 210 228 246 264 282  
13 31 49 67 85 103 121 139 157 175 193 211 229 247 265 283  
14 32 50 68 86 104 122 140 158 176 194 212 230 248 266 284  
15 33 51 69 87 105 123 141 159 177 195 213 231 249 267 285  
16 34 52 70 88 106 124 142 160 178 196 214 232 250 268 286  
17 35 53 71 89 107 125 143 161 179 197 215 233 251 269 287  
18 36 54 72 90 108 126 144 162 180 198 216 234 252 270 288

## FREE INFORMATION CARD

VOID after April 30, 1990  
Allow 6-8 weeks for delivery of first issue

## BUSINESS REPLY MAIL

FIRST CLASS PERMIT NO. 597 BOULDER, COLORADO

**Radio-Electronics.**

SUBSCRIPTION SERVICE

P.O. Box 51866

BOULDER, COLORADO 80321-1866

NO POSTAGE  
NECESSARY  
IF MAILED  
IN THE  
UNITED STATES



**BUSINESS REPLY MAIL**

FIRST CLASS PERMIT NO. 132 PITTSFIELD, MA

POSTAGE WILL BE PAID BY ADDRESSEE

**Radio-  
Electronics®**

READER SERVICE MANAGEMENT DEPT.  
P.O. Box 5192  
PITTSFIELD, MA 01203-9989

NO POSTAGE  
NECESSARY  
IF MAILED  
IN THE  
UNITED STATES



**Radio-  
Electronics®**

4SB00

Subscribe today to the magazine that keeps you up-to-date with the newest ideas and innovations in electronics. (If you already are a subscriber, do a friend a favor and pass this subscription card along to him.)

**check offer preferred**

- |   |   |
|---|---|
| <input type="checkbox"/> 1 Year—12 issues <b>ONLY \$17.97</b><br>(You save \$12.03 off single copy price) | <input type="checkbox"/> 2 Years ( <b>SAVE MORE</b> )—24 issues \$34.97<br>(You save \$25.03 off single copy price) |
| <input type="checkbox"/> Canada—12 issues \$23.97   | <input type="checkbox"/> Canada—24 issues \$46.97   |

ALL SUBSCRIPTIONS PAYABLE IN U.S. FUNDS ONLY

- |   |                                  |   |
|---|----------------------------------|---|
| <input type="checkbox"/> Payment enclosed | <input type="checkbox"/> Bill Me | <input type="checkbox"/> Check here if you are extending or<br>renewing your subscription |
|---|----------------------------------|---|

Name (Please Print) \_\_\_\_\_

Company Name (If applicable) \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

Allow 6-8 weeks for delivery of first issue

**BUSINESS REPLY MAIL**

FIRST CLASS PERMIT NO. 132 PITTSFIELD, MA

POSTAGE WILL BE PAID BY ADDRESSEE

**Radio-  
Electronics®**

READER SERVICE MANAGEMENT DEPT.  
P.O. Box 5192  
PITTSFIELD, MA 01203-9989

NO POSTAGE  
NECESSARY  
IF MAILED  
IN THE  
UNITED STATES



**For New  
Ideas  
In Electronics  
read Radio-  
Electronics®  
every month.**

**During the next  
12 months**

Radio-Electronics® will carry up to the minute articles on:

- Computers • Video
- Solid-state technology
- Outstanding construction projects
- Satellite TV • Telephones
- Radio • Stereo • Equipment Reports
- Test equipment • VCR's
- Servicing
- Industrial electronics



**NEW IDEAS AND INNOVATIONS  
IN ELECTRONICS APPEAR IN EVERY  
ISSUE OF RADIO-ELECTRONICS®**


**KEEP UP TO DATE! DON'T MISS  
ANY ISSUES!**

**SUBSCRIBE TODAY!**

**USE THE ORDER CARD ON YOUR  
LEFT!**

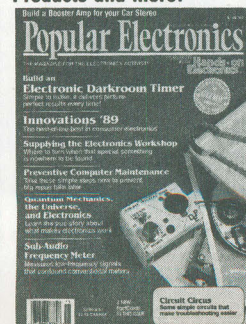**Popular Electronics®**

Delivers construction article after construction article....Exciting columns including Jensen on DXing, Freidman on computers, Test bench tips, Noll with Calling All Hams, New Products and more.



**SUBSCRIBE TODAY!**


**USE THE REPLY CARDS ON YOUR  
LEFT!**



# Introducing The SG80 AM Stereo-FM Stereo Analyzer™

**Now For The First Time, A High-Performance AM Stereo (C-QUAM)® - FM Stereo Analyzer Integrated Into One Unit, Allowing You To Performance Test, Troubleshoot, And Align To Manufacturers' Requirements**

**New**

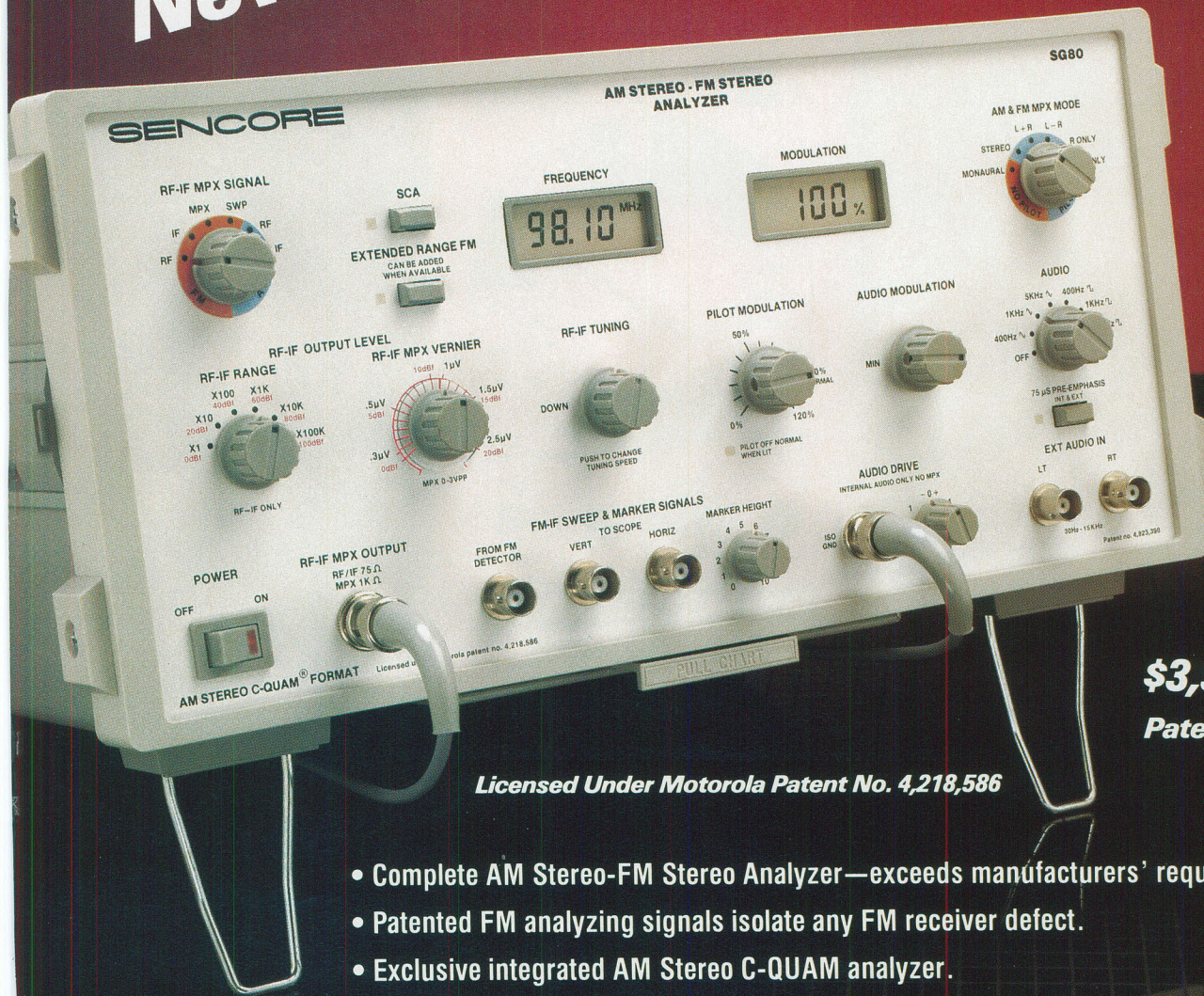

**\$3,995**  
**Patented**

**Licensed Under Motorola Patent No. 4,218,586**

- Complete AM Stereo-FM Stereo Analyzer—exceeds manufacturers' requirements.
- Patented FM analyzing signals isolate any FM receiver defect.
- Exclusive integrated AM Stereo C-QUAM analyzer.
- Digitally accurate performance tests meet EIA/IHF requirements.
- Exclusive, tuneable FM-IF Sweep and Markers—aligns all IF stages.
- Expandable FM features for future service needs, plus SCA compatible.
- Twice the capability for less than 1/2 the cost of stand-alone instruments.

C-QUAM is a registered trademark of Motorola, Inc.

CIRCLE 188 ON FREE INFORMATION CARD

**SENCORE**  
3200 Sencore Drive, Sioux Falls, South Dakota 57107

**Call 1-800-SENCORE**  
(736-2673)

**Ask About**  
**A 10 Day**  
**Video Preview**

**tech**  
**tape**






# THINK OF IT AS AN ELECTRONIC SWISS ARMY KNIFE.

**CAPACITANCE  
METER**





**FREQUENCY  
COUNTER**

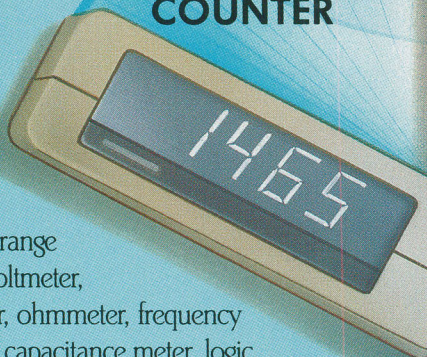

This 41 range digital voltmeter, ammeter, ohmmeter, frequency counter, capacitance meter, logic probe, transistor and diode tester features an extra-large LCD display, rugged drop-resistant case and high-energy fusing.

While you won't flip-out forks or knives, you will flip for the versatility of this low-priced wonder. For immediate delivery, see your local B&K-PRECISION distributor.

MEASURE TO THE  
**MAX**  
WITH MAXTEC

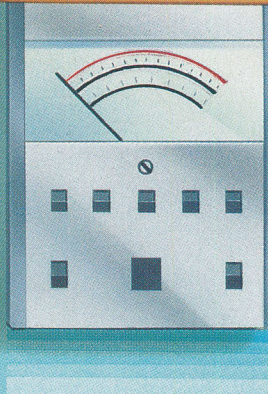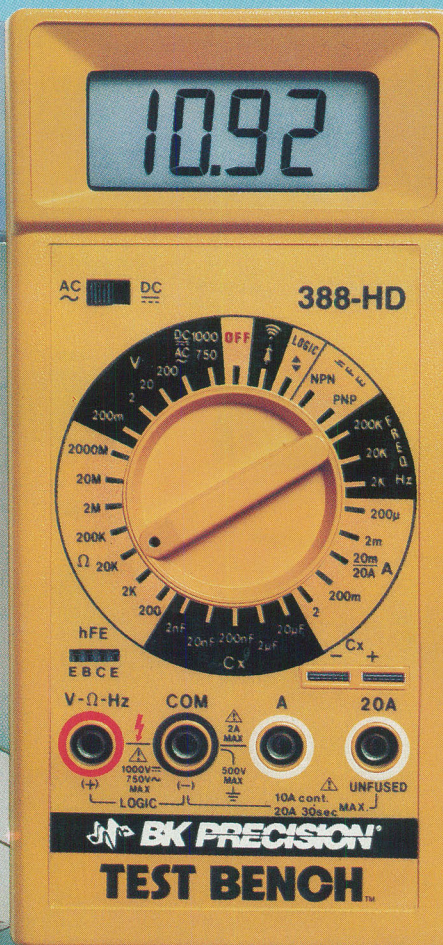

**TRANSISTOR  
TESTER**

What an idea the Swiss had... a hand-held device combining many different tools in one unit. The same inspiration is behind B&K-PRECISION's new Model 388HD Test Bench. It offers the capabilities of five popular instruments in one hand-held package.

**LOGIC  
PROBE**

**DIGITAL  
MULTIMETER**

**B&K-PRECISION  
TEST BENCH**

**\$129**



**BK PRECISION**

MAXTEC INTERNATIONAL CORP.

Domestic and International Sales  
6470 W. Cortland St. • Chicago, IL 60635  
312-889-1448 • FAX: 312-794-9740  
Canadian Sales, Atlas Electronics, Ontario.

CIRCLE 77 ON FREE INFORMATION CARD